SPECIAL SECTION—SERVICING WITH OSCILLOSCOPES

MAY 1978

Radio-Electronics

IND

THE MAGAZINE FOR NEW IDEAS IN ELECTRONICS

l about digital
ATA TRANSMISSION
ow a computer communicates

uild telephone accessory
UTO-DIALLER AND CASSETTE
ials and plays recorded message

ow to buy
OMPACT SPEAKERS
or pro systems

build add-on stereo
GRAPHIC EQUALIZER
with 12 bands and super specs

LUS:
obby Corner
quipment Reports
tate-Of-Solid-State
650 Computer Corner
ack Darr's Service Clinic
wo Hi-Fi Lab Test Reports
Getting Rid Of Noise In Mobile Installations

05
70989 34140

A GERNSBACK PUBLICATION

SYLVANIA ECG semiconductors
LINEAR MODULES AND INTEGRATED CIRCUITS
TECHNICAL MANUAL
SYLVANIA
ECG semiconductors

How to tell the parts apart.

When you've got the industry's broadest line of parts, one replacement guide is not always enough. That's why we've got a library.

We've got the master book, our "ECG Semiconductor Replacement Guide," the most complete handbook available.

And then there's our specialized manuals: The "CB Replacement Guide" that cross-references more than 5,500 parts for 73 different brands of CB equipment; our "Industrial MRO Replacement Guide" that lists ICs and power devices used in machine applications; our "Module & IC Replacement Guide" cross-referencing 3,000 non-repairable units used in 139 brands of consumer electronics equipment; and the "Linear Modules & IC Tech Manual" that gives 992 pages of design data for linear circuit applications.

You can get any or all of them at the same place you get your parts — your local Sylvania distributor.

When it comes to replacement parts, Sylvania wrote the books. **SYLVANIA** GTE

GTE Sylvania Distributor and Special Markets Div., 1025 Westminster Dr., Williamsport, PA. 17701

CIRCLE 33 ON FREE INFORMATION CARD

READY for BUSINESS

We've got it all together—the cost effectiveness and reliability of our 6800 computer system with a high capacity 1.2 megabyte floppy disk system. . . PLUS—an outstanding new DOS and file management system.

1 MEGABYTE DISK SYSTEM

DMAF1 introduces a new level of capability to small computer systems. This disk system features two standard size floppy disk drives using the new double sided disk and two heads per drive. Usable storage space of over 600 kilobytes per drive, giving a total of over 1.0 megabyte of storage on line at all times. Ideal for small business applications, or for personal "super" systems.

DMA CONTROLLER

The controller occupies one main memory slot in an SS-50 bus and uses the Motorola MC-6844 DMA controller. The combination of a DMA type controller and double sided disks give the system speed of data transfer unobtainable with smaller drives.

OPERATING SYSTEM

To compliment this outstanding hardware we are supplying equally superior software. The disk operating system and file management system is called FLEX. It is one of the most flexible and complete DOS's available for small systems, but just as important; it is easy to use.
No one can match the variety of compatible peripherals offered by Southwest Technical Products for the SS-50 bus and the 6800 computer system. Now more than ever there is no reason to settle for less.

DMAF1 Disk System (assembled)	**$2,095.00**
DMAF1 Disk System (kit)	**$2,000.00**
68/2 Computer with 40K of memory (assembled)	**$1,195.00**

SOUTHWEST TECHNICAL PRODUCTS CORPORATION
219 W. RHAPSODY
SAN ANTONIO, TEXAS 78216

CIRCLE 18 ON FREE INFORMATION CARD

Yesterday you could admire LED digital tuning in short wave.*

Today you can afford it.

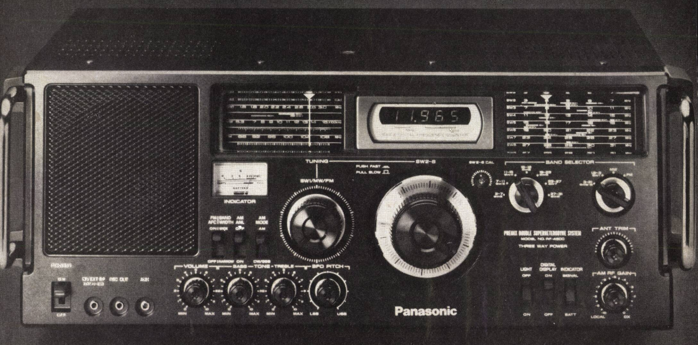

Introducing Panasonic's Command Series™ top-of-the-line RF-4800. Everything you want in short wave. Except the price. Like a five-digit LED frequency display. It's so accurate (within 1 kHz, to be exact), you can tune in a station, even before it's broadcasting. And with the RF-4800's eight short wave bands, you can choose any broadcast between 1.6 and 31 MHz. That's the full frequency range. That's Panasonic.

And what you see on the outside is just a small part of what Panasonic gives you inside. There's a double superheterodyne system for enhanced reception stability and selectivity as well as image rejection. An input-tuned RF amplifier with a 3-ganged variable tuning capacitor for exceptional sensitivity and frequency linearity. Ladder-type ceramic filters to reduce frequency interference. And even an antenna trimmer that changes the front-end capacitance for maximum reception from minimal broadcast signals.

To help you control all that sophisticated circuitry, Panasonic's RF-4800 gives you all these sophisticated controls. Like an all-gear-drive tuning control to prevent "backlash." Separate wide/narrow bandwidth selectors for optimum reception even in crowded conditions. Adjustable calibration for easy tuning to exact frequencies. A BFO pitch control. RF-gain control for increased selectivity in busy signal areas. An ANL switch. Even separate bass and treble controls.

And if all that short wave isn't enough. There's more. Like SSB (single sideband) amateur radio. All 40 CB channels. Ship to shore. Even Morse communications. AC/DC operation. And with Panasonic's 4" full-range speaker, the big sound of AM and FM will really sound big.

The RF-4800. If you had a short wave receiver as good. You wouldn't still be reading. You'd be listening.

---

*The ability to receive short wave broadcasts will vary with antenna size, time of day, operator's geographic location and other factors. You may need an optional outside antenna to receive distant short wave broadcasts.

Panasonic®
just slightly ahead of our time.

CIRCLE 66 ON FREE INFORMATION CARD

Radio-Electronics®

THE MAGAZINE FOR NEW IDEAS IN ELECTRONICS

Electronics publishers since 1908

MAY 1978 Vol. 49 No. 5

SPECIAL SECTION

69 **Servicing With Oscilloscopes**
- 70 **Why Triggered Scopes Are So Popular**
- 73 **Features Make A Scope Unique**
- 75 **How Much Bandwidth Is Enough**
- 76 **Facts About Scope Sensitivity**
- 77 **Two Are Better Than One**
- 79 **Delayed Sweep**
- 81 **So ..... Now Buy One**

BUILD ONE OF THESE

37 **Graphic Equalizer For Your Stereo System**
12-band-per-channel unit is a cinch to build and custom tailors your hi-fi system to your listening room.

41 **Automatic Telephone Dialer**
Preprogrammed dialer gets your number. Can be used with burglar alarm to give prerecorded messages.

COMPUTERS

44 **Digital Data Transmission**
Talking with peripherals—method, rates and interface schemes.

82 **Computer Corner**
Lets look at the 2650.

GENERAL ELECTRONICS

4 **Looking Ahead**
Preview of tomorrow.

47 **Mastering Mobile Noise Problems**
Eliminating interference can be simple. Here's how to find and get rid of most noise.

51 **Unusual Digital Clocks**
Part II: They tick, chime and swing—see how they work.

56 **Hobby Corner**
Part II: All about breadboards and breadboarding

84 **State of Solid State**
A TV modulator IC and a complete AM/FM radio on one IC.

STEREO HI-FI PRO SOUND

58 **Selecting Compact Pro Speaker Systems**
Buyers guide to these professional sound system staples.

65 **R-E Lab Tests Rotel-803 Receiver**
Overall FM performance rated "Excellent".

67 **R-E Lab Tests Garrard MRM-101 Phono Preamp**
Noise supressing unit removes objectionable clicks and pops.

TELEVISION

54 **CET Test Primer**
You can become a CET. Try this practice quiz.

90 **Jack Darr's Service Clinic**
How to ruin horizontal output transistors.

90 **Service Questions**
R-E's Service Editor solves reader problems.

EQUIPMENT REPORTS

24 **Tripplett 100-T Maintenance Kit**
26 **RCA VIP Computer**
28 **B&K Model 2810 DMM**
26 **Redco FM-30 Frequency Counter**
34 **RCA SelectaVision Videocassette Recorder**

DEPARTMENTS

136 **Advertising Index**
14 **Advertising Sales Offices**
14 **Editorial**
16 **Letters**
107 **Market Center**
6 **New & Timely**
99 **New Literature**
95 **New Products**
137 **Readers' Service Card**

ON THE COVER

That's a 12-band graphic equalizer you can build for your stereo system. It's just about everything a graphic equalizer should be plus it's fun to build. Check it out. Turn to page 37 now.

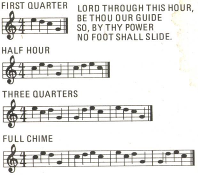

THIS MELODY IS PLAYED by some of the electronic clocks described in this issue. You'll find more details on page 51.

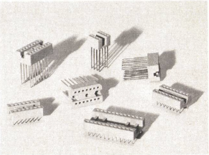

IF YOU ARE PROTOTYPING you'll need sockets like these plus a lot of other hardware. Find out what's available and where you can get it. Turn to page 57.

Radio-Electronics, Published monthly by Gernsback Publications, Inc., 200 Park Avenue South, New York, NY 10003. Phone: 212-777-6400. Second-class postage paid at New York, NY and additional mailing offices. One-year subscription rate: U.S.A. and U.S. possessions, $9.98, Canada, $12.98. Other countries, $14.98. Single copies $1.00. © 1978 by Gernsback Publications, Inc. All rights reserved. Printed in U.S.A.

Subscription Service: Mail all subscription orders, changes, correspondence and Postmaster Notices of undelivered copies (Form 3579) to Radio-Electronics Subscription Service, Box 2520, Boulder, CO 80322.

A stamped self-addressed envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

As a service to readers, Radio-Electronics publishes available plans or information relating to newsworthy products, techniques and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, Radio-Electronics disclaims any responsibility for the safe and proper functioning of reader-built projects based upon or from plans or information published in this magazine.

looking ahead

Projection TV: Projection TV's comeback as a consumer product (the first projection sets were sold in the late 1940's) seems to be gaining momentum, as manufacturers of conventional direct-view television hop on the bandwagon. Here's how the score stands at presstime: Advent, which started the whole thing, has three different sizes of its VideoBeam two-piece system and is expected to introduce a one-piece unit, still using the same three-tube approach. Electrohome of Canada, which makes the electronics for the VideoBeam system, is offering the Advent two-piece system there as well as a single-lens, single-tube conventional projector using what basically is a lens system in front of a small-screen television set. As many as 60 small companies assemble projection systems using TV sets made by others.

Cool at first to projection TV, existing set manufacturers are now looking at giant-screen television as an added market. General Electric is expected to show its first home projection system this month. "There's no question we'll be in it," says a Magnavox spokesman, but he states the product probably won't be on the market till next year. Sony, which has had a single-tube system on the market for several years (in fact, it started the trend to single-tube projection), is expected to come out shortly with a one-piece three-tube system.

Mitsubishi is already marketing a six-foot, three-tube two-piece system which resembles the Advent. Panasonic and Quasar, both subsidiaries of Japan's Matsushita, have demonstrated one-piece, three-tube systems—both using the same projection optics but different electronics and cabinetry—which they say will be offered later this year. Sharp has demonstrated a projection system in Japan and can be expected to offer one here eventually, as can Hitachi, which plans to be a partner with GE in the newly formed General Television of America.

Home projection TV's major problems have been bulk and lack of brightness. The bulk problem has been attacked by the development of one-piece systems that fold up when not in use. There has been no major breakthrough in brightness, but manufacturers are chipping away at the problem through the development of brighter tubes, better lenses and more reflective screens.

CB hurt by imports: The U.S. International Trade Commission has agreed that the American CB radio industry has been injured, or is likely to be injured, by Japanese imports, but split on how to remedy the problem. Three commissioners proposed a stiff increase in import duties on transceivers, while three recommended that domestic CB makers and their employees be declared eligible for special government aid to compensate for the inroads of imports. This leaves the final word up to President Carter, and his decision can be overridden by Congress.

The petition by American CB manufacturers for government action against imports came at a time when overproduction was obvious. Of course, Japanese manufacturers were also hit hard by the slowdown in sales and they have insisted that their competition hasn't contributed to the plight of American manufacturers, which they say is due to market conditions that have affected all CB makers.

Meanwhile, 23-channel CB's continue to show up in the marketplace, even though their sale was officially banned as of January 1. The FCC is cracking down, seizing illegal transceivers and issuing warrants.

In another development, the FCC said it returned nearly $5,000,000 in $4 license fees erroneously paid by CB applicants last year—and the fees keep rolling in. More than 30% of applicants sent money with their applications in January and February. The FCC's license-fee structure was voided by a Supreme Court decision in 1976. CB licenses—as well as all other FCC licenses—are now free, and no money should be sent with applications.

CPU's in toys: Microprocessor games and other amusements are becoming divorced from the television set—in the toy industry, anyway. The recent Toy Fair in New York provided strong evidence that hand-held, desk-top and projector games are substituting for video devices in toy stores. This presumably follows the remarkable success of Mattel's hand-held football, baseball and auto-racing games, which use LED's for displays and feature musical sound effects, and Milton Bradley's desk-top number-matching *Comp IV* game.

Here are some of the new games to entice the kiddies (and their parents) come Christmastime this year: Kenner, which holds merchandising rights to "Star Wars" products, is coming up with a two-player desk-top Star Wars "laser battle," with LED space-ship tracking system and scoring as well as nine sound effects. It also has a remote-controlled *R2D2* robot with sound effects and flashing lights, as well as a space target game. Milton Bradley will offer a missile game with sound effects and a flying saucer color-matching game. Its affiliate Playskool has a robot called *Alphie* that uses a set of plug-in program cards. Mattel is introducing a new game called *Mind Boggler*, said to be a matching challenge game similar to *Comp IV*.

Parker Brothers will field a hand-held gadget with a 2K byte memory, sound effects and lights, featuring six different games including one that permits the user to compose and store his own 48-note musical composition. Ideal has a two-player skeet-shoot game that projects the moving target on the wall, featuring gunshot sound effects and a bright burst when the target is hit. Even toy organs are becoming microprocessor-based; Concept 2000 showed one that automatically plays 12 pre-programmed songs or allows the user to play songs by following LED's mounted above the keys.

Does this mean toy makers are abandoning the television set as a display device? Probably not—but they are waiting for this part of the market to simmer down. Some day, said a Parker Brothers spokesman, "you'll probably see a video version of Monopoly and a lot of our other board games." But, like other toy makers, Parker presumably has lost interest in simple dedicated video games.

Meanwhile, RCA has stopped producing its *Studio II* programmable microprocessor video game, citing a generally disappointing market last Christmas for programmables. More to the point, probably, is the fact that RCA's was the only programmable video game that wasn't in color. The company said it's continuing design and development work on future games, which would mean it's still weighing a color version.

DAVID LACHENBRUCH
CONTRIBUTING EDITOR

An Extraordinary Offer to introduce you to the benefits of Membership in

ELECTRONICS BOOK CLUB

take any 4 of these unique electronics books (values to 65^{80}) for only 99¢ each

with a Trial Membership in the Book Club that guarantees to save you 25% to 75% on a wide selection of electronics books

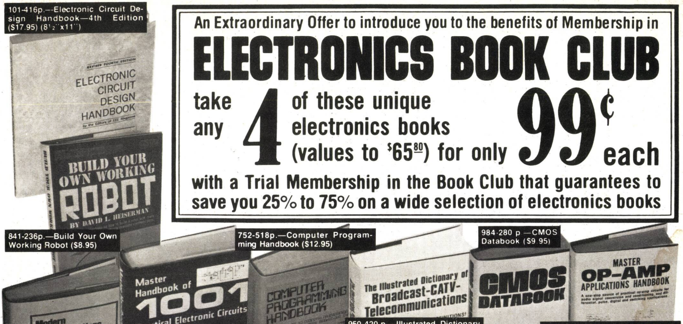
ELECTRONIC CIRCUIT DESIGN HANDBOOK
BUILD YOUR OWN WORKING ROBOT
BY DAVID L. HEISERMAN
Master Handbook of 1001 Practical Electronic Circuits
COMPUTER PROGRAMMING HANDBOOK
The Illustrated Dictionary of Broadcast-CATV-Telecommunications
CMOS DATABOOK
MASTER OP-AMP APPLICATIONS HANDBOOK
Modern Communications Switching Systems
BEGINNER'S GUIDE TO MICROPROCESSORS
3RD CLASS FCC LICENSE STUDY GUIDE
BY VICTOR F. C. VELEY
The Complete Handbook of Electrical & House Wiring
TOWERS' INTERNATIONAL TRANSISTOR SELECTOR
57 PRACTICAL PROGRAMS & GAMES IN BASIC
THE COMPLETE HANDBOOK OF VIDEOCASSETTE RECORDERS
HOW TO TEST ALMOST EVERYTHING ELECTRONIC
MODERN GUIDE TO DIGITAL LOGIC: Processors, Memories & Interfaces
Programming Microprocessors
HOW TO REPAIR HOME & AUTO AIR CONDITIONERS
COLOR TV CASE HISTORIES ILLUSTRATED
WORKING WITH THE OSCILLOSCOPE

101-416p.—Electronic Circuit Design Handbook—4th Edition ($17.95) (8½"x11")

841-236p.—Build Your Own Working Robot ($8.95)

752-518p.—Computer Programming Handbook ($12.95)

984-280 p.—CMOS Databook ($9.95)

800-602p.—Master Handbook of 1001 Practical Electronic Circuits ($12.95)

950-420 p.—Illustrated Dictionary of Broadcast/CATV/Telecommunications ($14.95)

856-476p.—Master OP-AMP Applications Handbook ($14.95)

678-276p.—Modern Communications Switching Systems ($17.95)

913-476p.—The Complete Handbook of Electrical & House Wiring ($10.95)

1010-200p.—Tower's International Transistor Selector—2nd Edition ($9.95)

995-182p—Beginner's Guide to Microprocessors ($8.95)

811-280p.—The Complete Handbook of Videocassette Recorders ($9.95)

893-322p.—Third Class FCC License Study Guide ($9.95)

1000-210p.—57 Practical Programs & Games in BASIC ($10.95)

132-168p.—How to Test Almost Everything Electronic ($6.95)

876-352p.—Color TV Case Histories Illustrated: Photo Guide to Troubles/Cures—Vol. 2 ($10.95)

985-280p.—Programming Microprocessors ($9.95)

472-96p.—Working With the Oscilloscope ($8.95)

709-294p.—Modern Guide to Digital Logic: Processors, Memories & Interfaces ($9.95)

520-208p.—How to Repair Home & Auto Air Conditioners ($8.95)

May we send you your choice of 4 of these practical time-and-money-saving books as part of an unusual offer of a Trial Membership in Electronics Book Club?

Here are quality hardbound volumes, each especially designed to help you increase your know-how, earning power, and enjoyment of electronics. Whatever your interest in electronics, you'll find Electronics Book Club offers practical, quality books that you can put to immediate use and benefit.

This extraordinary offer is intended to prove to you through your own experience, that these very real advantages can be yours...that it *is* possible to keep up with the literature published in your areas of interest, and to save substantially while so doing. As part of your Trial Membership, you need purchase as few as four books during the coming 12 months. You would probably buy at least this many anyway, without the substantial savings offered through Club Membership.

To start your Membership on these attractive terms, simply fill out and mail the coupon today. You will receive the 4 books of your choice for 10-day inspection. YOU NEED SEND NO MONEY. If you're not delighted, return the books within 10 days and your Trial Membership will be cancelled without cost or obligation.

ELECTRONICS BOOK CLUB, Blue Ridge Summit, Pa. 17214

Facts About Club Membership

- The 4 introductory books of your choice carry publishers retail prices of up to $65.80. They are yours for only 99¢ each (plus postage/handling) with your Trial Membership.
- You will receive the Club News, describing the current Selection Alternates and other books, every 4 weeks (13x times a year).
- If you want the Selection, do nothing, it will be sent to you automatically. If you do not wish to receive the Selection, or if you want to order one of the many Alternates offered, you simply give instructions on the reply form (and in the envelope) provided, and return it to us by the date specified. This date allows you at least 10 days in which to return the form. If, because of late mail delivery, you do not have 10 days to make a decision and so receive an unwanted Selection, you may return it at Club expense.
- To complete your Trial Membership, you need buy only four additional monthly selections or alternates during the next 12 months. You may cancel your Membership any time after you purchase these four books.
- All books—including the introductory Offer—are fully returnable after 10 days if you're not completely satisfied.
- All books are offered at low Member prices, plus a small postage and handling charge.
- **Continuing Bonus** If you continue after this Trial Membership, you will earn a Dividend Certificate for every book you purchase. Three Certificates plus payment of the nominal sum of $1.99 will entitle you to a valuable Book Dividend of your choice which you may choose from a list provided Members.

ELECTRONICS BOOK CLUB

Blue Ridge Summit, Pa. 17214

Please open my Trial Membership in ELECTRONICS BOOK CLUB and send me the 4 books circled below. I understand the cost of the books I have selected is only 99¢ each, plus a small shipping charge. If not delighted, I may return the books within 10 days and owe nothing, and have my Trial Membership cancelled. I agree to purchase at least four additional books during the next 12 months, after which I may cancel my membership at any time.

101 132 472 520 678 709 752
800 811 841 856 876 893
913 950 984 985 995 1000 1010

Name________________ **Phone**________

Address________________________

City___________________________

State________________ **Zip**__________

(Valid for new Members only. Foreign and Canada add 10%) RE-58

CIRCLE 24 ON FREE INFORMATION CARD

new & timely

"Interference" mars anniversary of Marconi's transatlantic message

It had been planned to mark the 75th anniversary of Guglielmo Marconi's historic first transatlantic communication, but an FCC technicality managed to cross the wires.

Back in early January, 1903, Marconi sent the first message across the Atlantic Ocean, transmitting it from a wireless station located in Wellfleet, MA, to a sister station on the south shore of England. At that time, flowery messages of greeting and congratulations were exchanged between President Theodore Roosevelt and King Edward VII.

This year, Wellfleet amateur radio operators thought it would be fitting for President Carter and Queen Elizabeth to exchange similar greetings. President Carter agreed; but the FCC ruled against it since there is a regulation forbidding "personal third-party messages" to be sent by amateur radio operators. If the Queen and President Carter had been amateur operators, there would have been no problem!

So, instead of a personal message to the Queen, President Carter released a general statement about how Marconi's invention had paved the way for instant communication "not only between heads of state, but peoples of all nations." The message was transmitted in Morse code via voice transmitter to amateurs around the world.

New one-handed keyboard for typing ASCII code

A hemispherically shaped keyboard, the *Writehander*, has been designed so that you can type ASCII code characters with just one hand. This format not only makes it easy to use while telephoning or sitting in an easy chair, it is an invaluable tool for those with injured or disabled hands who cannot use a conventional keyboard. The *Writehander*'s shape is easy to hold, and it comes with two different switch spacings to accomodate different hand sizes.

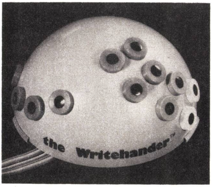

UNUSUAL DESIGN OF ASCII-encoded keyboard permits typing alphanumeric characters with one hand.

To operate the keyboard, place four fingers on four pressure switches and your thumb on one of eight other pressure switches. The four finger switches operate the lower four bits of the 7-bit ASCII code and select the group of characters (out of 16 groups) that contains the character you want. With your thumb, you press the appropriate switch from among the eight thumb switches to select the desired character.

The *Writehander* does not need a computer to operate any terminal that accepts parallel 7-bit ASCII code signals. Connection to the terminal is via ribbon cable with appropriate lines for the 7-bit ASCII code, a 1-bit fixed parity, strobe and acknowledge signals and the power and common ground lines. The *Writehander* can be powered from a 200-mA DC supply from 5 volts, regulated, or 7 to 25 volts unregulated. It carries a price tag of $98.

RCA fiber-optic cables used in optical communications

RCA's recently developed optical communications system features fiber optics, a technology that enables light waves to be transmitted via small lightweight glass or plastic cables. Dr. Ralph Simon of RCA explains that communications systems using fiber optics are capable of transporting a large amount of data, are not prone to static interference and are tamper-proof. Since data is transmitted at light frequencies, such a system has a great advantage over conventional wire or radiowave transmission because a single fiber-optic strand has the transmission capacity of hundreds of telephone wires.

The RCA communications system consists of a transmitter containing a high-speed gallium-aluminum-arsenide LED and a receiver consisting of a silicon photodiode.

Designed to be used in digital-data computer links, digital telecommunications and other optically isolated data systems, the fiber-optics data link sells for $850, minus the fiber-optics cable, which is available in different lengths at additional cost.

Ben Tongue becomes a Fellow in Radio Club of America

Ben Tongue, president of Blonder-Tongue Laboratories, was recently awarded a Fellowship in the Radio Club of America for "his outstanding contributions in the field of TV reception products." Before his association with Blonder-Tongue, Mr. Tongue was responsible for designing and producing the first audio and ultrasonic scanning spectrum analyzers for Panoramic Radio Corporation. Additionally, he holds over 30 patents, most in the field of low-noise, wideband amplification, and is also a director of Databit, Hauppauge, NY.

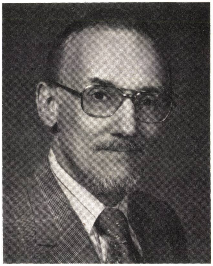

BEN TONGUE

Among his other credits Mr. Tongue lists membership in IEEE; two professional honor societies; the Antenna Committee of EIA; the Association of Computing Machinery; and the Audio Engineering Society.

Revised FCC/CB regulations—questions and answers

Revised FCC regulations governing CB equipment standards went into effect January 1, 1978. These regulations were devised to reduce the severity of current and potential interference posed by CB equipment, and specifically prohibit the marketing of any equipment not conforming to the new noise-reduction regulations.

To guide the general public, as well as those in the CB fraternity, the FCC has provided some typical questions received by the Commission, plus answers:

1. Can you still use your (previously acquired) CB after January 1? Answer: Yes.

2. Is it legal to sell your 23-channel CB to anyone? Answer: No.

3. What types of CB equipment are affected by the ban? Answer: All currently available 23-channel CB's; all units with fewer than 23 channels purchased prior to September 10, 1976; any receiver or transmitter with separate CB band not approved by the Commission; and most CB converters.

4. Are hand-held CB's (walkie-talkies) affected by the ban? Answer: Any such unit with a built-in mike, permanent antenna, internal batteries and receive and transmit

continued on page 12

Uncompromising performance. Incredible price. A professional 3½ digit DMM Kit for less than $70.

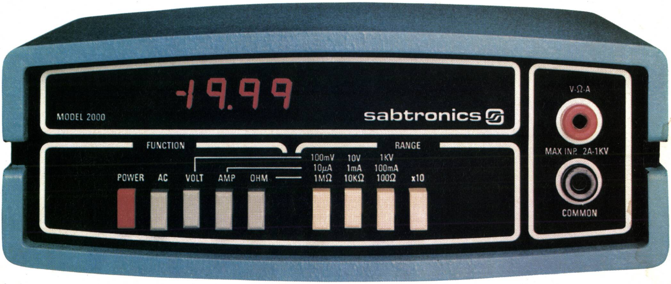

Incredible? True! Professionals and hobbyists alike are believers in this Sabtronics 2000, the only portable/bench DMM which offers such uncompromising performance at the astonishingly low price of $69.95.

Uncompromising performance you'd expect only from a specialist in digital technology such as Sabtronics: Basic DCV accuracy of 0.1% ± 1 digit; 5 functions giving 28 ranges; readings to ±1999 with 100% overrange; overrange indication; input overload protection; automatic polarity; and automatic zeroing.

The low price of $69.95? Simple: The Model 2000 is all solid-state, incorporating a single LSI circuit and high-quality components. You assemble it yourself, using our clear, easy-to-follow, step-by-step assembly manual. Kit is complete, including a high-impact case.

Now you too can have it! A professional-quality, 3½ digit Sabtronics Model 2000 DMM kit for only $69.95. If you don't have one in your lab, use the coupon below to order NOW.

BRIEF SPECIFICATIONS:

DC volts in 5 ranges: 100 µV to 1 kV • AC volts in 5 ranges: 100 µV to 1 kV • DC current in 6 ranges: 100 nA to 2 A • AC current in 6 ranges: 100 nA to 2 A • Resistance: 0.1 Ω to 20 MΩ in 6 ranges • AC frequency response: 40 Hz to 50 kHz • Display: 0.36" (9,1 mm) 7-segment LED • Input impedance: 10 MΩ • Size: 8" W x 6.5" D x 3" H (203 x 165 x 76 mm) • Power requirement: 4 "C" cells (not included).

GUARANTEE:

Examine the 2000 DMM kit for 10 days. If not completely satisfied, return unassembled for full refund of purchase price. (Less shipping and handling)

Use your Master Charge or Visa.
To order by phone call: (214) 783-0994

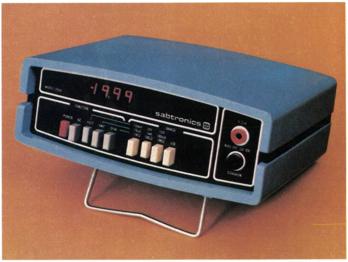

Made in U.S.A.

To: Sabtronics International, Inc. RE 5
13426 Floyd Circle, Dallas, TX 75243

Please send me________Sabtronics Model 2000 DMM kit(s)
at $69.95 each...................... $________
Shipping and handling, $5.00 per unit* $________
Texas Residents Add Sales Tax $________
TOTAL enclosed $________

Name____________________
Street____________________
City____________________
State____________ Zip________

*USA only. Canada $6.50. All other countries, $10.00 (surface mail)

sabtronics
INTERNATIONAL INC.
13426 Floyd Circle • Dallas, Texas 75243

Learn digital computer

NRI is the only school to train you at home on a real digital computer.

Learn computer design, construction, maintenance and programming techniques on your own programmable digital computer.

Qualified technicians are urgently needed for careers in the exciting new field of digital and computer electronics . . . and the best way to learn digital logic and operations is now available to you in NRI's Complete Computer Electronics Course.

This exclusive course trains you at home on your own digital computer! This is no beginner's "logic trainer", but a complete programmable digital computer that contains a memory and is fully automatic. You build it yourself and use it to define and flow-chart a program, code your program, store your program and data in the memory bank. Press the start button and the computer solves your problem and displays the result instantly.

The NRI digital computer is one of 10 kits you receive in the NRI Complete Computer Electronics Course. You build and use your own TVOM, and experiment with NRI's exclusive Electronics Lab. You perform hundreds of experiments, building hundreds of circuits, learning organization, operation, trouble-shooting and programming.

New NRI Memory Expansion Kit

The Model 832 NRI Digital Computer now comes with a new Memory Expansion Kit. Installed and checked out in 45 minutes, it doubles the size of the computer's memory, significantly increasing the scope and depth of your knowledge of digital computers and programming. With the large-scale IC's you get the only home training in machine language programming . . . experience essential to trouble-shooting digital computers.

editorial

It's A Great Little Library

If you've ever been stuck for service data on an old TV or radio that you are trying to revitalize. If you need data on any electronic part or test instrument and you can't seem to locate the information you need; try the ISCET/TECH. That's the Technical Electronic Clearing House, the technical library of the International Society of Certified Electronics Technicians.

What's in the library? Any and almost all electronics manuals, diagrams and magazines . . . antique radios, test equipment, antique tubes. If you haven't been able to find it elsewhere, Henry V. Golden, CET, the official librarian can probably locate it for you.

The library is a two-way street. If you've got old service literature and materials, don't throw them out . . . ship them to the Library instead. Henry Golden has no budget to pay for anything, but he can supply you with a tax-deductible receipt for the material and freight. It's a great way to dispose of materials that are outdated for your shop but still of value to other technicians.

The services of the library are available to members at no cost and to non-members at a very nominal cost. Membership is $25 per year, and entitles you to unlimited free use of the library's facilities. The only additional expense would be shipping or duplication costs.

If you have materials to send to the library, ship them prepaid to, ISCET Technical Clearing House, Henry V. Golden, CET, Librarian, 8015 Paseo, Kansas City, MO 64131. You'll be doing every technician in the world a service.

If you want information on becoming a member of the library, write Henry today. Membership in the Library is a great investment.

Larry Steckler

LARRY STECKLER
Editor

Radio-Electronics®

Hugo Gernsback (1884-1967) founder
M. Harvey Gernsback, editor-in-chief and publisher
Larry Steckler, KTX-3644, CET, editor
Arthur Kleiman, KTZ-3288, managing editor
Robert F. Scott, CET, W2PWG, KXK-8533, technical editor
Sonia Greenbaum, copy editor
Jack Darr, CET service editor
Leonard Feldman contributing high-fidelity editor
Karl Savon, semiconductor editor
David Lachenbruch, contributing editor
Earl "Doc" Savage, K4SDS, hobby editor
Vincent P. Cicenia, production manager
Harriet I. Matysko, circulation director
Sheila Wertling, circulation assistant
Arline R. Bailey, advertising coordinator

Cover design by Louis G. Rubsamen
Cover photo by Michael Wilson

Radio Electronics is a member of the *Institute of High Fidelity* and is indexed in *Applied Science & Technology Index* and *Readers Guide to Periodical Literature.*

Gernsback Publications, Inc.
200 Park Ave. S., New York, NY 10003
(212) 777-6400
President: M. Harvey Gernsback
Vice President: Larry Steckler
Treasurer: Carol A. Gernsback
Secretary: Bertina Baer

ADVERTISING SALES
Paul McGinnis
Director of Marketing

EAST
Stanley Levitan
Radio-Electronics
200 Park Ave. South
New York, NY 10003
(212) 777-6400

MIDWEST/Texas/Arkansas/Okla.
Ralph Bergen
The Ralph Bergen Co.
6319 N. Central Ave.
Chicago, IL 60646
(312) 792-3646

PACIFIC COAST
Mountain States
Jay Eisenberg
J.E. Publishers Representative Co.,
8732 Sunset Blvd.,
4th Floor,
Los Angeles, CA 90069
(213) 659-3810
Sales Mart Building
1485 Bayshore Blvd., Box 140
San Francisco, CA 94124
(415) 467-0125

SOUTHEAST
J.E. Publishers Representative Co.,
214-387-2424

MEMBER IHF INSTITUTE OF HIGH FIDELITY
AUDITED PAID CIRCULATION ABC
EIA

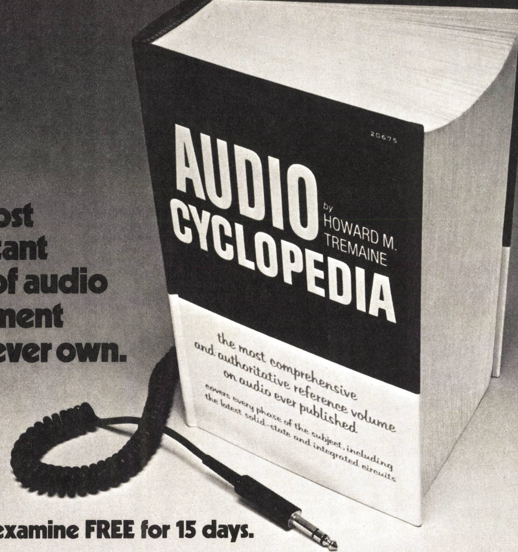
20675
AUDIO CYCLOPEDIA
by HOWARD M. TREMAINE
the most comprehensive and authoritative reference volume on audio ever published
covers every phase of the subject, including the latest solid-state and integrated circuits

he most
mportant
iece of audio
quipment
ou'll ever own.

ours to examine FREE for 15 days.

25 FACT-FILLED CHAPTERS ARRANGED IN "EASY-TO-FIND" QUESTION AND ANSWER FORM

- Basic Principles of Sound
- Acoustics, Studio techniques, and Equipment
- Constant-Speed Devices, Motors, and Generators
- Microphones
- Attenuators
- Equalizers
- Wave Filters
- Transformers and Coils
- Sound Mixers
- VU and Volume Indicator Meters
- Vacuum Tubes, Transistors, and Diodes
- Audio Amplifiers
- Disc Recording
- Cutting Heads
- Recording and Reproducing Styli
- Pickups
- Magnetic Recording
- Optical Film Recording
- Motion Picture Projection Equipment
- Loudspeakers, Enclosures, Headphones, and Hearing Aids
- Power Supplies
- Test Equipment
- Audio-Frequency Measurements
- Installation Techniques
- General Information, Charts and Tables

Be our guest. Examine the AUDIO CYCLOPEDIA free for 15 days. You'll find out why it is considered the most comprehensive and authoritative book ever written on the subject. And you'll get a FREE $3.50 bonus book to keep no matter what!

The AUDIO CYCLOPEDIA is literally a one-book audio library. It has long been considered "the bible" by amateur stereo buffs as well as professional technicians. That's why you'll find it in constant use not only in home workshops and at stereo centers, but also in recording studios, broadcast booths and concert halls.

This giant reference book is over 3" thick, and packed with 1,757 illustrated pages. It features 3,645 questions and answers and a 50 page "instant-find" index for subject identification. It is truly the big one in audio electronics and it puts all the information you'll ever need right at your fingertips, chapter by chapter.

Send for the AUDIO CYCLOPEDIA today. If you don't agree that it's the most important piece of audio equipment you own, just return it within 15 days. You won't owe a cent. And no matter what you decide, you'll get a free $3.50 copy of *The ABC's of Tape Recording* to keep just for mailing the coupon.

FREE-BOOK FREE-TRIAL COUPON

Save postage & handling costs. Full payment enclosed (plus tax where applicable). 15-day return privilege still applies.

Yes, please rush me the AUDIO CYCLOPEDIA (#21455) for my free trial. I understand if not completely satisfied, I may return it within 15 days, and owe nothing. Otherwise, it's mine to keep for only $39.95 plus postage and handling and local taxes (where applicable).
And, whatever I decide, a copy of "The ABC's of Tape Recording" (valued at $3.50) is mine free!

Name ____________________

Address ____________________

City ____________________

State ____________ Zip ____________

Mail to **Audel**
4300 W. 62nd Street
Indianapolis, Indiana 46206
A Division of Howard W. Sams & Co., Inc.

EC41

237R1

new & timely

continued from page 6

capabilities can be sold until *August 1, 1978*.

5. Can you trade in a CB for other radio gear? Answer: Yes, since the dealer is specifically prohibited from reselling the equipment. (It is of course up to the dealer to accept the trade-in or not.)

6. Will it be possible to give away 23-channel CB's? Yes, but only to family members, friends or charity; as door prizes; or as store giveaways (i.e., to the first 10 people entering the store on a given day). Prohibited are any transactions in which the recipient receives something of value from the giver, or any offer made to the customer if he agrees to purchase another item, or if he must pay to enter the store.

7. Can a 23-channel radio be sold for the parts it contains? Answer: Yes, but the generating components from both receiver and transmitter must be removed.

8. Is it legal to remanufacture a 23-channel CB radio in order to conform to the new regulations? Yes, if the unit is rebuilt to 40-channel operation, modified to meet the new standards, reidentified as a different model and has received a new grant of type acceptance from the FCC.

9. Can you sell a car, van, mobile home, etc., that has CB equipment in it? Answer: Yes, if the equipment has been permanently installed as an in-dash unit prior to January 1.

10. Can any 23-channel CB radio bought before January 1 be brought in for repair or exchange if proved defective? Answer: Yes. Repairs are not prohibited, and an exchange is legal since this is not considered marketing—the dealer is still prohibited from reselling the exchanged unit.

Further questions can be directed to John Reed or Frank Rose, Research and Standards Division, Room 7502, Federal Communications Commission, Washington, DC 20554. Any questions concerning particular CB models, CB converters or receiver/transceivers with CB bands should be sent to local FCC field offices, or to the FCC Laboratory, P.O. Box 40, Laurel, MD 20810 (301) 725-1585.

The editorial staff of **Radio-Electronics** wonders how the FCC plans to enforce these new rules. Or, for that matter, what the penalties will be.

Solar energy used to power traffic counter

A solar energy module, developed by Motorola Laboratories, was installed recently to power a six-lane traffic counter in Glendale, AZ. Although conventionally produced power for such counters is usually not expensive, it is often unavailable at counter sites, according to an Arizona Department of Transportation spokesman. Since the solar-cell array is capable of a more than 8-watt power output (due to Arizona's predominantly sunny climate) and can store enough energy in a reserve battery for 14 cloudy days as well as for night operations, it is hoped that the module may be an effective answer to the problem of supplying low-cost energy to the traffic counters.

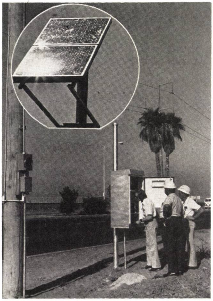

SOLAR-POWERED traffic counter being tested in Glendale, AZ. Inset shows solar silicon array.

The solar module is composed of many tine pyramidal shapes that intercept light rays, producing an output of about ½ watt per 3-inch cell. The unit's copper connections and glass and stainless steel construction are expected to give it a life expectancy of more than 20 years.

At present, Motorola solar energy modules are being used in remote communications links where conventional power sources are expensive and difficult of access.

Sears, Roebuck enters pay-TV market

Sears, Roebuck & Co., the national department store chain, has recently entered the pay-TV market by installing and marketing National Subscription Television in Los Angeles and environs. Subscribers to NST in LA presently number about 20,000, and it is surmised that the growing demand for pay-TV may have prompted the Sears move as well as the possibility that NST may not be able to keep up with the demand. Sears is the first department store chain to enter the pay-TV market.

RCA photomultiplier tube aids in tracing satellite remains

On January 24, 1978, the Soviet atomic-powered satellite, Cosmos 954, fell to earth over northeastern Canada and disintegrated. Since then, massive efforts were made to recover the dangerously radioactive satellite fragments. Among the methods used in the recovery operations is an RCA-developed photomultiplier tube, a light-sensitive device contained in nuclear detection instruments.

The photomultiplier tube is capable of detecting minuscule amounts of light, which are then converted to an electrical signal that can be measured electronically. Dr. Ralph E. Simon, division vice president, RCA Electro-Optics and Devices, explains how the tube works in a detection device:

"The tubes are encapsulated in an aluminum cylinder behind a scintillation crystal. When in the vicinity of a nuclear radiation source, blue flashes of light are picked up on the faces of several photomultiplier tubes . . . These signals are relayed to an electronic sorting bin that separates light sources by their signals . . . which are read out as TV-like pictures by means of an oscilloscope." The strength of the nuclear source is then interpreted by reading the curves on the scope. Dr. Simon adds that when used in nuclear detection devices, these photomultiplier tubes are more sensitive than Geiger counters. The tubes have been widely used in different areas; for example, in determining the radioactivity of the moon's surface; in monitoring nuclear test results; and in cancer diagnosis and research.

GLASS SURFACES OF PHOTOMULTIPLIER TUBES being treated at RCA Electro-Optics and Devices plant in Lancaster, PA. When installed in nuclear detection instruments, tubes can "see" nuclear radiation as blue flashes of light.

electronics at home.

NRI offers you five TV/Audio Servicing Courses

NRI can train you at home to service Color TV equipment and audio systems. You can choose from 5 courses, starting with a 48-lesson basic course, up to a Master Color TV/Audio Course, complete with designed-for-learning 25″ diagonal solid state color TV and a 4-speaker SQ™ Quadraphonic Audio System. NRI gives you both TV and Audio servicing for hundreds of dollars less than the two courses as offered by another home study school.

All courses are available with low down payment and convenient monthly payments. All courses provide professional tools and "Power-On" equipment along with NRI kits engineered for training. With the Master Course, for instance, you build your own 5″ wide-band triggered sweep solid state oscilloscope, digital color TV pattern generator, CMOS digital frequency counter, and NRI electronics Discovery Lab.

™Trademark of CBS Inc.

NRI's Complete Communications Course includes your own 400-channel VHF transceiver

NRI's Complete Communications Course will train you at home for one of the thousands of service and maintenance jobs opening in CB; AM and FM transmission and reception; TV broadcasting; microwave, teletype, radar, mobile, aircraft, and marine electronics. The complete program includes 48 lessons, 9 special reference texts, and 10 training kits. Included are: your own "designed-for-learning" 400-channel VHF transceiver; electronics Discovery Lab™; CMOS digital frequency counter; and more. You also get your all important FCC Radio-telephone License, or you get your money back.

CB Specialist Course also available

NRI also offers a 37-lesson course in CB Servicing with your own CB Transceiver, AC power supply, and multimeter. Also included are 8 reference texts and 14 coaching units to make it easy to get your Commercial Radiotelephone FCC License.

You pay less for NRI training and you get more for your money.
NRI employs no salesmen, pays no commissions. We pass the savings on to you in reduced tuitions and extras in the way of professional equipment, testing instruments, etc. You can pay more, but you can't get better training.

More than one million students have enrolled with NRI in 62 years.
Mail the insert card and discover for yourself why NRI is the recognized leader in home training. Do it today and get started on that new career. No salesman will call.

If card is missing write:

NRI SCHOOLS
McGraw-Hill Continuing
Education Center
3939 Wisconsin Avenue
Washington, D.C. 20016

Understanding Digital Electronics

New teach-yourself courses

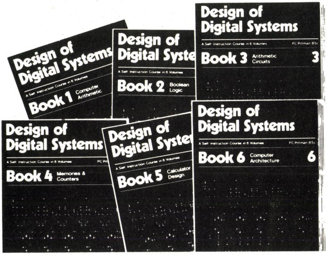
Design of Digital Systems
A Self Instruction Course in 6 Volumes
Book 1 Computer Arithmetic
Book 2 Boolean Logic
Book 3 Arithmetic Circuits 3
Book 4 Memories & Counters
Book 5 Calculator Design
Book 6 Computer Architecture 6
PC Pittman BSc

Design of Digital Systems is written for the engineer seeking to learn more about digital electronics. Its six volumes — each 11-1 / 2" x 8-1 / 4" are packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra to memories, counters and simple arithmetic circuits, and finally to a complete understanding of the design and operation of calculators and computers.

The contents of Design of Digital Systems include:

Book 1 Octal, hexadecimal and binary number systems; conversion between number systems; representation of negative numbers; complementary systems; binary multiplication and division.
Book 2 OR and AND functions; logic gates; NOT, exclusive-OR, NAND, NOR and exclusive-NOR functions; multiple input gates; truth tables; De Morgans Laws; canonical forms; logic conventions; Karnaugh mapping; three-state and wired logic.
Book 3 Half adders and full adders; subtractors; serial and parallel adders; processors and arithmetic logic units (ALUs); multiplication and division systems.
Book 4 Flip flops; shift registers; asynchronous and synchronous counters; ring, Johnson and exclusive-OR feedback counters; random access memories (RAMs) and read only memories (ROMs).
Book 5 Structure of calculators; keyboard encoding; decoding display data; register systems; control unit; program ROM; address decoding; instruction sets; instruction decoding; control program structure.
Book 6 Central processing unit (CPU); memory organization; character representation; program storage; address modes; input / output systems; program interrupts; interrupt priorities; programming; assemblers; computers; executive programs; operating systems and time sharing.

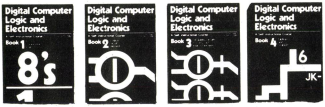

Digital Computer Logic and Electronics is designed for the beginner. No mathematical knowledge other than simple arithmetic is assumed, though the student should have an aptitude for logical thought. It consists of four volumes — each 11-1 / 2" x 8-1 / 4" — and serves as an introduction to the subject of digital electronics. Everyone can learn from it — designer, executive, scientist, student, engineer.

Contents include: Binary, octal and decimal number systems; conversion between number systems; AND, OR, NOR and NAND gates and inverters; Boolean algebra and truth tables; De Morgans Laws; design of logic circuits using NOR gates; R-S and J-K flip flops; binary counters, shift registers and half adders.

In the years ahead the products of digital electronics technology will play an important part in your life. Calculators and digital watches are already commonplace. Tomorrow a digital display could show your automobile speed and gas consumption; you could be calling people by entering their name into a telephone which would automatically look up their number and dial it for you.

These courses were written by experts in electronics and learning systems so that you could teach yourself the theory and application of digital logic. Learning by self-instruction has the advantages of being faster and more thorough than classroom learning. You work at your own pace and must respond by answering questions on each new piece of information before proceeding.

After completing these courses you will have broadened your career prospects and increased your fundamental understanding of the rapidly changing technological world around you.

The six volumes of Design of Digital Systems cost only: **$19.88**

And the four volumes of Digital Computer Logic and Electronics cost only: **$14.88**

But if you buy both courses, the total cost is only: **$29.90**

a saving of over: **$5.00**

SEVEN-DAY MONEY-BACK GUARANTEE: If you are not satisfied with your Cambridge course, return it within 7 days for a full refund.

To order your books, complete the order form below and send it together with your check or money order to GFN Industries, Inc., 6 Commercial Street, Hicksville, N.Y. 11801.

To: **GFN INDUSTRIES, INC.**
6 COMMERCIAL STREET, HICKSVILLE, NY 11801

Please send me:
___Sets of Design of Digital Systems $19.88__________
___Sets of Digital Computer Logic & Electronics $14.88______
___Sets of both courses $29.90__________
Sales tax (N.Y. residents) __________
Shipping and handling $2.50 per set __________
Enclosed is check/mo (payable to GFN Industries, Inc.)

Total $________

Name ____________________
Address ____________________
City/State/Zip ____________________

Prices include overseas surface mail postage. RE5B

letters

2650 KEYBOARD

This letter is in reference to the Radio Shack keyboard (No. 277-177) and to Mike Herbach's letter in the February 1978 issue.

It is quite easy to make the conversion from a "7E" code to a "1B" code as needed for the 2650, provided that you don't mind unsoldering the board from the keyboard. The information on how to do this is available from Jerry Heep, Project Engineer, Tandy Systems Design, 1800 One Tandy Center, Fort Worth, TX 76102.

I have already modified my board and it works perfectly.

KEITH LITTLE
The Computer People
Webster Groves, MO

EMERGENCY CB RADIO PATROL

Some of your readers might be interested to know that we have formed an Emergency Citizens Band Radio Patrol (E.C.B.R.P.). The aims of the patrol are to maintain a community of alert citizens to watch out for and report on crime, vandalism, accidents, hazardous drivers and dangerous road conditions, etc., and to render assistance whenever necessary to fire, police and civil defense departments and to local and federal agencies in case of emergency.

We also encourage, recognize and pay tribute to those members who perform outstanding public service by giving them awards for their efforts.

The $5.00 membership fee entitles you to a membership card, personal E.C.B.R.P. unit number, CB slang dictionary, copy of emergency procedures and official 10-code. For more information, send stamped, self-addressed envelope to E.C.B.R.P., Main P.O. Box 240, Yonkers, NY 10703.

B. MANDEL
Yonkers, NY

SOLDERING/DESOLDERING TRICKS

The article entitled "Tricks of Soldering/Desoldering" (January 1978 issue) contains a couple of errors of omission.

Table I lists manufacturers of soldering equipment, but fails to include American Beauty, a company that has manufactured soldering equipment and accessories for many years. Their products include irons from 20 watts to 550 watts, temperature-controlled irons and replacement tips.

Although various brands of fluxed braids for desoldering are listed in Table II, no mention is made in the article of their applications. The author writes that a DIP device can be removed with a special flat block tip but that this leaves old solder in the board. Why not use fluxed braid and a regular soldering iron to free the DIP, since the braid soaks up the solder and at the same time removes the old solder from the PC board pads.

MARVIN SMITH
Harbor City, CA

I read the article in the January 1978 issue on "Tricks of Soldering/Desoldering," and found it very interesting.

I have built many Heathkits, and I work for Quasar, where I do occasional repair work on production equipment.

Another reason to join RCA's QT Parts Program!
You get four free information packages every year.

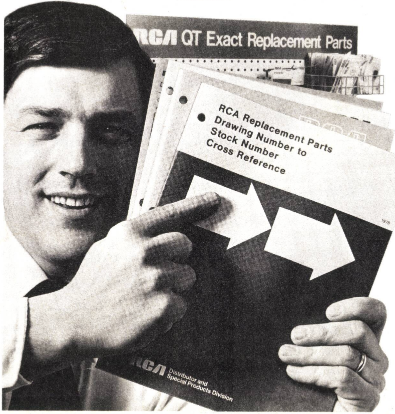
RCA QT Exact Replacement Parts
RCA Replacement Parts Drawing Number to Stock Number Cross Reference
1978
RCA Distributor and Special Products Division

RCA's QT-150 Parts Program is better than ever! Registered dealers receive four free information mailings per year through RCA's Direct Information Service program.

Quarterly mailings include:
- Complete Dealer Price Book — RCA Consumer Parts • Latest Price Supplement • RCA Drawing Number to Stock Number Cross Reference • Color TV Module Cross Reference • B&W TV Module Cross Reference • Dealer QT Inventory Control Form; and many other useful publications.

To join, contact your RCA Distributor and register as a QT Dealer. You will receive your package of 150 of the most-needed, fastest-moving parts to repair older TV sets. You will also receive your first quarterly information package. Every information mailing will include the latest price publication, plus additional information about RCA Parts required in your servicing business.

Don't forget, your QT Parts inventory program has automated annual drop-ship updating for your convenience. A special QT Parts Rack is also available to save time and space.

Call your RCA Distributor or write to RCA Distributor and Special Products Division, Deptford, N.J. 08096.

RCA QT Parts

The heat dissipation from a soldering iron tip is proportional to surface contact. When soldering or desoldering, touch a little solder to the iron tip first. This gives the iron tip a liquid surface that adheres to the surface of the terminal, increasing heat conduction by increasing surface contact. When the terminal is heated fast, less heat is conducted into the component.

JAMES R. GRANDSTAFF
Oak Park, IL

HAS TV IMPROVED?

In "Looking Ahead", December, 1974, page 4, you mentioned that AT&T promised to improve the audio quality of network TV broadcasting links in two years. However, three years have passed and I see little improvement. Although both TV sets in my home have been modified to reproduce sound through large, wide-range speaker systems, I still hear little sound outside the range of 100 Hz–5 kHz on any network TV show. Sometimes one of our local independent stations comes across with wide-range sound and the results are at times breathtaking. On the other hand, the orchestra on the NBC Tonight Show sounds so thin and miserable they might as well settle for a small combo.

Second, in "New and Timely" (January 1978 issue, page 12) it was mentioned that a NESDA Service Conference predicted a "throw-away" TV set, and also said, "Equipment will last for about five years before obsolescence." I am appalled by these statements, because with the shift from tubes to solid-state, along with the improved dielectric and encapsulating materials in use today, modern electronic equipment should last 20 or more years with proper care. I have seen 10- and 15-year-old transistorized equipment still in use and working as well as it did when it was installed.

Additionally, I was intrigued by Mr. Kubilus' letter ("Letters", January 1978 issue, page 16) regarding the superior serviceability of European radio and TV sets. I suspect one reason for this is that Europeans value their possessions more dearly and therefore expect them to last much longer and be more conducive to repair. American products are often made as cheaply and expediently as possible and are thrown away after only a few years' use.

MICHAEL KILEY
Palos Heights, IL

CLEANER DISSOLVES POLYSTYRENE

I feel that a few words of common sense are in order concerning GC's *Liqui-Cleen* silicone contact cleaner featured in the Equipment Report in the February 1978 issue.

Having worked in electronics parts sales in Honolulu, let me say that GC chemicals are popular with the military, industry, technicians and myself.

The article identifies the cleaner as 1,1,1, trichloroethane, which I have used in its pure state. I can tell you right now is definitely *will* dissolve polystyrene-type foam and plastics into solution (a particular need of mine), so it isn't entirely harmless to all plastics. Even in GC's popular *Spray-*

continued on page 22

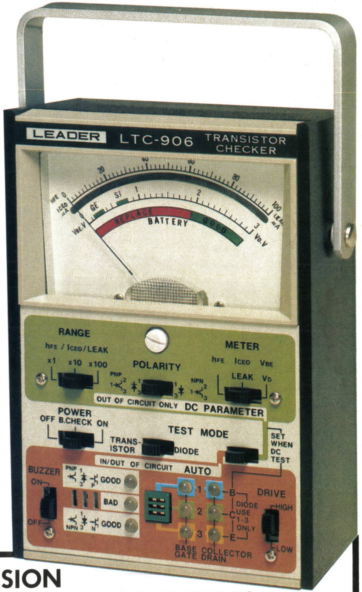

PRECISION SEMICONDUCTOR TESTING *AUTOMATICALLY* with LTC-906 by LEADER Instruments Corp.

Lights Up. Sounds Off. Measures. Identifies. Displays.

- A multipurpose, portable, transistor checker automatically better for laboratory, shop and school.
- Checks transistors, FETs, diodes, good or bad & in or out of circuit.
- Automatically tests a broad range of parameters with simple, program on-off switches — no confusing buttons or lead changes.
- Automatically identifies Germanium or Silicon, plus emitter base and collector.
- LED display plus audible tone indicates defective or good performance.
- Absolute meter readout of DC parameters.

SPECIAL INTRODUCTORY OFFER
NORMAL PRICE $159.95
$144.95
SPECIAL PRICE
OFFER EXPIRES AUG. 31, 1978
VISA master charge BANKAMERICARD

Automatic Mode	
Test Voltage	±2V, 10% duty cycle.
Test Current	4.5mA in LOW drive. 60mA max. in HIGH drive (short term).
Scanning Rate	0.1Sec per test, complete scan in 1 second.
Display	LED indicators Audible tone (may be silenced).
Automatic Check (in/out of circuit)	Good/Bad. Device polarity. Lead indication of transistor, FET, diode and other semiconductor devices. Identification by LED display.
Transistor Good/Bad Tests (out of circuit)	Good indicated by "good" LED and audible tone. "Good" light also indicates device polarity, NPN, PNP, N-Channel. "Bad" indicated by red LED, no audible sound.
Automatic Mode	*cont'd*
Electrode Identification Other Devices	Diodes; cathode and anode "good" light automatically illuminates. UJT's; "good" light illuminates for base material type; base gate light illuminates for emitter electrodes. SCR's; testing similar to transistors — NPN, PNP types flash "good" light.
Diode Good/Bad Tests (in/out of circuit)	"Good" light flashes rapidly, audible tone. Bad diode indicated by "bad" light — and lack of sound.
Transistor Electrode Identification	Absolute for base or gate electrodes; collector electrodes of most bipolar transistors; drain electrodes for MOSFET's
D.C. Parameter Mode	
Leakage Current (out of circuit)	Meter display. Full scale range: 100mA, 1000mA, for reverse diode current and Icbo/Iceo of transistor.
Gain (out of circuit)	Meter display of hFE range; X1, X10, X100 for a max. of 10,000.
V_{be} and V_d	0-3V full scale, ±6%. Test current, 2mA.
I_{ceo} and Leak	0-100, 0-1000, and 0-10,000μA full scale in 3 ranges, ±6%. Test voltage ±5V max.
h_{FE}	Base current 1μA. Collector current 30mA maximum. Test voltage ±5V max.
Power Supply	Internal: 9 Volt flat transistor battery required. External: 8 to 10 Volt DC supply, 25mA minimum.
Size & Weight	4⅜" W x 6" H x 2⅜" D; Approx. 1 lb.

212-687-2224 THE TEST EQUIPMENT SPECIALISTS

TOLL FREE HOT LINE
800-223-0474
54 West 45 Street, New York, N.Y. 10036

ADVANCE ELECTRONICS

More that's new, exciting, and unique...

New Nostalgic, Whisper-Quiet Cooling

Our Casablanca® Fan Kit adds just the right touch to home, porch, or patio – cuts cooling costs too! It operates for pennies a day, is finished in baked bronze enamel, and features 52-inch simulated wood grain blades. For more charm add the optional Globe Lamp. Accessory Swag Chain Mounting Kit also available. **Only $99.95.**

New The fantastic – "Cointrack" Metal Locator

Designed with the "coin-shooter" in mind, this kit features discrimination so incredibly good you'll be finding "treasure" in areas where high "junk" content makes operation with other locators all but impossible! Features a search coil optimized for coin shooting, pushbutton tuning for maximum sensitiviy–effortlessly. Search head is waterproof so you'll never be out of the action! Runs on 6 AA cells (not supplied) or from an optional accessory rechargeable battery pack. **Only $149.95.**

Exciting! A Timely Starter Kit – for You.

Handsome Wood Grain Cabinet

Super accuracy in a highly reliable timepiece. The GC-1107 displays time in a 12 or 24 hour format and even has a snooze control for the sleepy-head! **Only $27.95.**

Optional Deluxe Timing Light with distributor advance meter!

New A professional Ignition Analyzer for the Hobbyist

Designed for the auto hobbyist yet perfect for the professional, the Heath CO-2600 Kit provides the features you want in a quality ignition analyzer! A big 12" CRT displays rock steady parade and super-impose patterns, it's switch selectable for 4, 6, or 8 cylinder use, has a dual range voltmeter, and features individual cylinder selection for carburetor balancing and cylinder analysis. Includes adaptor for GM HEI systems and works with standard, transistorized or C-D ignition systems.
Analyzer, only $399.95. Timing Light, only $47.95.

Unique! The Dieter's Ultimate Weapon

Easily 4 to 5 times more accurate than conventional scales, the GD-1186 Kit boasts precision electronics, displays your weight to the tenths of a pound, has 300 lb. capacity, and runs on batteries so it's totally safe to use – even after you shower! **Only $99.95.**

Your Key To Tomorrow!

Heath self-instruction courses provide frame and foundation for your future in electronics. Learn everything from the principles of DC and AC electronics to microprocessor interfacing and programming. The texts provided use proven "programmed" instruction methods along with audio records (or optional cassettes) to reinforce text material. Component parts are included with each course for "hands-on" experience using optional electronic trainers. These Heath courses let you learn electronics at your own pace and at lowest cost!

See the latest – from fans to floppies...in the NEW FREE Heathkit Catalog! Send for it.

CIRCLE 100 ON FREE INFORMATION CARD

in your FREE Heathkit Catalog!

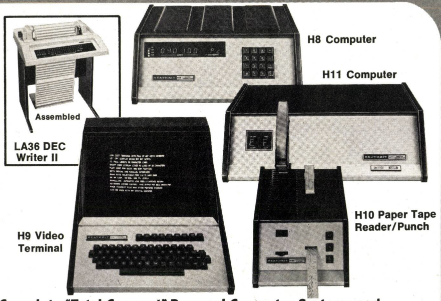

Complete "Total Concept" Personal Computer Systems and Systems Software: Economy, power and service backup from a single source!

Heathkit Computers and System Software are designed for complete continuity from top to bottom. **The 8080A based H8 computer** is a good example. It features a front panel ROM monitor program readout, 8-bit operation, a heavy duty power supply and a host of other user benefits. Like all Heathkit Computers, it's easily expanded. Includes BASIC, assembler, editor and debug software for only $375.

Our most sophisticated computer, the H11, utilizes the famous DEC LSI-11 CPU for 16-bit operation. Has a 4096 x 16 read/write MOS semiconductor memory and 38 high speed data, address, control and synchronization lines. Executes and includes the powerful 400+PDP-11/40 instruction set. It also includes a complete software package for only $1295.

Heathkit Peripheral Devices follow the same total concept philosophy. **Our H9 12" CRT ASCII Video Terminal** has all standard serial interfaces, auto scrolling, erase mode, long and short form and plot mode displays and ASCII 67-key keyboard for just $530. **If you need hard copy, the LA36 DEC Writer II** is perfect. Fully compatible with the H8 and H11, this incredible terminal has a 7 x 7 dot matrix print head, selectable 10, 15 and 30 CPS print speeds, half or full duplex operation and much more for a low $1495. **Our low cost mass storage peripheral is the H10 Paper Tape Reader/Punch.** Precise ratchet/solenoid drive, 50 CPS max read rate, 10 CPS max punch rate and the features of similar units that cost far more than $350.

FREE!

HEATHKIT CATALOG! SEND FOR YOUR COPY TODAY—OR VISIT YOUR HEATHKIT ELECTRONIC CENTER!

Mail Coupon Today

or bring it in person to any of the 50 Heathkit Electronic Centers (Units of Schlumberger Products Corporation) listed at right, where Heathkit products are displayed, sold, and serviced. (Retail prices on some products may be slightly higher.) Prices quoted above are mail order net F.O.B. Benton Harbor, Michigan. Prices and specifications subject to change without notice.

Heath Company, Dept. 020-410
Benton Harbor, Mi. 49022

HEATH
Schlumberger

Heath Company, Dept. 020-410
Benton Harbor, Mi. 49022

Please send me my FREE catalog.
I am not on your mailing list.

Name ____________________

Address ____________________

City ____________________ State ____________

Zip ____________

GX-347

Send the coupon or visit the Heathkit Electronic Center nearest you today!

Units of Schlumberger Products Corporation. Retail prices on some products may be slightly higher.

ARIZONA — Phoenix, 2727 W. Indian School Rd. (602) 279-6247.

CALIFORNIA — Anaheim, 330 E. Ball Rd. (714) 776-9420; **El Cerrito,** 6000 Potrero Ave. (415) 236-8870; **Los Angeles,** 2309 S. Flower St. (213) 749-0261; **Pomona,** 1555 Orange Grove Ave. N. (714) 623-3543; **Redwood City,** 2001 Middlefield Rd. (415) 365-8155; **Sacramento,** 1860 Fulton Ave. (916) 486-1575; **San Diego (La Mesa),** 8363 Center Dr. (714) 461-0110; **San Jose (Campbell),** 2350 S. Bascom Ave. (408) 377-8920; **Woodland Hills,** 22504 Ventura Blvd. (213) 883-0531.

COLORADO — Denver, 5940 W. 38th Ave. (303) 422-3408.

CONNECTICUT — Hartford (Avon), 395 W. Main St. (Rte. 44) (203) 678-0323.

FLORIDA — Miami (Hialeah), 4705 W. 16th Ave. (305) 823-2280; **Tampa,** 4019 West Hillsborough Ave. (813) 386-2541.

GEORGIA — Atlanta, 5285 Roswell Rd. (404) 252-4341.

ILLINOIS — Chicago, 3462-66 W. Devon Ave. (312) 583-3920; **Chicago (Downers Grove),** 224 Ogden Ave. (312) 852-1304.

INDIANA — Indianapolis, 2112 E. 62nd St. (317) 257-4321.

KANSAS — Kansas City (Mission), 5960 Lamar Ave. (913) 362-4486.

KENTUCKY — Louisville, 12401 Shelbyville Rd. (50) 245-7811.

LOUISIANA — New Orleans (Kenner), 1900 Veterans Memorial Hwy. (504) 722-6321.

MARYLAND — Baltimore, 1713 E. Joppa Rd. (301) 661-4446; **Rockville,** 5542 Nicholson Lane (301) 881-5420.

MASSACHUSETTS — Boston (Peabody), 242 Andover St. (617) 531-9330; **Boston (Wellesley),** 165 Worcester Ave. (Rte. 9 just west of Rt. 128) (617) 237-1510.

MICHIGAN — Detroit, 18645 W. Eight Mile Rd. (313) 535-6480; **E. Detroit,** 18149 E. Eight Mile Rd. (313) 772-0416.

MINNESOTA — Minneapolis (Hopkins), 101 Shady Oak Rd. (612) 938-6371.

MISSOURI — St. Louis (Bridgeton), 3794 McKelvey Rd. (314) 291-1850.

NEBRASKA — Omaha, 9207 Maple St. (402) 391-2071.

NEW JERSEY — Fair Lawn, 35-07 Broadway (Rte. 4) (201) 791-6935; **Ocean,** 1013 State Hwy. 35 (201) 775-1231.

NEW YORK — Buffalo (Amherst), 3476 Sheridan Dr. (716) 835-3090; **Jericho, Long Island,** 15 Jericho Turnpike (516) 334-8181; **Rochester,** 937 Jefferson Rd. (716) 244-5470; **White Plains (North White Plains),** 7 Reservoir Rd. (914) 761-7690.

OHIO — Cincinnati (Woodlawn), 10133 Springfield Pike (513) 771-8850; **Cleveland,** 5444 Pearl Rd. (216) 886-2590; **Columbus,** 2500 Morse Rd. (614) 475-7200; **Toledo,** 48 S. Byrne Rd. (419) 537-1887.

PENNSYLVANIA — Philadelphia, 6318 Roosevelt Blvd. (215) 288-0180; **Frazer (Chester Co.),** 630 Lancaster Pike (Rt. 30) (215) 647-5555; **Pittsburgh,** 3482 Wm. Penn Hwy. (412) 824-3564.

RHODE ISLAND — Providence (Warwick), 558 Greenwich Ave. (401) 738-5150.

TEXAS — Dallas, 2715 Ross Ave. (214) 826-4053; **Houston,** 3705 Westheimer (713) 623-2090.

VIRGINIA — Alexandria, 6201 Richmond Hwy. (703) 765-5515; **Norfolk (Virginia Beach),** 1055 Independence Blvd. (804) 480-0997.

WASHINGTON — Seattle, 2221 Third Ave. (206) 682-2172.

WISCONSIN — Milwaukee, 5215 W. Fond du Lac (414) 873-8250.

CIRCLE 100 ON FREE INFORMATION CARD

LETTERS

continued from page 17

Kleen, 1,1,1 trichloroethane is found in weaker solution, yet GC cautions that it shouldn't be used on polystyrenes, e.g., cheap switches, some plastic cases and, especially, clear plastic dial covers for transistor radios. For truly component-safe, clean-and-be-gone work, I use GC's audio/video tape head cleaner spray on my bench.

GARY S. VIVEIROS
Honolulu, HI

AMERICAN VS. EUROPEAN TV's

Having just spent three years in West Berlin, I can say Edward M. Kubilus' seven points on European TV's are quite accurate (see "Letters," January, 1978).

However, I would like to continue the discussion a bit further. For those of you who have had the opportunity to view German color television, did you ever stop and make an objective comparison between a "typical" color TV presentation in Germany and one in the U.S.? If you did, I'm sure you noticed quite a difference. The colors all seemed brighter. The picture had better contrast and focus and was, overall, just sharper.

After a little research, you found that the German overall signal bandwidth is 5.5 MHz as opposed to our 4.5 MHz bandwidth. They have 625 lines per frame, we have 525 lines per frame. One might ask, what does this do for me? Compare the pictures again and the answer becomes immediately obvious.

And the differences did not stop with the picture. Did you look at the TV's physical appearance? What happened to all the external color controls? Didn't find any, did you? The Germans use a color TV transmission system called PAL. Through this system, the TV station controls the color on each and every TV set. This is done by transmitting a color control signal in addition to the normal video and sound information. And it works!

I guess the point to this discussion is to make the American public aware of the way things really are. I wholeheartedly agree with the editorial response to Mr. Kubilus' letter. I believe the TV industry is taking the American consumer for a long and profitable ride, and Mr. American Consumer doesn't know or doesn't care!

GERALD W. GLAVE
San Jose, CA

MAGNETIC SEMICONDUCTOR

If we ever find a "magnetic semiconductor" such as the one suggested by Andrew Fraser in his October 1977 letter, we can replace his iron block with an inductor and use another screen and magnet on the opposite side. By alternately screening magnets of opposite polarity from a centered coil we then have a solid-state AC generator.

SCOTT C. COBAIN
Woodbridge, VA

CHANGE IN FORMULA

With respect to the article, "10-Function Digital Clock," by Jeffrey G. Mazur in the August 1977 issue, I would like to suggest a small change in the formula for calculating R_L in the relay circuit of Fig. 4.

In this circuit, R_L in series with the relay is calculated in the following manner:

$$R_L = \frac{12}{I_{RELAY}} - R_{RELAY}$$

This value of R_L gives just enough current in the circuit for which the relay is designed. Hence, the relay is used without any safety margin—to cover the variations in relay performance due to handling and usage as well as variations of circuit current due to voltage and resistance variations (both relay and external resistances). Therefore, the working of the relay is unreliable.

Normally, in relay circuits, circuit current is taken as one and a half to two times the operating or pickup current of the relay, providing adequate safety margin between the pickup and circuit currents. In view of this, I have altered the formula for calculating R_L as

$$R_L = \frac{12}{1.5 \text{ to } 2 \times I_{RELAY}} - R_{RELAY}$$

This reduces the value of R_L, making the working of the relay in the circuit reliable. If the value of R_L turns out to be very small or negative, then it is not required in the circuit. In such a case, a relay having a pickup current of approximately one-half of the circuit current must be selected.

R. GOPALA RAO
Bangalore, India

R-E

Only The ORIGINAL Gives You All Three

1—The name that distinguishes the GENUINE from the others.
2—Smooth working, machined, undercut mating parts. Powerful non-slip leverage. A patented CHANNELLOCK advantage.
3—Reinforcing flange practically eliminates stress breakage. Another patented CHANNELLOCK advantage.

No other plier does so many jobs so well as a genuine CHANNELLOCK tongue'n-groover. Be sure you get the real thing. Look for the trademark on the handle. Sizes from midget 4½" to giant 16"

CHANNELLOCK, INC. • Meadville, Pa. 16335

CHANNELLOCK®
The ORIGINAL Tongue-'N-Groover

Send For Our Free Catalog

CIRCLE 25 ON FREE INFORMATION CARD

INTERFACE AGE

The magazine that brings the computer home.

You want to learn all you can about personal computing. **Interface Age** tells it all. In simple, easy to understand language.

Each issue of **Interface Age** revolves around the latest information in the world of microcomputing. Articles, letters, new products, opinions, humor, experiments and new programs to help you choose and understand your computer and use it to full capacity.

Did you know your personal computer can –

- Help you start a business at home providing services to others.
- Increase your child's educational opportunity.
- Analyze real estate, stock market and other investments.
- Show you how to save money by computing and simplifying income tax & deduction records.
- Inventory your household items, store shopping lists and establish a recipe bank to plan daily meals.
- Control your small business with accounting and inventory control systems.

Technology has brought the computer to your world. **Interface Age** brings it home.

Order your subscription to **Interface Age** NOW with this convenient coupon. Save $7 over newsstand price. **12 Monthly Issues: $14 U.S.; $16 Canada/Mexico; $24 International. 24 Issues: $24 U.S.; $28 Canada/Mexico. 36 Issues: $36 U.S.; $42 Canada/Mexico.**

Name____________________
Address____________________
City__________ State______ Zip______
☐ Visa Card ☐ Master Charge
Acct. No.____________ Exp. Date______
Signature____________________
Check or money order (U.S. Funds drawn on U.S. Bank)
Make checks payable to: **INTERFACE AGE MAGAZINE**
P.O. Box 1234 Dept. RE5 Cerritos, CA 90701
☐ *Please send information on issues available back to 1975.*

equipment report

Triplett Model 100-T Maintenance Kit

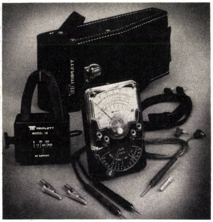

CIRCLE 103 ON FREE INFORMATION CARD

TRIPLETT'S *MODEL 310* "SHIRT-POCKET" VOM has been around for a long time. I've had one for many years that's still going strong. They even made a FETVM version, and now they have released the *model 100-T* maintenance kit that includes the *model 390* VOM, a thermistor probe, the *model 10* clamp-on AC Current Adapter, the *model 101* Line Separator, the *model 311* extension cord set, batteries and instructions. The *model 100-T* is manufactured by the Triplett Corp., Bluffton, OH 45817 and sells for $120.

The *model 390* VOM has all the ranges of the *model 310*: DC voltages on a 0–3-volt scale up to 1200 volts, at 20,000 ohms-per-volt, AC voltages on the same scales at 5000 ohms-per-volt, DC current up to 600 mA and four ohmmeter ranges. Two temperature ranges, one from −50 to +150° F and the other from +50 to +300° F, are included.

The *model 100-T* contains a small thermistor probe with an aluminum shield to protect the thermistor. This shield can be removed for readings requiring surface contact; for example, to read the case temperature of power transistors, the temperature of bearing housings, etc. The probe is calibrated by pressing a button on the probe body and setting the ohms adjust control for zero. This control is a thumbwheel type, mounted on the left side of the case, right under your left thumb. You can use the probe to check air conditioners, refrigerators, furnaces, and ovens, and it can also be used for free air, surface and liquid measurements.

One of the handiest items included in the *model 100-T* is the *model 10* clamp-on AC Current Adapter, which can be plugged into the top end of the VOM case and locked. The whole unit then becomes a clamp-on AC adapter. The VOM is set to the 0–3 VAC range. The selector switch of the *model 10* adapter can be set to read AC current in six ranges, from 0–6 amp up to 0–300 amp. The *model 10* must be clamped around only one wire to read accurately. For times when you can't get at a single wire, the plug-in *model 101* Line Separator, also included, can be used. The clamp is hooked through the ring. It has three ranges—direct, divide-by-10 (giving full-scale reading of 0–600 mA AC) or divide-by-20 for a low range of 0–300 mA AC. For tight spots in breaker-boxes where even the little VOM can't go, an extension cord, the *model 311*, also included, may be used. This is 42 inches long. Then only the *model 10* is pushed into place to read the current.

continued on page 26

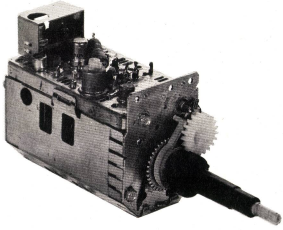

The Best of Everything Has Its Price

Even tuner service. From the beginning our goal has been to provide the best tuner service, not the cheapest. The extra dollar you might pay at PTS is peanuts when you consider the reliability and standards of excellence we apply to every job. Thousands of PTS customers must agree or we wouldn't be the world's largest tuner service company.

See The Yellow Pages For The PTS Servicenter Nearest You Or Contact:

PTS ELECTRONICS, INC.
P.O. BOX 272 BLOOMINGTON, IN 47401 812-824-9331

CIRCLE 88 ON FREE INFORMATION CARD

NTS trains you on tomorrow's equipment. Today.

Microcomputers, digital systems and more... from the first name in home study.

Now NTS training programs include an even wider choice of solid-state digital equipment than ever before offered in any electronic home study course. Advanced NTS/Heath digital color TV (25" diagonal with optional programming capability), NTS/Heath digital computer, digital test equipment, digital stereo receiver (70 watts per channel) plus much more state-of-the-art equipment to make your training exciting and relevant. Learn servicing and maintenance easily with step-by-step Project Method lessons and kits.

An all-new full color catalog shows you exactly what each of the fourteen courses cover, and every piece of equipment you receive.

Send for it today and see for yourself what's really happening in electronics training technology at NTS. It's free. Just send the coupon.

NO OBLIGATION. NO SALESMAN WILL CALL.
APPROVED FOR VETERAN TRAINING.

NATIONAL TECHNICAL SCHOOLS
TECHNICAL-TRADE TRAINING SINCE 1905
Resident and Home-Study Schools
4000 South Figueroa St., Los Angeles, Calif. 90037

NATIONAL TECHNICAL SCHOOLS Dept. 206-058
4000 South Figueroa Street, Los Angeles, California 90037

Please send FREE Color Catalog and Sample Lesson.

- ☐ **Color TV Servicing**
- ☐ **B & W TV and Radio Servicing**
- ☐ **FCC License Course**
- ☐ **Electronic Communications**
- ☐ **Electronics Technology**
- ☐ **Audio Electronics Servicing**
- ☐ **Digital Electronics**
- ☐ **MicroComputers/MicroProcessors**

Name ____________________
Address ____________________
Apartment Number ____________ Age ____________
City ____________________
State ____________________ Zip ____________

☐Check if interested in G.I. Bill information.
☐Check if interested ONLY in classroom training in Los Angeles.

Looking at microprocessor design?
"LOOK" with the right SCOPE...

B&K-PRECISION Model 1474 $999
including probes

B&K-PRECISION 30MHz dual-trace scope

Thirty-MHz bandwidth and signal delay line make the B&K-PRECISION Model 1474 ideally suited for developing µP and related interface circuits. Short duration pulses that are unviewable on conventional lab scopes are clearly visible on the 1474.

☐ Built-in signal delay line permits view of leading edge of high-frequency pulse rise times.

☐ Rise time 11.7nS or less

☐ Triggers beyond 50MHz. Typical response is less than −6dB at 49MHz.

☐ 5mV/cm vertical sensitivity

☐ PDA CRT with P31 phosphor

☐ Algebraic addition and subtraction of CH. A and CH. B displays

☐ Built-in high- and low-pass filters

☐ Most cost-effective 30MHz scope available

Available from your distributor.

B+K PRECISION
DYNASCAN CORPORATION
6460 West Cortland Street
Chicago, Illinois 60635 • 312/889-9087
In Canada: Atlas Electronics, Ontario
Intl. Sls: Empire Exp., 270 Newtown Rd., Plainview, L.I., NY 11803

CIRCLE 73 ON FREE INFORMATION CARD

EQUIPMENT REPORT
continued from page 24

The *model 390* VOM uses two batteries, a 1.5-volt unit for all ohms ranges except the 1K range, which uses a 15-volt battery. The low ohms ranges are protected by a 1/16-amp fuse located under the 1.5-volt battery. The batteries are easily accessible by removing a small plate on the back of the case.

A leather carrying case, *model 379*, is available. **R-E**

RCA VIP Computer Kit

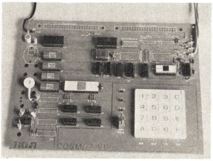

CIRCLE 104 ON FREE INFORMATION CARD

THE RCA *V*IDEO *I*NTERFACE *P*ROCESSOR IS A hobbyist microcomputer with a graphic video output. As soon as it is assembled and operational, you become acquainted with the system by loading and running an assortment of video games, including "Kaleidoscope" and (my favorite) "Armored Vehicle Clash." After you gain this initial familiarity and have some fun, you can graduate to writing 1802 machine language and CHIP-8 programs.

The VIP is constructed on a single 8½ × 11-inch PC board that holds the CDP1802 microprocessor, 2048 words of user RAM, a 512-word ROM-based operating system, a 3.521280-MHz crystal oscillator, a video display generator IC, a cassette recorder interface and various system related IC's. A 5-volt, 600-mA power-supply module is part of the package. On-board memory can be increased to 4096 words (a higher current supply may be needed), and parallel I/O ports can be added by filling wired, empty IC positions. Standard 44-pin connectors can be used to expand up to 32,000 memory bytes, and beyond the 19-line on-board I/O limitation.

Programs, data and system control commands are entered through a 16-key hexadecimal keypad. Depressing a key switch on the keyboard operates the Q light, affects the on-screen display and generates an audio tone (the speaker is not included). The uppermost 256-byte portion of memory is displayed in a format that is 64 bits horizontal by 32 bits vertical. The video output is monochrome and noninterlaced, and must be connected to a video monitor, the video circuits of a TV receiver, or an external RF modulator for hookup to a TV antenna terminals. User programs are started at address 0000 by flipping the reset toggle switch from RES to RUN. To access the 512-word operating system at address 8000, key C is held while the reset switch is flipped.

The operating system has four functions—memory write, memory read, tape write and tape read. When memory contents are entered and checked, the address and contents are displayed simultaneously at the bottom of the TV screen, so you can keep track of what you are doing. The video format can be expanded to 64 × 64 bits or 64 × 128 bits for higher resolution by writing your own video refresh interrupt routine in machine language. Video format expansion uses more memory for the display (512 bytes or 1024 bytes). Using the video display slows down the processor because of the time it spends translating memory contents into a video display pattern. The operating system saves the processor registers on the last page of memory for debugging programs.

The CHIP-8 interpreter is a 512-byte program that you must load manually, or from tape, into locations 0–01FF. CHIP-8 user programs, such as games, are then loaded starting at 0200. The language is a series of 31 two-byte instructions that let you control up to 15 variables, run a timer, display patterns, generate a variable-duration audio-output tone, convert binary to decimal, obtain random numbers and perform skips and subroutine jumps. You can create all kinds of static and moving displays with relatively few instructions. The CHIP-8 interpreter should be stored on cassette tape to save reloading and checking each time you want to use it.

A VIP operating manual, the MPM-201 1802 microprocessor manual, and data sheets describing the ROM, video display IC and 1802 microprocessor are included. The VIP manual includes all the details, but a beginning computer hobbyist will find a reference book or two helpful. Twenty video games are listed, plus some short "getting-started" programs.

Kit assembly requires good soldering technique since a single short between the necessarily close PC traces keeps the unit from creating its pretty pictures. While the VIP is basically designed to be used for fun, it can be expanded to perform useful control and calculation work.

After I resolved a couple of self-inflicted assembly errors, the system performed flawlessly. Programing mistakes did have the annoying habit of wiping out CHIP-8, but shifting to the tape cassette mode of operation made recovery easy. I used both an inexpensive time-worn audio cassette recorder and a better-grade Heathkit tape deck. The tape deck loaded programs successively nine times out of 10, but the less expensive recorder performed only once out of every three times.

The *model CDP18S022 VIP Kit* is priced at $275. An order form is available from RCA Solid State Division, Box 3200, Somerville, NJ 08876. **R-E**

Redco Model FM-30 Frequency Monitor

CIRCLE 105 ON FREE INFORMATION CARD

THE RELIABLE ELECTRONICS DESIGN COMPANY, 11823 Slauson, Santa Fe Springs, CA 90670, manufacturers of frequency counters for communications and amateur work, as well as CB accessories, such as preamps and speech processors, has developed the *model FM-30* frequency-monitor counter with a range of 1.0 MHz to 40 MHz. This low-cost unit (sug-

continued on page 28

AUTOCOMP

The GAS SAVER!

ELECTRONIC MICROPROCESSOR COMPUTES TRUE MPG AS YOU DRIVE.

AN IMPORTANT AUTOMOTIVE BREAKTHROUGH!

Microprocessors, the electronic devices of the future, assist our daily living in a multitude of ways. This advanced technology has now been combined with SpaceKom-AUTOCOMP's exclusive fuel and flow sensors, to provide an important automotive breakthrough. The AUTOCOMP mounts in or on your dash, and by pushbutton control provides LED readouts of the following driving functions: Instantaneous MPG, Average MPG, Fuel Used, Distance Traveled, and Correct Time. With this valuable data at your fingertips, you can drive your vehicle more efficiently and derive the following important benefits:

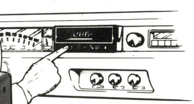

REDUCE YOUR FUEL COSTS

By monitoring fuel consumption you can improve your driving habits and significantly cut fuel bills. You will know precisely how changes in acceleration, speed, wind, weight, hills, etc., are affecting fuel economy. AUTOCOMP gives you a true and continuously updating readout of Instantaneous MPG as you drive, allowing you to adjust your driving for safer and more economical conditions on a minute by minute basis. By alerting you when fuel consumption increases, AUTOCOMP can easily save enough money to pay for itself in the first year it is installed!

MONITOR YOUR ENGINE'S PERFORMANCE

AUTOCOMP's Average MPG feature lets you monitor fuel consumption on a day by day or week by week basis. You can tell when your engine is causing you to burn extra gas by not running at peak performance. This information cues you when it's time for a tuneup, and helps you avoid the costly repairs of a major breakdown.

ENHANCE THE VALUE OF YOUR VEHICLE

AUTOCOMP is a modern electronic instrument which will give your dash the look and functionality of a true instrument panel. Its microcircuit electronic design will provide trouble-free operation to enhance the beauty and value of your vehicle for as long as you drive it.

ADD EXCITEMENT TO YOUR DRIVING

AUTOCOMP is today's most exciting automotive accessory. In addition to saving you money and giving you greater command of your driving, AUTOCOMP will enhance your driving fun and pleasure. Checking the readout of its various functions as you drive is a sure-fire method of breaking up the monotony of long trips.

Just press the buttons! AUTOCOMP instantly flashes the requested information in a bright red LED readout!

FUEL USED 12.9

When the FUEL button is depressed, the display indicates the amount of fuel the vehicle has used since last fill-up, beginning of trip, or last reset (up to 1000 gallons).

DISTANCE TRAVELED 85.2

When the DIST button is depressed, the display indicates the distance the vehicle has traveled since the last reset (up to 1000 miles).

INSTANTANEOUS MILES/GALLON 23.7

When the INST MPG button is depressed, the display indicates how many miles per gallon the vehicle is attaining at each moment (up to 200 mpg).

AVERAGE MILES/GALLON 20.9

When the AVE MPG button is depressed, the display indicates the average miles per gallon the vehicle has attained since the last reset (up to 200 mpg).

TIME 11.26

When the TIME button is depressed, the display indicates the correct time (in hours and minutes). The clock may instead be used to display ELAPSED TIME.

INSTALL AUTOCOMP YOURSELF!

*AUTOCOMP can be installed on most American and Japanese make autos and vans except those with fuel injection. Because of their non-standard speedometer gears, AUTOCOMP is **not** recommended for European imports. Complete step-by-step illustrated instructions make AUTOCOMP a most rewarding fun experience for the do-it-yourselfer. Equipment supplied include the Speedsensor which simply screws onto the speedometer cable and digital Flowsensor which easily installs onto the fuel line. Free consultation is offered by mail or telephone if any problems are encountered. Installation by an independent mechanic will of course add to the cost. No responsibility for any additional costs can be accepted by SpaceKom-AUTOCOMP.

SPECIFICATIONS:

Fuel Used: ±5% typical
Distance: ±2%
Avg. MPG: ±5%
Inst. MPG: ±5%
Clock: 1 Min./Mo. typical
Size: 3¼"Hx6"Wx1½"

AUTOCOMP®

PRICED AT JUST $129^50

FOR ORDERS ONLY

CALL TOLL FREE ANYTIME!

1-800-423-2355 Ext. 601
In California 1-800-232-2175 Ext. 601
For more information call 805-965-1015

GUARANTEE

AUTOCOMP is covered by a 1 year Manufacturers Limited Warranty. A copy of this warranty may be obtained free of charge by writing SpaceKom-AUTOCOMP.

SPACEKOM-AUTOCOMP
212 E. Gutierrez Street
Santa Barbara, CA 93101

Please send me _______ AUTOCOMP(s) at $129.50 each. (California residents must add 6% sales tax.)

Car on which AUTOCOMP will be installed* ____________________
Make Model Year

Factory Cruise Control? ☐ Yes ☐ No

Total enclosed (Cal. res. add tax) $ ____________________

USE YOUR CHARGE CARD!
☐ BankAmericard (VISA)
☐ Master Charge (Interbank #____________________)

Charge #____________________

Signature ____________________ Exp. Date ________

PRINT NAME____________________

ADDRESS ____________________

CITY ____________________

STATE ____________________ ZIP ________

CIRCLE 1 ON FREE INFORMATION CARD

You can be sure

more times in more circuits in more places than with any other multimeters on the market today

Each Sencore DVM is backed with 15 Megohm input impedance for one third less circuit loading on every measurement. That means 50% higher accuracy than other DVMs.

DVM38 **$395**

3½ DIGIT .1% DCV ACCURACY AUTO-RANGING DVM

A "prime" standard at your fingertips for measurements you can trust. Auto-ranging for extended low-level range and ease of operation. 15 Megohm input impedance assures .1% reading accuracy is maintained in solid state circuits. Highly sensitive, yet fully protected to 2000 VDC overloads. Hi-Lo Power Ohms circuit simplifies in-circuit resistance measurements.

DVM37 New **$268**

3½ DIGIT .1% DCV ACCURACY PORTABLE DVM

Prime standard .1% accuracy on the bench or in the field for less than $250. The DVM37 is the most accurate portable DVM you can buy, with 15 Megohm input impedance for 50% more accuracy. Includes automatic features—Auto Zero, Polarity, Decimal, Overrange. Fully protected inside to over 2000V on all functions, including Ohms, and protected outside with super-rugged case. Full ranges for every test. Fingertip "Push-On" switch in probe saves batteries as power is applied only when needed.

DVM32 **$225**

3½ DIGIT .5% DCV ACCURACY PORTABLE DIGITAL MULTIMETER

Bench and field master for digital accuracy measurements anywhere. 0.5% DCV accuracy, backed with 15 Megohm input impedance. Exclusive battery-saving Auto-Display turns the display on automatically when you make a measurement. 2000V input protection on all functions and ranges—including Ohms.

DVM36 **$158**

3½ DIGIT .5% DCV ACCURACY POCKET PORTABLE DVM

Pocket portable lab accurate performance that fits every budget with highest performance-to-price benefits of any meter. .5% DCV accuracy, backed with 15 Megohm input impedance for lowest circuit loading. Full protection to 1000 V on all functions and ranges—including ohms. Drop-proof case. Battery-saving "Push On" button in probe.

DVM35 **$134**

3 DIGIT 1% DCV ACCURACY POCKET PORTABLE DVM

Fast, direct reading digital accuracy for the man on the go. Same features as DVM36, except 3-digit, 1% DCV accuracy, backed by 15 Megohm input impedance that is ten times more accurate than analog meters.

New **DVM37**

DVM38

BACKED BY SENCORE'S 100% MADE RIGHT LIFETIME GUARANTEE

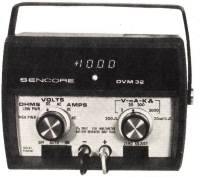

DVM32

DVM36

In stock at your favorite local Sencore Full Line Distributor.

SENCORE
DIGITAL MULTIMETER SPECIALISTS
3200 SENCORE DRIVE, SIOUX FALLS, SD 57107 (605) 339-0100

CIRCLE 17 ON FREE INFORMATION CARD

EQUIPMENT REPORT
continued from page 26

gested retail price, $99.95) uses a through-line circuit for continuous monitoring of any low-band frequency, especially CB frequencies. It measures only 4 inches wide, 1.25 inches high and 6 inches deep, making it easy for top-of-dash or console mounting.

The 5-digit readout has ½-inch-high, easy-to-read LED digits. A selector switch on the panel lets you read the CB channel frequency in MHz, and three places to the right in the 1-kHz position. Setting the switch to the 0.1-kHz position allows you to read to 100 Hz. The placement of the decimal point is automatic. The meter sensitivity is less than 1.0 watt, and is rated as being able to handle up to 1000 watts PEP without damage.

The all solid-state circuitry uses standard TTL logic, with a crystal-controlled clock oscillator for greater stability. The basic *model FM-30* operates at any DC voltage between 10.5 and 16. It has built-in reverse-polarity protection and can be used with either positive or negative ground electrical systems. A cigarette-lighter plug is provided for quick installation or removal.

The display reacts quickly, almost instantaneously, when changing channels. It is used in a through-line hookup. Two SO-239 connectors on the rear panel are provided so the unit can be hooked up quickly. The *model FM-30* can be used with base stations, using the optional AC/DC power supply available.

We checked the unit out on a couple of CB sets, and the results agreed with those of our lab standards. Instrument stability is good, and the display is steady. Two-way radio technicians, or the dedicated CB'er who likes to know whether he's right on-channel or not, will find the *model FM-30* a useful item for troubleshooting sets using frequency synthesizers! **R-E**

B&K-Precision Model 2810 Digital Multimeter

THE B&K-PRECISION COMPANY HAS DEVELOPED a new 3.5-digit DMM, the *model 2810*. This instrument is a true multimeter that reads AC and DC voltage, current and resistance. It has all the handy features: automatic zeroing, automatic polarity indication, as well as some special features that make it even more useful in a variety of electronic measurement applications.

The *model 2810* has a 10-megohm input impedance on all voltage ranges. AC and DC voltages are read on the same 1–10 scales. Both voltage scales start at 0–100 mV and go up to 1000 volts in five ranges. There is 100% overrange capability on all ranges except for the 1000-volt ranges. This means that you can set the meter to the 10-volt range and read any voltage up to 19.99 before changing ranges. Voltages greater than 19.99 will show a blinking LED readout of 1999. This blinking readout also represents the infinity or open-circuit readout for all ohms ranges.

AC and DC currents share the basic ranges—from 1.0 mA full-scale to 1000 mA or 1.0 amp. For DC readings, the polarity indicator shows which way the current flows. Once again, there is 100% overrange capability for all but the top range.

There are seven resistance ranges, one of which is special. First, there is a 0–10-ohm

continued on page 30

EDMUND SCIENTIFIC

ELECTRONIC DIGITAL RAIN GAUGE

• Never Needs Emptying

Remotely measure rainfall in the comfort of your home in tenths of inches (up to 999.9"). Gives total rainfall count for hr., day, wk., etc. Push reset button indoor counter for new period and to empty outside collector. Outdoor collector mounts easily on fence, roof, etc. Incl. 30 ft of waterproof wire. Runs on 9-V trans. radio batt. (not incl.).

No. 72,165EH **$49.95** Ppd.

Deluxe Model (in hundredths to 99.99")

No. 72,319EH **$69.95** Ppd.

GET PROFESSIONAL TIMING ACCURACY WITH LOW-COST LED STOPWATCHES

Used at AAU, NCAA, and the Olympics this two function stopwatch times single segments of events with time in/out delays. Press the button and stopwatch displays time action stopped — then resumes with next button press. Accurate to 1 sec./yr.; bright LED display reads to 59:99.99, runs on disposable batts. (incl.); lanyard; 1-yr. warranty.

No. 1695EH **$39.95** Ppd.

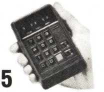

Hand-held electronic digital stopwatch counts up, down, and sounds alarm. Full range (9 hr. 50 min. 59 sec.); bright LED display; matrix keyboard; start/stop reset buttons. Batteries. Size: 2¾x4¼x1$^{1}/_{8}$".

No. 1692EH Ppd. **$59.95**

SAVE OVER 40%

—DELUXE AM/FM WALL RADIO

Great surplus buy saves you over 40% on brand new AM/FM Deluxe Wall Radio w/ handsome silver/black control panel. Mount anywhere den, kitchen, bedroom, office, workshop. Self-cont. Philco-Ford radio chassis (14¼x3$^{13}/_{16}$x3½") w/11 transistors, vol. control, AM/FM hi sensitivity tuner, AFC 2¾" dia. speaker, 7½" 110V AC cord. Orig. cost $30 ea. in 3000 quant. for nat'l. motel chain. Buy several now.

No. 72,275EH (READY TO PLAY!) **$17.50** Ppd.

GET EARLY STORM WARNINGS ON BOTH LAND AND SEA...

SAVE $10

STORMALARM warns you about storms the way a smoke alarm warns you about fire. This sensitive weather radio lets you track tornadoes, hurricanes, severe thunderstorms, and other inclement weather conditions by sounding an alarm. Unlike standard weather radios that must be constantly monitored, STORMALARM monitors itself! Regularly $46.50 you can save $10 by ordering now. Triggered by a signal from the National Weather Service Stations, it sounds a full blast in the event of emergency weather conditions. Also has 3 standard weather channels for detailed reporting. Features 40-50 mile range, continuous beeper alarm, flashing warning light, 2¼" dia. speaker, antenna, external antenna input, 117VAC to 9VDC converter, instr. Size 3x5x1¼"

No. 72,297EH **$36.50** Ppd.

Free Catalog

GIANT MAGNET, LITTLE PRICE!

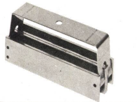

Tie a line to our over-150 lb. lift ceramic magnet and haul up treasure from the sea. 4 ceramic magnets, in series, between steel plates. A 1-lb. "giant"!

No. 42,318EH (1x1¼x4$^{3}/_{8}$")

$11.95 Ppd.

SAVE 50% — 8 x 20 MONOCULAR

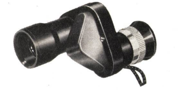

Top-quality Spy Scope, a $30 value, now $14.95! Special purchase saves you 50%. 100% coated optics, 305 ft. field of view. Only 2 oz - stores in pocket, purse, glove box.

No. 1568EH **$14.95** Ppd.

Send for your FREE 164 page Edmund Scientific Catalog with over 4000 bargains

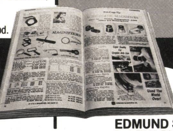

ORDER *FREE CATALOG* HERE

EDMUND SCIENTIFIC CO.
Dept. EH-10, Edscorp Bldg.
Barrington, New Jersey 08007

Send GIANT 164 Page Catalog packed with unusual bargains.

Name______________________
(Please Print)
Address____________________
City_______________________
State____________Zip________

TO ORDER PRODUCTS USE THIS COUPON

EDMUND SCIENTIFIC CO.
Dept. EH-09, Edscorp Bldg.
Barrington, N.J. 08007

☐ Enclosed please find check/M.O.
Charge My ☐ Amer. Exp. ☐ BAC (VISA) ☐ MC
Interbank #________ Acct. #____________
Card #______________ Exp. Date________
Sig. ______________________________

30 DAY GUARANTEE
You must be completely satisfied with any Edmund item or return it within 30 days for a full refund.

☐ **Please send me the following items I have indicated below:**

Stock No.	Qty.	Price
N.J. residents add 5% sales tax.	Handling	$1.00

Name______________________
Address____________________
City__________State__________Zip__________

CIRCLE 31 ON FREE INFORMATION CARD

range (that's the special one), then there are ranges of 0–100, 1K, 10K, 100K, 1000K and 10 megohms. To use the 0–10-ohm range, set both controls to the 10-ohm position. A special zero-adjust control works on this range only.

The 0–10-ohm range is useful for resistance measurements of flyback windings, deflection yoke windings, etc. The normal resistance is shown on many schematics and on all Sams Photofacts schematics. If a winding resistance is given as 7.8 ohms, and you see a reading of only 3 or 4 ohms, there's a good chance that the winding has some shorted turns in it. We ran this test on several flybacks, both good and bad, and it gave us the right answer every time. When you take readings in this area, even the normal slight resistance of the test leads is important. Therefore, just short the test prods and adjust the readout for 0000. This removes the lead resistance, which will be about 0.4 ohm, or so.

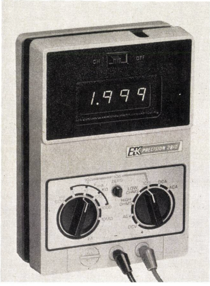

CIRCLE 106 ON FREE INFORMATION CARD

The ohmmeter is dual voltage. The 0–10-ohm range is always low ohms and transmits less than 0.2 volt across semiconductor junctions so that they won't turn on. The highest range (10 megohms) is always high ohms, which delivers a higher voltage. The middle ranges can be switched to either high or low ohms as needed.

The low ohms range is also useful for checking those tiny resistors (3.3 ohms, etc.) found in solid-state circuits. These resistors are critical, since they're generally used in bias circuits and it takes only one-tenth of an ohm or so to throw some circuits way out. Nulling out the contact resistance will let you read the resistors accurately.

The *model 2810* has the accuracy typical of digital meters. It's rated at ±0.5% of reading, or 0.1% of full scale on DC voltages. Similar accuracy is obtained on AC voltages, resistance and current. This feature comes in handy when reading the fractional voltages so common in solid-state sets, especially those using IC's. If a schematic states 5.4 volts is necessary at a given point, this is really meant! Quite often a schematic will show DC voltages that come from *inside* the IC for each pin. This can be a valuable clue to the proper voltage. If these voltages are within a small percentage of normal, the chances are that particular IC is good. If they're off, or missing entirely, and the supply voltage is normal, the IC is apt to be bad. A great many IC voltages such as this will be in the 0–10 range, which is where precision readings are useful.

The *model 2810* is powered by four C-cell dry batteries. Stock dry-cells, alkaline batteries or NiCads can be used. A NiCad recharging unit is available. The jack for the battery charger is already on the case. You can test the battery condition quickly by simply setting the *model 2810* to the 0–10 VDC range, then touching the hot test prod to the charging socket terminal and to a battery-test jack on the other side of the instrument.

All voltage current and resistance ranges are overload-protected. A 2-amp, 3AG fast-blow fuse is conveniently mounted right on the front panel next to the test-lead jacks. A spare fuse and holder come with the instrument. Diode protection against overload is also provided on the current ranges.

The following accessories are available that extend the range of the *model 2810:* A high-voltage probe (*model PR-28*) extends the range to 40 kV DC, and also extends the AC voltage ranges to 20 kV at 60 Hz. There is also a 10-amp current shunt (*model ES-28*). The demodulator probe (*model PR-23*) can read from 15 kHz to 250 MHz, and an isolation-direct probe (*model PR-21*) takes DC voltage readings in circuits with high RF signals.

The 3.5-digit LED readout has 0.3-inch-high, bright red 7-segment digits. The circuitry uses dual-slope integration for greater accuracy and stability. Precision IC-type resistor

continued on page 34

IN ELECTRONICS ok HAS THE LINE...

DIP/IC INSERTION TOOL WITH PIN STRAIGHTENER

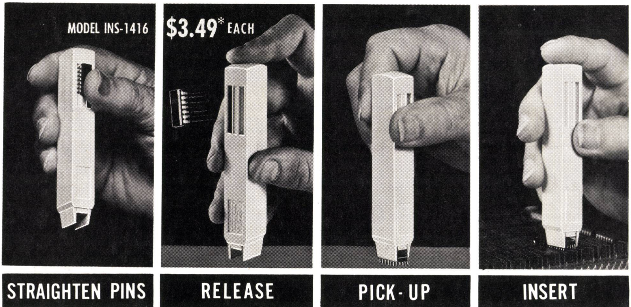

* MINIMUM ORDER $25.00, SHIPPING CHARGE $1.00, N.Y. CITY AND STATE RESIDENTS ADD TAX

OK MACHINE AND TOOL CORPORATION
3455 CONNER STREET, BRONX, NEW YORK, N.Y. 10475 U.S.A.
PHONE (212) 994-6600 TELEX NO. 125091

CIRCLE 51 ON FREE INFORMATION CARD

Keep CB out of your TV.

VITEK FILTERS ARE 100% GUARANTEED TO ELIMINATE CB INTERFERENCE

Chances are you've already tried a CB filter . . . and it didn't work. Vitek has developed a unique, patented filter that is guaranteed to keep CB interference out of any TV set, or your money back.

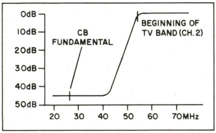

Fig. 1 High-Pass Filter

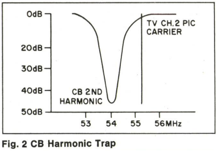

Fig. 2 CB Harmonic Trap

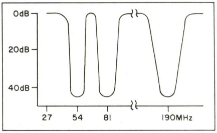

Fig. 3 Harmonic Traps for CB Transceiver

The Vitek filter is actually two units in one. First, it's a high pass filter (Fig. 1) that passes TV but rejects frequencies below 50 MHz. Second (and this is what makes the Vitek unit unique), it is a very stable, sharply tuned trap that keeps CB harmonics out of the TV. (Fig. 2)

Harmonic radiation is a problem because a CB next door can hit your TV set with a signal 1000 times stronger than a TV transmitter 50 miles away. The biggest troublemakers are the second harmonic (54 MHz) and the 3rd harmonic (81 MHz). Only Vitek provides a trap that takes out the harmonics but doesn't interfere with TV reception.

You get a patented trap (tuned to channel 2 or channel 6, whichever is used in your area) *plus* a quality high pass filter for only $10.95, direct from the manufacturer.

GUARANTEED PROTECTION FOR CBs TOO!

If you're a CBer, you'll want a Vitek transceiver trap. It gives you more than 40 dB of extra attenuation of the 2nd, 3rd, and 7th CB harmonics (fig. 3). With a Vitek between your CB and antenna, you're completely free from blame. If your neighbors complain, simply give them one of our "NON-INTERFERENCE CERTIFICATES" (10 supplied with each Vitek unit) and they will realize that any problems they may be having are the result of poor selectivity on their TV sets. It advises them to buy a filter to make up for the deficiencies of the TV set manufacturers. Guaranteed to eliminate harmonic radiation, the Vitek transceiver filter is only $9.95.

FREE BOOKLET

This booklet tells you all you need to know about the causes and cures of CB interference. It's yours to keep, even if you decide to return the filter for a full refund.

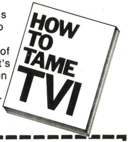

Vitek Electronics, Inc.
200 Wood Ave.
Middlesex, N.J. 08846

Please send me:

___ TV set filters (channel 2 trap) @ $10.95 each. Total ______

___ TV set filters (channel 6 trap) @ $10.95 each. Total ______

___ CB transceiver traps @ $9.95 each, plus 10 free NON-INTERFERENCE certificates for each trap. Total ______

Free "HOW TO TAME TVI" booklet with every order.

☐ Send COD.
☐ Send Postage paid. (Check or money order enclosed.)

100% MONEY BACK GUARANTEE.

NAME ______
ADDRESS ______
CITY ______ STATE ______ ZIP ______

CIRCLE 61 ON FREE INFORMATION CARD

JUST $495 GETS YOU THIS DUAL TRACE GOULD SCOPE PLUS TWO X10 PROBES.

You know that's a great price. Especially when you consider the outstanding performance you get with this Gould OS245A oscilloscope.

And you get clear, bright displays. 5mV /div. sensitivity and exceptionally versatile trigger performance. It's ideal for TV or general electronic service work; perfect for hobbyists and educational institutions. You can rely on Gould to live up to these specs:

- DC to 10 MHz; dual trace
- Trigger performance in excess of 15 MHz
- TV trigger facilitates solid synchronization with TV signals
- Portable; weighs just 11 lbs.
- Carries full *two year warranty* on all parts and labor excluding normal calibration, fuses and minor maintenance.

Just one phone call gets you action.

Don't miss out on this bargain. Pick up the phone now and call us toll-free at 800-325-6400. (In Missouri call 800-342-6600). We'll rush you free literature and ordering information on the OS245A as well as other Gould oscilloscopes applicable to your needs. Gould Inc., Instrument Systems Division, 3631 Perkins Avenue, Cleveland, Ohio 44114.

CIRCLE 87 ON FREE INFORMATION CARD

BLURRED PICTURE

I've had the same problem three times in this Heathkit GR-180. The picture is perfect at turn-on, then 5 seconds later it slowly goes out of focus to a huge smear! I checked and changed the tubes . . . no help.—K. F., Miami, FL.

I *think* you'll find the basic cause of this problem is a drop in the focus voltage. The drop is not to zero, but to about 1 to 2 kV. Read the focus voltage right at the base pin of the picture tube. Also, pull the socket and check this pin; if the color is light green, check the socket contact!

(Feedback: "I followed your advice. Everything in that focus circuit was messed up. I cleaned the socket; the 4.7-megohm resistor in series was about 6 megohms and the 1V2 socket was bad. That stopped the original trouble.

"The set played for a short time, then it went completely black. What now? I found that the boost voltage was dropping to about +380. So, I changed the boost rectifiers, D701 and D702. This got it!")

HORIZONTAL DRIFT

The original complaint on this GE SB chassis was an intermittent loss of high voltage. I changed the 0.0027- and 0.0068-µF capacitors across the horizontal-hold coil and corrected this problem. Now I had a new problem: In about 15 minutes, the picture would fall out of horizontal sync. It could be brought back by adjusting the hold control. However, the next time the set was turned on, the picture was out of horizontal sync again. I've changed numerous parts, but have not solved the problem. Please enlighten me.—C. H., Alplaus, NY.

I hate to make positive statements, for I'm wrong so often! However, this has all the symptoms of thermal drift. *Something* in that oscillator circuit is changing the value as it warms up. Kill the automatic frequency control (AFC) and see if the oscillator runs on-frequency after the problem appears. If it is quite a way off, the AFC may be OK and the problem is in the oscillator resonant circuit.

(Feedback: "I monitored the AFC voltage and found that it changed about 7 volts between turn-on and sync failure. I changed the 6.8-megohm AFC plate load resistor, but this didn't help. So, I went back and tried another capacitor in place of the 0.0027-µF capacitor I had just inserted. This helped! The picture slid sideways a bit but did not fall out of sync. Then, I tried all four of the 0.0027-µF capacitors I had, and all showed some instability in this circuit. Finally, I tried a 0.0033-µF 10% capacitor which was all I had in stock, and this one worked!")

(Comment: Your capacitor stock wasn't in very good shape! I've run into this at times. Evidently, you did find one that had a zero temperature coefficient. This was enough so that the circuit could be tuned.) R-E

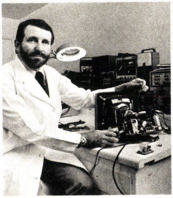

FOR PROFESSIONALS . . .
and those who want to be

Easy programs of service training you can pursue at home or shop. Unique. Broadly illustrated. Written in famous *Easi-Read*™ style. Practical, fast-paced, easy-to-learn upgrading for student and longtime technician, whatever your specialty. Expand and deepen your professional competence, and boost your personal and business earnings.

THE KEY: **Forest Belt's Service Training MONOGRAPHS**

Every MONOGRAPH deals thoroughly with its subject. No sketchy, glib abstracts of how things work; but deep, detailed explanations and illustrations that show you explicitly how to understand, analyze, troubleshoot, and repair—how to be a crackerjack technician. Fix just one extra set, faster and better, and it finances your entire MONOGRAPH subscription, in any category.

Introductory MONOGRAPH: *"Easi-Way*™ Solutions for Electronics Math and Formulas." You won't believe this MONOGRAPH until you see it. Using an uncomplicated calculator, you can solve virtually any electronic problem in *minutes,* even in *seconds.* New insights to formula-handling; you DO NOT have to know algebra! Covers formulas in the FCC License exams, parallel resistance, frequency, resonance, decibels, dozens of others. All are easy with this unique method. Follow direct step-by-step rules. Even if you're good at math, this technique saves a world of time and effort.

Order this introductory MONOGRAPH separately if you want proof. It offers a fine example of the unique training approach awaiting you in all **Forest Belt's Service Training MONOGRAPHS.** They do not just rehash stuff you could find in old books and magazines. Every MONOGRAPH brings you original, carefully developed, thoroughly tested ways and means of servicing, of running your business, of utilizing new tools and equipment. You will find your MONOGRAPHS subscription an indispensable servicing tool, and a valuable training device for yourself and your technicians.

FOUR CATEGORIES TO CHOOSE FROM

A—BASICS IN ELECTRONIC SERVICING (New)—Applied fundamentals, mainly for experienced technicians, but equally usable by students and beginners. Instead of expounding raw theory, these MONOGRAPHS guide you to everyday, practical understanding and application of vital electronic principles. Unique training concept introduces genuine familiarity with test instruments, along with knowledge of test procedures, diagnosis, and analysis. These intensive, thorough Training MONOGRAPHS assure you specific knowledge so crucial to servicing efficiency, no matter what your specialty. Typical titles in this group include "Ohm's Law—Use It To Make Servicing Easier" and "Triggered Scopes—Eight Hours to Familiarity." Our Introductory MONOGRAPH (see above) was the first title in this indispensable series.

B—$UCCESS IN ELECTRONIC$ (New)—Almost anyone will agree that, without success, you cannot enjoy any business. This group of MONOGRAPHS shows, in a most unusual way, how YOU can succeed in all of the multiple facets that contribute to an electronics career. Employed technician, service manager, shop owner, maintenance engineer, student, instructor—everyone in electronics needs these specific techniques to make the electronics business pay more. Let this unique, practical, and profitable philosophy of $uccess work for you. One example: "$uccess and More Money for Service Technicians."

C—MODERN COMMUNICATIONS ELECTRONICS (New)—For anyone involved in CB servicing, FM two-way radio, or aircraft and marine radio communications. Know for sure how key stages work, and exactly how to troubleshoot and repair even the tough ones. These MONOGRAPHS keep you abreast of all the new stuff you can't afford not to know: phase-locked loops, single sideband, CBI/TVI, keyboard channel entry, and whatever is yet to come. Learn the professional techniques that are peculiar to communications servicing, how to adjust, tune up, measure, and diagnose. See how others boost efficiency and profits in this lively field.

E—MODERN VIDEO SERVICING—The television servicing business has NOT gone downhill, except for technicians who fail to keep up with the advances. Transistors, integrated circuits, digital technology, automatic tuning and color correction, video games, home video players/recorders—all respond easily to modern methods in this group of MONOGRAPHS. You'll discover that many of today's best techniques are faster, simpler, and more easily understood than those used so long for older TV receivers.

Satisfaction Guaranteed. You may cancel your subscription anytime you wish. We will rebill copies that have been sent to you, at the single-copy price plus $1 per shipment, subtract that from your subscription payment, and refund the remainder.

Two primary goals of any successful training program:

To keep you on top of electronics, so you cannot be edged out by competition or better technicians

To boost your ability to fix sets, which brings you more profits and better wages

All **Forest Belt's Service Training PROGRAMS,** including these MONOGRAPH series, stress these two goals. Our PROGRAMS bring you up-to-date training that is practical—training you can put to work immediately—training which fulfills our motto that

Learning **and** *Earning* **BELONG TOGETHER!**

Only By Subscription
Published approximately bimonthly (six per year) in each category.

☐ I don't want to miss any **Service Training MONOGRAPHS.**
Enter my subscription immediately. Begin with No. 28A0101 *"Easi-Way*™ Solutions for Electronics Math and Formulas." Send future MONOGRAPHS in categories checked, as they are published.
I enclose ☐ $45 each for these categories:
A☐ B☐ C☐ E☐
(next 6 MONOGRAPHS in each category checked)
☐ $175 for all four categories (next 24 MONOGRAPHS)

☐ Let me see. Send only MONOGRAPH No. 28A0101 *"Easi-Way*™ Solutions for Electronics Math and Formulas."
I enclose $11 ($8 single-issue price plus $3 per-order handling/postage)

☐ Show me more. Send only the next MONOGRAPH in category indicated below
I enclose $11 for each category checked:
A☐ B☐ C☐ E☐

Send check or Money Order. No COD.
In Canada, add 20% to all prices.

Name ____________ Age ______

Address ____________ Phone ______

City ________ State ______ Zip Code ______

☐ Send bulk-subscription price sheet for school/association orders.

Name of School or Association ____________

MAIL TO: Forest Belt's Service Training MONOGRAPHS
P.O. Box 68120 Indianapolis, IN 46268

EQUIPMENT REPORT

continued from page 30

networks are used for the attenuators.

All in all, the *model 2810* is quite a fine piece of test equipment that should give long service. It is obtainable for $119.95 from B&K-Precision/Div. of Dynascan, 6460 West Cortland, Chicago, IL 60635. **R-E**

RCA Model VBT200 SelectaVision Videocassette Recorder

CIRCLE 125 ON FREE INFORMATION CARD

THIS PAST HOLIDAY SEASON SAW MANY MANUfacturers scurrying to market VCR's (*v*ideo-*c*assette *r*ecorders), whose public acceptance has been proven by the over 100,000 Sony *Betamax* VCR's sold in the U.S. even *before* the last holiday season.

One of the most highly advertised recorders is RCA's *model VBT200 SelectaVision*, which was offered initially for $1000, but is available for as little as $850 at some outlets. This unit uses the VHS (*V*ideo *H*ome *S*ystem) format, as contrasted with the Beta format used by Sony and other manufacturers. The *model VBT200*, however, offers two speeds for up to four hours of recording or playback time on a single cassette, while most other machines offer only two hours. The *model VBT200* also has two other *exclusive* features—a built-in fluorescent digital clock and a remote-wired pause control, plus a "dew" light, lighted tuner dials, switchable output channels and an auto-set indicator.

The *model VBT200* is *not* designed to be portable; it has no carrying handle, weighs over 38 pounds, and measures 19 inches wide, 7 inches high and 15½ inches deep! Power consumption is 45 watts from a 110-to-130-volt 60-Hz power supply; no portable power source is offered or recommended.

If you've never used a videocassette recorder before, it will take a little getting used to, since there are some controls and terminology that may puzzle you at first. Also, installing the recorder, while no problem in most cases, is a little confusing until you figure out what's happening.

Basically, the regular TV antenna is connected to the VCR, which has its own VHF/UHF tuners. Another cable goes from the VCR output to the TV antenna input. The antenna signals *always* go to the VCR tuners, but may *also* be directed to the TV. This way you can record on one TV channel (using the VCR tuner) while watching another channel (using the TV tuner). It is not necessary to monitor the VCR while recording—so you can even record with the TV off, while you're asleep or away from home. When you *do* have the TV set on, you can choose whether to watch the signal going to the VCR unit or TV by using the VCR/TV SELECT switch. If you choose the VCR switch setting, just set the TV to Channel 3 or 4 (whichever channel is not used in your viewing area) and tune with the VCR tuners. Selecting the TV setting lets you operate the TV in the regular way, whether the VCR is recording or turned off altogether!

To playback a recording, the VCR-TV SELECT switch must be set to VCR, with the TV set tuned to Channel 3 (or 4).

An eight-pushbutton color-coded keyboard controls the tape functions: EJECT (which lifts the entire tape cassette compartment), REWIND, STOP, FAST FORWARD, PLAY, RECORD, AUDIO DUB and PAUSE. As in most recorders, the PLAY and RECORD pushbuttons must be pressed together to record. The AUDIO DUB pushbutton allows you to record your *own* sound track on a prerecorded tape by using an external microphone plugged into the front-panel MIC jack; it erases the original sound track but does not affect the TV picture. The PAUSE pushbutton stops the tape and allows you to edit out commercials, for example, when recording; it also erases the screen on playback when you want to interrupt your viewing for short periods. One of the special features of the *SelectaVision* recorder is a 20-foot remote PAUSE-CONTROL switch that plugs into a jack on the rear of the unit.

The built-in digital clock is another plus. Other VCR's either use external add-on clocks, or have LED displays that are not visible in bright lighting. The *model VBT200* uses bright, blue-green ½-inch-high fluorescent digits, with AM-PM indicators and a flashing dot to indicate seconds. The time-display setting and command controls are located under a flip-up panel. Three two-position toggle switches allow you to advance the

continued on page 35

SENCORE VALUE FROM FORDHAM

TRANSISTOR & FET TESTER
Model TF 46 Portable Super Cricket
■ Completely portable ■ Automatic ■ Simple to use
■ Automatic power shut-off after 10 minutes

FREQUENCY COUNTER
Model FC 45
■ Frequency range coverage for every use from audio through VHF
■ Better than FCC accuracy.
■ High sensitivity for circuit testing ■ Easy-to-use pushbuttons.
■ Direct readout.

AUTOMATIC CB ANALYZER
Model CB 42
■ The total CB service bench ... simplified.
■ Combines 5 units in one for complete testing;
1) Frequency Counter; 2) RF-IF Generator; 3) Audio Generator; 4) Digital RF Wattmeter; and 5) Special CB Tester

TV-VTR-MATV & VIDEO ANALYZER
Model VA 48
■ New patented Bar Sweep patterns for simplified speed alignment ■ All RF & IF signals for injection before the detector from one cable ■ All drive signals for every stage after the detector — tube and solid state ■ Uses standard color bars and patterns ■ 100% accurate Ringer yoke and flyback test ■ Accurate drive signal monitoring ■ Video sweep generator ■ Bias and B+ substitute power supply.

FOR PRICING AND TO ORDER
CALL TOLL FREE
(800) 645-9518
For N.Y. State call (516) 752-0050

FREE 164 page catalog of over 3000 items ... test equipment, CB, tools, tubes, components and electronic supplies

fordham radio
1978 electronics catalog

FORDHAM
RADIO SUPPLY CO., INC.
855R Conklin St.
Farmingdale, N.Y. 11735
YOUR ONE STOP DISCOUNT CENTER

CIRCLE 59 ON FREE INFORMATION CARD

EQUIPMENT REPORT

continued from page 34

time either at a fast or slow speed (1 hour-per-second or 1 minute-per-second), to display the time-of-day or the auto-set time, and to turn the built-in auto-set on or off. When the auto-set is on, the VCR will turn on at the auto-set time if the power is on, and a red LED indicates that the unit is in the auto-set mode. When the VCR is operated this way, it shuts off automatically at the end of the tape.

A mechanical pushbutton-reset digital tape counter with a MEMORY switch is provided. When rewinding, the tape stops at "000" (actually "999" to allow for system backlash) when the MEMORY switch is on. This allows you to "zero" the tape at any point other than just the beginning. A two-speed switch lets you select either the SP (two-hour *S*tandard *P*lay) mode or LP (four-hour *L*ong *P*lay) mode for recording. On playback, the unit senses the correct speed automatically.

The *model VBT200* contains six other lights: a red LED on-off light located next to the power switch; a yellow LED DEW light that indicates when excessive moisture has triggered a disable switch. The *VBT200* remains disabled until the excessive moisture evaporates. There are lights inside each of the VHF and UHF tuner drum dials to show channel tuning in green digits; and a green LED indicator to show that the AFT (*a*utomatic *f*ine *t*uning) switch on the front panel is on.

One other control on the front panel is the TUNER/CAMERA input switch. When you record from the VHF input or the UHF input, you use the TUNER switch position; when you record from a video camera or from a video output of another VCR for dubbing, this input switch must be set to the CAMERA position.

The back panel contains the UHF, VHF, video and audio inputs and outputs, with screw terminals for UHF inputs and RCA phono jacks for the rest. A miniature phone jack is included for the PAUSE control. Another handy switch is the CHANNEL 3/4 output selector. Some VCR's require separate converters for each channel, whereas the *SelectaVision* VCR only requires a flick of a switch.

Two manuals come with the *SelectaVision*: the *Operating Instructions* and spiral-bound *Simplified Instruction Cards*. The instruction booklet contains adequate installation information, except it does not cover camera use or dubbing. The *Simplified Instruction Cards* show the switch positions and operations for each use, except again for camera use or dubbing. **R-E**

Belar, Motorola lead AM stereo field tests

The National AM Stereophonic Radio Committee recently presented to the Federal Communications Commission a 455-page report assessing field tests on AM stereophonic systems. This report (containing data only, with no specific recommendations) indicated that Belar Electronics Laboratory, Inc. and Motorola Inc. have emerged as leaders in developing AM stereo systems capable of competing with FM stereo systems on an overall performance level.

The Belar system was cited for its overall simplicity, most easily demodulated signal and compatability with existing monophonic receivers. The Motorola entry, called C-QUAM (*C*ompatible *QU*adrature *A*mplitude *M*odulation) performed best in a high noise environment (including skywave transmissions), but its signal-demodulation technique is highly complex. Magnavox has also developed an AM stereo system, less sophisticated than Motorola's but more complex than the Belar system.

Copies of the report can be obtained for $20 from the Electronics Industries Association, 2001 Eye Street, NW, Washington, DC 20006.

Although the Radio Committee (and many AM radio broadcasters and receiver manufacturers) would like the FCC to render an early decision regarding AM stereo broadcasting, it does not seem likely that an answer is forthcoming right away. And, if the ruling does come about, manufacturers say the success of the system will depend on the development of an IC demodulator that will allow the AM stereo system to be truly competitive with FM stereo systems. Additionally, the FCC and national AM committee privately express fear that since so far the most interest shown in the system comes from Japan, this will again mean U.S. manufacturers may miss the boat as far as being the first to get their products on dealers' shelves, as was the case with CB radios.

NEXT MONTH

A special section on personal computers in the June issue is something special you won't want to miss. Fundamentals, languages, accessories and a detailed directory. Don't miss it.

LEADER Instruments Corp. **OSCILLOSCOPES**

Model LBO-507

20 MHz, TRIGGERED
- Single trace; automatic trigger for highly stable, bright display.
- 17.5nSec rise time.
- 10mV/cm to 20V/cm Vertical Sensitivity; 11 steps.
- Displays signals to 27 MHz with ease.

OUR PRICE $399.50 probes included
REG $469.00

Model LBO-508

20 MHz, DUAL TRACE
- Add, subtract modes on CH-1 & CH-2 facilitate easy checkout for simultaneous pulses, signal levels, distortion & noise cancelling.
- Front panel X-Y operation for phase shift measuring, sweep alignment, vector scope service.
- 17.5nSec rise time.

OUR PRICE $586.45 probes included
REG $689.00

Model LBO-515

25 MHz, DELAYED SWEEP, DUAL TRACE
- Built in variable delay circuitry — 1μSec to 5 Sec.
- 5mV/Div. Vertical Sensitivity.
- Rectangular, 8 x 10Div CRT with internal graticule.
- Selectable synchronization, automatic, normal, single trace and reset modes.
- 14nSec rise time.

OUR PRICE $1185.75 probes included
REG $1395.00

Model LBO-520

30 MHz, FIXED DELAY, DUAL TRACE
- Dual trace, 30 MHz bandwidth.
- 5mV/cm Vertical Sensitivity.
- Fixed delay facilitates hi-speed readings of the leading edge of a pulse or pulse train.
- Add, subtract, alternate selection, chopped, and front panel X-Y modes.

OUR PRICE $849.95 probes included
REG $999.95

FREE
20 KΩ/V VOM Multimeter
$29.95 VALUE
With any order from this ad. Ad must accompany order.

Call TOLL FREE (800) 645-9518 In N.Y. State call (516) 752-0050

FORDHAM
RADIO SUPPLY CO., INC.
855R Conklin St.
Farmingdale, N.Y. 11735

Mastercharge, BankAmericard, VISA and C.O.D.'s accepted

YOUR ONE STOP DISCOUNT CENTER
Send for new 1978 catalog of over 3,000 items ... 164 pages of test equipment, CB, tools, tubes, components and electronic supplies.

ADD $3.00 TO COVER SHIPPING, HANDLING & INSURANCE. N.Y. Res. add approp. sales tax.

CIRCLE 59 ON FREE INFORMATION CARD

Formerly
RCA
Instruments

"Piece by piece, my bench is becoming all-VIZ."

"I repair and maintain all types of sophisticated electronic devices, so I need test equipment I can depend on.

"Lately, I've become disillusioned with many leading manufacturers' instruments. This one doesn't work right, that one doesn't have the right features, some aren't easy to use, and many force you to do things their way instead of your way.

"That's why I'm glad to see many more new VIZ instruments — they're reliable, easy to use, and priced right.

"VIZ's pulse and function generators are good examples of what I like. The pulse generator has a 5Hz-5MHz range, pulse width from 100ns to 0.1 sec, and is TTL and CMOS compatible, making it ideal for digital troubleshooting. The function generator has sine, sawtooth, and square wave output from 1Hz-1MHz, frequency stability of 200 ppm/°C, and is simple to use.

"Other instruments I've liked include VIZ's new FET VOM VoltOhmyst™, their versatile dual-trace scope, and their 60MHz frequency counter with selectable 10 or 100mV input sensitivity, built-in 1kHz audible side tone, and a high-stability 10.000MHz crystal time-base for long-term accuracy.

"Once you've seen and tried VIZ test equipment, you'll understand why I'm sold on VIZ."

VIZ Test Instruments Group

335 East Price Street Philadelphia, PA 19144 (215) VI-4-2626

☑ The Circuit Tester line
Accuracy and stability assured

© VIZ

7001

CIRCLE 39 ON FREE INFORMATION CARD

BUILD

Graphic Equalizer For Your Stereo System

This versatile audio accessory lets you obtain maximum enjoyment from your stereo system by compensating for bumps in the response of your speakers and listening room.

JOE GORIN

NO AUDIO SYSTEM HAS PERFECTLY FLAT frequency response. Although cartridges and amplifiers can be made very close to perfect, even the best speakers have major bumps and dips in their frequency response. Rooms affect the response of a speaker in a myriad of ways. Even the records played on an audio system are not flat. Alltogether, an audiophile can spend thousands of dollars on a system and end up with a jumbled mess for a frequency-response curve. Traditional bass and treble controls are not adequate to overcome the problems in the overall response of an audio system.

Enter the graphic equalizer. With individual controls for frequency spans narrower than an octave, an equalizer can be used to compensate for response deficiencies in the system. It is called an equalizer because it can make the system response to all frequencies roughly equal; it is graphic because the position of the slide controls forms a graphic representation of the response of the unit.

Applications

In an average room, 90% of the sound you hear has been reflected from the room's surfaces. The amount of reflected sound varies greatly with frequency. Thus, a speaker that sounds dull and bassy in a room with heavy draperies and soft furniture can sound sizzling and harsh in a room full of sliding glass doors and tiled floors. The response can even change with the number of people in the room! Furthermore, a room with parallel walls resonates at the frequency for which the wall-to-wall spacing is a half wavelength. A speaker placed away from the walls and floor of a room will have only one-eighth the bass response of the same speaker placed in a corner, due to wall reflections. A graphic equalizer can correct many of these problems, and even make the sound of a good speaker even better.

Many recording studios use a graphic equalizers. A recording engineer can use the equalizer to bring out various instruments or change the character of the sound. It is common practice in the recording industry to add treble boost to compensate for the rolloff in inexpensive radios and record players. The graphic equalizer can undo what the recording engineer did and make the recording sound more realistic.

In reinforced sound systems, acoustic feedback causes ringing or oscillation at various frequencies. By reducing the gain at these frequencies, a flatter response and higher volume can be maintained. The frequency response of the human ear is far from flat at low levels. Weighting filters used in laboratory testing have a very irregular frequency response. All these applications can be enhanced by the use of a graphic equalizer.

The suboctave equalizer described here solves the two biggest problems with commercialy assembled units. The price range for 10-band equalizers is about $200–$600. Since this unit was designed specifically for the hobbyist, it can be sold

SPECIFICATIONS

Frequency Response	10 Hz—100 kHz ±3 dB
Nominal Control Range	±10 dB
Nominal Gain	0 dB
Rated Output	2 volts RMS
S/N Ratio @ Rated Output	92 dB—100 dB*
Distortion @ 1 kHz @ Rated Output	.02%
Input Impedance	50,000 ohms—150,000 ohms*
Output Impedance	600 ohms
Input Overload	8.5 volts RMS—3 volts RMS*

Note: All controls centered
*For alternate wiring and component changes listed in text.

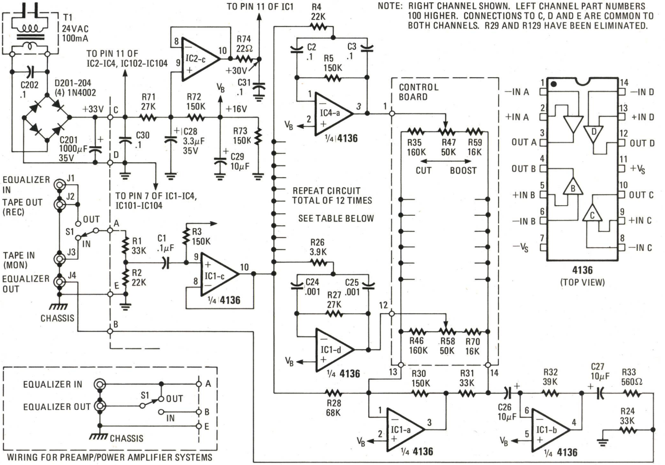

CONTROL BAND TABLE

BAND NO.	CENTER FREQ.	RESISTOR		CAPACITORS
		INPUT	FEEDBACK	
1	28	R4 = 22K	R5 = 150K	C2 = C3 = .1μF
2	51	R6 = 12K	R7 = 82K	C4 = C5 = .1μF
3	89	R8 = 6.8K	R9 = 47K	C6 = C7 = .1μF
4	160	R10 = 3.9K	R11 = 27K	C8 = C9 = .1μF
5	280	R12 = 22K	R13 = 150K	C10 = C11 = .01μF
6	510	R14 = 12K	R15 = 82K	C12 = C13 = .01μF
7	890	R16 = 6.8K	R17 = 47K	C14 = C15 = .01μF
8	1.6K	R18 = 3.9K	R19 = 27K	C16 = C17 = .01μF
9	2.8K	R20 = 22K	R21 = 150K	C18 = C19 = .001μF
10	5.1K	R22 = 12K	R23 = 82K	C20 = C21 = .001μF
11	8.9K	R24 = 6.8K	R25 = 47K	C22 = C23 = .001μF
12	1.6K	R26 = 3.9K	R27 = 27K	C24 = C25 = .001μF

FIG. 1—SCHEMATIC OF ONE CHANNEL of the equalizer. The remaining eleven channels use filter components listed in the table.

PARTS LIST

All resistors ¼ watt, 10% or better.
R1, R31, R34, R101, R131, R134—33,000 ohms
R2, R4, R12, R20, R102, R104, R112, R120—22,000 ohms
R3, R5, R13, R21, R30, R72, R73, R103, R105, R113, R121, R130, R172, R173—150,000 ohms
R6, R14, R22, R106, R114, R122—12,000 ohms
R7, R15, R23, R107, R115, R123—82,000 ohms
R8, R16, R24, R108, R116, R124—6800 ohms
R9, R17, R25, R109, R117, R125—47,000 ohms
R10, R18, R26, R110, R118, R126—3900 ohms
R11, R19, R27, R71, R111, R119, R127, R171—27,000 ohms
R28, R128—68,000 ohms
R32, R132—39,000 ohms
R33, R133—560 ohms
R35-R46, R136-R146—160,000 ohms
R47-R58, R147-R158—50,000 ohms, 10% linear slide potentiometer
R59-R70, R159-R170—16,000 ohms
R74—22 ohms
C1, C30, C31, C101, C130, C131—0.1 μF, disc +80% -20%
C2-C9, C102-C109—0.1 μF, 100 volts, 10%
C10-C17, C110-C117—.01 μF, 100 volts, 10%
C18-C25, C118-C125—.001 μF, 100 volts, 10%
C26, C27, C29, C126, C127, C129—10 μF, 25 volts, electrolytic
C28, C128—3.3μF, 35 volts, electrolytic
C202—1000 μF, 35 volts, electrolytic
D201-D204—1N4002 rectifier diode
IC1-IC4, IC101-IC104—RC4136 (Raytheon), XR4136 (XR) μA4136 (Fairchild) or equal quad op-amp
S1—double-pole, double-throw miniature toggle switch
T1—24-VAC, 100-mA, wall-mount transformer
Misc.: J1-J4, J101-J104—phone jacks, PC boards, wire, chassis, knobs.

The following parts are available from Synergistic Sound Systems, 1608 S. Douglas Ave., Loveland, CO 80537:

Amplifier and control PC boards, $7.00 each. Both boards are 3/32 inch G-10, tin-plated. Complete kit of parts without cover, $90.00. Solid walnut assembled, unfinished cover $10.00 (available only with complete kit). All prices postpaid in U.S. Colorado residents add sales tax.

in kit form for under $100. Although commercial units are generally designed to be rack-mount compatible, and thus about 18 inches wide, this compact unit is only 9 inches wide. It is even available with a professional-looking walnut case! The design uses no inductors and a minimum of different values of capacitors to make it insensitive to magnetic fields and saturation problems. Also, it is easier and cheaper for the hobbyist to acquire the parts. With 12 bands-per-channel, a slightly more accurate response can be formed than with a 10-band unit, and, of course, the suboctave equalizer is more flexible than bass/treble controls or even 5-band units. Another benefit of the build-your-own equalizer is that it can be specifically wired for either tape-monitor or preamp/power amplifier connections. Thus, the overload characteristics and signal-to-noise ratio can be optimized for the application.

How it works

The schematic of one channel of the

unit is shown in Fig. 1. For a simplified diagram of one band, see Fig. 2. Op-amp IC3-d, with R14, R15, C12 and C13 form a bridged-T bandpass filter. Capacitors C12, C13 and resistor R14 are the "T" that is bridged by resistor R15. At low frequencies, the high impedance of the capacitors blocks the signal. At high frequencies, C12 and C13 short IC3-d's output to its negative input. The resulting negative feedback keeps the output at the same voltage level as the positive input, thus preventing a signal from passing through.

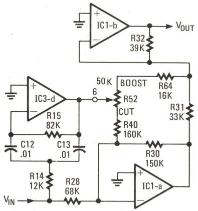

FIG. 2—SIMPLIFIED CIRCUIT of one channel. Cut or boost depends on setting of R52.

Near the center frequency of the filter, the signal flows through R14 to the center of the "T." From there, it is phase-shifted by passing through C12, inverted by the op-amp and then phase-shifted again by C13. The two phase shifts and the phase inversion cause the signal coming through C13 to be nearly in phase with the input signal, thus adding to it and resulting in signal gain. Resistor R15 damps the "T" to control Q and filter gain. Figure 3 shows the frequency response of the filter at eleven evenly spaced settings of control R52. The dashed line represents the output of IC3-d.

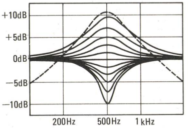

FIG. 3—FREQUENCY RESPONSE of Band 6 as control pot is varied through 11 positions.

For frequencies outside the passband of IC3-d, the signal is amplified by IC1-a and IC1-b with gains of R30/R28 and R32/R31, respectively. When the wiper of R52 is set to the CUT position, frequencies in the passband of IC3-d are partially cancelled because the signal fed to the top end of R40 has been inverted by IC3-d. When R52's wiper is moved toward the

---

Radio-Electronics Lab Test

LEN FELDMAN

A COMPLETED VERSION OF THE GORIN 12-band dual channel graphic equalizer was put through its paces in our laboratories to verify the specifications of this ultra compact add-on component. Since the unit is so compact, we feel that the designer of this equalizer was wise to keep the power supply step-down transformer removed from the equalizer package itself. This arrangement contributed to the excellent signal-to-hum-and-noise readings we obtained, which measured 85-dB below a 1-volt input reference level.

Insertion loss of the equalizer, with all slide controls set to their mid-position, was approximately 1.5 dB. Figure 1 is a scope photo of our spectrum analyzer, in which successive frequency sweeps from 20 Hz to 20 kHz were taken with maximum and minimum settings of each of the twelve slide controls on the equalizer. Approximately 12-dB of boost or cut is available at each of the twelve center frequencies. The response plots disclose an interesting characteristic of the equalizer. While boost settings affect a fairly wide band of frequencies for each control (relatively low Q response), the maximum attenuation settings of each lever result in frequency dips that are quite a bit narrower in terms of the frequencies that they affect. Most commercially made equalizers that we have tested in the past exhibit completely symmetrical boost and cut characteristics as opposed to the asymmetrical results obtained with this home-built unit.

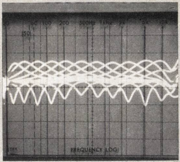

FIG. 1

In one sense, the asymmetry turns out to be a desirable feature for the user. In attempting to compensate for deficient speaker characteristics of a high-fidelity component system, one often wishes to provide a very gradual rise in response at specific frequency regions in the audio spectrum, and the boost characteristics of this equalizer makes this possible. On the other hand, when one is faced with problems of standing waves in a given listening room, it is desirable to be able to attenuate or cut a very *narrow* band of frequencies so that the audible affects of standing waves are minimized without seriously affecting overall musical balance. The narrowband attenuation characteristics of the equalizer (when the slide controls are used to *cut* response at a given center frequency) are suited for this application as well.

Additional measurements

For a 1-volt input signal, total harmonic distortion measured 0.005% with a 1-kHz input signal. At the frequency extremes of 20 Hz and 20 kHz, harmonic distortion measured 0.09% and 0.027%, respectively. Even with all the controls set to their maximum boost settings, distortion remained quite low. These extreme settings resulted in an output voltage of approximately 4 volts (for a constant 1.0-volt input), a gain of approximately 12 dB, and distortion measured 0.0035% at 1 kHz, 0.14% at 20 Hz and 0.14% at the 20-kHz high-frequency extreme. Intermodulation distortion measured 0.009% with all the controls set to flat and actually decreased to 0.006% with all the controls in their maximum boost positions.

Figure 2 illustrates the overall response of the equalizer with controls all set to maximum boost (upper trace) and to maximum cut (lower trace). With controls centered, response was flat from 20 Hz to 20 kHz, within 0.5 dB.

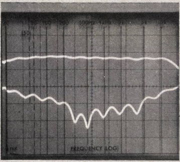

FIG. 2

Summary

In our opinion, this home-built equalizer offers graphic equalization capabilities of more expensive, commercially built units at just a fraction of the cost of such units. Examination of the layout of the equalizer suggests that it would be relatively easy to assemble.

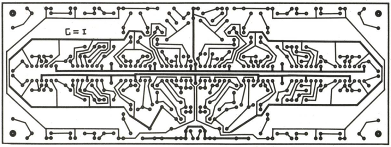

FIG. 5—**PATTERN FOR AMPLIFIER BOARD** is half-size. Enlarge to exactly 8 inches across.

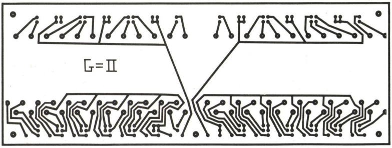

FIG. 6—**HALF-SIZE** pattern for control board that holds the slide pots.

BOOST end, the signal from IC3-d adds to the output. When the wiper is centered, signal additions and cancellations are equal and the response is flat. The resistors are selected for a nominal range of ± 10 dB at the center frequency of the bridged-T. With a linear-taper potentiometer, the boost or cut versus position is shown in Fig. 4. It is close enough to linear on a dB scale so as not to require specially tapered potentiometers.

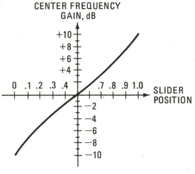

FIG. 4—**HOW RESPONSE VARIES** with the position of slider on a linear-taper potentiometer.

Next month we will conclude this article with a further discussion of circuit operation followed by construction, installation and operating details. Included in construction details will be several interior photographs and step-by-step instructions that you will need to successfully complete this stereo graphic equalizer with the minimum of effort and a maximum of pleasure. **R-E**

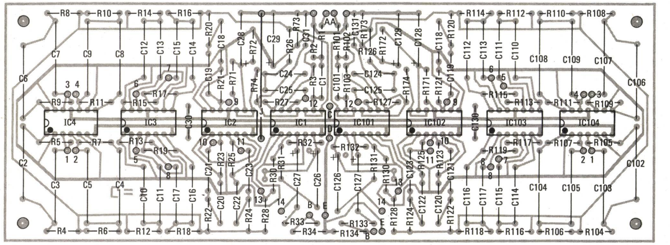

FIG. 7—**HOW PARTS ARE POSITIONED** on the amplifier board. Right and left halves of board are almost mirror images.

FIG. 8—**THE SLIDE POTS** and their associated fixed resistors are mounted on control board as shown here.

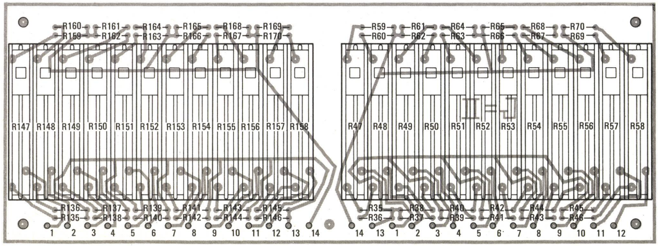

Protect Your Home—

Build Autodialer And Cassette Interface

A fire, intruder or other emergency in your unattended home can result in serious losses. Use this autodialer to alert neighbors or authorities.

JULES H. GILDER

A BURGLAR BREAKS INTO YOUR HOME, tripping an alarm in the process, but nothing seems to happen. Minutes later he is caught in the act by the police. They were called automatically by the cassette autodialer. Activated by switches in the intruder or fire alarm systems or by a panic button, the autodialer dials a preprogrammed number and plays a prepared message. The device attaches to your telephone and a cassette recorder.

> **WARNING**
> Current FCC rules (Part 68) forbid direct connection of customer-owned equipment that is not FCC type approved to telephone company lines. To use unapproved equipment, an approved protective coupler must be installed. Check with your local phone company for details.

If you desire, several different numbers, each with a different message, may be dialed in sequence. This comes in handy when local laws prohibit burglar alarm dialers from calling the police directly. In this case, several friends or relatives can be dialed in turn, to make sure that at least one is alerted and will call the police.

Dialing can be done in two ways: Either by pulsing a relay that has contacts in series with one of the leads to the telephone or by pulsing a solenoid that presses and releases the cradle button. This version is shown in a photograph. The first method is easiest and does not require a mechanical linkage to the phone. However, telephone company tariff regulations may require you to use a special coupling device between the dialer and telephone. If you don't want the expense of the coupler and want to avoid the possibility of trouble with the phone company, use the solenoid approach.

With the solenoid actuator the cradle button, which is depressed when you hang up the phone, is released and pressed a number of times corresponding to the numbers dialed. This action accomplishes the same results as the contacts on the telephone dial; it opens and closes the telephone circuit each time a pulse is applied.

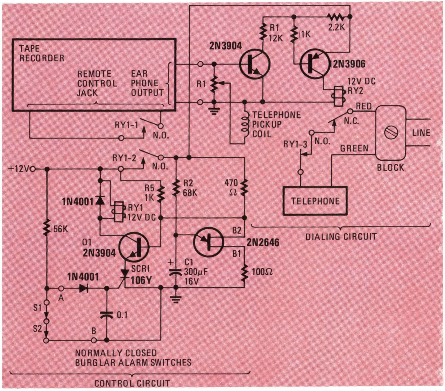

FIG. 1—THE AUTODIALER consists of an ordinary cassette recorder and a few simple components. Pulses recorded on tape dial a selected phone and then a pre-recorded message is played.

The autodialer circuit

The automatic cassette dialer circuit (Fig. 1) consists of the recorder, the control circuit and the dialing circuit. You can use any cassette recorder that has a remote control jack and a jack for an external microphone. Information that is recorded and played back is well within the frequency response of even the least expensive units.

The control circuitry couples the unit to any existing intruder alarm system that has a series of normally closed switches. When a switch is opened, the gate of the SCR is disconnected from ground and a positive pulse is applied to it. The SCR turns on and locks in. Once the SCR is triggered, its gate loses control. The device continues to conduct even when the gate is returned to ground.

When SCR1 is triggered, it completes the emitter-to-ground circuit of Q1. The transistor conducts and energizes relay RY1. This applies power to the recorder and to the dialer's disconnect timer circuit through contacts RY1-1 and RY1-2. At the same time, normally open contacts RY1-3—in series with the red line—are closed to complete the circuit to the telephone.

The recorder starts and plays back the programmed tape. The recorder output is fed through control R1 to a ring-type telephone pickup coil and fed directly to the pulse-detection circuit that opens and closes RY2. The coil induces the audio signals from the recorder into the telephone line. Relay RY2 has normally closed contacts in series with the normally open contacts of RY1 and the telephone. When RY2 opens and closes in accordance with the prerecorded pulses, it is dialing the telephone.

(If the solenoid method of dialing is used, the RY1 and RY2 series contacts are placed in the power lead to the solenoid so it pulls in and then releases with each dialing pulse.)

The audio message follows the dialing pulses. It will not key RY2 because its level is much lower than that of the pulses.

If more than one phone call is to be made each message, except the last, must be followed by a tone that is 5 to 10 seconds long. This tone causes RY2 to open the telephone line long enough for it to disconnect and prepare the telephone for the next call.

After the disconnect tone, the next number is dialed and message transmitted in the same way as the first. After the last message, the autodialer is turned off by a timer built around a 2N2646 unijunction transistor. When the delay determined by T=R2 × C1 has elapsed, the timer produces a pulse that turns off Q1. This interrupts the current path through the SCR and releases RY1, disconnecting power from the autodialer and opening the phone-line circuit.

Construction

The construction of the autodialer will be largely determined by the method of dialing used. If the series relay is used, the whole unit may be enclosed in a small Bakelite case. If the solenoid dialing scheme is chosen, then a 5 × 9 × 2-inch chassis is suggested. This allows the phone to sit on top of it and provides a firm foundation for the vertical arm that will hold the pulsing solenoid, as shown in Fig. 2.

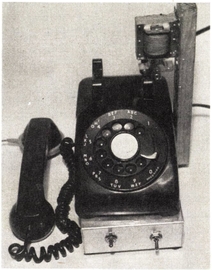

FIG. 2—AUTODIALER WITH SOLENOID that pulses the cradle button. The two toggle switches in the base are not used.

The vertical arm should be 10 inches high and is easily constructed from a piece of wood 2 inches wide and 1 inch thick. To position the supporting arm, place the telephone on the chassis the way it normally will be placed. Then mark the spot where the arm is parallel with the receiver cradle. Fasten the vertical support with two screws.

Next, place the solenoid against the support and let the plunger hang down. Lower the solenoid until the plunger depresses the cradle button, mark the spot on the support and fasten.

With the mechanical work out of the way, the rest of the device is relatively simple to fabricate. The circuit can be built on perforated board or on a PC board of your own design. The autodialer can work from a pair of 6-volt lantern batteries that are generally used in alarm systems, but a regulated 12-volt DC power supply can be used.

Installation and operation

If the solenoid dialing method is used, installation simply means placing the telephone on the chassis, taking the receiver off the hook, and allowing the solenoid plunger to hold the cradle button down.

If the series-relay dialing method is used, one of the leads from the telephone, preferably the red one, is connected in series with the contacts of RY1 and RY2. In both cases, the telephone pickup coil is then placed on the earpiece of the handset of the telephone. Before placing the unit into operation, play the entire message tape and time it. Add 5 seconds on to this time and then set the unijunction oscillator so that it will produce a pulse after that period of time has elapsed. This is done by adjusting the value of R1 until the desired delay is obtained.

You are now ready to test the cassette autodialer. Connect the unit to your burglar alarm system so that in the untriggered position A and B are normally shorted. Now momentarily depress the alarm TEST switch or open one of the switches in the alarm circuit.

If the dial pulses recorded on the tape do not cause the relay to operate, the volume is too low. It may be necessary to rerecord them at a higher volume.

If the voice message causes the relay to kick in and out, the volume is too high. Lower the volume or rerecord.

The pulse programmer

The pulse programmer in Fig. 3 is primarily intended to be used with the cassette autodialer alarm system. It is

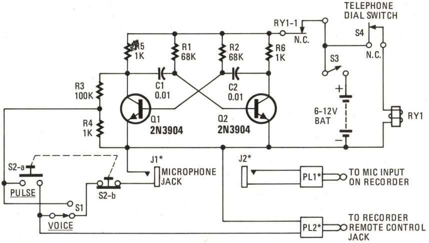

*PL1-MINIATURE PHONE PLUG
PL2-SUBMINIATURE PHONE PLUG

J1 AND J2-MINIATURE AND SUBMINIATURE
JACKS TO MATCH PLUGS ON RECORDER MIKE

FIG. 3—PULSE PROGRAMMER uses a multivibrator to develop the audio tone pulses that dial the phone or perform other operations. Mike signal feeds through programmer to recorder.

used to program tapes, which can then dial a telephone or control some other circuitry. However, a little bit of imaginative thinking will quickly make you realize that there are many other applications. For example, you can combine the programmed tapes with the recorder and dialer portions of the autodialer and produce an automatic telephone dialer. A C-60 cassette used for this application could easily store one hundred phone numbers. Another use for the pulse programmer is in synchronizing tape/slide presentations. Tones recorded on the tape are used to short out the remote-control contacts of the projector and thus cause the slide mechanism to advance.

The pulse programmer can also be used to prepare tapes that will control a sequence of events, such as turning lights on and off in your house while you are away. If endless cassettes are used, things can periodically be turned on and off.

The heart of the pulse programmer is a two-transistor astable multivibrator. The frequency of oscillation of the multivibrator is determined by R1, R2, C1, and C2. By setting R1=R2 and C1=C2 the frequency of oscillation is $f=1/T$ where $T=1.38 \times R1 \times C1$. For the components shown, the oscillation frequency is about 1 kHz.

The oscillator provides the tones that will be recorded onto the tape for controlling the relay at the output of the recorder.

Not all tape recorders have a high-impedance microphone input, so the voltage-divider network R3/R4 provides the desired high resistance load to the oscillator. The voltage divider also prevents any damage to the recorder from excessively high oscillator voltages.

To get the multivibrator to produce tone pulses that correspond to the digit pulses produced by a telephone, its output circuitry is controlled by relay RY1, which itself is controlled by the telephone dial. The telephone dial may be removed from any old telephone or purchased surplus.

The relay is needed because the pulsing contacts of the phone dial are normally closed, and normally open contacts are needed to control the output of the multivibrator. The relay is connected so that when the dial is operated it produces a series of tone pulses for each number dialed. If, for example, a 3 is dialed, the relay will close and open three times producing three pulses. The pulse rate of the dial is about 10 pulses-per-second.

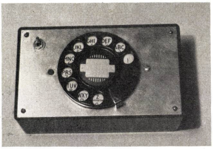

PULSE PROGRAMMER with its electronics (Fig. 3) and telephone dial are built into a small plastic utility box or similar housing.

Building the programmer

The pulse programmer is built into a plastic utility box that measures 6¼ × 3⅝ × 2 inches. This size box will accommodate the standard telephone dial as well as the multivibrator circuit, relay and battery.

The 3¼-inch hole in the cover plate required for the dial can easily be cut with a hole saw. It is best to use a variable speed drill on low, if one is available. If not, pump the trigger switch on and off so that the hole saw only makes a few revolutions at a time. By working slowly and carefully you will get a perfect hole. The dial can be mounted to the cover plate with two screws and Z brackets. (For PL2, any wire can be connected to the plug's tip or body.)

Installation

To connect the pulse programmer for use, a four-conductor shielded cable is needed. This cable should have a miniature and subminiature plug on both ends. The miniature plug (PL1) goes to the tape recorder's microphone input, while the subminiature one goes to the remote control jack so the recorder can still be controlled by the push-to-talk switch on the microphone.

To program a series of pulses from the telephone dial, turn on S3 and place S1 in the PULSE position and operate the telephone dial. This feeds a train of tone pulses to the recorder input. When you are finished recording pulses, flip the switch to the VOICE position and record your message. Additional pulses of longer duration, such as those used to separate messages in the autodialer, can be made by operating pushbutton S2. This will produce an output pulse for as long as it is held down, regardless of what position S1 is in.

(Material for this story and for the articles, "Amplifier for Hands-Off Telephone" and "Turn-On Appliances Via Long Distance" in the March and April 1977 issues was taken from the author's book, Telephone Accessories You Can Build. *Published by Hayden Book Co., Rochelle Park, NJ 07662, Price $3.95.—*Editor) **R-E**

Matsushita develops new video disc system

Matsushita of Japan recently announced the development of its *Visc II* video disc system that uses the same material (polyvinylchloride) and techniques used in manufacturing LP records. A further similarity to LP techniques is provided by the system's diamond stylus, which drives a piezoelectric transducer to reproduce the information contained in the hills and valleys of the disc. The disc is uncoated, it revolves at 450 RPM and plays up to one hour per side.

Groove depth is about 1 μm, with the undulations at the bottom of the grooves about 0.1 μm high. Spacing between hills on the Matsushita disc is about 0.5 μm at a maximum recording frequency of 10 MHz. The video luminance signal is recorded as an FM carrier signal with a tip frequency of 4.3 MHz and a white peak frequency of 6.3 MHz. The cartridge installed on a radial trolley with zero tracking error is kept synchronized with the spiral groove.

Matsushita claims that all components for the system are easily available, and the *Visc II* can be produced for between $480 and $600. No actual production plans have been released yet; the company says it has to line up disc manufacturers as well as program material.

"Feedback TV" entertains cable subscribers

Warner Cable Corporation, a subsidiary of Warner Communications, Inc., has made a new "feedback TV" system available to its 30,000 subscribers in the Columbus, OH, area. Viewers participate in TV shows in progress by merely pushing a button to register an opinion or answer program questions.

How the system works: A box of electronic equipment is installed next to the TV set, plus a control box that looks like a pocket calculator. There are 30 channels on the control box, two of which are "participatory." These two channels let the viewer "talk back" to the TV.

One of the two participatory channels features a morning "Sesame Street" type of program; the other splits the programming between "Columbus Alive" (resembling the "Today Show") and a game program. On these shows, subscribers press the buttons to inform program officials how they feel about the program material, to suggest topics for discussion, or to answer game show questions.

Another type of programming is envisioned. Merchants would display their merchandise (such as electronic equipment); the viewers can then order what they want by pushing the appropriate button. The computer has the viewer's address, phone number and account number, so that the product and bill can then be sent to him.

The remaining channels in the Warner cable system present traditional programs, premium or pay-TV and community service programs. The company presently has a franchise to serve 30,000 homes in Columbus and expects this number to increase as "feedback TV" catches on.

Microcomputer convention to be held in Dallas, TX

The International Microcomputer Exposition will be held in Dallas, from September 29 through October 1, 1978. Several groups, including the American Association of Microprocessor Engineers, will be sponsoring the event, which will be geared to every level from professional engineers to beginning computer hobbyists. A panel of experts will be present to answer questions. Write International Microcomputer Exposition, 413 Carillion Plaza, 13601 Preston Rd., Dallas, TX 75240.

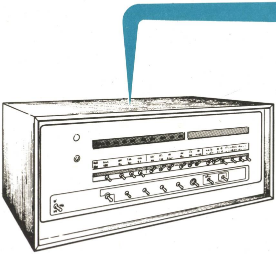

Digital Data

How A Computer

The value of a computer is greatly enhanced when the
peripheral devices, such as a CRT terminal,
transmission methods, transmission rates and

THERE ARE MANY WAYS TO TRANSMIT BINARY DATA FROM ONE location to another. With the advent of the personal computer, it is important that we understand these different ways so that we can understand how a computer communicates with a peripheral device.

Transmitting digital data

Digital devices communicate with other digital devices on a direct current (DC) basis. Within this DC signaling there are two transmission modes—bit-serial and bit-parallel.

In the bit-serial mode each bit is transmitted sequentially. Figure 1 shows a DC circuit in which a receiving device is connected to a bit-serial transmission mechanism. This hypothetical mechanism consists of a plate that has seven electrically isolated segments. One segment for each of the five bits required to transmit a character, plus two additional segments that serve to transmit a space in between each transmitted character. A wiper arm makes contact with each segment individually and completes one revolution for each character transmitted.

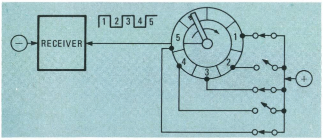

FIG. 1—BIT-SERIAL TRANSMISSION. For illustrative purposes only, the transmitter is shown as an electromechanical device. The transmitted character consists of five data bits.

Each segment is wired to a sensing contact, which, in turn, can be operated by a mechanical component of the transmitter such as a paper-tape sensing pin. Current flows in the circuit connecting this transmitter to the receiver when the wiper arm crosses a segment whose associated sensing contact is closed. Because the wiper arm tests each segment sequentially, the circuit responds accordingly, and the generated code bits are presented serially to the receiver.

Bit-parallel transmission is performed by preparing all the character bits simultaneously and then issuing a clock signal to indicate to the receiver that a character is ready (see Fig. 2).

From this you can see that bit-serial transmission requires only one circuit to send a complete character whereas in bit-parallel transmission, a separate circuit is required for each character bit (plus the clocking information). The advantage of bit-parallel transmission is that data can be transmitted faster because all bits within a character are made available simultaneously. This is why bit-parallel interfaces are normally used to connect up to a high-speed printer whereas the slower teletypewriter circuits use bit-serial transmission.

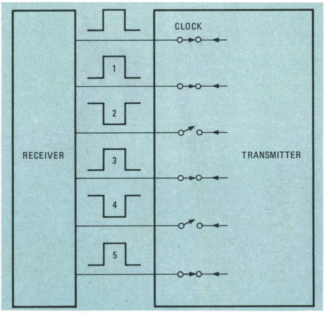

FIG. 2—BIT-PARALLEL TRANSMISSION. All data bits are transmitted simultaneously over five individual circuits.

Transmission method

A communications receiver accepts and acts upon the information contained within the transmitted signal. If the circuit operates in the bit-serial mode, the receiver must know when the first bit of a character is available and the time interval separating each sequential bit. In the bit-parallel mode the receiver must distinguish between the idle condition of the circuit and the occurrence of a character. The transmitter and the receiver must be synchronized, and, because there is no mechanical linkage between them, the timing information must be conveyed on the circuit connecting them. This synchronization is estab-

ransmission—
ommunicates

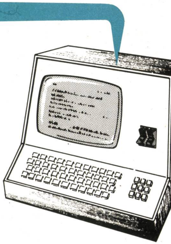

omputer has the capability to communicate with rinter or floppy disc. Here's a look at the various nterface schemes that are available for use.

PHIL HUGHES

lished by one of two methods: *asynchronous* or *synchronous*.

In asynchronous transmission the timing information is derived from each character transmitted. The normal idle condition of an asynchronous circuit is current-on (called *mark*). To initiate operation, the transmitter precedes each character with a *start* (current-off) bit. This current-off condition (called *space*) advises the receiver that a character will follow and that it should start looking at the predetermined intervals for the character bits. The transmitter follows the last data bit with a return to the normal idle condition by adding a *stop* (current-on) interval. The length of this interval is determined by when the next character is available for transmission. The term asynchronous is synonymous with *start/stop* and implies that the receiver comes to rest between each character. The start bit provides the synchronization with each incoming character.

The bit-serial transmission mechanism shown in Fig. 3 is similar to that shown in Fig. 1, but with the addition of start and stop bits. Note that the stop bit has a fixed length, but this is meaningful only when there is a continuous flow of characters, otherwise the stop bit is indistinguishable from the idle (mark) condition of the line. This, according to old Western Union operators, is where the expression 'just marking time' comes from.

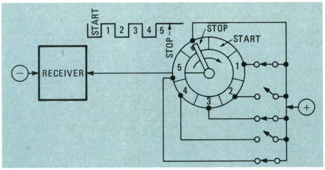

FIG. 3—ASYNCHRONOUS SERIAL TRANSMISSION includes start and stop bits in addition to the data bits.

In a bit-parallel circuit the receiver uses a timing or clock pulse to signal the arrival of data. The clock contact shown in Fig. 2 is operated whenever a character is available.

The synchronous transmission method is more sophisticated than the asynchronous mode. It assumes that the transmitter and receiver are being driven at identical clock rates and that the corresponding functions of each (bit generation by the transmitter and the detection of that bit by the receiver) occur at the same time. The clock rates of the transmitter and receiver are matched by the transmission of a timing pattern. These timing patterns are called synchronization (or sync) characters.

In some systems during idle line time (when no data is ready for transmission), a continuous stream of sync characters is transmitted. In other systems, a fixed number of sync characters are sent immediately preceding the data characters. In all systems, the receiver does a bit-by-bit comparison of the incoming bit stream to the bit configuration of the sync character. When a match is detected, the receiver is said to be *locked-on*, and the data characters can be sent without additional timing information. The receiver can then distinguish between the individual bits of a data character because the position of the sync character has been established.

In asynchronous transmission, timing information is included with each character. This timing overhead represents from 20% to almost 50% of the character time, depending on what code is being transmitted. Synchronous transmission has the advantage of handling its timing overhead with a few sync characters at the beginning of a message. This significantly reduces transmission overhead attributable to timing information.

Transmission rates

Digital data can be transmitted at many different speeds, and individual devices can frequently operate at two or more rates. These rates can be expressed as characters-per-second (CPS), words-per-minute (WPM) and *baud* or bits-per-second, the term baud is used interchangeably with bits-per-second. For bit-serial transmission, the meaning of characters-per-second is clear. For bit-parallel transmission, bits-per-second and characters-per-second are equivalent because each bit requires a separate circuit. Bit-serial devices have a varying number of bits in each character, and transmission facilities are concerned with the maximum number of electrical transitions they are required to handle. Therefore, bit-serial devices and transmission limitations are expressed in terms of bits-per-second.

To determine the transmission rate, we must first determine the number of bits contained in a transmitted character. This number is generally not equal to the number of bits that are required to define the character because transmission-overhead bits must be added. For example, the ASCII code requires only seven bits to define a character, but the synchronous transmitter adds a parity bit for error checking. Thus, transmitting the ASCII code over a synchronous data link requires eight bits-per-character. The following formula can be used to compute the data rate on a synchronous link:

Bits-per-second = characters-per-second × bits-per-character
(data bits + parity bit).

For asynchronous transmission, add the start and stop bits as well as a parity bit. If the start and stop bit times are equal to the character bit times, then 10 bit times (seven data bits + parity + stop + start) are required to transmit an ASCII character. Actually, in asynchronous transmission the stop bit is frequently longer than the data bits. For example, an ASCII teletypewriter requires a stop bit that is equal to twice the length of a data bit, thus requiring 11 bit times to transmit a character. The Baudot (an older five-bit level code) teletypewriters generally require a stop bit that is equal in length to 1.42 bit times. Because of this difference between various asynchronous transmitters, the character is expressed in terms of bit-lengths. This bit-length-per-character is called the *unit code.* For example, an ASCII code with a parity bit, a start bit and a stop bit equal in length to one data bit is a 10 unit code. A Baudot device with five data bits, a start bit, and a 1.42 unit stop bit form a 7.42 unit code. Table 1 shows some common devices and representative code lengths.

TABLE 1–UNIT CODE FOR COMMON DEVICES

	Bell System Baudot TTY	**Western Union TTY**	**10 characters per second ASCII TTY**	**30 characters per second ASCII terminal**
Start	1	1	1	1
Data bits	5	5	7	7
Parity bits	Not used	Not used	1	1
Stop	1.42	1	2	1
Total unit code	7.42	7	11	10

Using the unit code concept, the following formula determines the data rate for asynchronous circuits:

Bits-per-second = characters-per-second × unit code.

Communications interface

The communications interface is the electrical connection between the computer and the communications equipment. The latter is generally a data set or modem. (A modem is a device that converts DC signals into AC signals suitable for transmission over telephone circuits and then converts them back to DC signals for reception.) The computer equipment is either an I/O port or a terminal.

It is fairly common for two pieces of computer equipment to be connected together. Although this does not fit into the strict definition of a communications interface, the definition can be stretched a little. The two pieces of connected equipment are generally called the *data terminal equipment* and the *data communications equipment.* Since the data terminal equipment will exist whether the terminal is connected to a communications interface or to a computer, the terminal itself can be defined as the data terminal equipment. Data communications equipment refers to either the data equipment or the computer. In other words the data communications equipment will always refer to whatever it is that you are connecting to a terminal. Now that we have the hardest definition out of the way let's look at a couple of common interfaces. We'll see what they are, how they differ and how they are applied.

Figure 4 shows a 20 mA (20-mil) current-loop interface. The circuit has only two wires, with the earth commonly used in place of one wire. A mark condition or logic 1 is defined as a complete circuit; a space or logic 0 is an open circuit; and information is transmitted as is shown in Fig. 3. This circuit is the standard interface for teletypewriter devices.

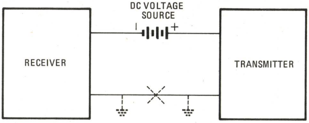

FIG. 4—20-MIL CURRENT LOOP for serial data transmission. Some systems replace the return path with a common ground. This reduces the number of wires running between the transmitter and receiver to one.

The other common interface is the Electronic Industries Association (EIA) No. RS-232-C. This interface is the most popular even though it predates integrated circuits and is therefore not tailored to IC levels. The telephone companies use this standard as the interface with which their data sets are designed to operate.

The RS-232-C standard is defined in terms of voltage levels. A voltage from +3 to +15 is defined as a space or logic 0, and a voltage from −3 to −15 is defined as a mark or logic 1. The transmitter specifications are from +5 to +15 volts for a space, and −5 to −15 volts for a mark. This allows for noise and a loss of up to 2 volts in the circuit.

A standard RS-232-C communications circuit consists of a data path in both directions, a ground return and status and control lines. Table 2 shows the standard pin assignments for the most common signals and the direction of data flow. Note that if a computer is directly connected to a terminal, it is necessary to alter some connections such as attaching the receive-data lead from the terminal to the transmit-data lead of the computer and vice versa.

TABLE 2–STANDARD RS-232-C PIN ASSIGNMENTS

Pin No.	Description	Data direction
1	Protective (chassis) ground	
2	Transmitted data	From terminal
3	Received data	To terminal
4	Request to send	From terminal
5	Clear to send	To terminal
6	Data set ready	To terminal
7	Signal ground	
8	Data carrier detect	To terminal
20	Data terminal ready	From terminal

The protective ground is equivalent to the third pin on a standard household electrical outlet. It insures that the chassis potential of all the equipment is equal, which should result in a longer equipment life. It also eliminates possibly hazardous potential differences between chassis. Signal ground is used as the reference for all the interface levels.

Transmitted data is the data that comes from the transmitter and is sent to a receiver; receive data is transmitted in the other direction, with the information to be displayed.

All other RS-232-C interface signals are for supervisory or control purposes. Some send information to the terminal, and others request information from the terminal. *Data set ready* signals the terminal that the communications equipment is powered up and ready. *Data terminal ready* indicates that the terminal is powered up and ready.

The *request to send* and *clear to send* lines are used for handshaking between the terminal and data set. When the terminal wants to send data, it activates the *request to send* line and then waits for the communications equipment to activate the *clear to send* line before data is actually sent. This gives the data set time to turn on the transmit signal. The delay between *request to send* and *clear to send* is called *line turnaround time* and can vary between 0 and 200 ms. The actual delay is selected based on circuit characteristics and then set by the circuitry within the data set. **R-E**

Noise Interference In Mobile Rigs

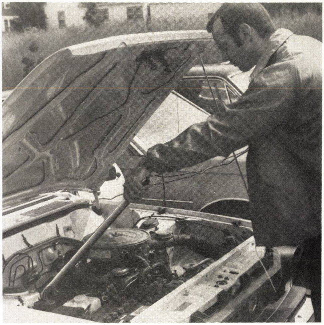

How To Get Rid Of It

Eliminating interference in mobile radios can be simple when you find the source. Here's how to find and get rid of most noise.

JOSEPH J. CARR

NOISE INTERFERENCE IS PERHAPS ONE OF THE MOST IRRITATING problems encountered when installing a mobile rig. Some noise problems seem so difficult to eliminate that many simply put up with the irritation, and accept it. However, most noise problems are relatively easy to solve, and are amenable to almost simplistic solutions.

The first step in troubleshooting any mobile noise problem is to identify the *types* (notice the use of the plural form!) of noise present. Generally, noises come in bunches, each of which must be solved by a slightly different approach. Is it, for example, spark plug/ignition noise? Is it alternator whine? Or is it the sloshy-sounding tick of the gasoline level sensor in the fuel tank? You should not fall prey to the trap of assuming that only one form of noise is present, even when they sound enough alike to mask each other.

Suppression methods

Table 1 shows the most common types of noise in mobile broadcast and communications receivers, along with their recommended cures. Be aware, though, that many transceivers may not be able to use all of these techniques because of the high current demands of the transmitter. For example, if the L-section filter is used to suppress alternator whine, the recommended choke will have too high a resistance for a 100-watt transmitter. In these cases, you could open the transceiver and insert the filter in the power-supply line feeding the receiver and thus leave the power-supply line feeding the transmitter circuits intact. If this is possible, it will also allow you to fuse the power-supply line feeding the receiver at a much lower current than the rating of the primary fuse for the transmitter. It has been known to happen, especially where solid-state receivers are used, that the receiver power supply could burn up rather spectacularly, yet the power-supply current would not blow the 25- to 50-ampere fuse needed to sustain the normal transmitter supply current.

Also, be aware that some automobile manufacturers will have installed some suppression techniques that could be superior to those given in this article for specific automobile models. This is especially true for alternator whine or where a grounding or shielding problem in the vehicle has been detected. A call to the local automobile dealership or to the field-service department of the auto maker often yields rich information.

The capacitor method of suppressing ignition noises works well on the old-fashioned Kettering coil/breaker-points type of ignition that is standard on almost all cars, but it may not work or may cause damage to the newer solid-state ignition systems. In this case, contact the car manufacturer (either the car maker if it is O.E.M. equipment or the ignition manufacturer if it is an after-market product).

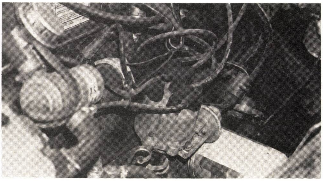

FIG. 1—IGNITION SYSTEM is the most dominant source of RF interference in automotive installations. Early amateur radio operators often used ignition coils from Model-T cars as transmitters.

The ignition system (shown in Fig. 1) is not the only source of spark-like interference. There are numerous small DC motors in your car that are often overlooked. One of the prime offenders is the motor (see Fig. 2) that drives the blower in the heating/air-conditioning system.

Standard suppressors

Some of the suppression techniques recommended (see Table

TABLE I

SYMPTOM	CAUSE	CURE	COMMENTS
Popping static at a regular rate. Varies with engine RPM.	Ignition system	Check for deteriorated resistance ignition wire. Bypass capacitor from battery terminal of ignition coil to ground (0.5-μF).	Check antenna ground.
High-pitched ragged howl.	Generator	0.1 to 0.5-μF from armature terminal to ground and/or L-section filter at radio power lead. Do *not* bypass field terminal.	Applicable only to older U.S. and some imported cars.
High-pitched, nearly "pure" whistle. Varies with engine RPM.	Alternator	Check car manufacturer's service manual. Install a 0.1 to 0.5-μF capacitor at alternator and/or L-section filter at radio power lead.	
"Frying eggs" sound.	Regulator	Bypass input and output terminals of regulator to ground with 0.1-μF capacitors.	May also indicate a defective regulator.
Popping (slow). Does not vary as engine RPM varies.	Gas gauge sender unit.	Bypass lead-in wire as close to tank as possible. (0.5-μF).	Usually found under carpet in trunk. Consult manufacturer's service manual.
Popping sound as brake is depressed.	Brake-light switch.	0.5-μF across switch.	
Horn noise.	Horn	0.5-μF across horn winding.	May be masked by sound of horn.
Electrical motor whine. Does not vary with engine RPM.	Motors	0.5-μF across winding.	

Capacitor types: For AM radios, use only automotive-type bypass capacitors or coaxial types. For FM or CB radios, use only coaxial automotive bypass capacitors.

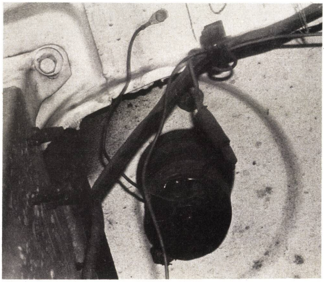

FIG. 2—HEATER/AIR CONDITIONER BLOWERS and other DC motors are often overlooked as sources of noise.

1) may already be installed in the car by the auto manufacturer, while you must add the others yourself. Note that vehicles equipped with only an AM radio may not have adequate bypass capacitors for high-frequency suppression, but many cars having AM/FM radios will have the correct capacitors. What is needed are *coaxial* bypass capacitors, such as those manufactured for amateur and CB use by Mallory and others.

Ignition system suppression uses a 0.1- to 0.5-μf capacitor across the primary side of the ignition coil and some resistance (approximately 10,000 ohms) in series with the spark plugs. Be absolutely sure to connect the capacitor to the battery terminal of the ignition coil (see Fig. 3) and not to the distributor terminal. (The distributor terminal of the coil is identified by the wire that runs to a grommet or connector on the side of the distributor, while the wire on the battery terminal of the ignition coil seems to disappear into the car's main wiring harness.) Use a coaxial bypass capacitor, then disconnect and discard the existing AM suppression capacitor.

The series resistance can take any of several forms. You could, for example, use copper ignition wires and then insert one of those little black barrel-shaped noise-suppression resistors in the line. I do not recommend this method, however, because the resistor could work loose and leave you stranded in the middle of nowhere. The car manufacturers usually supply the vehicle with either radio resistance wires or resistor spark plugs. In the case of some imported cars, resistor inserts or caps that attach to the spark plug electrodes are installed. The resistance wire, used on most American cars, works well in suppressing spark plug noise, but has the habit of deteriorating every couple of years. It does, however, provide very credible suppression of spark plug noises!

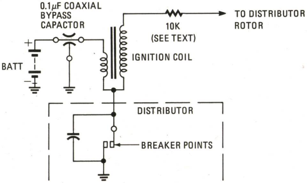

FIG. 3—KETTERING IGNITION SYSTEM was the most common before the electronic ignition system was introduced. Noise suppression involves addding a 0.1-μF capacitor on the primary side of the ignition coil and some resistance in series with the spark plugs if the engine does not already have this resistance present. The series resistance can take the form of resistance-type ignition wires or barrel-type resistors that are inserted in the spark plug wires.

Figure 4 shows how to mount the coaxial bypass capacitor to the alternator frame to reduce the high-pitched whistle-type interference. As in *all* noise suppression capacitor installations, it is critical to keep the leads between the capacitor and the alternator as short as possible.

The *correct* terminal on the alternator (or generator if your car is older or imported) is the larger of the two terminals. This high-current terminal carries the charge to the battery. Do not attach a capacitor to the smaller terminal, or damage may result.

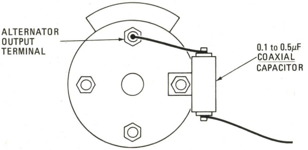

FIG. 4—ALTERNATOR WHINE is reduced by adding 0.1 to 0.5-μF coaxial capacitor to alternator as shown. Check with auto manufacturer for correct value or damage may result. To further reduce noise, an L-section filter can also be added at the input power line feeding the radio.

Also, check with the automobile manufacturer about the correct capacitor value for your particular car model. A value between 0.1 to 0.5 μF is usually recommended. However, there have been several cases reported where certain alternators have resonated with the added capacitance, and this resonant condition resulted in alternator damage. It is better to check it out than not!

In the "old days" when generators were used and the voltage regulator was a chattering bank of three high-current relays in a little black box, the recommended cure was a 0.1-μf capacitor connected to both the battery and generator terminals of the regulator and a series R–C network with a short (less than 1 μs) time constant from the field terminal to ground. But this is no longer the best advice. In modern cars, the regulator is either all solid-state or partially solid-state (the high-current pass element is a relay), so only a 0.1-μF coaxial capacitor from the battery terminal to ground is required.

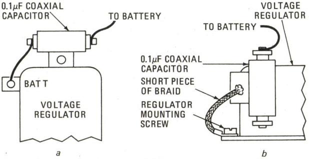

FIG. 5—REGULATOR CAUSED NOISE is reduced by adding a 0.1-μF coaxial capacitor in series with the battery terminal. Two possible methods for mounting the capacitor is shown in *a* and *b*.

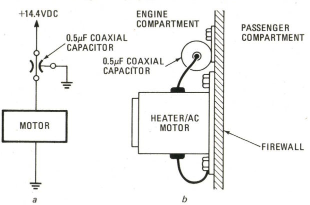

FIG. 6—DC MOTOR NOISE is reduced by adding 0.5-μF coaxial capacitor across motor winding as shown in *a*. Possible mounting location is shown in *b*.

Figure 5 shows two alternate methods for mounting the coaxial capacitor. Note that any existing AM suppression capacitors must be removed prior to installing the coaxial capacitors. Figure 5-a shows what can be termed the "common-sense" mounting method, while Fig. 5-b shows a little more clever method if the mechanical construction of the regulator allows it. Most regulator terminals are threaded to accept a No. 10-32 machine screw to hold the wire, so use a Mallory bypass capacitor that is similarly threaded. If only the female version is available, cut a No. 10-32 stud from a machine screw. Be absolutely sure that the connection between the capacitor and the terminal is tight or problems will occur at high charging currents. Use a piece of battery grounding braid or the tinned shield from a RG-8 or RG-11 coaxial cable to ground the capacitor body. Solder the end of the ground strap to the capacitor.

Figure 6 shows the method for suppressing the noise from a small DC motor such as the heater/air-conditioner blower. The 0.1-μf coaxial capacitor must be mounted as close as possible to the motor, a feat that is a lot easier to write about than actually do in most cases! Also, be sure that the motor housing is well grounded; the antirattle compounds that are sometimes used often provide a good DC ground but a poor RF ground.

Receiver defects

Component failures can create a noise problem in a vehicle that is otherwise free of excessive interference. The most common problem is the failure of certain noise-suppression components in the power-input circuit to the receiver.

Figure 7 shows a typical (well almost typical) power-input circuit to the receiver portion of a transceiver. Capacitor C1 rarely opens up (if it is used at all) because it is a spark-plate capacitor that consists of two pieces of copper foil sandwiched across a small square of fishpaper insulator. But if capacitors C1–C4 (especially capacitor C2) should open up, or if coil L1 should short out without shorting to the chassis (in which case it would burn out the fuse), then noise will result.

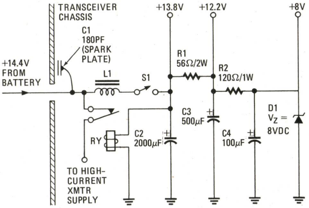

FIG. 7—TYPICAL POWER-INPUT CIRCUIT to mobile radio. If capacitors C1-C4 open up or if L1 should short, noise will enter the radio through the power supply line.

If the antenna input choke, or the lead from the antenna terminal on the transmit/receive relay, is placed parallel and beside the power-supply line from the battery, then there is a good chance that noise pulses will be picked up and cause interference in the RF amplifier. This type of noise problem, which incidentally is seen fairly often, is best corrected by either repositioning the antenna line or by placing it inside a shielded enclosure.

The best way to determine whether the problem is in the radio is by substitution, although this is not the most practical way where amateur mobile installations are concerned. But if it is possible to temporarily install some other rig then try it. If there is *reduction* in noise with the new rig (or, very rarely, the elimination of noise), then the problem is in the rig.

Antenna and radio grounding

Do not overlook the grounding connections for the antenna and the transceiver chassis as a possible cause of noise problems. The antenna should be checked by substituting it with a known good antenna. Although it is not resonant at the HF or VHF ham bands, you may use for test purposes only, an ordinary low-cost AM car-radio antenna. Attach the correct cable adapter and plug it into the transceiver antenna connector. Ground the base of the test antenna to a conductive chrome or bare steel fixture on the car—it is not usually necessary to mount the antenna.

When checking ground connections, it is advisable not to rely on an ohmmeter because the readings can be highly misleading. Like the tube tester, if the reading indicates it is bad, then you better believe it, but if it indicates it is good, then it may *still* be bad. In the case of the antenna, if an ohmmeter indicates that the coaxial cable shield is open, then you have found the source of your trouble—not to mention transmitter tune-up problems. However, if the ohmmeter reads some low resistance, then you must make the substitution test to verify that the ground is the cause of the problem.

Similarly, the radio chassis may look grounded to the DC power supply but to RF it actually might be at a sufficiently high impedance to produce a noise voltage high enough to interfere with reception.

Modern automobiles frequently use a clay- or putty-like anti-rattle compound between the dashboard and the firewall. Noise may result if the dashboard and the firewall are used as the ground return for the transceiver's DC power supply. The solution is to connect a heavy conductor between the radio chassis, the major dashboard braces *and* the firewall. Use either battery braid or an outer shield from a length of heavy coaxial cable.

The problem of noise caused by poor chassis grounding has been compounded in recent years by the use of lock-mount brackets and antitheft consoles over the transmission hump. This type of mounting is particularly popular with CB'ers, but is also used in low-power HF and two-meter amateur rigs.

Many less experienced mobile installers will use the coaxial cable shield as the DC ground return wire. This will not cause any DC-related problems unless the transmitter is a high-power unit that requires a large current from the supply circuit. It does, however, create potential noise problems because the RF impedance is quite high! If the radio has a ground wire, use it; if not, make one.

If you use a slide mount, you should take special care of the copper-finger connectors that bring power to the set. As long as they are not corroded and have not lost their spring tension, they work well, but let them deteriorate and you will hear it in the loudspeaker! The best solution is to route the ground wire directly to the firewall, but if theft is a problem in your area, then be sure to maintain the connections on the slide mount.

Antenna or power-line noise

Once the radio chassis and antenna grounding have been attended to and eliminated as possible sources of the noise, the next consideration is whether the noise is entering via the antenna or the power line. To determine this, disconnect the antenna and note whether or not the noise level is reduced. Some amateurs seem to believe (erroneously) that the type of noise indicates how it enters the set. Ignition noise, especially, can enter the set by either the antenna or power line, and the proper corrective action for each is different.

Antenna-related noise, for example, is often caused by the inadequate shielding action of the hood or body panels, or it can be caused by RF reradiation from the tailpipe of some other vehicle. Noise that enters on the power line, on the other hand, is often caused by the incorrect placement of the power cable itself, or by induction from another cable.

It is good practice to take note of whether the car has recently been serviced, or has recently been returned from the body shop following accident repairs. Sometimes, the fiberglass and plastic components materials used to repair body damage, or an incorrectly reinstalled antenna ground, can cause noise that did not exist before. For instance, in an actual case of a car with an all fiber glass body, the AM/FM radio has a great deal of motor noise that had not been there prior to repairs on the right rear-quarter panel. It turned out that the antenna ground to the tailpipe had not been reconnected, which was causing the interference.

After the tune-up

Another possible cause of a flare-up in motor noise is an improper motor tune-up job. If the noise occurs for the first time right after a tune-up, then suspect that something was wrong with the job.

In some cases, I have discovered that the mechanic substituted straight copper high-voltage wires for the resistance wires specified by the manufacturer. Use an ohmmeter to check whether the mechanic substituted the incorrect wire. First, check the wire from the high-voltage terminal on the coil to the center terminal on the distributor. If this wire does not have a resistance of several thousand ohms, then get back to that garage and have the mechanic install the correct spark-plug wires.

It is equally important to check the wires if the noise has appeared gradually, and it has been 25,000 miles or two years since the high-voltage wires were last replaced. The carbon-wire filament used in these cables deteriorates after a while and to a point where internal arcing occurs. Besides causing rough engine idle, this will also cause radio-frequency interference in the radio receiver.

A sure sign of deteriorated ignition cables is a low-speed popping noise that is most noticeable when the car is idling. This condition is caused by having one open-circuited spark plug. If you have ever observed the ignition waveforms of a multicylinder engine with such a problem on an automotive oscilloscope, then you probably saw the pulse amplitude on the offending cylinder go so high that it passed right off the top of the screen!

Some amateurs operating in the low-frequency (75-meters, mostly) bands use a low-value RF choke in series with the receiver antenna line inside the transceiver cabinet. This RF choke is usually placed in the receiver side of the transmit/receive relay circuit. Figure 8 shows an RF choke made up of a few turns of No. 22 enameled wire wrapped around a red-core toroid. This technique can work as high as the 20-meter band, and a colleague on mine claims that it works even into the 27-MHz Citizens band. However, inductance at the high end of the HF spectrum becomes appreciably reactive at those frequencies and will not only dull the noise-pulse spike but also impede the RF signal!

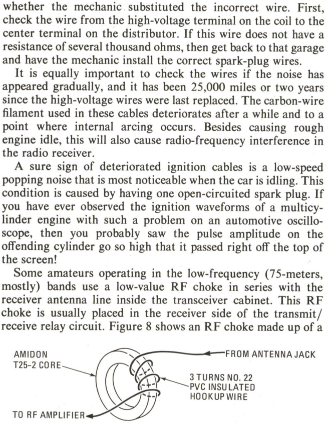

FIG. 8—NOISE CAN ALSO BE REDUCED by placing an RF choke in series with the antenna line inside of the receiver.

Alternator whine is one of the most annoying forms of interference to mobile rigs. It usually enters through the power line and is difficult to suppress. It even affects two-meter rigs, (normally immune because of the remoteness of 144-MHz from the stronger noise-pulse harmonics) because the whine penetrates the audio stages.

Figure 9 shows an L-section filter, long popular in the auto entertainment electronics market. The problem with using this filter is that the choke's high DC resistance will cause appreciable voltage drop when the transmitter is keyed. The choke is

continued on page 114

Unusual Electronic Clocks

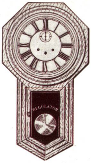

Pendulums

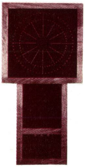

Displays Chimes

Part 2—Conclusion of the roundup covering electronic clocks designed for installation in wall and mantel cabinets.

FRED BLECHMAN, K6UGT

LAST MONTH WE INTRODUCED YOU TO the world of unusual electronic clocks—those electronic clocks housed in the more traditional cabinets and having such features as chimes and pendulums. Now let's complete the roundup.

Heath

The *Electronic Clock Chimes* is an accessory that fits into the cabinets of the Heath *model GC-1195* floor and *model GC-1197* shelf *Super Clocks*. It electronically synthesizes a natural, mechanical chime sound and reproduces the Westminster Chimes melody of London's Big Ben clock. The notes are the same as those first used on the clock in the University Church tower of St. Mary, Cambridge, England, and selected for the Victoria Clock Tower in the House of Parliament in 1859. There, the hour is still struck on the old bell, Big Ben, after the four famous musical phrases have been played on the smaller bells. The music (Fig. 6) was inspired by a phrase from Handel's symphony "I Know That my Redeemer Liveth," and the words and music were arranged by William Crotch in 1793.

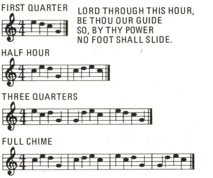

FIG. 6—WESTMINSTER CHIMES MELODY is struck by several of these clocks.

Synthesization is the production and control of sound, including music, by duplicating the pitch, timbre and loudness contour. The pitch is the sound's dominant frequency, the timbre is its time-varying frequency spectrum and the loudness contour is its amplitude or modulation envelope. Synthesis of the chime notes uses this principle.

HEATH GC-1197 Digital Shelf Clock may be used with Heath electronic clock chimes.

Each note frequency that is used in chime-note synthesis is generated by the note synthesizer and related to the other note frequencies by a multiple of $12\sqrt{2}$. Therefore, there is a constant frequency change between each successive note, just as in a piano scale. This note-frequency relationship establishes what is known as an even-tempered scale. In this unit, the entire scale can be adjusted approximately $1\frac{1}{2}$ octaves with the pitch control, to transpose the tune into various musical keys. The pitch of these notes falls within the range of most clock chimes.

Four notes sound on the quarter-hour, eight on the half-hour, twelve on the three-quarter hour, and the full 16-note passage is sounded on the hour, followed by a monotone striking the number of hours. Actually, only five notes are used—four for the melody and one for the striking hour. A tick-tock sounds continuously, and controls are provided for volume, pitch and sound decay.

It's easy to build

Construction is straightforward and the Heath assembly manual, as usual, is excellent. Twenty-two IC's, 24 diodes, 7 transistors, a speaker and many other components fit onto a single $4\frac{3}{4}$-inch × 10-inch PC board. Power and display segment signals are provided by the clock

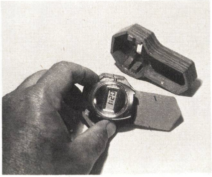

DO-IT-YOURSELF case made from balsa wood. "Clock module" is LCD wristwatch.

in which this unit is installed via a 9-pin connector and two clip leads. The display segments are decoded by the chimes electronics to program the times, the tune and the hour-tone sound. Heath will *not* give you information on how to mate these chimes to any other clocks but their *Super Clocks*, and to use these chimes with any other clocks voids the chime warranty.

The circuitry used in this unit involves advanced digital and musical theory, well beyond the scope of this article. If you're interested in specific details, write Heath for the price of the *Electronic Clock Chimes Manual* (Part No. 595-1896-02). Heath Company, Benton Harbor, MI 49022.

Sankyo

The Sankyo *model 803 AL* is a digital alarm clock in a wooden case, and it features Westminster Chimes. Although the digits are driven electromechanically, electronics control the number of times the tune, which is played on a motor-driven music box, is repeated. The full 16-note Westminster Chimes tune, shown in Fig. 6, plus chords, takes 13 seconds to play, and is switch-selectable at the beginning of every hour or at alarm-set time. It plays only once on the hour, but when the unit is set in the alarm mode, the tune repeats five times. The control circuit uses an R–C time constant to bypass a cam on the music-box drum that operates the cutoff switch. The time constant is set to complete its cycle during the fifth playing of the tune, after which the cam switch shuts off the circuit. A small motor drives the music box through a set of high-quality plastic gears.

SANKYO 803AL Digital 24-hour alarm Westminster Chimes clock.

The digital display consists of four silk-screened translucent orange plastic drums on a common shaft, driven by a small 60-Hz synchronous clock motor and the associated gears. A single 0- to 60-second wheel turns once per minute. A 24-hour alarm drum, which can be set in 10-minute intervals, trips a microswitch to sound the chimes at the selected time.

To set the time display, place an index finger in a depression in a knob on the side and turn the knob with your fingertip to activate the unit-minutes drum. You can go forward or backward; the other digits change sequence by means of molded tabs on their drums. A low-high switch sets the level of a single incandescent bulb that is used to light the display from within.

A three-position switch selects chime operation—hourly, off or alarm. There is no sound on the quarter-hour, half-hour, or three-quarter hour.

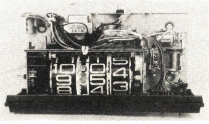

SANKYO 803AL. The digits are printed on translucent drums, driven by a clock motor. A single incandescent bulb lights the number drums from inside. The "chimes" are played by motor-driven music box.

This unique and beautifully styled clock is ruggedly made and can be obtained from any Sankyo dealer. However, it is *not* available in kit form. Sankyo Seiki (America) Inc., 149 Fifth Avenue, New York, NY 10010.

Solid-State Time

This Fosket-designed *Electronic Pendulum Clock* is intended as a mantelpiece clock; it is over 10 inches wide and almost 11 inches long. It comes complete with an early-American maple case, four lathe-turned spindles, a crown and two ruby lenses—a large one for viewing the time and a smaller one for viewing the pendulum. The pendulum electronics are sophisticated but assembly is simple. In fact, the entire assembly of this clock is simple enough for a beginner.

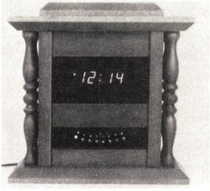

SOLID-STATE TIME. Completed elegant maple mantel-style digital clock with swinging electronic pendulum. Time exposure shows all pendulum LED's lighted.

A completely preassembled *Liton model LT-701* 12-hour clock module, with four large 0.7-inch-high bright digits and a blinking colon handles the timekeeping and display functions. A wall-plug transformer is used to supply power and the 60-Hz input from the 117-VAC line. The module processes the 60-Hz input to perform timekeeping with long-term accuracy. Pushbutton and toggle switches set the alarm and display times. An alarm buzzer was included in the kit we built, but it was necessary to add the circuitry shown in Fig. 7 to make the sound louder. (The components for this extra circuitry may be included in the kits being shipped by the time you read this article.) In addition, it was necessary to add a switch for displaying seconds, as shown in Fig. 7.

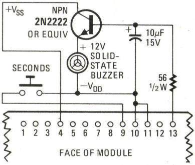

FIG. 7—ALARM DRIVER and seconds display switch added to Solid-State Time's clock.

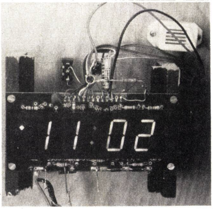

SOLID-STATE TIME alarm buzzer is driven by a simple transistor circuit wired directly to clock module.

The module and the switches are mounted on the back panel, with lots of room and accessibility.

The pendulum

The pendulum assembly is built onto a separate PC board that mounts on the inside front of the case and is connected to the clock module with only three wires. Figure 8 shows the physical layout of the pendulum, which consists of eight small LED's, wired so that both a small LED and a jumbo LED light simultaneously. A unique feature of this pendulum is that its rate of travel varies throughout its swing, the action closely simulating that of a real pendulum. This is accomplished by using a PROM (*P*rogrammable *R*ead-*O*nly *M*emory) furnished already programmed for this specific design.

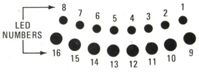

FIG. 8—SOLID-STATE PENDULUM has miniature and jumbo LED's.

Pendulum electronics

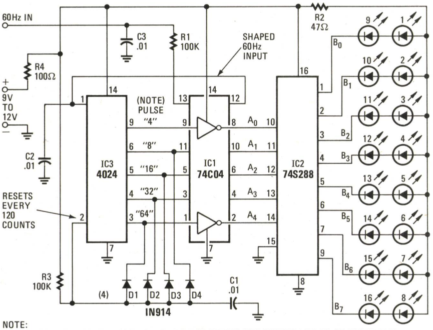

NOTE:
EACH FOURTH NEGATIVE-GOING INPUT PULSE CAUSES ONE OUTPUT LINE TO GO POSITIVE IN BINARY SEQUENCE. SEE FIGURE 10.

FIG. 9—COMPLETE PENDULUM CIRCUITRY. The 60-Hz line waveform is processed by binary counter and a PROM to light the LED pairs in a realistic sequence.

Figure 9 shows the complete pendulum circuitry. The 60-Hz signal coming from the AC line is slightly squared by resistor R1 and capacitor C3 and further squared by one inverter section of hex inverter IC1. This 60 pulse-per-second signal is fed into IC3, a binary ripple counter. Each time the pulse at the input changes from positive to ground (negative-going pulse) the counter advances one count, and the output pins count up in binary code. All the output pins are not used; in this application, pin 9, which counts every fourth pulse, has the lowest count. Output pins 9, 6, 5, 4 and 3 are fed through inverters to address PROM IC2 to determine which pair of LED's will be turned on at any instant. A 74S288 PROM is used, although a properly programmed 8223 or 74188 might also work.

Figure 10 shows how the state of each output pin of IC3 is affected by the incoming pulses. Note that pin 9 changes state every four pulses, creating a new address for the PROM. Also, note that diodes D1, D2, D3 and D4 (Fig. 9) hold the IC3 reset line low (until the 120th pulse, at which time output pins 3, 4, 5 and 6 are all high (64 + 32 + 16 + 8 = 120). At that instant, since all the diodes are now blocked, the reset line goes high through resistors R3 and R4, and the counter starts back at 0. Now, since the output lines change state every fourth pulse, and it takes 120 pulses to reach reset, that means that 120 ÷ 4 = 30 "words" are formed in 120 pulses, or 2 seconds. These words are different combinations of highs and lows fed through five IC1 inverters to address the PROM.

Although no tick-tock or chimes are available with this unit, its construction, beautiful cabinet, alarm, seconds display and unique "programmed" pendulum make this a real conversation piece for the inexperienced builder. Solid-State Time, Box 2159, Dublin, CA 94566.

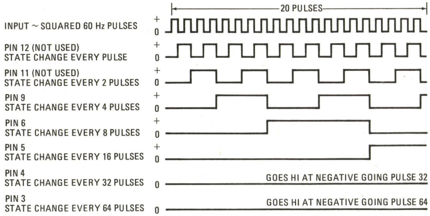

FIG. 10—OUTPUT PULSES as related to input to binary counter IC3. For example, output signal at pin 9 changes state for every four input pulses on pin 1.

Do-it-yourself digital wall clock

Here's a simple idea that will cost you almost nothing (if you own a spare LCD wrist watch) and will create an unusual conversation piece or addition to your dollhouse!

Figure 11 shows the front view (shown slightly smaller than half-size) of the *Micro-Regulator*, a microversion of the *Regulator* wall clock. You can use Fig. 11 as a model or find a mail-order or clock-catalog color photograph that you prefer. Make sure the face is larger than your own watch. Mount the clock drawing or photo on a thin piece of cardboard, and make a rectangular cutout in the clock face to match the display portion of the watch you'll use. An LCD readout is best; since it's on all the time, there are no buttons to push. Make the "cabinet" from balsa wood and glue, using wood strips to hold the watch snugly in position against the inside of the watch face. Cover the sides and back of the cabinet with maple- or walnut-colored self-adhering vinyl, trim the vinyl with a razor blade and then hang it on the wall for all to see!

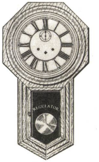

FIG. 11—CLOCK PHOTO or drawing from catalog is basis for home-made cabinet.

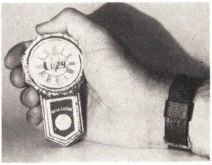

DO-IT-YOURSELF WALL CLOCK, actual clock fits easily into the palm of your hand.

No winding or time-setting is required, except when battery-changing time comes around once a year or so. You can carry this idea a little farther—with larger conventional or digital watches, digital clocks, and finally full-size *Regulator* designs with chimes, pendulums and tick-tock, but isn't that how this article began? **R-E**

You Can

Qualifying is easy. Correct answers to

About the CET Program

In 1965, the National Electronics Service Dealers Association Incorporated (NESDA) developed the Certified Electricians Program. Since that time, it has become a highly accepted, widely publicized accomplishment. Manufacturers have acknowledged and approved the program. The U.S. Department of Labor has recognized the importance of the CET plan. International Correspondence Schools, Division of In-Text, offers the CET test as a goal for their graduate electronic service/repair course students. Today, dozens of schools are using the CET exam as a standard by which to judge their curriculum content. The list of registered CET's includes radio station engineers, college professors, trade school instructors, military officers, electronic writers, electronics parts distributors, personnel, manufacturers, representatives and top service technicians from every state, plus several foreign countries.

The CET test is a multiple-choice examination, offered to electronics technicians. Technicians who pass and show proof of four years' experience and/or schooling are awarded an internationally recognized certificate suitable for framing.

A technician or student in electronics with less than four years' experience and/or schooling may apply for the associate level exam, which may be administered by the Certification Administrator in his area or, under special circumstances, at his school. The exam is the basic electronics portion of the full CET exam and must be passed with a score of 75% or better. A successful Associate CET receives a wall certificate valid for four years or until the time he is eligible to take and pass the journeyman-level exam.

A fully certified technician must pass an entire CET exam, which consists of the basic electronic portion plus any one or more of several journeyman exams. He must also have four or more years' experience in electronics. The exams are available or are being prepared in the areas of: Radio-TV (Consumer Electronics), Industrial Electronics, Communications, Audio, MATV and Medical Electronics.

SINCE THE CET (*C*ERTIFIED *E*LECTRONICS *T*echnicians) program was started in 1966 by the National Electronic Associations, Inc. (NEA), over 10,000 CET certificates have been issued to electronics technicians.

The purpose of the CET tests is to give qualified technicians international recognition and to upgrade the profession. All 50 states and 16 foreign countries now have registered CET's.

While the CET exam committee of ISCET (*I*nternational *S*ociety of *C*ertified *E*lectronics *T*echnicians) is composed of instructors from colleges, vocational schools, high schools, and commercial educational institutions, it also includes practicing service technicians. Thus, the exam is practical and valid for anyone in the electronic technology field.

By far the largest number of CET's come from the service end of consumer electronics, which is appropriate since the most critical need for recognition of competency and achievement is in the consumer area.

How to become a CET

Four years of experience and/or schooling, plus passage (by 75% or better) of the written exam, are required of every prospective CET. Any combination of experience and schooling is acceptable. For instance, a technician could qualify by having had two years of vocational electronics study, plus one year of military electronics experience, plus one year of working for a TV-radio repair shop. Or, he could have had four years of on-the-job experience as a technician in industrial, communications, or any other area of electronics work. Correspondence courses count, and any time spent in work, such as in parts supply companies, the phone company, or electrical jobs, can help fulfill the time requirement.

The written test consists of two sections: The Associate Level section, which contains seventy-five questions, *and* any one of several Journeyman Options (another seventy-five questions). The associate level contains questions that are basic for any phase of electronics work; the journeyman option questions are more specifically slanted toward a particular field of electronics. The option categories you may take in addition to the associate-level section are: Consumer Electronics, Biomedical, Industrial, Audio, MATV and Communications.

A technician with less than the required four years of schooling and/or experience may take the associate-level part of the test only. Passing the associate level qualifies you for the associate CET certificate and wallet card, and allows you membership in ISCET. Once you have a total of four years' experience, you may take the remainder of the CET exam (an option of your choice) and can become a full CET.

Preparing for the exam

Since everyone has to take the associate-level portion of the CET exam, let's take a look at some questions similar to those found in that portion. The Associate Level sections are:

Section 1. Basic mathematics
Section 2. DC circuits
Section 3. AC circuits
Section 4. Transistors and semiconductors
Section 5. Electronic components and circuits
Section 6. Test instruments
Section 7. Tests and measurements
Section 8. Troubleshooting and network analysis

Section 1 questions, basic mathematics

Here are 10 questions similar to those you will find in Section 1 of the Associate Level test. In the next article in this series, we will give the answers to these questions and provide 10 more questions

Be A CET

hundred or so questions in your specialty and you are in.

DICK GLASS

for Section 2. Analyze each question carefully and take your time. Simply place a check mark next to the correct answer.

1. Which statement is true regarding Fig. 1.

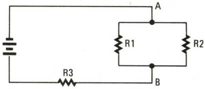

FIG. 1

( ) a. the total resistance between A and B is equal to $\sqrt{R3^2 + (R1 - R2)^2}$
( ) b. total current flow is through R3
( ) c. $R_T = \dfrac{R1 + R2}{R1 \times R2}$
( ) d. if R1 is smaller than either R2 or R3, the current flow through R1 will be larger than through either R2 or R3

2. Figure 2

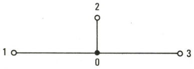

FIG. 2

( ) a. could be a vector display of an electronic circuit's inductive, capacitive, and resistive impedances
( ) b. is equivalent to the formula, $Z = \sqrt{L^2 + C^2}$
( ) c. is equivalent to the formula, $Z = \sqrt{R^2 + L^2 + C^2}$
( ) d. will mathematically equal zero if each leg (01, 02 and 03) is equal in impedance

3. A resistor dissipating 5 watts of power with 1 mA of current flowing through it would be what value?
( ) a. 5 ohms
( ) b. 5000 ohms
( ) c. 500,000 ohms
( ) d. 5 megohms

4. A resistor color-coded green, blue, red and another resistor coded yellow, violet, red are connected in parallel. What is the equivalent resistance?
( ) a. 2553 ohms
( ) b. 2555 ohms
( ) c. 25,533 ohms
( ) d. 2,555,330 ohms

5. Which statement is true regarding Fig. 3?

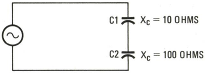

FIG. 3

( ) a. total capacitance equals 110 ohms
( ) b. C2 is the smaller-value capacitor
( ) c. total capacitive reactance is less than 10 ohms
( ) d. increasing the frequency will increase the reactance

6. A transformer has a turns ratio of 5:1. With 10 amps flowing in the primary, which of the following is true?
( ) a. 5 amps is flowing in the secondary
( ) b. 10 amps is flowing in the secondary
( ) c. 2 amps is flowing in the secondary
( ) d. 50 amps is flowing in the secondary

7. Two resistors dissipate 5 watts of power each and are connected in parallel. The same resistors connected in series and dissipating 5 watts each would give a combined equivalent dissipation of:
( ) a. 10 watts
( ) b. 5 watts
( ) c. 2.5 watts
( ) d. 7.5 watts

8. What is the wavelength (in meters) of a 300-kHz radio wave?
( ) a. 32.8
( ) b. 3.28
( ) c. 10
( ) d. 1000

9. Increasing the wire size in a coil will have what effect?
( ) a. decreases the inductance
( ) b. increases the "Q"
( ) c. increases the inductive reactance
( ) d. increases the impedance

10. In a series-resonant circuit, increasing the series resistance (R) will:
( ) a. lower the resonant frequency
( ) b. raise the resonant frequency
( ) c. sharpen the frequency response curve
( ) d. broaden the frequency response curve

The next article in this series will review the correct and incorrect answers to the Section 1 questions and present Section 2 questions. Once you feel you are ready to take the Associate or Journeyman CET exam, write to ISCET, Ron Crow, CET, Executive Director, 310½ Main St., Ames, IA 50010 (515-232-4720). ISCET will send a listing of Certification Administrators you can contact to take the test. CET study guides are also available from ISCET. **R-E**

hobby corner

Part II—A look at the various breadboarding and prototyping systems available (including a brand-new one) for building your own circuits from scratch.

EARL "DOC" SAVAGE, K4SDS, HOBBY EDITOR

LAST MONTH, WE LOOKED AT VARIOUS breadboards that are used to build and test your circuit after you've designed it. This month, we'll look at various prototyping systems that are used to build the prototype.

Prototyping boards

After your circuit has been thoroughly developed and tested on your breadboard, the next step is usually to hard-wire it. Even if you plan to build the circuit on a dedicated PC board ultimately, it is often advisable to construct a prototype for immediate use and further testing. There are a number of prototype systems you can use. Table 2 summarizes the characteristics of several prototyping systems. In this table the column marked "Density" indicates how closely components can be packed on the boards. Some universal PC boards have the highest potential density (can hold more components in a small area). Note that, as in the case of breadboarding systems, some of these system components are also interchangeable.

TABLE II—PROTOTYPING CHARACTERISTICS

					Circuit Element		Component Socket		
Manufacturer	**Pattern**	**Index**	**Density**	**Method of Wiring**	**Stability**	**Ease of Change**	**Required**	**Can Be Used**	**Speed of Use**
OK Machine & Tool Corp. 3455 Conner St. Bronx, NY 10475	.1 × .1-in. Universal PC boards	No	Medium to high	Wire-wrap	Good to fair	Good to fair	Yes	●	Medium to high
Saxton Products, Inc. 215 N. Rte. 303 Congers, NY 10920	Several types	Yes	Low to medium	Solder	Good	Good	No	Yes	Medium
Vector Electronic Co., Inc. 12460 Gladstone Ave. Sylmar, CA 91342	.1 × .1-in. Plain & Universal PC boards	Some	Low to high	Trad. solder	Good	Poor	No	Yes	Slow
				Wire-wrap	Good to fair	Good to fair	Yes	●	Medium to high
Vero Electronics, Inc. 171 Bridge Rd. Hauppauge, NY 11787	.1 × .1-in. Universal PC boards	No	Low to high	Pen-wire	Good to fair	Fair	No	Yes	High

The *DeC* system has introduced two innovations to prototyping: The first is the manner in which components are attached to the boards, which are called *Blob-Boards*. These boards are *not* drilled but the copper strips are heavily "roller-tinned." To attach a component, you simply hold a lead on the strip where it is to be fastened and use your soldering iron to deposit a blob of solder at that point. When the solder blob cools and hardens, the lead is electrically and mechanically attached. For best results, follow the recommended procedure of tinning each lead before soldering it to the board. The speed of the *DeC* system is shown in Table 2 and is classified as Medium because of the time required to tin the leads, but this system does make for a more dependable connection.

Note that it is equally easy to *remove* a component from a *Blob-Board*. Just touch the blob with a hot iron and pull the lead away. It is so easy to change components, in fact, that the manufacturer recommends that they be used in circuit design and development. And, indeed, they can be used in this manner with the advantage of having a prototype immediately when you finish. However, this method is more time-consuming than using a breadboard, and the overall construction time will be greater unless the circuit is relatively simple and few changes have to be made.

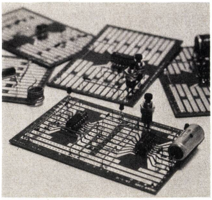

BLOB-BOARDS with prototype circuits built on them.

The second *DeC* system innovation involves the foil patterns of the *Blob-Boards*. These foil patterns are exactly like the bus structure of the various types of breadboarding DeC's. In addition, they are indexed identically! This makes it simple to transfer a circuit from DeC to *Blob-Board*—a lead is brought out from tie point D10 on the DeC and attached to D10 on the *Blob-Board*. The price you pay for this simplicity, however, is that you cannot have a high-density board.

Blob-Boards are available in various sizes, capacities and in configurations other than those that match the DeC's. There is a straight matrix board. Of special interest is the *BCB2*, which has a configuration and index identical to that of the Continental Specialties *Experimentor* breadboard sockets. The *BCB2* also matches some of the AP Products and E & L sockets, although these sockets are not indexed.

The remaining prototyping systems

(OK, Vector and Vero) are based on perforated .1 × .1-inch boards. Each system contains universal PC boards in various sizes, shapes and foil patterns. Vector also makes a plain perforated board without copper.

Wiring methods

In using any of these systems, the hobbyist must choose the best wiring method for each project. This should be given careful thought so we'll look at them in some detail. The methods are *traditional wiring, wire-wrapping* and *pen-wiring.*

Traditional wiring hardly needs explaining. For years we have been using this technique: Cut the wire, strip and bend the ends, squeeze them around the connections using needle-nose pliers, then solder. This old tried-and-true method, however, makes inefficient use of space, time and effort. There are better and more efficient methods for most modern circuits. However, some circuits require a heavier gauge wire than is normally available to the hobbyist in pen-wiring and wire-wrapping. Therefore, you should continue using traditional wiring for those circuits that carry a larger current, such as power supplies and buses, tube circuits and the like.

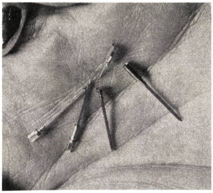

VERO WIRE-WRAP TERMINALS.

In the wire-wrapping technique, connections are made by simply wrapping wire ends around rectangular pins or terminals. An inexpensive special wire-wrapping tool insures a tight wrap and a good electrical and physical bond.The actual wrapping is very fast, but the speed is rated as medium to high because pins with rectangular cross-sections *must* be provided

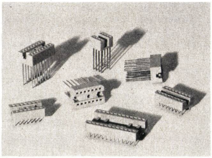

VERO IC SOCKETS; wire-wrap and solder versions.

TABLE III—PROTOTYPE WIRING SELECTION

Wiring Method	When To Use
Traditional: cut, strip and solder	Circuits carrying heavy currents; except for power supplies and buses, AF and RF final amplifiers, tube circuits.
Wire-wrap	Absolute maximum density required. Circuit element(s) that are especially heat sensitive. Wrap terminals can be provided for all (or most) connections. Many circuit changes are anticipated.
Pen-wire	Minimum board or component thickness required. Use of sockets is impractical. All other cases.

Of course, sockets and the like are readily available with wrap-pins (tails), but capacitors, resistors, etc., are not. You *cannot* wire-wrap on round pins or leads because there are no sharp corners to bite into the wire to produce a dependable low-resistance connection. There are three ways to provide wrap terminals: using wire-wrap sockets for the direct insertion of DIP's, transistors, etc.; wire-wrap sockets for the direct insertion of DIP "headers" (these have solder terminals on one side and pins on the other side that are inserted into a DIP socket) to which components have been soldered; and board feed-through pins with wrap-tails on one end and solder terminals on the other.

Every connection that does not have a proper terminal must be soldered. If there are a great many connections, the primary benefit of wire-wrapping is defeated, and you should probably use the pen-wiring method.

For old timers (like me) with an innate mistrust of anything that is not nailed down and well soldered, here are a few facts about wire-wrapping. First, you can inspect a wire-wrap connection visually for quality; if it looks all right, it is good. Second, a good wire-wrap connection is more dependable electrically than a good-looking solder joint; its resistance is as low and usually lower than that afforded by soldering. Finally and most surprising, a good wire-wrap connection is more stable mechanically than a good solder joint, especially in the case of a modified wrap in which the first turn or so is made with the insulated part of the wire. And you may be interested to know that wire-wrapping is not new — it was developed by Bell Laboratories some 30 years ago and has been time-tested. Now, we old hands can use wire-wrapping without that nagging worry that it just couldn't possibly hold up!

Because wrapped connections are readily *un*wrapped, they can be changed more easily than solder joints. In most cases, the same tool can be used for both wrapping operations. The price of wire-wrap tools manufactured by OK Machine and Tool Corporation ranges from about $6 for a simple manual model with a built-in stripper to $35 for an electrically driven unit.

Most wire-wrap systems require that you cut wire to length and end-strip it *before* wrapping. Furthermore, one individual wire is required between each two connections. Vector's *Slit-N-Wrap* wire-wrap tool automatically overcomes both of these problems.

The *Slit-N-Wrap* has a built-in device that slits the insulation *as the wrap is being made.* In addition, the tool holds a roll of wire and feeds it out as you move from one connection to another. This can save a great deal of time because the wire does not have to be cut and stripped and because you can make daisy-chain connections; you can start at one joint, move to a second and, *using the same continuous piece of wire,* proceed to a third connection, and so on.

Vector's *Slit-N-Wrap* manual tool is available in a kit with wire, an accessory knife for about $25. An electrically driven model costs $75.

If you use the cut-and-strip method of wire-wrapping, you can save some time and effort two ways. First, there are kits available containing precut and pre-stripped wires of many lengths and colors. Second, OK Machine and Tool Corp. produces a good wire dispenser with a built-in cutter and stripper ($3.50 with wire). Not to be overlooked is the advantage that the dispenser retains the wire on the spool until *you* are ready for it.

Pen-wiring, the third wiring process, is especially useful in prototyping, and maybe one the hobbyist will prefer. It is quick and easy, and no special posts or terminals are needed, although you can obtain some handy ones for board feed-through and the like. The pen-wiring process uses a pen-like device that holds a small spool of wire on the upper end. The wire is fed down through the body of the tool and out the pointed tip.

In using the pen-wiring technique, just move the point around a terminal or lead (round, square or whatever) to make two or three turns of the wire. Trail the wire out to the next joint, make two or three turns and, then, proceed on to the next joint in daisy-chain fashion. In the process, the insulation is not removed from the wire. In fact, the insulation *should* not be removed because it is made of a special composition that causes it to be

continued on page 105

BUYING GUIDE

Compact Pro Speakers

HISTORICALLY, HIGH-POWERED SOUND REinforcement loudspeaker systems have been heavy and large. Not only are these speakers difficult to transport, they also require special skills for permanent mounting. Lately, however, smaller, more compact systems are displacing these giant systems. The smaller speakers can handle reasonable amounts of power while being easy for one person to operate and transport.

How can you recognize a compact sound reinforcement speaker system? Certain characteristics are self-evident. First, you should be able to carry the speaker yourself. This places upper limits for size and weight in the vicinity of 0.1 cubic meters (3.5 cubic feet) and 20 kilograms (44 pounds), although I'm sure most readers can carry more than this. Second, the speaker should deliver high sound-pressure levels, i.e., 105 dB to 110 dB at 3 meters (10 feet). Finally, you should be able to plug the speaker into a medium-size power amplifier (100 watts into 8 ohms) without sending woofer-cone fragments into the front row. In short, the compact sound reinforcement speaker system closes the gap between the home hi-fi speaker and the big sound reinforcement speaker.

Now that you know some of the system's basic characteristics, you may ask why they are gaining in popularity. Traveling musicians find the portability a genuine asset. Small speaker systems eliminate having to wrestle big boxes through narrow doorways and up and down stairs. And when it's time to go home, compact speakers do not need to be transported by a van or station wagon.

Sound installers find the speakers' compact size very convenient for mounting in small auditoriums, churches and lounges. Even in large auditoriums, the compact speaker works well in a distributed system. The small size also works well in a discotheque system, although a low-frequency equalizer should be used to provide more thump in the low end. In total, the compact system provides added flexibility when you must tailor the sound to a particular room.

The flexibility of compact systems becomes apparent again if stacking is desired. Stacking—placing one speaker on top of another—increases the horizontal penetration and spread of a sound system while reducing vertical radiation. Column speaker systems have used this principle effectively for years.

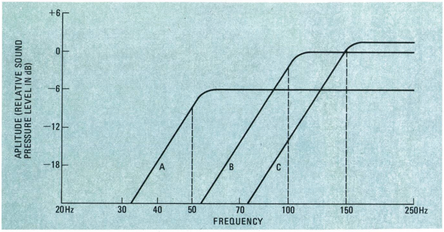

FIG. 1—FREQUENCY RESPONSE can be tailored to different needs. Speaker system A has the best bass response but provides a lower overall output. Speaker system C has a much higher overall output but at a sacrifice in bass response.

If these features are attractive to the speaker buyer, how does he choose the compact system best for him? The answer, quite logically, depends on an honest appraisal of his needs and budget. Every feature, or the quality of every feature, has its cost, which may be in dollars and cents or in performance tradeoffs. The following discussion will examine how all these factors interrelate.

Frequency response

The first consideration when you buy a speaker, whether it be for hi-fi or sound reinforcement, is the system's frequency response. Flat-amplitude response over the entire audio range is usually the goal. However, in a compact system, response to the extreme lows and highs at high power levels does not come inexpensively. So, let's take a look at the first tradeoff.

For low frequencies, the speaker-system designer reaches a compromise by juggling amplitude, efficiency, box volume and cost factors. Often distortion and power handling play a role in this compromise. Figure 1 shows the results of three design approaches, each using the same enclosure volume. The examples are intended to be general, but it should be noted that a ported cabinet gives the designer extra flexibility over a closed cabinet. A port allows the cabinet to be tuned for more low-end response, given a particular driver.

The designer of system "A" chose a 3-dB-down (half-power) frequency at 50

---

* The following article was written while the author was a Senior Development Engineer at Shure Brothers Inc., Evanston, IL.

Compact professional speakers fill the gap between hi-fi speakers and cumbersome full-size pro speakers. Here's what you should know before you buy.

RONALD J. BREY*

Hz. However, since a compact system was designed, he could not use a large cabinet to achieve the desired response; instead he used a woofer with a low resonance frequency. Unfortunately (and here is the tradeoff), to achieve that low resonance frequency, some potential woofer efficiency was sacrificed.

The designer of system "B" has taken the opposite approach to system "A." Instead of 50 Hz, the 3-dB-down frequency is 100 Hz, the result of this sacrifice being a 6-dB higher level at 200 Hz.

The designer of system "C" has taken a completely different approach. Many woofers are used to achieve good power handling. However, with many woofers in the same box, each one adds less volume and, consequently, the low-frequency response suffers. However, with good power handling, an equalizer for boosting the bass plus a higher-powered amplifier can restore the low end.

Once the speaker is on the market, you must consider the tradeoffs. If you like a deep low end and possess a good-size amplifier, system "A" will probably fit the bill. On the other hand, if amplifier power is at a premium or high sound-pressure level is needed, system "B" will be a better choice. And if small cabinet size is a must, while amplifier power comes easy, system "C" is the best option.

A number of factors go into the low-frequency melting pot. You should pick the product that has the best mix of factors for your needs and budget. And when you look at the budget, don't forget that extra amplifier watts cost more money.

What should you look for next in high-frequency performance? Should it be flat response and high efficiency? The answer is a qualified "yes."

Flat-amplitude response at the high end is usually desirable. However, a room that is acoustically bright (with hard floors and walls) requires a reduced high end for listener comfort. A compact system should have some means of attenuating the high frequencies, whether it be a potentiometer, a switch, or an equalizer. And if a speaker has a high-frequency level control, don't be afraid to move it from the flat position.

Tweeter efficiency for compact sound reinforcement systems is usually no problem. Woofer efficiency is usually harder to achieve, so tweeters are often padded down to the level of the woofer.

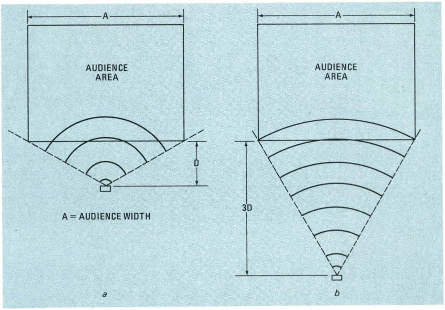

FIG. 2—WIDE POLAR RESPONSE enables speaker to cover greater area from a shorter distance as shown in *a*. Narrow polar response requires greater distance between speaker and audience to cover same area as shown in *b*.

Polar response

One important difference between the compact sound reinforcement speaker and the larger speakers is in polar response. A big sound reinforcement speaker is often designed to project long distances in a narrow arc, while the compact speaker is usually designed to cover shorter distances in a wider arc. The reason for the difference is shown in Fig. 2. To cover the same width at a closer distance, the speaker shown in Fig. 2-a has to have a wider high-frequency coverage angle than the speaker shown in Fig. 2-b.

Such a wide polar response also works well in stage monitoring in case a performer wishes to move around during a performance. Although monitors with a narrow coverage angle are sometimes needed, they require the performer to stay in one location in order to hear himself properly.

The wide polar response for a compact system is easily achieved at low frequencies because of the long wavelengths. As a rule of thumb, a direct radiator (cone) loudspeaker is essentially nondirectional until the wavelength becomes shorter than three times its diameter.[1] This, in turn, means that special methods are often needed to achieve wide polar response at high frequencies.

Two such methods for broadening high-frequency polar response are by using an acoustic lens or multiple drivers facing different directions. The acoustic lens, which can take many shapes, slows wave propagation near the edges of a tweeter opening to obtain a circular wavefront with wider polar response.[2] The multiple-driver method takes narrow-beam tweeters and, through careful placement, collectively achieves a wider polar response. If the tweeters are not carefully positioned, the collective polar response may be narrower rather than broader than a single speaker.

A straightforward method of achieving wide high-frequency polar response is by using a horn. A few designs use a sectoral horn (see Fig. 3). The side walls of the horn define the horizontal pattern, so a

You gotta shop around.

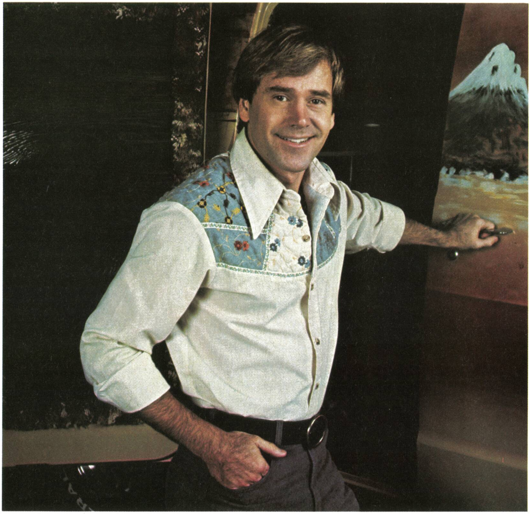

When you do, you'll probably pick CIE. You can't afford to settle for less when it comes to something like electronics training that could affect your whole life.

When you shop around for tires, you look for a bargain. After all, if it's the same brand, better price—why not save money?

Education's different. There's no such thing as "same brand." No two schools are alike. And, once you've made your choice, the training you get stays with you for the rest of your life.

So, shop around for your training. Not for the bargain. For the best. Thorough, professional training to help give you pride and confidence.

* * *

If you talked to some of our graduates, chances are you'd find a lot of them shopped around for their training. They pretty much knew what was available. And they picked CIE as number one.

Why you should shop around yourself.

We hope you'll shop around. Because, frankly, CIE isn't for everyone.

There are other options for the hobbyist. If you're the ambitious type—with serious career goals in electronics—take a close look at what we've planned for you at CIE.

What you should look for first.

Part of what makes electronics so interesting is it's based on scientific discoveries—on ideas! So the first thing to look for is a program that starts with ideas and builds on them!

That's what happens with CIE's Auto-Programmed® Lessons. Each lesson takes one or two principles and helps you master them—before you start using them!

How practical is the training?

This is the next big important question. After all, your career will be built on what you can do—and on how well you do it.

Here are ways some of CIE's troubleshooting programs help you get your "hands-on" training...

With CIE's Experimental Electronics Laboratory... you learn and review the basics—perform dozens of experiments. Plus, you use a 3-in-1 precision Multimeter to learn testing, checking, analyzing!

When you build your own 5 MHz Triggered-Sweep, Solid-State Oscilloscope you take your first real professional step. You use it as a doctor uses an X-ray machine—to "read" waveform patterns... lock them in... study, understand and interpret them!

When you get your Zenith 19-inch Diagonal Solid-State Color TV you apply your new skills to some real on-the-job-type troubleshooting! You learn to trace signal flow... locate malfunctions... restore perfect operating standards—just as with any sophisticated electronics equipment!

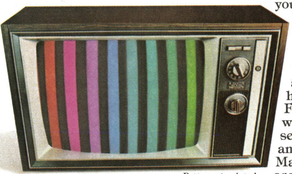

Pattern simulated.

When you work with a completely Solid-State Color Bar Generator—actually a TV signal transmitter—you study up to ten different patterns on your TV screen... explore digital logic circuits... observe the action of a crystal-controlled oscillator!

Of course, CIE offers a more advanced training program, too. But the main point is simply this:

All this training takes effort. But you'll enjoy it. And it's a real plus for a troubleshooting career!

Do you prepare for your FCC License?

Avoid regrets later. Check this out before you enroll in any program.

For some troubleshooting jobs, you must have your FCC License. For others, employers often consider it a mark in your favor. Either way, it's government-certified proof of specific knowledge and skills!

More than half of CIE's courses prepare you for the government-administered FCC License exam. In continuing surveys, nearly 4 out of 5 CIE graduates who take the exam get their Licenses!

Shop around... but send for CIE's free school catalog first!

Mail the card. If it's gone, cut out and mail the coupon. If you prefer to write, mention the name and date of this magazine. We'll send you a copy of CIE's FREE school catalog—plus a complete package of independent home study information! For your convenience, we'll try to have a representative contact you to answer your questions. Mail the card or coupon—or write: CIE, 1776 East 17th St., Cleveland, OH 44114.

CIE Cleveland Institute of Electronics, Inc.
1776 East 17th Street, Cleveland, Ohio 44114
Accredited Member National Home Study Council

☐ **YES...** I'm shopping around for the **right** kind of career training in electronics troubleshooting—and CIE sounds well worth looking into. Please send me my FREE CIE school catalog—including details about troubleshooting courses—plus my FREE package of home study information! **RE-34**

Print Name________________

Address__________ Apt.______

City________________

State__________ Zip______

Age______ Phone__________
(area code)

Check box for G.I. Bill information:
☐ Veteran ☐ Active Duty

Mail today!

120° angle between the side walls will create a 120° horizontal pattern. This horizontal pattern will generally hold until the very high frequency range, depending on the horn dimensions. A few words of caution—the vertical pattern of the sectoral horn varies with the frequency and decreases with increasing frequency, so that a horizontal orientation of the horn is generally preferred. Such horns should not, however, be confused with many presently on the market that have a marked flare in the side, top and bottom walls. At high frequencies, these horns show a definite narrowing of both the horizontal and vertical polar patterns.

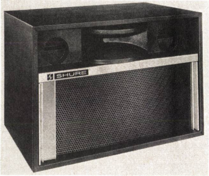

FIG. 3—SIDE WALLS OF HORN define horizontal radiation pattern while top and bottom walls define vertical radiation pattern.

Power handling

Power handling for compact systems is usually more of a problem for the tweeters than the woofers. Although most manufacturers supply a high-frequency or system power-handling specification, you should be aware that no standard exists for power handling. Manufacturers differ in their power-handling measurement philosophies. For example, some believe that a good power test is a 100-hour speaker system performance test without failure or degradation. The test signal consists of a tape recording of various representative live performances in conjunction with a power amplifier driven into peak clipping typical of the loudspeaker application.[3] The nominal impedance of the speaker system and the amplifier output voltage at clipping determines the power rating. It is felt that this test simulates actual use better than sinewaves, swept sinewaves or pink noise, and that it is important to know the power rating of the largest power amplifier that can be used with the loudspeaker system. Other manufacturers prefer the latter measurement signals, and can make a good case for using them. Depending on the measurement method, the results can vary significantly.

Where does this leave you as a potential customer? You can either accept the manufacturer's rating or rely on word-of-mouth from other users. In any case, you should not exceed the manufacturer's suggested maximum amplifier power rating (if it is given) for the speaker, even though precautions such as fuses may prevent speaker damage. Then, if a power-handling catastrophe occurs, you can approach the manufacturer with a legitimate complaint. But, if you hook up a speaker rated at 100 watts to a 200-watt amplifier, don't expect much sympathy from the manufacturer (although you may get some anyway)!

Sensitivity

Since high sound-pressure levels (SPL's) are one goal of compact sound reinforcement speaker systems, you may be concerned with how large an amplifier is needed to achieve those levels. The answer is provided by the speaker system efficiency, which is the acoustical power output of the system versus electrical power input into the system. Because efficiency is usually difficult and time-consuming to measure, on-axis sensitivity is specified instead.

TABLE 1—CONVERSION FACTORS to change other sensitivity ratings to EIA.

DISTANCE CONVERSION VALUES		POWER CONVERSION VALUES	
Distance	**Subtract** dB	**Power** (watts)	**Subtract** dB
3 feet	20.0	0.01	10.0
1 meter	19.2	0.1	20.0
4 feet	17.5	0.5	27.0
6 feet	14.0	1.0	30.0
2 meters	13.2	1.5	31.8
3 meters	9.7	2.0	33.0
10 feet	9.5	4.0	36.0
15 feet	6.0	10.0	40.0
5 meters	5.2	25.0	44.0
20 feet	3.5	50.0	47.0

Example: Given 95.5-dB SPL at 4 feet, 1-watt input.
EIA equivalent = 95.5 − 17.5 (distance conversion) − 30 (power conversion) = 48-dB SPL.

On-axis sensitivity relates the SPL produced at a certain distance by a speaker system to electrical power input. Many manufacturers specify EIA (*E*lectronic *I*ndustries *A*ssociation) sensitivity, which is measured at 9.2 meters (30 feet) with an electrical input of 1 mW. Although the driving signal and speaker impedance rating can vary with each manufacturer (which moderately affects results), you can use the rating to compare similar speaker systems.

Some manufacturers specify on-axis sensitivity at distances less than 30 feet and at powers greater than 1 mW. Unless some unusual test conditions are used, the numbers can be converted to EIA sensitivities. Table 1 shows how many dB should be subtracted to convert other ratings to EIA sensitivity.

Home high-fidelity loudspeakers generally have EIA sensitivities in the SPL range of 30 dB to 45 dB. Comparing a popular hi-fi speaker to a popular compact sound reinforcement system, their EIA sensitivities are 42 dB and 48 dB, respectively, a 6-dB difference. For every 3-dB decrease in sensitivity, twice the power is needed to obtain the same SPL. So the 6-dB difference means the speaker with the lower sensitivity requires four times the amplifier power to achieve the same SPL. Four times the amplifier power (for instance, going from a 50-watt amplifier to a 200-watt amplifier) translates into quite a few dollars and a lot of weight.

Speaker enclosures

When you have narrowed your choice of compact speakers down to a few on the basis of their acoustic properties, you should look at their construction. You probably want the speaker to look good and at the same time provide reliable service. Additionally, you may want some convenience items for mounting and carrying.

The first item to check, and probably the most difficult to find information on, is the speaker's construction material. Generally, two kinds of wood are used for cabinet construction: particleboard (sometimes referred to as flakeboard or pressboard) and plywood. Particleboard keeps cabinet costs down, but it weighs more and deteriorates more rapidly if it gets wet. Plywood, on the other hand, because it contains long wood fibers and is of a laminated construction, is stronger and less affected by temperature and humidity.

The wood thickness should be at least ½ inch for strength; ⅝-inch or ¾-inch material is generally preferred. However, here's another tradeoff: the thicker the wood, the more it will weigh and cost.

Certain manufacturers use thermoplastic structural foam as a basic cabinet material. Some cabinets use thermoplastic extensively, while others use it in special areas, such as in the baffle board

continued on page 100

Radio-Electronics Tests Rotel Model RX-803 FM/AM Receiver

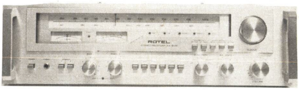

CIRCLE 101 ON FREE INFORMATION CARD 1

LEN FELDMAN
CONTRIBUTING HI-FI EDITOR

THE MODEL RX-803 RECEIVER (SEE FIG. 1) IS Rotel of America, Inc.'s third most powerful all-in-one stereo component. The three-dimensional gold-colored front panel has the unusual dial-area opening that is characteristic of other Rotel receivers. This odd-shaped opening permits the signal-strength and center-of-channel tuning meters to appear below the linearly calibrated FM frequency scale and the AM frequency scale. A stereo indicator light is placed between the two meters, while program source indicator lights are evenly spaced below the right-hand section of the frequency dials. A large tuning knob to the right is coupled to an effective flywheel/dial-pointer combination. Five small pushbuttons below the dial opening take care of FM muting, the selection of either 75- or 25-μs FM de-emphasis (the latter used for FM Dolby reception, in combination with a separate external Dolby decoder not provided), mono/stereo selection, loudness and −15-dB audio muting.

Additional pushbuttons along the bottom of the panel are used for POWER turn-on, SPEAKER selection (either or both sets of speakers can be connected), TONE DEFEAT, low- and high-cut filters, tape monitoring and tape dubbing of up to two connected tape decks. A headphone jack is located near the POWER on-off pushbutton. Rotary controls include dual concentrically mounted BASS and TREBLE knobs, a program selector (including positions for PHONO 1 and PHONO 2, AM, FM and AUX), a calibrated BALANCE control and a step-type calibrated master VOLUME control that attenuates signals in 2-dB steps down to −24 dB (from maximum setting), and in larger dB increments from that level downward.

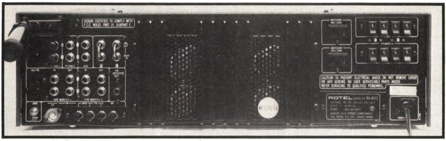

2

The rear panel of the *model RX-803* contains low-level, high-level and antenna input jacks; preamplifier-out/main amplifier-in jacks (interconnected by wire jumpers); and a ground terminal and FM detector (multiplex) output jack. This array of connections is located on the left-hand side of the rear panel, far removed from the twin sets of spring-loaded speaker terminals and the two convenience AC receptacles at the far right. The antenna terminals permit using either 300-ohm or 75-ohm coaxial transmission lines, and, in addition to the external AM antenna terminal, there is a built-in pivotable ferrite-bar AM antenna. European-type DIN multiple-pin connectors are also provided for one of the tape circuits and one of the two phono circuits. Output transistors, covered with protective screening and mounted on vertically finned heat-sink structures, occupy the center of the rear panel (Fig. 2).

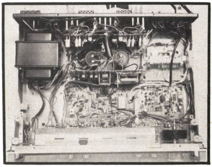

3

An internal view of the chassis is shown in the photo of Fig. 3. The large PC board in the front contains the entire FM-IF, stereo multiplex, AM and tone-control amplifier circuits. Two identical vertically mounted power-amplifier modules are located near the rear of the chassis, with the power transformer on one side and the separate RF front-end on the other side. A pair of 10,000-μF filter capacitors (for the B+ and B− output-transistor power supplies) are nestled between the two power amplifiers.

The FM front-end uses a dual-gate FET RF stage and a four-gang tuning capacitor. Extensive use is made of IC's in the FM-IF section,

MANUFACTURER'S PUBLISHED SPECIFICATIONS:

FM TUNER:
Usable Sensitivity: mono, 1.8 μV (10.4 dBf). **50-dB Quieting:** mono, 3.2 μV (15.2 dBf). **S/N Ratio:** mono, 70 dB; stereo, 65 dB. **Harmonic Distortion:** mono, 0.1% at 100 Hz and 1 kHz, 0.3% at 6 kHz; stereo, 0.3% at 100 Hz and 1 kHz, 0.5% at 6 kHz. **Frequency Response:** 30 Hz to 15 kHz, +0.3, −1.0 dB. **Capture Ratio:** 1.5 dB. **Selectivity:** 75 dB. **Spurious Rejection:** 90 dB. **Image Rejection:** 85 dB. **IF Rejection:** 95 dB. **AM Suppression:** 60 dB. **Stereo Separation:** 43 dB at 1 kHz; 30 dB at 30 Hz to 15 kHz.

AM TUNER:
Sensitivity: 250 μV/M (internal antenna); 12.5 μV (external antenna).

AMPLIFIER:
Power Output: 70 continuous watts-per-channel into 8 ohms, 20 Hz to 20 kHz. **Rated Harmonic Distortion:** 0.2% (0.08% at 1 watt). **IM Distortion:** 0.2% (0.1% at 1 watt). **Damping Factor:** 50 into 8 ohms. **Input Sensitivity:** phono 1 & 2, 2.5 mV; high level, 150 mV. **Phono Overload:** 200 mV. **Frequency Response:** phono, RIAA ±0.3 dB. **Bass and Treble Control Range:** ±10 dB at 100 Hz and 10 kHz. **Low- and High-Filter Cutoff:** 40 Hz and 12 kHz (12 dB-per-octave). **S/N Ratio:** phono, 75 dB, IHF "A"-weighted; high level, 90 dB, IHF "A"-weighted. **Audio Muting:** −15 dB.

GENERAL SPECIFICATIONS:
Power Consumption: 520 watts maximum, 120 volts, 60 Hz. **Dimensions:** 19¼ W × 5.7 H × 16⅛ inches D. **Net Weight:** 30.9 lbs. **Suggested Retail Price:** $480.

the AM circuitry and the stereo-decoder section. Fixed ceramic-type filters are used in the FM-IF section, and a wideband quadrature-detector circuit recovers composite FM audio signals that are then fed to a phase-locked-loop stereo decoder requiring no tuning coils or capacitors.

Tone control is handled by the familiar Baxandall negative-feedback circuit, while cutoff filters each use dual R–C filter networks to approach 12-dB-per-octave slopes. Each power output module uses a differential amplifier input stage and complementary pairs of NPN-PNP direct-coupled output transistors. An electronic protection circuit combined with a relay guards against speaker damage or amplifier overload. As further protection, there are fuses in series with all secondary windings of the power transformer. Positive and negative output voltages are just over 47 each, while the lower voltages required by the tuner and low-level amplifier sections are all electronically regulated. You can place a simple strapping plug inside the chassis for U.S. or European and other foreign voltages.

FM measurements

Table 1 summarizes measurements made for the FM tuner section. The results can be compared with the manufacturer's published specifications shown elsewhere in this report. Usable sensitivity was an impressively low 1.6 μV (9.3 dBf) in mono and 4.5 μV (18.3 dBf) in stereo. More important, 50-dB quieting was reached with signal inputs of only 2.5 μV (13.1 dBf) in mono and 32 μV (35.3 dBf) in stereo. Signal-to-noise ratio was a bit better than claimed in both mono and stereo, as were most of the other secondary measurements. While most of the mono and stereo distortion measurements were lower than claimed, this was not the case for our 100-Hz stereo measurements, which resulted in a 0.4% reading.

Figure 4 is a spectrum analysis showing the desired and crosstalk output signals for one channel, including the standard 75-μs de-emphasis. The unusual crosstalk peak at around 200 Hz was thought at first to be a result of a defect in our sweep system; however, repeated static measurements showed that this slight reduction in separation at the 200-Hz frequency does occur. At its worst, however, there is still nearly 40 dB of stereo separation. So whatever the cause of this phenomenon, it can be ignored for all practical purposes. Note, too, the excellent 19-kHz filtering that occurs at the end of the sweep to remove unwanted subcarrier output signals.

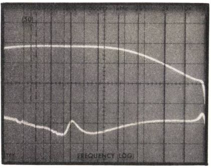

4

Amplifier measurements

The amplifier of the *model RX-803* delivered 77-watts-per-channel into 8-ohm loads with a 1-kHz test frequency before the THD reached its rated 0.2% value. There was some

TABLE 1
RADIO-ELECTRONICS PRODUCT TEST REPORT

Manufacturer: **Rotel of America, Inc.** Model: **RX-803**

FM PERFORMANCE MEASUREMENTS

SENSITIVITY, NOISE AND FREEDOM FROM INTERFERENCE	**R-E Measurement**	**R-E Evaluation**
IHF sensitivity, mono: (μV) (dBf)	1.6 (9.3)	Superb
Sensitivity, stereo (μV) (dBf)	4.5 (18.3)	Very good
50-dB quieting signal, mono (μV) (dBf)	2.5 (13.1)	Excellent
50-dB quieting signal, stereo (μV)	32 (35.3)	Excellent
Maximum S/N ratio, mono (dB)	71	Very good
Maximum S/N ratio, stereo (dB)	68	Very good
Capture ratio (dB)	1.1	Excellent
AM suppression (dB)	60	Excellent
Image rejection (dB)	86	Very good
IF rejection (dB)	95	Excellent
Spurious rejection (dB)	93	Very good
Alternate channel selectivity (dB)	77	Very Good
FIDELITY AND DISTORTION MEASUREMENTS		
Frequency response, 50 Hz to 15 kHz (±dB)	+0, −1.3	Good
Harmonic distortion, 1 kHz, mono (%)	0.11	Excellent
Harmonic distortion, 1 kHz, stereo (%)	0.19	Excellent
Harmonic distortion, 100 Hz, mono (%)	0.19	Very good
Harmonic distortion, 100 Hz, stereo (%)	0.40	Fair
Harmonic distortion, 6 kHz, mono (%)	0.13	Excellent
Harmonic distortion, 6 kHz, stereo (%)	0.20	Excellent
Distortion at 50-dB quieting, mono (%)	0.38	Excellent
Distortion at 50-dB quieting, stereo (%)	0.35	Very good
STEREO PERFORMANCE MEASUREMENTS		
Stereo threshold (μV) (dBf)	5.0 (19.2)	Very good
Separation, 1 kHz (dB)	42	Excellent
Separation, 100 Hz (dB)	40	Excellent
Separation, 10 kHz (dB)	26	Good
MISCELLANEOUS MEASUREMENTS		
Muting threshold (μV) (dBf)	2.0 (11.2)	Excellent
Dial calibration accuracy (±kHz at MHz)	100 at 98	Very good
OVERALL FM PERFORMANCE RATING		Excellent

TABLE 2
AMPLIFIER PERFORMANCE MEASUREMENTS

POWER OUTPUT CAPABILITY	**R-E Measurement**	**R-E Evaluation**
RMS power/channel, 8-ohms, 1 kHz (watts)	77.0	Very good
RMS power/channel, 8-ohms, 20 Hz (watts)	74.0	Very good
RMS power/channel, 8-ohms, 20 kHz (watts)	70.0	Good
RMS power/channel, 4-ohms, 1 kHz (watts)	100	Very good
RMS power/channel, 4-ohms, 20 Hz (watts)	87	Good
RMS power/channel, 4-ohms, 20 kHz (watts)	85	Good
Frequency limits for rated output (Hz-kHz)	15-20	Good
DISTORTION MEASUREMENTS		
Harmonic distortion at rated output, 1 kHz (%)	0.065	Very good
Intermodulation distortion, rated output (%)	0.15	Good
Harmonic distortion at 1-watt output, 1 kHz (%)	0.025	Excellent
Intermodulation distortion at 1-watt output (%)	0.03	Excellent
DAMPING FACTOR, AT 8 OHMS	35	Very good
PHONO PREAMPLIFIER MEASUREMENTS		
Frequency response (RIAA ±dB)	0.3	Very good
Maximum input before overload (mV)	230	Excellent
Hum/noise referred to full output (dB) (at rated input sensitivity)	72 (77 wt'd)	Excellent
HIGH LEVEL INPUT MEASUREMENTS		
Frequency response (Hz-kHz, ±dB)	8-40, 1.0	Excellent
Hum/noise referred to full output (dB)	90	Excellent
Residual hum/noise (minimum volume) (dB)	100	Excellent
TONAL COMPENSATION MEASUREMENTS		
Action of bass and treble controls	See Fig. 5	Very good
Action of secondary tone controls		N/A
Action of low-frequency filter(s)		Excellent
Action of high-frequency filter(s)		Good
COMPONENT MATCHING MEASUREMENTS		
Input sensitivity, phono 1/phono 2 (mV)	2.5/2.5	
Input sensitivity, auxiliary input(s) (mV)	150	
Input sensitivity, tape input(s) (mV)	150	
Output level, tape output(s) (mV)	150	
Output level, headphone jack(s) (V or mW)	563 mV (8 ohms)	
OVERALL AMPLIFIER PERFORMANCE RATING		Very good

power margin at the low-frequency end of the spectrum, too, but at 20 kHz, the amplifier was able to deliver only its rated 70-watts-per-channel. Intermodulation distortion came close to its rated 0.2% value, but decreased significantly at all lower power levels, well below the 0.08% claimed for a 1-watt output.

As for the preamplifier, all input sensitivities were precisely as claimed by the manufacturer. Phono overload was even higher than the rated 200 mV. RIAA equalization accuracy was within 0.3 dB from 30 Hz to 15 kHz, and even unweighted phono hum and noise was an impressive 72 dB referred to an input sensitivity of 2.5 mV.

Tone control range of BASS and TREBLE is shown in Fig. 5; the pivot point of these controls is set at around 700 Hz. The flat response curve in Fig. 5 was achieved with the tone controls defeated, and in a separate point-by-point sweep, was found to extend from 8 Hz to 40 kHz for the −1-dB rolloff points.

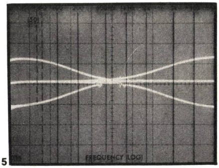

5

TABLE 3

RADIO-ELECTRONICS PRODUCT TEST REPORT

Manufacturer: Rotel of America, Inc. **Model: RX-803**

OVERALL PRODUCT ANALYSIS

Retail price	$480
Price category	Medium
Price/performance ratio	Excellent
Styling and appearance	Very good
Sound quality	Excellent
Mechanical performance	Excellent

Comments: Rotel not only maintains a family resemblance between its higher-, medium- and lower-powered sets, but also provides a great degree of control and switching facility even in their more moderately powered, modestly priced sets. Of course, 70-watts-per-channel is not a low amount of power, but in view of the power race which seems to be going on in receivers one tends to lose sight of that fact. The power output of the *model RX-803* was great enough to drive our standard low-efficiency air-suspension lab speaker systems to well over 100-dB sound-pressure levels in a 14 × 22-foot listening room. The sound quality was quite transparent, with little transient distortion or even occasional clipping. The tuner section actually outperforms the amplifier section by a small margin. The front-panel de-emphasis switch makes conversion to FM Dolby reception simple, particularly if you aleady own a cassette deck with a built-in Dolby decoder. Just about every published FM performance specification was met or exceeded. AM performance, on the other hand, is average and typical of many high-fidelity receivers. Phono performance was excellent, and there was no evidence of phono overload even when relatively high output cartridges were used. Residual hum and noise in phono, under actual listening conditions, was extremely low—almost inaudible. From an aesthetic standpoint, we would have preferred it if Rotel had omitted those protruding handles on the front panel; they really serve no purpose whatever.

On a straight power-versus-price comparison, the *model Rotel RX-803* offers extremely good value when compared with similarly rated, better-known receivers.

Summary

Table 2 contains a summary of all amplifier measurements made on the *model RX-803*. Table 3 contains an overall product analysis as well as our summary comments regarding the listening qualities of the receiver. We found that the controls performed smoothly and up to expectations. FM calibration was accurate to within 100 kHz or better across the entire FM dial. Although the Rotel of America line of hi-fi equipment is perhaps not as familiar to most readers as some other more popular items, the *model RX-803* deserves high marks for quality. **R-E**

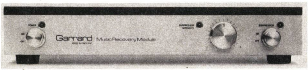

CIRCLE 102 ON FREE INFORMATION CARD

1

Garrard MRM-101 Noise Supressor Phono Preamp

GARRARD'S *MODEL MRM-101* IS *NOT* ANOTHER record player, despite the company's acknowledged reputation in the turntable field. Rather, the *model MRM-101* (the initials stand for *M*usic *R*ecovery *M*odule) is intended to remove the objectionable popping and clicking noises that are heard when a phono pickup meets a scratch in the groove of a record being played. Unlike an earlier impulse noise suppressor manufactured by SAE (the *model 5000*), the Garrard device, shown in Fig. 1, also contains a complete preamplifier-equalizer circuit so that the outputs from the *model MRM-101* can connect to a high-level pair of inputs on your amplifier or receiver, such as the auxiliary inputs.

The front panel of the *model MRM-101* has only a few easy-to-use controls. At the left is a power on-off switch with an associated indicator light. A symmetrically positioned control knob at the extreme right turns the suppressor circuitry on and off, and an indicator light near this control illuminates when the suppression circuit is introduced. The remaining larger knob at the right adjusts the sensitivity at which the scratch suppression operates. Turning this control to the right causes the unit to be triggered by relatively smaller scratches in the record, while turning the knob counterclockwise increases the scratch amplitude required to trigger the suppression circuitry. Triggering of the suppressor is indicated by a third indicator that flashes only when a scratch is being detected and suppressed.

The rear panel contains both phono-tip and DIN input and output terminals, as well as a grounding terminal to which the turntable ground wire must be connected.

How it works

The *model MRM-101,* in addition to con-

MANUFACTURER'S PUBLISHED SPECIFICATIONS:

Input: suitable for cartridges having outputs of 0.7 to 2.0 mV-per-cm-per-sec. **Input Impedance:** 47,000 ohms. **Frequency Response:** 20 Hz to 20 kHz, ±1.5 dB (including RIAA equalization). **Dynamic Range Via Suppressor:** greater than 80 dB. **Nominal Output:** 300 mV. **THD at Nominal Output, 1 kHz:** (direct) less than 0.01%; (via suppressor) less than 0.1%. **Channel Balance:** better than 2.0 dB at 1 kHz. **Output for 1.0% THD at 1 kHz:** (suppressor out) 8.0 volts; (suppressor in) 2.5 volts. **Output Impedance:** 3300 ohms. **Rated Load Impedance:** greater than 10,000 ohms. **Power Requirements:** 120 volts AC, 50 to 60 Hz, 7 VA. **Dimensions:** 14⅞ W × 2.8 H × 11¾ inches D. **Weight:** 8.16 lbs. **Suggested Price:** $200.

taining a preamplifier/equalizer circuit, has a scratch-detection circuit that recognizes the waveform of a scratch and distinguishes it from the peaks of recorded music. In order to allow the scratch-detection circuit sufficient time to remove the scratch, both audio channels are individually delayed by a few milliseconds without limiting the audio frequency range of the signal path. After the scratch is recognized, a specially designed network isolates the signal for a sufficient length of time to enable the scratch noise to pass out of the channel delay lines, after which the signal paths to the output terminals are restored. The duration of the signal interruption is so slight that the listener does not have time to detect the absence of music. An internal view of the *model MRM-101* is shown in Fig. 2.

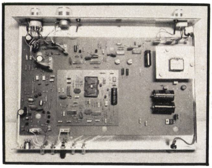

2

TABLE 1

RADIO-ELECTRONICS PRODUCT TEST REPORT

Manufacturer: **Garrard** Model: **MRM-101**

PREAMPLIFIER/NOISE SUPPRESSOR PERFORMANCE MEASUREMENTS

SPECIFICATIONS	**R-E Measurement**	**R-E Evaluation**
Frequency response (including equalization) (Hz-kHz)	20-20, ±1 dB	Excellent
Suppressor in	20-20, ±3 dB	Good
Voltage gain, 1 kHz (dB)	35.5	Good
Nominal output (mV)	300	(Reference value)
Output for 1% THD (V)		
Suppressor out	10.0	Excellent
Suppressor in	2.0	Fair
Distortion at nominal output (%)		
Suppressor out	0.015	Excellent
Suppressor in	0.10	Good
S/N ratio (dB, unweighted)		
Suppressor out	77	Excellent
Suppressor in	70	Excellent
EVALUATION OF CONTROLS, CONSTRUCTION AND DESIGN		
Ease of installation		Excellent
Arrangement of controls		Excellent
Action of controls and switches		Very good
Design and construction		Excellent
Ease of servicing		Very good
OVERALL PREAMPLIFIER PERFORMANCE RATING		Good

TABLE 2

RADIO-ELECTRONICS PRODUCT TEST REPORT

Manufacturer: **Garrard** Model: **MRM-101**

OVERALL PRODUCT ANALYSIS

Retail price	**$200**
Price category	**Medium**
Price/performance ratio	**Very good**
Styling and appearance	**Excellent**
Sound quality	**Very good**
Mechanical performance	**Very good**

Comments: To date, we have tested only two products (SAE's *model 5000* and Garrard's *model MRM-101*) that claim to remove (at least audibly) those annoying pops and ticks from records damaged by scratches and dirt. Neither of these products claim to remove or reduce random surface noise, for which other forms of filtering are required. Both are effective in reducing the audible impulse noises such as those caused by scratched records. The chief difference between the SAE *model 5000* and the Garrard *model MRM-101* lies in that the latter unit is a full preamplifier-equalizer and therefore provides the necessary RIAA equalization and voltage gain so that its output signals can be connected directly to a high-level pair of inputs. This has advantages and disadvantages. The disadvantage is that since the preamplifier-equalizer is connected only in the phono circuitry, ticks and pops from other program sources (an FM station playing a scratched record) will not be reduced by the *model MRM-101*. The advantage is that by retaining total control of the cartridge signal from its introduction into the preamp/equalizer circuitry through the time-delay and impulse-noise elimination circuitry, an optimum interface is provided between the phono signal and all subsequent required circuitry. We believe that the Garrard unit is a bit more effective than the SAE unit in eliminating or reducing the effects of less severe scratches; while both seemed equally effective in reducing the impact of really severe gouges and scratches. If you own many severely damaged or scratched records, the Garrard *model MRM-101* offers what amounts to new life for them. It is easy to use and install and did not seem to materially change musical coloration when the suppressor circuitry was introduced.

Preamp-equalizer tests

Since the *model MRM-101* is a full preamplifier-equalizer, our first tests concerned this primary function. Test results are summarized in Table 1.

An input signal of 5 mV (at 1 kHz) was required to produce the nominal output of 300 mV; this was equivalent to a gain of just under 36 dB. With the suppressor out of the circuit, overload occurred at a 10-volt output, which translates to an input overload capability of around 166 mV. This is more than adequate to handle high-output cartridges even when they track heavily modulated grooves. With the suppressor turned on, however, the maximum output before a THD of 1.0% is reached was considerably lower—2.0 volts. This translates to an input capacity (at 1 kHz) of around 33 mV—a rather low figure in terms of some of today's dynamically recorded discs and one that indicates choosing lower-output cartridges. Since Garrard lists an input range of 0.7 mV to 2.0 mV-per-centimeter-per-second, we recommend a cartridge whose output is at the lower end of that range. (Most cartridge manufacturers state a nominal output for a velocity of 3.54 centimeters-per-second, which works out to approximately a 2.5-mV nominal output for the 0.7 mV-per-centimeter-per-second extreme of the recommended range.)

The unweighted S/N ratio of the *model MRM-101* is high enough so that when such lower-output cartridges are used there is still plenty of dynamic range available between the lower noise-and-hum floor and the upper distortion-level ceiling of this preamplifier.

Testing the suppressor

The most effective way to test the ability of the *model MRM-101* to reduce or remove audible pops and ticks caused by scratches in discs is to play a variety of scratched records. Our record collection has no shortage of such damaged records and we spent several hours listening to the way in which this amazing device was able to improve the reproduction. To be perfectly fair, not every type of scratch was totally inaudible, but most of our damaged discs became quite listenable when played through the *model MRM-101*. It is important to set the device's sensitivity control to its optimum point (this can be done only by careful listening and switching back and forth between the suppressed and unsuppressed modes). The results are extremely effective, and, in nearly all cases, our tests revealed there was no audible change in musical content with the suppression feature turned on—only a complete or substantial reduction of the audible pops and clicks.

Demonstrating the effects of the suppressor feature graphically while playing a disc was beyond the capability of our laboratory equipment because of the random quality and brevity of the scratches and pops produced by a typically damaged disc. We therefore attempted to create our own repetitive signal to approximate the waveform generated when a pop is reproduced or picked up by a stylus in a groove. After much experimentation, we managed to create a signal resembling such a waveform. It consisted of an upper mid-frequency

continued on page 104

Forest Belt tells...

What You Need To Know About Oscilloscopes

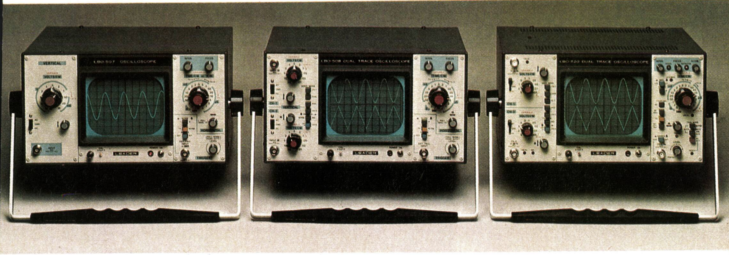

OSCILLOSCOPES ARE COMING INTO THEIR OWN. INDUSTRIAL and broadcast technicians have known for years how indispensable a scope is. However, in many home-electronics service shops, the scope has often been an instrument that gathered dust on a shelf under the bench. A technician set it up only as a last resort. Even then, he could seldom convince himself that what he saw on the scope face could really help him fix anything.

Today's successful repair expert knows better. No single instrument has been proved more versatile and useful in the hands of a skilled technician.

Three factors have contributed to its spectacular rise in popularity:

1. Test equipment you buy today is easier to use than ever before. Manufacturers have invested both money and effort in designing oscilloscopes that are simpler to operate, just as the instruments themselves have grown more sophisticated.

2. Technology in home-electronic devices leaves no room for "cut-and-try" troubleshooting. An oscilloscope is the only instrument that lets you see complex, sensitive signals the way they really are.

3. You have available, as never before, the means for learning how to use unfamiliar equipment. There is no excuse not to learn. Conscientious technicians rise to the challenge of high-technology diagnosis and repair, and incorporate the oscilloscope smoothly into their troubleshooting procedures.

This Special Section reviews maintenance-type and service-type oscilloscopes; featured are the state of the art—what instruments you can buy and use—hints to speed scope-trace analysis—familiarization with modern features. Whether you are a beginning technician or an old maintenance hand, this discussion should help dispel any apprehension you may have about modern oscilloscopes.

CONTENTS

Why Are Triggered Scopes So Popular. 70

Scope Features Make Them Unique 73

How Much Bandwidth Is Enough 75

Facts About Scope Sensitivity 76

Two Are Better Than One 77

Delayed Sweep Is No Mystery 79

So. . . . Shop Around. 81

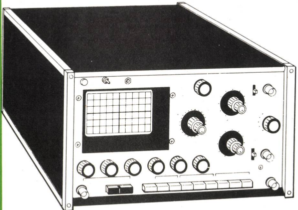

Why Are Triggered Scopes So Popular?

There's more than one reason, and you should know them all

YOU DON'T HAVE TO THINK BACK very far to remember when a triggered-sweep oscilloscope was rarely seen in a service shop. Only "egghead" technicians had them, or tried to use them for troubleshooting, especially around TV sets. You generally thought of triggered-sweep scopes in relation to a Tektronix, Hewlett-Packard, Marconi or some other exotic brand of TV set. They were called lab scopes; and you were considered special if you knew how to use one.

For TV and home-electronics servicing, the only scope used in those days was a recurrent-sweep type. The sweep ran continuously, pulling the beam across the CRT face to form a baseline, then quickly returning for another trip across. You set the sweep at some frequency that would synchronize a few cycles of a desired signal and hold the display steady enough for viewing. Recurrent-sweep scopes did a sufficiently accurate job, and they were easy to understand and use. At least they seemed that way.

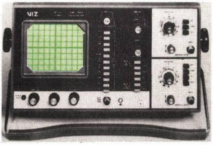

VIZ Model WO555

Today, as you know if you've looked around your distributor's shelves or thumbed through any test-equipment catalogs, you can hardly find a new recurrent-sweep scope to buy. There are a few models (see Table 1), but they are an exception now rather than the rule. Why is this so?

A dozen technicians would give you twelve different answers. However, only a couple of reasons need concern you as they apply to servicing.

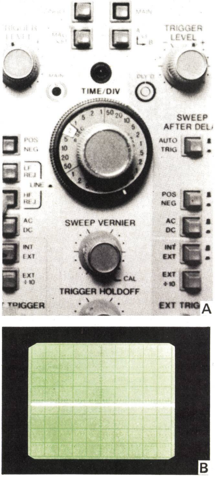

FIG. 1—TIMEBASE KNOB MAY BE LABELED Time/Cm or Time/Div. At sweep settings longer than 1 ms, the trace (here auto-triggered) flickers or becomes a mere scanning spot.

For one thing, a triggered scope gives you more information about a waveform than a recurrent-sweep scope. You will see why, as you read further.

And, believe it or not, despite the awe with which older technicians regard a triggered-sweep scope, it actually is easier to use—or to learn to use—than a recurrent-sweep type. Usually, the difficulty lies with technicians who have been taught to view waveforms mainly in terms of *frequency*, as is necessary with a recurrent-sweep scope. When you think of waveforms in terms of *time*, most of the mystery about a triggered scope disappears. In fact, any waveform, except perhaps a sinewave, can be analyzed more easily in terms of time than by its frequency.

On a timebase

Consider how a triggered-sweep scope draws its trace: The scope *sweep* moves the CRT beam from left to right across the CRT face. The Sweep control has *time* markings (Fig. 1-a) that indicate *how long it takes the sweep* to move from the exact left of the graticule to the rightmost position (usually out of sight).

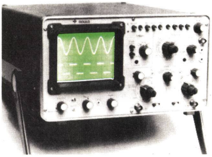

Gould Model OS 1100

This is easy to observe if you have a triggered scope that runs with a sweep time as slow as, say, 50 milliseconds per-division (expressed as 50 ms-per-division). This means the beam takes 50 ms to traverse each marked square (usually 1 centimeter) of the graticule. Since most scopes have 10 divisions from left to right, the scope sweep swings the beam all the way across in 500 ms, or one-half second. Try it, with the scope set for automatic triggering, and you can watch the spot move from left to right.

As you turn the sweep's Time/Division knob to shorter and shorter times, the beam is swept faster and faster. At 20 ms-per-division and 10 ms-per-division, you can still see the spot move across the screen, but very rapidly. At 5 ms-per-division, the trace line appears to flicker.

At 2 ms-per-division and shorter time periods, the beam sweeps across the 10 divisions so rapidly that the eye sees a fairly steady trace. At 1 ms-per-division, the spot moves across the screen in only a hundredth of a second (one-thousandth of a second for each division). At this and faster speeds, the beam moves fast enough and phosphor tube persistence is long enough that the moving spot appears as a solid trace line (Fig. 1-b).

Looking at signals

Now, what can you deduce from this timebased sweep? For a few moments, ignore whatever you remember of waveform frequencies, and just examine one complex TV signal: the *composite video*. A useful way to analyze this signal is by observing how the oscilloscope (in this instance, a triggered-sweep model) displays this familiar signal.

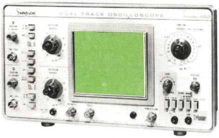

Simpson Model 452

A scope test probe connected to the video-detector output of a TV receiver feeds a composite video signal into the scope's vertical amplifier. As it sweeps across the screen, the CRT beam, instead of forming a straight trace line, also deflects upward and downward in accordance with the instantaneous voltages in the video signal. The patterns thus traced are called the *waveshape*. The spacing of these patterns across the screen corresponds to respective time positions of each point in the waveform.

For example, let's assume the sweep is triggered (or begun) at the tip of the vertical-sync pulse, as shown in Fig. 2-a. (Later on in this article, you'll learn exactly how to control this pulse.)

With the sweep set for 2 ms-per-division, 10 graticule divisions represent a total timebase of 20 ms. Next, count the graticule divisions. The tip of the next vertical pulse *after triggering* falls about 8.4 divisions beyond the first division. At 2 ms-per-division, this represents a time duration of 16.8 ms, or the time occupied by one field of video in the composite video signal. It represents the time distance between two vertical-sync intervals (blanking and pulse).

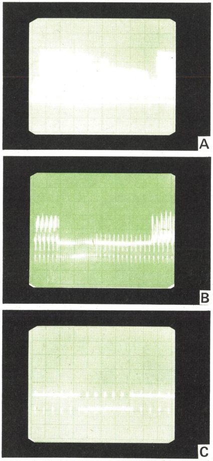

FIG. 2—TELEVISION VERTICAL FIELD can be spread and delay-triggered to show vertical interval in detail or expanded to reveal serrated sync pulse.

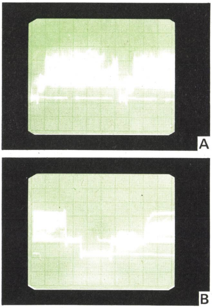

FIG. 3—TELEVISION HORIZONTAL LINE, with horizontal-sync pulses and burst, can also be widened for measuring and examination.

Analyzing the waveform shape is one crucial reason for viewing the signal in the first place. If you know the timing between the high spots of any waveform, you can choose a timebase that spreads out any portion of the signal you wish to examine.

For example, suppose you want to take a closer look at the exact makeup of the vertical-sync interval shown in Fig. 2-a. With a setting at 2 ms-per-division, you cannot accurately determine the time duration of the vertical-sync pulse and blanking. Nor can you examine the waveform in any detail.

The solution, of course, is to shorten the sweep's timebase. Setting the switch to 1 ms-per-division makes the interval between video fields occupy twice as much graticule space. Shortening the time to 0.2 ms-per-division (Fig. 2-b) displays the makeup of the pulse more thoroughly. This setting spreads the whole interval—blanking, vertical pulse, equalizing pulses and inactive (blanked) lines—over about 6.8 divisions. The duration, therefore, is about 1.36 ms. It is almost possible to distinguish the horizontal-sync serrations in the vertical pulse. And you can easily see the equalizing pulses that ride the blanking pedestal.

By the time you shorten the timebase to 50 μs-per-division, the sync pulse itself is spread over 3.7 graticule divisions. The duration of the pulse alone is 185 μs. Figure 2-c shows the serrations and equalizing pulses clearly.

Close detail

It is evident by now that you can view a complicated waveform much more clearly with a triggered-sweep scope than with a recurrent-sweep type. You can spread out a signal on virtually any timebase within the range of the scope sweep. Triggering also allows you to observe a waveform, pulse train, or an individual pulse of almost any shape or duration. You merely select a timebase and triggering point that shows whatever detail you desire.

To clarify this even further, consider a single horizontal line of the video composite signal. You will probably recall, from your studies of TV fundamentals, that a complete horizontal line—pedestal, sync pulse and video—occurs every 63.5 μs. If you want to examine one line closely, you must make it cover a wide portion of the scope graticule. A 10-μs-per-division setting of the sweep spreads the 63.5-μs line over more than six divisions (see Fig. 3-a). The video, the front and back porches of the pedestal, the color burst on the back porch and the pulse tip itself are clearly visible. You can verify the proportions of the sync pulse, make sure the burst is normal and assess whether some fault in the TV receiver is compressing the video, smearing it, or degrading the sync pulse.

TABLE 2—TRIGGERED-SWEEP OSCILLOSCOPES

Brand	Model	Bandwidth (MHz)	Sensitivity (mV/div)	Dual-Trace modes		② Signal Delay	CRT			Sweep Range		Magnifier	Trigger			Probes		Prices		
				Chop	Add		Rectangular	PDA	Graticule Illum.	from (μsec)	to (sec)		TV	HF Rej (kHz)	Variable Delay	Model	Included	Under $600	$600-$1300	Over $1300
B & K Precision	1432	15	2	①	✓					0.5	0.5	5X	✓			PR-37	✓		✓	
	1461	10	10							1.0	0.5	5X	✓			PR-31	✓	✓		
	1471B	10	10	①	No					1.0	0.5	5X	✓			PR-34	✓	✓		
	1472C	15	10	①	✓				edge	0.5	0.5	5X	✓			PR-36	✓		✓	
	1474	30	5	①	✓	✓		✓	edge	0.2	0.5	5X		30+		PR-36	✓		✓	
Conar	255	6	10							1.0	0.5								NA	
Eico	480	10	10							0.1	0.5		✓			LCD-10	✓	✓		
	482	10	10	No	No					0.1	0.5		✓			LCD-10	✓	✓		
Gould	OS245A	10	5	①	No		✓			1.0	0.5	③	✓			PB13	✓	✓		
	OS260	15	5	④	No		✓	✓	edge	0.5	0.2	10X				PB13	✓		✓	
	OS1100	30	2	✓	✓	✓	✓	✓	int	0.2	2.0	10X		10+	Yes	PB13	✓		✓	
	OS3300B	50	5⑤	✓	✓	✓	✓	✓	int	⑥	⑥	10X		10+	⑦	PB13	✓			✓
Heath	IO4510	15	1	✓	No	✓	✓	✓	edge	0.1	0.2	5X				PKW-105			⑧	
	IO4541	5	20							0.2	0.2							⑧		
	IO4550	10	10	No	No					0.2	0.2	5X						⑧		
	IO4555	10	10							0.2	0.2	5X						⑨		
	IO4560	5	100							0.2	0.2							⑨		
Hewlett-Packard	182C (180 series)	35⑩	10	✓	✓	✓	✓	✓	FG	.05⑩	1.0	10X		15+	⑪					✓
	1740A (1700 series)	100	5⑤	✓	✓	✓	✓	✓	FG	.05	2.0	10X		4+	⑦					✓
Hickok	515	15	10							0.5	0.2	5X	✓			SP-6	✓	✓		
	517	15	10	①	✓					0.5	0.2	5X	✓			SP-6, 7	✓		✓	
	532	30	10	✓	✓	✓				.05	2.0	4X		10+	Yes	SP-7	✓		✓	
Leader	LBO502	15	10						edge	NA	NA	5X					✓	✓		
	LBO507	20	10							0.5	0.2	5X	✓					✓		
	LBO508	20	10	①	✓					0.5	0.2	5X	✓						✓	
	LBO515	25	5	✓	✓		✓		int	⑫	⑫	10X	✓	10+						✓
	LB0520	30	5	✓	✓	✓	✓	✓	edge	0.2	0.5	10X	✓						✓	
Lectrotech	TO-55	10	10						edge	0.5	0.2	5X	✓			PR-10		✓		
	TO-60	15	10	✓	✓				edge	0.5	0.2	5X	✓			PR-10		✓		
Philips	PM3211	15	2	✓	✓		✓	✓	NA	0.5	0.2	5X				NA			✓	
	PM3212	25	2	✓	✓	✓	✓	✓	int	0.2	0.5	10X	✓			PM-9336	✓		NA	
	PM3214	25	2	✓	✓	✓	✓	✓	int	⑫	⑫	10X	✓		⑦	PM-9336	✓		NA	
	PM3226⑬	15	2	✓	No		✓	✓	NA	0.5	0.2	5X				PM-9337			✓	
	PM3233	10	2	④	No	✓	✓	✓	edge	0.2	0.5	5X	✓			PM-9337			✓	
Sencore	PS29	8	10						edge	0.2	0.1	5X	✓			39G80	✓	✓		
	PS163	8	5	✓	✓				edge	0.1	0.1	5X	✓			39G80	✓		✓	
Simpson	452	15	5	①	No				edge	0.2	0.5⑭	5X	⑭		⑮	✓				
	455T	12	10							0.5	0.5⑭	5X	⑭		⑮	✓				
Tektronix	SC502 (500 series)	15	5	✓	⑯	✓	✓	✓	int	0.2	0.5	10X							✓	
	T935 (900 series)	35	2	①		✓	✓	✓	int	0.1	0.5	Var	✓		Yes	P6062A	✓			✓
	7704A (7000 series)	75⑰	5	✓	✓	✓	✓	✓	int	.005	5.0⑰	10X	✓	50+	⑦					✓
Telequipment	D32⑱	10	10	①	No		✓			0.5	0.5	5X	✓			10:1	✓		✓	
	D61A	10	10	No	No					0.5	0.5	5X	✓					✓		
	S61	5	5							1.0	0.5							✓		
Viz	WO-527A	15	10							0.5	0.5	10X	⑭			WG-478		✓		
	WO-555	15	10	✓	✓	✓				0.5	0.5	10X	⑭			WG-478	✓		✓	

NOTES (see copy)

NOTES

NA — Information not made available by mfr.
FG — Floodgun Illumination
Opt — Optional extra
Int — Internal
Var — Variable
1 — Switches automatically to Chop mode at sweep times slower than 0.5 msec.
2 — Delay line in vertical amplifier(s) to allow viewing leading edge of displayed waveform.
3 — Has both 5x and 10x magnification.
4 — Dual beam, not dual trace. Beam switching not necessary.
5 — Vertical 5x magnifier raises sensitivity by that factor.
6 — Two time bases: A is 0.1 usec to 1.0 sec/div.
B is 0.1 usec to 0.5 sec/div.
7 — Incorporates both intensified and delayed trigger, using multiple time bases; has 10-turn delay multiplier.
8 — Kit version priced substantially less.
9 — Kit only.
10 — With models 1807A vertical amp and 1820C time base plug-ins.
11 — Only in models 1821A and 1825A time base plug-ins.
12 — Two time bases: A is 0.2 usec to 0.5 sec/div.
B is 0.2 usec to 0.1 sec/div.
13 — Single-trace version is model PM3225.
14 — Plus TVV and TVH sweep positions, usually with matched triggering.
15 — Fixed trigger delay for VITS display at special VITS setting of time base.
16 — Has A minus B mode, but no flipover for A plus B.
17 — With models 7A18 vertical amp and 7B53A-05 time base plug-ins.
18 — Battery-operated portable; AC-operated too.

You can look even closer at the pulse itself. Just spread the signal some more. Try a sweep setting of 2 μs-per-division, as shown in Fig. 3-b. On a live scope, you can even count burst cycles. More significantly, you can verify that the burst is not being attenuated by either poor alignment or some other defect preceding (or in) the video detector.

A triggered scope with certain extra features can even let you select and study the VITS and VIR signals when they come through the network linkage. These signals occupy lines 17, 18 and 19 of each vertical field, yet they're not always transmitted. The VITS signals also differ with each network. A scope with a variable delay on the trigger can single out those lines and examine the signals in detail. How you manipulate these extra features brings up the question: Exactly how does a triggered scope trigger? And the answer will be given later on in this article.

Meanwhile, you should now be fairly insulated against thinking any more about waveform *frequencies*. Using a triggered scope, you'll fare much more successfully if you think of waveforms in terms of length or duration.

TIMEBASE CHART

A guide to the handiest Time/Div setting at which to start viewing common signals.[1]

Signal	Suggested Time/Div
Low-end audio	0.2 ms
High-end audio	50 μs
TV fields	2 ms
TV lines	10 μs
TV vertical sync only	5 ms
TV horizontal sync only	20 μs
CB xmtr output modulated 1000 Hz	0.2 ms
EIA noise signal (for CB noise blankers)	0.5 μs

[1] Synchronizing stable displays of the above signals depends, sometimes, on critical trigger settings.

Scope Features

They might determine which one you will buy

PRICE SHOULD NOT BE THE CHIEF criterion in purchasing one oscilloscope instead of another. Just as with other products, you may not get a bargain by saving money. Yet, the opposite side to this coin is that spending more money does not automatically assure greater value.

Shopping for an oscilloscope entails a panorama of choices. I am not going to suggest what kind of scope you should buy, but rather offer some shopping hints.

The next several paragraphs will acquaint you with key features found in various triggered oscilloscopes. On the basis of this knowledge, you can then select a scope best suited to the kind of servicing or maintenance you provide. You will recognize conveniences that add confidence and accuracy to your analyses and diagnoses.

I assume you are already familiar with recurrent-sweep scopes and know whether they satisfy your purposes. Therefore, this article will confine itself to a discussion of triggered scopes, from the least expensive to large, elaborate and costly models.

First, shop for the features that you need, and only then explore the prices of the models that interest you.

Second, expect and ask for a demonstration of any and all features. Do not settle for a quick verbal run-through of what the scope will do. *See* the scope display the waveforms you want to inspect. For that much money, a test-instrument salesman can take the time this requires. If he can't, find one that will.

Third, insist on a week's trial in your shop. Introduce the instrument to your workaday problems and make sure it will do everything you want done. If it won't, perhaps you need a more elaborate instrument—or perhaps you just need a lesson or two in operating it. Understand the instrument. Ask your salesman to come and explain anything that confuses you. *Do not* play know-it-all. You're paying too much money to buy something you can't use.

Heath IO-4550

Finally, examine more than one brand and model of scope. It is not a waste of time, you will be living with your purchase a long time. Be sure you like its appearance, its smoothness of operation and its capabilities. If the controls are hard to find or manipulate; if the probes do not fit the instrument or your hand well, or do not clip on easily for tests; if the panel size and arrangement do not fit your bench or your working habits—you will never be truly satisfied. Since dissatisfaction inevitably leads to avoiding using the instrument, that's no way to make it a profitable investment.

So, shop around; you'll be glad you did.

Simple (but important) features

Some minor features that are common, yet not all-pervasive, should be mentioned right away.

Examples abound in the cathode-ray tube (CRT). A P31 phosphor tube is generally used in triggered scopes because of its medium persistence. Almost no one uses the shorter-persistence P1 phosphor tube in a triggered scope. A P31 phosphor tube can be aluminized, which allows slightly more brilliance; this tube is labeled P31A. A P31 tube delivers a green trace; a P11 tube delivers a blue trace. Some scopes offer an optional longer-persistence P7 phosphor tube, but it is doubtful you would need it for servicing. A storage-type CRT actually holds a selected pattern for an hour or more, but it's expensive and not needed for ordinary service work.

Today's scopes have both round and rectangular CRT screens, and most are flat-face. The vertical viewing size (called the Y-axis) of a rectangular CRT runs 8 centimeters (8 cm), typically; the horizontal viewing size (the X-axis) is 10 cm.

Some graticule divisions are as small as 0.79 cm; a few as large as 1.29 cm, most are 1.0 cm exactly. Round CRT screens generally are covered by a mask with a rectangular graticule grid. A standard size for the grid on a 4-inch-round tube is 8 by 8 cm; for a 5-inch-round tube, 8 by 10 cm or 10 by 10 cm. A very few are marked in inches. And an occasional graticule sports vector markings for B–Y/R–Y displays from color TV.

How or if the graticule is lighted may matter to you. An external graticule with sidelighting (Fig. 1-a) achieves one effect; usually some areas are brighter than others. Internal graticule lighting (Fig. 1-b) provides much more even lighting but is also more expensive.

Some Hewlett Packard models use a CRT that incorporates a technique called *floodgun* graticule lighting. A set of special elements inside the CRT flood the phosphor tube with electrons and produce a glow over the whole CRT screen. Black graticule lines etched on the CRT face show in strong contrast to the glowing phosphor. Figure 1-c shows this effect. The intensity of this backlighting effect can be varied to increase the visibility of the etched graticule grid.

A characteristic called *post-deflection acceleration* (PDA), sometimes known just as *post acceleration*, turns up in some sales pitches. The term refers to applying high voltage to an accelerator anode *beyond* the deflection plates. (An ordinary electron gun accelerates the beam before deflection.) Acceleration after deflection improves the linearity of the sweep across the screen and produces a brighter and, usually, a sharper trace than usual.

EICO Model 480

Do not overlook the importance of a sharp trace. A scope for triggered applications should have an *astigmatism* adjustment in addition to the usual focus knob. The Astigmatism Adjust control (typically, a tiny screwdriver pot) may be located on the front panel, perhaps at the rear, but it must be accessible.

In examining the fine detail possible with a wideband triggered scope, a thick trace line can hide significant flaws, such as ringing or overshoot. The astigmatism adjustment helps refine the beam to a tiny round pinpoint. You adjust it in conjunction with the focus knob to obtain a trace that is thin and sharp on both the Y-axis (rising or falling lines) and the X-axis (horizontal trace lines). Hickok, in their *model 532* triggered 30-MHz dual-trace scope, claims a beam thickness no more than 0.006 inch.

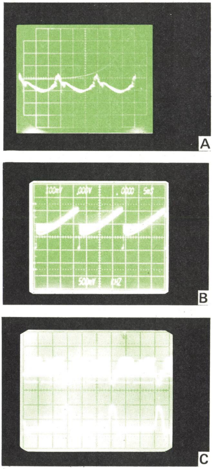

FIG. 1—SIMPLER FEATURES OF SCOPES, such as graticule lighting, often bring more convenience to operation. Shown here are (*a*) edge lighting, (*b*) internal graticule, and (*c*) unique floodgun lighting.

Many triggered oscilloscopes include what manufacturers term a built-in delay line. This feature is located in the vertical amplifier section to delay the signal a few nanoseconds. If there are two channels, as in a dual-trace instrument, each channel has this *signal delay* line.

The purpose of this feature is to slow down the arrival time at the CRT of the signal that will be viewed. During internal triggering, the sweep does not begin until the trigger amplifier perceives a slope of whatever polarity and amplitude have been chosen by the triggering-control settings. However, the same signal, coming through the vertical amplifiers, causes a vertical deflection of the CRT beam. The sweep doesn't start until part of that signal has occurred. Therefore, you do not see the leading edge of the viewed waveform because of the trigger setting. This is especially a problem for waveforms that have leading edges with a very fast risetime.

A short delay holds the vertical signal back until several nanoseconds after the sweep triggers. Thus, you see *all* the waveform, including some trace line ahead of the leading edge.

Do not confuse this *signal delay* with delayed trigger, which is entirely different. You find the delayed-trigger feature in expensive scopes; you will learn what it is and how it performs later on in the article.

A trace expander, usually called a magnifier, comes in handy for examining complex waveshapes in detail. Pressing this button simply spreads the trace out to five or ten times the normal scan.

Non Linear Systems MS-15

If you activate the magnifier, you must consider the multiplier in any timebase measurements. Some scopes expand the trace ×5, some ×10, and a few expand it to both. Imagine a timebase setting of 10 μs-per-division, for example. Turn on a ×10 magnifier, and what originally occupied one division on the screen now covers all 10 divisions. Hence, the *effective* timebase has become 1 μs-per-division.

Make sure the Horizontal Position knob moves the trace far enough left and right to let you see all the expanded trace. Normally, the magnifier spreads out what is at the centerline of the graticule. To see other portions of the display, use the Position knob.

Examine the reduction of beam brightness when you use the magnifier feature. In a few scope sweeps, with sweep times in microsecond ranges, you may be almost unable to view the trace when it is expanded—even after turning up the beam intensity. If this sort of operation is important, find a model that develops a trace display that is bright enough to view even a 1-μs pulse spread out to five graticule divisions. The brightest scope models incorporate a CRT with PDA or apply a high (above 5-kV) accelerating potential to the CRT.

An occasional scope includes a vertical expander, but, generally, flipping the VOLTS/DIV switch accomplishes the same effect.

The range of the sweep times may be of concern in some instances. For ordinary service measurements and testing, a 50-ms-per-division sweep time should be quite slow; and 0.5-µs-per-division should be satisfactory at the fast end. If you expect to work on personal computers, digital process control, or other similar gear, you sometimes may need a faster sweep—perhaps as fast as 0.1 µs-per-division. This faster sweep, supplemented by a X5 magnifier, would let you examine and/or count pulses no more than 10 ns apart. Sweep ranges beyond these ranges would be a bonus, unless they are necessary for some specific servicing use. A trial period in your shop will tell.

These are a few of the small but crucial features you might overlook in selecting a scope. An alert salesperson will point out and explain the significance of many other features. You, the customer, must also be aware. It's your money being spent; you hope to spend it wisely.

Scope Bandwidth

How much is enough? And exactly what is it?

YOU NEED TO UNDERSTAND what is meant when scope specifications refer to the bandwidth. Some manufacturers state the bandwidth in a nonstandard way, making a scope seem more wideband than it really is (compared with others).

It is not simple to compensate the vertical amplifiers of an oscilloscope to pass a band of frequencies all the way from 0 volts DC to many, many megahertz. This is why wideband scopes cost more. And not even the the best vertical amplifier can come out perfectly flat; it is likely to favor some frequencies. However, careful design can hold the variances in frequency response within a relatively narrow range. The standard tolerance is 3 dB.

To meet this standard tolerance, an oscilloscope must neither attenuate nor peak any signals, within its rated bandwidth, more than 3 dB. In other words, the vertical amplifier could boost signal voltages as much as 1.4 times the normal voltage at certain frequencies, and diminish them by 0.7 times at others, and still remain within accepted specifications.

Most significant is the bandwidth over which the scope's vertical amplifiers will meet this 3-dB standard. Since rolloff is more pronounced at higher frequencies, bandwidth is often expressed in terms of the highest frequency. That is, a 15-MHz scope displays signals up to that frequency with no more than 3-dB loss (sometimes stated as −3 dB) or peaking.

However, be sure the scope you buy meets this 3-dB standard across its whole bandwidth. A specification that claims the scope response is "down 3 dB at 15 MHz" could be peaked at that frequency and have a severe dip at various frequencies below 15 MHz. What you should expect is response *within* 3 dB across the entire bandwidth—from DC to 15 MHz. If the specification states exactly that, you can trust it; dependable manufacturers are careful of their claims. But read specifications closely; 3.5 dB or 4 dB is not the same—and, even though accurate, is difficult to compare with standard bandwidth figures.

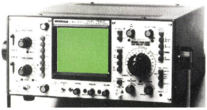

Leader LBO-520

If you have any doubts, have your new instrument checked and calibrated by an instrument lab. (Don't go by your signal generator; it may peak more erratically than any scope.)

So, how much bandwidth is necessary? A recent popular use for oscilloscopes is in viewing the output of CB transceivers. Citizens band RF signal output is usually about 27 MHz. To measure the signals accurately, you need a scope with a bandwidth to 30 MHz.

You can *see* the 27-MHz RF output on a 15-MHz scope. If all you're interested in is the shape of the modulation, this lesser bandwidth is acceptable and usable. However, the display will be small and calibrations inaccurate. What is worse, weak signals, such as those generated by oscillators and mixers inside the CB transceiver, may be so attenuated that they cannot even trigger a sweep. Therefore, if you expect to work regularly with 27-MHz signals, consider a 30-, 40-, or 50-MHz oscilloscope bandwidth.

In digital pulse work, whether in a microcomputer or a modern TV receiver tuning system, wide bandwidth becomes important from another standpoint. To examine short-duration pulses, you need a scope with a *risetime* that is adequate to reveal the pulse shapes without distortion.

Technically, *risetime* is the period required for the leading edge of a pulse to rise from 10% to 90% of its final amplitude. Risetime relates closely to bandwidth. If you need a particular risetime to view and measure certain pulses accurately, you can divide 0.35 by the risetime (in seconds) and find the 3-dB bandwidth required (in Hertz).

For example: Suppose you need a 10-ns risetime—that's 0.00000001 second. You can use your scientific calculator to solve this risetime/bandwidth computation. Enter 0.35 and press the divide pushbutton. Using scientific notation, it's easier to express nanoseconds as (10^{-9}) seconds. So, enter 10 (for 10 ns); press the exponent button and enter a negative 9. Press the equal sign pushbutton, and the answer appears (in Hertz): 35,000,000. Therefore, you need a 35-MHz scope.

Another example: You need a 2-ns risetime for extremely quick pulses. Divide 0.35 by 2 (10^{-9}). You need a scope with a bandwidth to at least 175 MHz.

Typically, a 10-ns risetime will suffice, except in fast microprocessors. If you know enough about computer equipment to be able to service it, you know what risetimes are involved in the pulse trains. Use the $0.35/T_R$ formula to find what bandwidth you need in an oscilloscope.

An interesting sidelight on this: If a manufacturer has stated the bandwidth specification in some nonstandard fashion, you can compute the actual 3-dB bandwidth from the specified risetime. So far, no scope maker I know uses any standard specification for risetime except the usual 10% to 90% method.

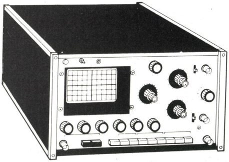

Scope Sensitivity

A most important scope characteristic

THERE IS A SPECIFICATION THAT might be crucial in some types of servicing. The term *sensitivity* (occasionally called *minimum deflection ratio*) refers to how much signal voltage is required to produce a usable display. On most scope screens, a display that occupies at least two of the vertical (Y-axis) divisions gives a fairly good view of the waveform. Four divisions are more than enough.

However, vertical amplifier sensitivity is rated as the signal voltage that is required to deflect the trace vertically by one division, which usually is one centimeter (1 cm). Thus, an instrument that takes 5 mV to display a waveform one division high is not as sensitive as one that needs only 2 mV for the same size trace. An oscilloscope rated at 5 mV-per-division sensitivity can satisfactorily display smaller signals than one rated at 10 mV-per-division.

Watch out for the difference between peak-to-peak (P-P) and RMS-sensitivity ratings. If sensitivity is listed with RMS voltage, and this is not uncommon, you must multiply by 2.8 to obtain a peak-to-peak sensitivity figure. Thus, a scope that is rated for sensitivity at 2 mV RMS (it is acceptable to omit *per-division* or *per-centimeter*), is not as sensitive as a scope rated at 5 mV P-P.

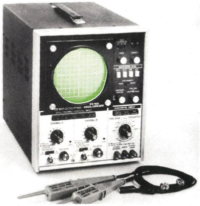

Sencore Model PS163

What sensitivity value is needed to show a three-division display from a 10-mV signal? Obviously, a value of 3.3-mV (or better) sensitivity will manage nicely—providing the bandwidth is sufficient to accommodate the signal.

Using this three-division criterion, a scope with sensitivity of 2 mV-per-division displays well any 6-mV P-P signal. A scope with a sensitivity of 5 m-V-per-division needs a 15-mV P-P signal to show a sizeable display. Of course, you can *see* a 5-mV signal, or even a 2-mV signal, but only as a much smaller trace. You also may have difficulty getting such a small signal to trigger.

You can spot the rated sensitivity of a scope by examining its vertical amplifier input knob (Fig. 2-a). It can be labeled in volts-per-division (Volts/Div) or per-centimeter (Volts/Cm or V/Cm). The smallest voltage listed on the settings is the per-division sensitivity of the scope. (If the instrument has a vertical expander, divide the lowest voltage-per-division setting by the expander multiplier. Thus, a scope with 5 mV-per-division as the bottom setting, and with a x 5 vertical magnifier, has an *effective* sensitivity of 1 mV-per-division.)

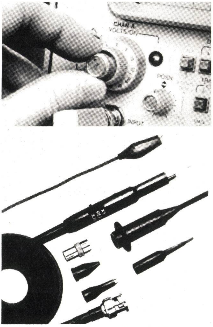

FIG. 2—INPUT ATTENUATOR KNOB calibrates vertical amplifier(s) to measure amplitude of input signal. Low-cap test probe introduces ×10 multiplier that must be taken into consideration.

The maximum calibrated peak-to-peak voltage may also be important to you. It is the highest voltage on the vertical-input switch. For example: At 20 volts-per-division, an 8- by 10-cm graticule lets you view a waveform of 160-volts P-P amplitude.

When you service TV receivers, you encounter signals as low as 10 mV P-P or 15 mV P-P. In CB radios, at least in the transmitter and synthesizer, signals as weak as 20-mV P-P are usual, Hence, a scope with a sensitivity less than 5 mV-per-division P-P may not let you view, comfortably, some of the desired signals.

Measuring signal amplitudes with today's oscilloscopes is simple enough. You merely count the divisions occupied by the display and multiply by the voltage indicated at the setting of the input switch. For example, with the input switch set to 0.1 volts-per-division and a display that is about 3.4 divisions high, you are viewing a waveform that is 0.34 volt (or 340 mV) in amplitude. The same simple arithmetic works for any setting of the volts-per-division switch.

There are three things to remember: (1) Voltages are peak-to-peak. (2) Voltages measured by the scope are accurate to 3 dB only within the bandwidth of the scope. (3) The CAL/VAR knob with the input switch must be set at its calibrated (CAL) position. Fancier scopes include a light—in addition to the switch knob shown in Fig. 2-a—that warns you if you have left the variable knob at an uncalibrated spot. You use this knob only when you want to set the display at some specific size for whatever reason.

One other factor could mislead your peak-to-peak amplitude measurements: the test probe. Most tests should be performed with a low-capacitance probe such as shown in Fig. 2-b. So, when using the probe in the low-capacitance position, don't forget to multiply by 10 whatever voltage the graticule and switch indicate. Or, if loading is not a worry, turn the probe to its direct or 1:1 position.

Dual Trace Scopes

Two are often better than one

PROBABLY NO TEST INSTRUMENT has caught on so fast lately as the dual-trace triggered oscilloscope. Its primary advantage lies in letting you view more than one signal waveform at a time. However, that's not its only capability, nor even its most useful. Once you're truly familiar with a dual-trace instrument, you can make it perform a whole string of unusual and versatile functions. First, you need to know exactly how a dual-trace scope works. Otherwise, some of its operations will confuse you more than help you.

Simple dual-trace scope models operate in what is known as an *alternate mode*. A switcher inside the instrument alternately activates two traces and two vertical-input channels. You may be able to visualize this sequence easier by following through on your own or on a borrowed scope.

Conar Model 225

Imagine a video signal fed into vertical amplifier Channel A and nothing being fed into Channel B. With the triggering set for Channel A internally, the incoming signal fires the sweep. The TIME/DIV knob is set at 10 μs-per-division to display the horizontal video lines and, of course, the sync pulses. The sweep completes trace A and its display, then it blanks the beam and snaps it back to the left side.

The switcher instantly does three things: (1) It applies a DC vertical-deflection voltage that moves the beam down to a position where it can form another trace, which will be trace B. (2) It triggers the beam again, similar to the trace A triggering, and the sweep pulls the beam across at the same time/division rate as for trace A. (3) It switches the vertical deflection to the output of vertical amplifier Channel B. With no input, trace B remains flat, just a baseline. But trace B would display any signal that you feed into the Channel B input jack.

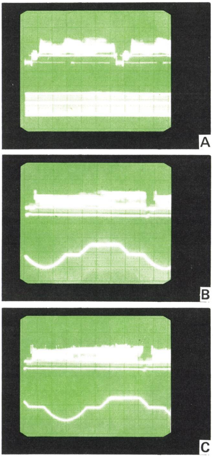

FIG: 3—DUAL-TRACE DISPLAY LOCKS on one signal or the other, unless both are in phases. (*a*) Horizontal line on trace A, supply ripple on trace B and triggering from trace A; also, timebase is too fast for ripple. (*b*) Timebase set to accommodate 16.7-ms duration of both TV field and ripple waveform; but slight phase variance lets one crawl. (*c*) Composite triggering locks both displays despite minor phase difference.

At the end of trace B, the sweep shuts off and the switcher lets the position deflection move the beam back up to trace A. The beam then waits for another trigger in Channel A. This alternating action between Channels A and B accounts for the term, *alternate mode*.

Now, imagine feeding a TV horizontal-sweep signal into Channel B. (Drape a test lead near the TV yoke.) Set the Channel B VOLTS/DIV switch for a comfortable display. Since both the Channels A and B input signals run at the same repetition rate, the timebase need not be changed. The switcher alternates displaying trace A and then trace B, with their respective signal displays.

But remember that the triggering is coming only from Channel A, internally. You can, in most dual-trace scopes, switch the triggering to Channel B. In that case, the sweep doesn't start until the Channel B signal reaches the chosen triggering amplitude (and slope direction). Trace B is completed and the switcher moves the beam up so the sweep can run trace A. Then, the sweep stops and waits for another trigger from the Channel B signal.

The single trigger and timebase limit a dual-trace scope in one way. Suppose you feed a power-supply ripple signal into Channel B. Leave the video signal fed into Channel A. You adjust the VOLTS/DIV switch on the Channel B side to accommodate the small signal amplitude. Set the trigger back to Channel A.

Once the sweep displays the video waveform on trace A, the switcher pulls the beam down to form trace B. However, the trigger comes from Channel A and the timebase is still set at a 10-μs-per-division speed that displays horizontal TV pulses.

This sweep rate is far too fast for a signal that has a per-cycle duration of almost 17 ms. The waveform on trace B just blurs, since it cannot synchronize. Figure 3-a shows the dual-trace result.

Thus, you discover one significant limitation of a dual-trace scope: You cannot view widely divergent waveforms simultaneously (unless they bear a harmonic relationship—but that's another story).

Now, to carry this demonstration one additional step, make two changes in the scope settings. Move the TIME/DIV switch to a position more suited for the ripple signal—say, 2 ms-per-division. Then, switch the trigger source to Channel B internal.

The trace B signal, if you place the trigger level correctly, locks in solidly (Fig. 3-b). Note that, with this new timebase, you can now see vertical-field video on trace A. If the AC power at your bench differs in phase from that at the TV station, the display on trace A may crawl slowly, because the ripple signal is not in phase with the video. Switch the trigger source back to Channel A internally; the vertical fields lock in and the ripple signal crawls.

This exercise proves that a dual-trace scope can accommodate different-shaped waveforms just as long as their time durations are similar.

Now, here's one more little trick. A few scopes allow you to obtain a composite trigger—from both Channels A *and* B. When you do this, triggering in the alternate mode jumps from one channel to the other as the channels alternate, and, lo and behold, *both* signals lock in solidly. Each display is triggered internally by its own waveform. That slight phase difference between AC power and video-field rate no longer upsets the triggering.

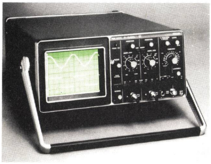

Philips Model 3211

Dual traces set the stage for many servicing simplifications. Here are some examples: Imagine an audio generator output to Channel A and to an audio amplifier under test, with the output of the amplifier to Channel B. You can compare any change in waveshape, particularly if you use squarewaves. You can measure input-to-output voltage gain directly, using the VOLTS/DIV switches and graticule. Channel B lets you calculate the power output easily across the amplifier dummy load: just square the voltage measured and divide by the load resistance.

For stereo amplifiers: Feed the same squarewave generator signal to both left and right channels. Connect the left amplifier output to scope Channel A and the right output to Channel B. Compare the waveshape and phase differences between channels. You can check balance accuracy. Look for distortion in either channel. Take one probe and trace any distortion you see. A dozen other possibilities will suggest themselves to you when you're familiar with the instrument.

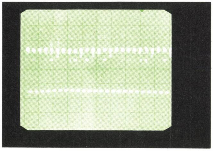

FIG. 4—CHOPPED-MODE DUAL TRACE appears like this at faster sweep speeds (shorter sweep times). Alternate mode is better when sweep time-per-division is 0.1 ms or less; chopped mode at 0.2 ms or more.

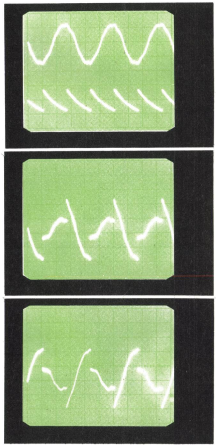

FIG. 5—ADD MODE CAN BE USEFUL IN costlier scopes, although most prevalent use is for subtracting—a function often called *common-mode rejection*.

In CB radios: Feed a 1000-Hz audio signal to the scope's Channel A and to the mike input of the transmitter. Feed the transmitter RF output to Channel B. Modulate the transmitter; then, compare the waveform of trace A with the modulation envelope on trace B.

Leave Channel B connected as a monitor for RF output. Use Channel A to troubleshoot the circuits inside the unit. If the scope has sufficient bandwidth, you can check RF right down in the synthesizer or phase-locked loop, or any other oscillator. Don't bother changing the timebase from 0.2 ms; unmodulated RF shows up as a thick display, its size depending on amplitude and the setting of the Channel A VOLTS/DIV switch.

Alternating the sweep to form two traces works fine as long as the sweep times are short. However, some flickering appears (even with one trace) when the sweep time reaches 1 ms-per-division or 2 ms-per-division. Switch to the dual trace, alternate mode, and you can observe flicker at 0.5 ms-per-division and 1 ms-per-division. It can become quite distracting; at 2 ms or 5 ms, such flickering makes the traces hard to watch.

Therefore, high-priced scopes that can afford such refinements have what is called a *chopped* mode. Instead of the timebase determining when the internal switcher goes from trace A to trace B, a chop oscillator operates the switcher. This chop oscillator runs at 200 kHz–500 kHz (250 kHz is usual). It causes the switcher to flip back and forth between Channels A and B too rapidly for the eye to follow. Thus, even at slow sweep times, there is absolutely no appearance of switching from one trace to another.

At a 250-kHz chop rate, each trace is chopped up into tiny 2 μs bits. Channel A displays for 2 μs, then Channel B displays for 2 μs. Intervals of 2 μs exist between each visible segment, but they are too small to observe at slow sweeps. In fact, only two seemingly continuous displays can be seen until sweep timing becomes as short as 50 or 20 μs-per-division. At that point, you begin to detect segment patterns in the traces.

Figure 4 shows this effect. However, in the alternate mode, switching happens so fast at these sweep speeds, you would not use the chopped mode.

This explains how you select which dual-trace mode to use. At sweep settings between 20 ms-per-division and 0.2 ms-per-division, you select the *chopped* mode—unless there's some other good reason to stay in the alternate mode. At sweep settings from 0.2 ms-per-division to the shortest time setting on the knob, select the *alternate* mode. Some dual-trace models select the best mode automatically, as you set the TIME/DIV switch.

An *add* mode, common among dual-trace scope designs, adds the two displays together algebraically and displays them as one signal on one trace. Figure 5 shows an example. Channel A has a 17-ms sinewave; Channel B displays an 8.5-ms sawtooth waveshape. They are visible separately in Fig. 5-a. In Fig. 5-b, they are shown added together. Where phases coincide, the amplitude is greater; where phases are opposed, the amplitude is smaller.

A *rejection* or *subtract* mode is possible if the scope has a capability for reversing the polarity of the Channel B signal. When the signal in Channel B is normal, the add mode gives you signals A + B. Reverse the polarity of signal in Channel B, and the same mode gives you A − B. In some circumstances, you can use this capability to eliminate unwanted portions of certain waveforms.

X–Y mode

Technicians sometimes ask, "With a triggered scope, how can I use sweep alignment equipment?" They realize that feeding the generator baseline signal to the trigger input does not work. Nor do most triggered scopes have a horizontal input jack–at least, not labeled as such, although a few do.

The answer lies in a feature that is now part of virtually all triggered scopes: the *X–Y mode*. (One scope manufacturer calls it "A-vs.-B" mode.) This feature is not complicated. When you switch a dual-trace, dual-channel scope to the X–Y mode, one channel (usually Channel B) serves as a horizontal input channel. In single-trace scopes, the trigger amplifier becomes an X-axis amplifier; the X-input then is through the external trigger jack.

To the X-input arranged in this fashion, you connect the horizontal signal from a sweep generator. If one Y-channel has been converted to an X-channel, adjust its VOLTS/DIV switch for a baseline trace that fills the graticule from side to side. The scope's sweep no longer functions at all, nor does the trigger. Only the signal from the sweep generator forms the horizontal or X-axis trace.

Channel A, or whichever channel remains the Y-axis amplifier, accepts the response-curve signal from the video detector or demodulator probe. Otherwise, operation is similar to that for alignment with a recurrent-sweep scope.

You can use the X–Y mode for any purpose that suits the horizontal and vertical inputs of an older scope: Lissajous figures, phase comparisons, vectorscope displays, curve-tracer hookups, and the like.

Delayed Sweep

You won't find it on inexpensive instruments

YOU DON'T FIND DELAYED TRIGGERING on an inexpensive triggered scope Delayed triggering has long been considered a feature reserved for lab scopes used for broadcast-station monitoring. Typically, a service technician worked his entire career without ever seeing or even learning how to operate such a sophisticated device.

Scopes within the price reach of a serious technician now have delayed triggering. As you troubleshoot the digital systems of TV receivers, video games and personal computers, you may find this feature virtually indispensable. Not only does it help you pin down faults, delayed triggering can help you understand digital operations better than any teaching device I can think of.

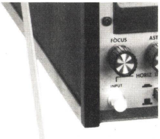

Hickok Model 532

Delayed triggering allows you to select precisely any portion of a waveform or pulse train you want to examine closely. For example, suppose you want to observe only the vertical interval reference (VIR) signal. (Why? To make sure it reaches the video detector unattenuated by the IF's.) You simply delay the trigger until the signal fed into the oscilloscope reaches line 19 (or the preceding line). To view the VITS signal on lines 17 and 18, you delay the trigger slightly less.

Figuring out delays sounds a bit complicated but it's not. You do not have to calculate delay times. In fact, you manage the whole operation visually. Elaborate scopes are designed for easy manipulation.

To simplify delayed-trigger operation, you will find a *sweep intensifier* system built into today's sophisticated oscilloscopes. With the Hewlett-Packard and Tektronix models that include this feature, you determine how much sweep is to be intensified by setting a knob that is concentric with the timebase switch knob. This Delay Time knob follows the same calibration marks (TIME/DIV) as for sweep time. Here's how you use the delay facility. Follow these steps using the photos of Fig. 6 and Fig. 7 as a guide, or go through them with your own scope.

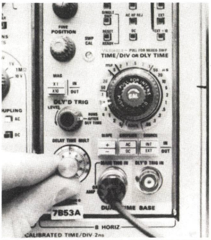

FIG. 6—VARIABLE DELAYED TRIGGER is a feature of more costly triggered scopes. Basically, a timebase determines how much of a waveform is to be viewed and a delay multiplier sets the time allowed to elapse before triggering fires the sweep.

1. Turn the Delay Time knob (Fig. 6-a) until you can see a portion of the display being brightened. Generally, this is at the start (left end) of the display. In Fig. 7-a, the brigher segment has been moved to the right of center, so you can see it better. If you can't see the intensified portion plainly, reduce the overall sweep intensity.

Ordinarily, try an approximate delay-

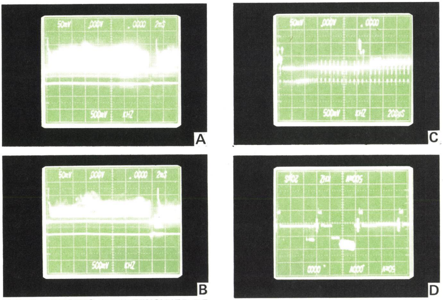

FIG. 7—EFFECTS OF INTENSIFIED DElay system. (*a*) Brighter bit of display indicates *where* delay will affect triggering. (*b*) Delay time set to encompass vertical-sync interval in video. (*c*) Delay system activated, displaying period selected by Delay Time knob and Trigger Delay multiplier. (*d*) ×10 magnifier expands trace to make VIR signal easy to examine.

Lectrotech dual trace unit.

time setting at one-tenth of the main sweep time. For example, Fig. 7-a shows the result of an intensifier setting of 0.2 ms with a main sweep time of 2.0 ms. You can refine the setting later. Although it's called delay time, you are setting the *duration* of intensified display that will presently be spread out for examination.

2. Find the Delay Multiplier knob (see Fig. 6-b). This is a decimal counter, connected inside to a precision multipotentiometer. This multiplier lets you choose exactly how much delay time you want between the *start* of the waveform and the portion you want to observe closely. The dial is tightly calibrated. But with this system, you don't usually have to concern yourself with the delay time itself. Just turn the potentiometer and observe the intensified portion of the sweep slide along the display. Superimpose the intensified portion of the sweep over the display segment you want to examine. In Fig. 7-b, the delay time has been moved over to intensify the vertical-sync interval.

3. Now, refine the Delay TIME/DIV setting so that it *includes* all the display segment you want to examine close-up but no more than that. If necessary, also refine precisely the *position* of the intensified segment by readjusting the Delay Multiplier knob.

4. Activate the trigger-delay feature. The Hewlett-Packard *model 1740A* has a pushbutton labeled DELAYED. On the Tektronix *model 7704*, you pull outward on the same knob (Fig. 6-a) you use to set the delay time/division. In either instance, and in other scopes with this arrangement, the display opens up precisely that portion of the waveform you marked with the intensifier.

B&K Model 1432

In case you do want to know the amount of delay time, in ms or µs, multiply the Delay TIME/DIV setting by the delay multiplier digits; the main dial shows 10's, the subdial shows units.

For example, in Figs. 6 and 7, the delay time was set for 0.2 ms-per-division. The delay multiplier has been set to 81 on its dial. Multiplying 0.2 by 81 gives 16.2 ms. The delayed trigger lets 16.2 ms of the original waveform go by without being seen. Then, upon triggering the sweep moves at a speed determined by the Delay TIME/DIV setting—in this case, 0.2 ms-per-division. At this point, across the 10 divisions of the scope graticule, you are looking at a 2-ms waveform that includes one vertical-sync interval of composite video, beginning 16.2 ms after the triggering point that was set initially for the main sweep.

5. You can carry this procedure one step further with the ×5 or ×10 magnifier. If you center exactly a portion of the delayed-sweep display, the magnifier spreads it out. Figure 7-d shows refined detail of a VIR signal on line 19 of the vertical interval.

"ANYONE WHO EXPECTS TO STAY in electronics beyond 1980 had better know how to operate a top-grade oscilloscope." So insisted Forest Belt at an interview shortly after completing preparation of this Special Section of **Radio-Electronics.**

"Not that they shouldn't understand scopes already," he went on. "Any good technician or engineer should. But, let's face it, plenty of them don't. They waste an hour or two every day sweating over repair and maintenance problems that would not be tough if they only had a good oscilloscope and kept it dusted off."

As Forest writes in the introduction to this section, there is no excuse not to learn. One new item aimed at making the learning easy is a Forest Belt *Service Training Monograph* just out this month. Its title: "Triggered Oscilloscopes—Four Hours to Familiarity." It is the first of two *Monographs* about triggered scopes in his Electronic Basics series. This illustrated *Monograph* No. 48A0202-24 takes its reader smoothly through a sequence of hands-on exercises that show exactly how triggered scopes work inside and out. Step by step, any student, engineer, or technician discovers what waveforms mean, how to display and analyze them, and what to do when they look wrong.

A companion *Monograph*, entitled "Triggered Oscilloscopes—More Hours to Advanced Understanding," (No. 58A0305-24) will be published next month.

Each *Monograph* sells for $8. Add $3 to your check for postage and handling. (That's $11 for one, $19 for both.) Order from Forest Belt's *Service Training Monographs*, Box 68120, Indianapolis, IN 46268.

So...Shop Around

Find exactly what you need. . . .
then buy your scope.

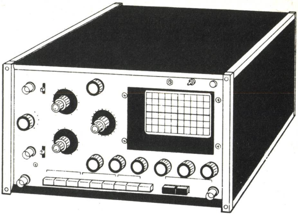

Table 1—Recurrent-Sweep Oscilloscopes

Brand	Model	Bandwidth (MHz)	Sensitivity (mV/cm)	CRT			Graticule		Sweep Range		Price $
				Inches	Shape	Phos-phor	Size (in)	Illum	from (Hz)	to (kHz)	
B & K Precision	1403A	5	10	3	Rnd	P31	10 cm		10	110	230
Conar	250	4①	250①		Rnd	NA			10	500	NA
Eico③	427	0.5	10	5	Rnd	NA			10	100	220
	435	4.5	50	3	Rnd	NA	2x3″	✓	10	100②	240
	460	4.5	35	5	Rnd	NA	4x4″	✓	10	100②	210
	462	10	10	5		P31	3x6cm		10	1000	NA
	465	6①	35①	5	Rnd	NA	6x10cm	✓	10	100②	330
Leader	LBO310A	4	NA	3	Rnd	NA	8x10 div		10	100	210
	LBO511	10	20	5	Rnd	NA	8x10 div	✓			300

NA Information not made available by mfr.
① Approximate mfr specification not standard
② Plus TVV and TVH sweep positions.
③ Available in kit form at less cost.

In very high-priced oscilloscopes, you encounter the "mainframe and plug-in" concept. For example, the Tektronix *model 7704* scope has a whole list of plug-ins.

In shopping for this kind of scope, you must first decide what kind of mainframe you want. What kind of CRT, which plug-in capability, whether you want on-screen readouts (see the Fig. 7 photos), and several other considerations come into play in choosing a mainframe.

Next, you have to decide which vertical amplifier module you need. You can obtain modules with four or more traces instead of just one or two. Bandwidth size is an important consideration here. Some modules have greater sensitivity than others. What you need determines your selection.

Then, you choose the timebase and the triggering system. Do you want plain or delayed triggering? HF rejection or not? How about TV triggering (usually an extra)? The Tektronix *Series 7000* scopes offer at least seven alternative modes just in timebase modules.

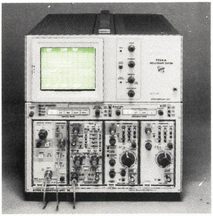

Tektronix Model 7704A.

Overall, you have a large number of options; check catalogs thoroughly and ask a sales engineer to go over your entire requirements. (*Note*—you may become frustrated in this attempt if you're a service technician. Few salespeople for sophisticated scopes have had servicing experience. They may not really know what your needs are. They are accustomed to selling to engineering, industrial maintenance and laboratory customers. So go slowly. Determine that any scope you buy will do exactly what you need it for.)

You find there are two more openings to fill on the *model 7704* mainframe. A digital voltmeter, itself containing three or four options, fits into one plug-in slot. Submodules include a digital VOM, an AC voltmeter, a thermometer probe (finds TTL IC's that are bad or becoming bad) and others. A frequency counter could fit into the other opening.

More modules are available for various specific purposes. Catalogs and alert salespeople can show you endless ways to make your expensive scope more versatile than you might have dreamed possible.

Telequipment Model D32.

And that's the name of this game. If you are a technician with an eye to a long and profitable career, soon you will take the step toward a really top-notch oscilloscope. I do not recommend buying a fancy triggered instrument just to say you have one. Instead, buy it to make your job easier, faster, more certain and more professional.

To accomplish that, take your time shopping. Find absolutely what you *need*. Be sure you are taught how to use that particular model to the best advantage. The oscilloscope you buy must save you time and make you more money. That's why a great scope is worth its cost.

R-E

computer corner

6502

An in-depth look at the widely used 6502 microprocessor.

WILLIAM BARDEN, JR.

THE MOS TECHNOLOGY MCS6502 MICROprocessor is one of the most widely used microprocessors today, especially in hobby computers where it is second only to the 8080. The Commodore PET, Apple, KIM-1 and Ohio scientific microcomputers are a few that use the 6502. Let's look at some of the hardware and software characteristics of the 6502.

6502 signals

The 6502's chief selling point is that it is an easy IC to interface, more so than the 8080. Only one power supply is required, +5 volts. Rather than a cumbersome two-phase clock, the 6502 uses an internal clock that requires only an external R–C network or crystal. Like the 8080, up to 64K (65,536) bytes of external memory can be used directly. Unlike the 8080, I/O devices are *memory-mapped,* meaning that I/O devices must share the 64K address with memory. All inputs and outputs are TTL-compatible.

Figure 1 shows the pinout of the 6502.

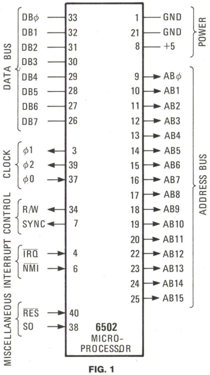

FIG. 1

There are 16 address lines, designated AB15 through AB0, and eight data lines designated DB7 through DB0; these data lines are bidirectional. (Here, as in many other microprocessors, AB0 and DB0 represent the least-significant bits.)

The clock lines are $\phi 0$, $\phi 1$ and $\phi 2$. Figure 2 shows the connections for the R–C network providing 1 percent accuracy for the clock frequency. Lines $\phi 1$ and $\phi 2$ are system clock outputs, defining a two-phase clock.

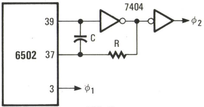

FIG. 2

Like other microprocessors, the 6502 can execute a variety of instructions. Instruction lengths are one, two, or three bytes, and execution times range from two *cycle* times (2 μs) to seven cycle times (7 μs). During the course of each instruction, the one to three bytes of the instruction is *fetched* from memory by a memory read for each byte. After the CPU has fetched the instruction, the *execution* portion of the instruction is implemented. The execution portion may require additional memory reads or

TABLE 1—6502 INSTRUCTIONS

Instruction Mnemonic	Explanation
ADC	Adds 8-bit operand to accumulator with carry
AND	ANDs 8-bit operand to accumulator
ASL	Shifts operand one bit left
BCC	Branches on no carry
BCS	Branches on carry
BEQ	Branch on equal
BIT	Tests operand bits
BMI	Branches on minus
BNE	Branches on not equal
BPL	Branches on plus
BRK	Software interrupt
BVC	Branches on no overflow
BVS	Branches on overflow
CLC	Clears carry
CLD	Clears decimal mode
CLI	Enables interrupt
CLV	Clears overflow
CMP	Compares 8-bit operand with accumulator
CPX	Compares 8-bit operand with X index
CPY	Compares 8-bit operand with Y index
DEC	Decrements 8-bit operand
DEX	Decrements X index
DEY	Decrements Y index
EOR	Performs exclusive OR on 8-bit operand and accumulator
INC	Increments 8-bit operand
INX	Increments X index
INY	Increments Y index
JMP	Jump to new location
JSR	Jump to subroutine
LDA	Loads 8-bit operand to accumulator
LDX	Loads 8-bit operand to X index
LDY	Loads 8-bit operand to Y index
LSR	Shifts operand one bit right
NOP	No operation
ORA	Performs OR on 8-bit operand and accumulator
PHA	Pushes accumulator into stack
PHP	Pushes program counter into stack
PLA	Pulls accumulator from stack
PLP	Pulls program counter from stack
ROL	Rotates operand one bit left
ROR	Rotates operand one bit right
RTI	Return from interrupt
RTS	Return from subroutine
SBC	Subtracts 8-bit operand from accumulator with carry
SEC	Sets carry
SED	Sets decimal mode
SEI	Disables interrupt
STA	Stores accumulator into memory
STX	Stores X index into memory
STY	Stores Y index into memory
TAX	Transfers A to X
TAY	Transfers A to Y
TSX	Transfers S(tack) to X
TXA	Transfers X to A
TXS	Transfers X to S
TYA	Transfers Y to A

THE COUNTERS YOU REALLY WANT

AT AFFORDABLE PRICES.

A Model for every need.

MODEL 380. 1 Hz to 80 MHz, 10 ppm **$209**
MODEL 380X. 1 Hz to 80 MHz, 1ppm **$269**
MODEL 385. 1 Hz to 512 MHz, 10ppm **$419**
MODEL 385X. 1 Hz to 512 MHz, 1ppm **$499**

Perfect for communications, CB, audio, TV and digital work, servicing and laboratory applications.

All 4 field-proven models feature full 7-digit display with automatic decimal and full autoranging. Our exclusive SPEED READ mode provides fast update (5/sec) time for easy tuning and adjusting.

Handsome, rugged metal case with brushed aluminum panel including all-angle tilt stand. (Low cost rack mounting kits for standard 19" rack also available.) All models come packaged in a plastic carrying case that protects the unit in shipment and in use.

Why settle for less than the best. See these hard-working counters at your distributor now.

HICKOK
the value innovator

INSTRUMENTATION & CONTROLS DIVISION
THE HICKOK ELECTRICAL INSTRUMENT CO.
10514 Dupont Avenue • Cleveland, Ohio 44108
(216) 541-8060 • TWX: 810-421-8286

CIRCLE 19 ON FREE INFORMATION CARD

writes, reads or writes to an I/O device, or simply perform internal processing, such as incrementing a register.

The R/W output is low for memory or I/O writes and high for reads. Transfer of data occurs during clock $\phi 2$. The direction of data transfer is determined by the state of the R/W line. As the 6502 always places known addresses on the address lines, the address, clock, and R/W signals are sufficient to control all memory and I/O reads and writes. The SYNC output identifies which cycles are fetch cycles in the instruction.The primary use of SYNC is to allow single instruction execution by using the RDY line.

The RDY line is an input used by a slow memory or I/O device to halt the microprocessor until the device can respond. Bringing down RDY during clock $\phi 1$ will halt the CPU until the signal is disabled. Lines RDY and SYNC can be used in control-panel microcomputers to execute a single instruction at a time.

There are two direct interrupts available for the 6502: IRQ and NMI. NMI is a nonmaskable interrupt that can never be disabled. A negative-going edge on NMI causes the CPU to transfer control to an NMI interrupt routine in memory. Interrupt IRQ is a maskable interrupt that can be enabled or disabled by the software program. If IRQ is not disabled, an external interrupt on this line causes a

continued on page 114

FREE
SHOP SUPPLIES
NATCAM
catalog
Shopping center for small and precision tools

A fine selection of small tools, measuring instruments, hard-to-find items for shop, home and lab. Convenient one-stop shopping for technicians, engineers, craftsmen, hobbyists. Major credit cards accepted, satisfaction assured. Get your NATCAM catalog today.

National Camera, Inc.
2000 West Union Ave., Dept. GBA
Englewood CO 80110 USA

CIRCLE 7 ON FREE INFORMATION CARD

Good soldering begins with the right solder selection

Different soldering applications require different alloys and different fluxes. Even different combinations of the two. You can't solder stainless steel, a pc board or aluminum with the same material. It just won't work. And that's a fact.

Now Multicore makes soldering easy. Not only to select the right solder. But to use it also. The flux is included in the solder as multiple cores. And in just the right ratios. There's no mess. Nothing to add. Think of it. Multiple cores for better distribution of the flux. You solder faster. Use less solder. Get better results. And that's a fact too.

Prove it to yourself.

Send For Your Solder Sampler Kit

Consists of 5 special solders each in a feed-out metal dispenser. Totals over 60 ft. for every solder requirement.

ELECTRICAL: Best general purpose solder with non-corrosive rosin flux for all types of wiring. Savbit® formula protects soldering iron tip from wearing out.

ELECTRONIC: A 60/40 tin/lead alloy, but extra thin (22 gauge) for electronic applications. Non-corrosive rosin flux cores.

STAINLESS STEEL AND SILVER JEWELRY: A tin/silver alloy with special flux; contains no lead. Blends in so well, you can hardly tell where its been used.

ALUMINUM: Special flux and silver alloy combination for soldering aluminum. There's nothing like it on the market.

PLUMBING AND SHEET METAL: For most metal joining applications except aluminum. Uses acid type flux.

ALL 5 FOR $8.95 Shipping and handling included

Plus Bonus Pak of Emergency Solder

A flat, tape-like solder that melts with a match, ideal for most on-the-spot emergency repairs

MULTICORE SOLDERS
DEPT. RE 578, WESTBURY, N.Y. 11590

☐ Send me a "Solder Sampler Kit" at the special $8.95 price (limit of one per person) and include my bonus Emergency Solder.

NAME ____________
ADDRESS ____________
CITY/STATE/ZIP ____________

Check or money order must accompany order
N.Y. State residents add approp. Sales Tax

FREE Solder User's Guide
No purchase required. Just circle reader service card.

Multicore SOLDERS

CIRCLE 58 ON FREE INFORMATION CARD

state of solid state

A TV modulator IC from National that produces a composite video modulated RF signal.

KARL SAVON, SEMICONDUCTOR EDITOR

DESIGNERS OF TV GAMES, TV TYPEWRITERS and microcomputer accessories must have digital know-how, yet be proficient in video and RF techniques. They sometimes borrow oscillator-modulator circuits that use coils that have to be wound, tapped and tuned, calling for time-consuming analog skills. The designers dream of putting color and sound into their systems, but more often than not are discouraged by the complications entailed. Now, National Semiconductor's LM1889 TV video modulator circuit generates a VHF signal complete with audio and color, with little more trouble than adding another integrated circuit to the schematic.

Figure 1 shows the circuit block diagram of the LM1889, which includes two RF oscillators that operate to 100 MHz. The oscillators are usually tuned to VHF low-band Channels 3 and 4. Either oscillator is selected by applying a voltage to the external R–L–C tank circuit. The sound oscillator is isolated from the rest of the IC, and can be externally frequency-modulated with a varactor diode or by switching a capacitor across the tank. External components add the sound.

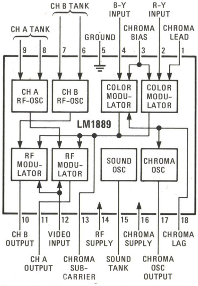

FIG. 1--LM1889 TV VIDEO MODULATOR IC accepts luminance, sync, chrominance and audio inputs and produces an RF modulated composite video signal.

The crystal-controlled color oscillator feeds two chroma modulators with quadrature signals (90° out-of-phase with each other). Chroma is generated using the R–Y and B–Y color-difference inputs to control the phase of the color-output signal. Burst-keying of the B–Y input inserts the reference burst during horizontal blanking. Two RF modulators add video, chroma and sound to the selected carrier frequency.

The internal sound oscillator uses a positive feedback differential amplifier. Difference amplifiers make good oscillators because the oscillations are amplitude-limited by the transistor cutoff that unloads the tank circuit. Oscillators that limit by shorting or otherwise loading the tank circuit reduce the oscillator stability and the waveform purity. The tank circuit for the sound oscillator is connected between pin 15 and the pin 16 power-supply input.

The two RF oscillators are positive feedback difference amplifiers similar to the sound oscillator. Voltage regulators are provided that hold the output of the RF oscillator to within about ±2 kHz of the tuned frequency over a 12- to 16-volt supply range. Each modulator is powered from the corresponding oscillator so that an oscillator-modulator combination is enabled as a block.

The RF modulators are double-balanced circuits that are fed from the chroma subcarrier on pin 13 and the video input on pin 12. If pin 12 and pin 13 are

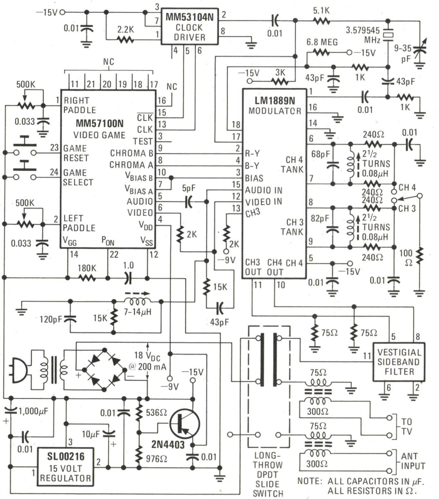

FIG. 2--TV GAME CIRCUIT uses the LM1889 modulator and MM57100 video game IC.

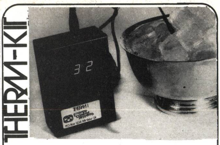

THERM I:
DIGITAL HEAT SENSOR

- THERM I kit: $69.95 (assy. $20 additional)
- *Battery operated
- *3 digit .3" LED display
- *Rugged handheld anodized aluminum case with 15' probe lead
- *Range: -31 degrees to 225 degrees F (-35 to 125 C) ± 1 degree C
- *May calibrate in degrees F or C

Other members of the THERM family include:
*THERM II: LCD display for ultra-low power dissipation.
*MINI–THERM: plugs directly into DVM for readout in mV/ degree F or C.
Check, money order, Master Charge or Visa accepted (include expiration date with credit card orders, please add 3% for charges.)
Calif. residents please add 6½% sales tax.
Add $1.25 for UPS shipping costs.

(415) 941–2764
P.O.Box 4477 Mtn. View CA 94040

ecs energy control systems

CIRCLE 82 ON FREE INFORMATION CARD

PROFESSIONAL DISCOUNTS

Texas Instruments
electronic calculator

TI-1750 LCD	$19.35	SR-40	$23.25
TI-2550 III	23.25	SR-51 II	47.05
Little Prof	12.55	TI-57 **NEW**	63.00
Dataman **NEW**	19.95	TI-58 **NEW**	95.79
TI-5100	38.75	TI-59 **NEW**	219.95
TI-5015 **NEW**	63.00	PC-100A	147.00
TI-5050 M	77.55	MBA	63.00
TI-5040 PD	95.00	Bus Anylst	26.95
TI-30 SP	16.98	TI-Programmer **NEW**	49.95
Dataclip	28.09	TI-1790 **NEW**	39.95

Ask for TI Digital Watches

HEWLETT hp PACKARD

		HP-27	$140.00
HP-10 **NEW**	$139.00	HP-29C **NEW**	156.00
HP-19C **NEW**	275.00	HP-80	235.00
HP-21	64.00	HP-67	360.00
HP-22	100.00	HP-91	260.00
HP-25	100.00	HP-92 **NEW**	500.00
HP-25C	128.00	HP-97	599.00

We're HP's authorized franchise dealer — all accessories are professionally discounted.

Also SCM, Olivetti, Casio, Canon, APF, Sharp, Craig, Sanyo, Record-A-Call, Norelco-Phillips and more. All at great prices!

Norelco NT-1	**$164.00**	Sanyo 9908	**$249.95**
Norelco 186	**245.00**	Sanyo 8000A	**199.95**

WE WILL BEAT OR MEET ANY COMPETITORS' PRICE IF HE HAS MERCHANDISE ON HAND. *All units shipped in original factory cartons with accessories according to manufacturers' specifications.* In Calif. call (213) 370-5795 or **CALL (800) 421-0367** (other than CA). Above prices are for cash only. BankAmericard/Visa & Master Charge prices differ. Send money order. Pers. ck (2 wks to clear): In CA add 6% sales tax. Add $3.50 min. shipping charges. WE SHIP AIR on request. Subject to availability. Send mail orders to DEPT. EM-J.
WRITE OR CALL FOR FREE CATALOG.

WRITE OR CALL FOR FREE CATALOG
WILSHIRE — 2 STORES — HAWTHORNE
CALL
tk enterprises Dept. RE-d
16611 HAWTHORNE BLVD., LAWNDALE, CA 90260
(213) 370-5795 • **(800) 421-0367**

CIRCLE 16 ON FREE INFORMATION CARD

biased at the same DC voltage, the modulator would be perfectly balanced and there would be no RF output. A DC offset between pin 12 and pin 13 unbalances the modulator and determines the unmodulated RF-carrier level.

The 3.58-MHz chroma oscillator also uses a difference amplifier. This oscillator requires an external R–C circuit and crystal. Oscillator-output terminal pin 17 drives the external 3.58-MHz crystal circuit. The crystal network has two 90° out-of-phase outputs that are the chroma-modulator inputs.

The color modulators are double-balanced circuits. As with the RF modulators, these stages must be biased with a DC offset between pin 2 and pin 3 and between pin 4 and pin 3 to set the subcarrier level.

Figure 2 is the schematic of a complete game circuit, in which the National Semiconductor MM57100N game IC is used to generate the video, chroma and sound inputs for the LM1889. Note that the 2N4403 power-supply regulator is the only discrete transistor. Figure 3 is a monochrome character generator display circuit that demonstrates how simple it is to use the LM1889.

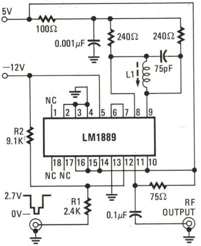

FIG. 3--MONOCHROME MODULATOR for character generator display.

The LM1889 TV video modulator has a maximum current drain of 45 mA. The minimum chroma-oscillator output is 4 volts P-P with up to 20-pF loading, and the minimum sound-oscillator output is 2 volts P-P. The minimum RF-oscillator level is 200 mV P-P. For more information, write to National Semiconductor Corporation, 2900 Semiconductor Drive, Santa Clara, CA 95051. **R-E**

NEXT MONTH

Great special section on personal computers. Everything from what they are to who makes what. Don't miss it. Reserve your copy of the June issue of **Radio-Electronics** today.

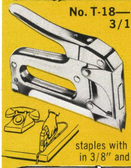
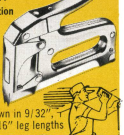
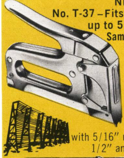
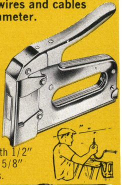

ARROW
AUTOMATIC
STAPLE GUNS

CUT WIRE & CABLE INSTALLATION COSTS
. . . without cutting into insulation!

SAFE! Grooved Guide positions wire for proper staple envelopment! Grooved Driving Blade stops staple at right depth of penetration to prevent cutting into wire or cable insulation!

No. T-18—Fits wires up to 3/16" in diameter.
BELL, TELEPHONE, THERMOSTAT, INTERCOM, BURGLAR ALARM and other low voltage wiring.
Uses T-18 staples with 3/16" round crown in 3/8" and 7/16" leg lengths.

No. T-25—Fits wires up to 1/4" in diameter.
Same basic construction and fastens same wires as No. T-18.
Also used for RADIANT HEAT WIRE
Uses T-25 staples with 1/4" round crown in 9/32", 3/8", 7/16" and 9/16" leg lengths

NEW! Intermediate No. T-37 – Fits wires and cables up to 5/16" in diameter.
Same basic construction as Nos. T-18 & T-25.
Also used for CATV and DRIVE RINGS in stringing wires.
Uses T-37 staples with 5/16" round crown in 3/8", 1/2" and 9/16" leg lengths.

No. T-75—Fits wires and cables up to 1/2" in diameter.
RADIANT HEAT CABLE, UF CABLE, WIRE CONDUIT COPPER TUBING or any non-metallic sheathed cable.
Also used as DRIVE RINGS in stringing wires.
Uses T-75 staples with 1/2" flat crown in 9/16", 5/8" and 7/8" leg lengths.

ARROW FASTENER COMPANY, INC.
271 Mayhill Street, Saddle Brook, N. J. 07663

CIRCLE 26 ON FREE INFORMATION CARD

Advanced Electron

Should your career in electronics go beyond TV repair?

CREI prepares you at home for broader and more advanced opportunities in electronics— plus offers you special arrangements for engineering degrees

There is no doubt television repair c be an interesting and profitable care field. TV repair, however, is only one the many career areas in the fast growi field of electronics.

As an indication of how career are compare, the consumer area of electro ics (of which TV is a part) makes up le than one-fourth of all electronic equi ment manufactured today. Nearly twi as much equipment is manufactured f the communications and industrial field Still another area larger than consum electronics is the government area. Th is the uses of electronics in such areas research and development, the spa program, and others.

Just as television is only one part the consumer field, these other fields electronics are made up of many care areas. For example, there are compute electronics, microwave and satelli communications, cable television, eve the broadcast systems that bring pr grams to home television sets.

As you may realize, career oppo tunities in these other areas of electro ics are mostly for advanced technica personnel. To qualify for these highe level positions, you need college-leve training in electronics. Of course, whil it takes extra preparation to qualify fo these career areas, the rewards ar greater both in the interesting nature o the work and in higher pay. Further more, there is a growing demand fo personnel in these areas.

Unlike most other home study schools CREI programs are devoted exclusivel to preparing you for careers in advance electronics. All of CREI programs ar college level. And CREI gives you both theory and practical experience in advanced electronics.

Unique Design Lab

A unique feature of CREI training is its Electronic Design Laboratory Program, which trains you to actually design circuits. It also helps you understand the theories of advanced electronics and gives you extensive practical experience in such areas as tests and measurements, breadboarding, prototype construction, circuit operation and behavior, characteristics of electronic components and how to apply integrated circuits.

reer Training at Home

Only CREI offers this unique Lab rogram. It is a complete college lab nd, we believe, better than you will find n most colleges. The "Lab" is one of he factors that makes CREI training nteresting and effective. And the pro-essional equipment in this program be-omes yours to keep and use throughout our professional career after you com-lete the training.

ngineering Degree
REI offers you special arrangements or earning credit for engineering de-rees at certain colleges and universities s part of your home study training pro-ram. An important advantage in these rrangements is that you can continue our full time job while "going to college" ith CREI. This also means you can pply your CREI training in your work nd get practical experience to qualify or career advancement.

ide Choice of Programs
CREI gives you a choice of specializa-tion in 14 areas of electronics. You can select exactly the area of electronics best for your career field. You can spe-cialize in such areas as computer elec-tronics, communications engineering, microwave, CATV, television (broad-cast) engineering and many other areas of modern electronics.

FREE Book
In the brief space here, there isn't room to give you all of the facts about CREI college-level, home study programs in electronics. So we invite you to send for our free catalog (if you are qualified to take a CREI program). The catalog has over 80, fully illustrated pages describ-ing your opportunities in advanced elec-tronics and the details of CREI home study programs.

Qualifications
You may be eligible to take a CREI col-lege-level program in electronics if you are a high school graduate (or the true equivalent) and have previous training or experience in electronics. Program arrangements are available depending upon whether you have extensive or minimum experience in electronics.

Send for this FREE Book describing your opportunities and CREI college-level programs in electronics

Mail card or write describing qualifications to

CREI
**CAPITOL
RADIO
ENGINEERING
INSTITUTE**

**McGraw-Hill Continuing Education Center
3939 Wisconsin Avenue Northwest
Washington, D.C. 20016**

Accredited Member National Home Study Council

GI Bill
CREI programs are approved for training of veterans and servicemen under the G.I. Bill.

service clinic

How to ruin horizontal output transistors.

JACK DARR, SERVICE EDITOR

THERE ARE QUITE A FEW WAYS TO DEstroy a brand-new horizontal output transistor, after finding the original transistor is shorted. Probably the best (and most common) method is to insert the new transistor and then apply full power to the set. Make sure that you do not check the flyback, low-voltage DC power supply or anything else. Following these principles can easily lead to what a British friend once called "a benchful of dead output transistors lying on their backs with their little legs sticking up in the air."

There are many other ways, none original. If I haven't tried them, someone else has. If you don't like the results, there are a few simple tests that will help hold transistor mortality down to a minimum. First, before inserting the new horizontal output transistor, check the DC supply voltage, which is regulated in the majority of sets. Make sure that this voltage is not *too high*.

If the DC voltage is high, then the voltage regulator isn't working. It should hold the voltage down to normal even under no-load conditions. The horizontal output stage is really a *voltage multiplier:* If you feed in, say, 125 volts, the output will be 25,000 volts. In other words, the output is directly proportional to the input voltage; hence, the use of the regulators. What happens is that the input voltage is multiplied by 200. Every 1-volt rise in the DC input means a 200-volt rise in the output! These excessively high voltages can break down perfectly good horizontal output transistors, as well as many other components.

Auxiliary circuits

The modern TV set may have quite a few auxiliary circuits driven from the flyback. These are low-voltage DC power supplies, or boost voltages, each one has its own rectifier and filter circuits. If the diodes in these circuits short, this overloads the flyback and output transistor. Therefore, check all the diodes for shorts. I cannot emphasize enough that these diodes must be fast-recovery diodes. Stock silicon types will not work in such circuits.

One of the best and safest tests is to use a variable-voltage line transformer, which costs about the same as a large horizontal output transistor. Don't insert the horizontal output transistor. Connect a current meter across the DC-output fuse holder, and connect a DC voltmeter to the output voltage. Then bring the line voltage up slowly. Both meters will indicate whether the DC voltage is too high; vary the voltage adjustment and see if it shows the right reaction.

If this checks out so far and you can find no obvious shorts in the flyback loads, then insert the transistor and bring the voltage up slowly. The size of the DC-output fuse will indicate approximately what the normal current should be. For example, if the fuse is a 1.5-amp unit, the current should be around 900 to 1000 mA maximum. If you see more than 1.2 amp and the line voltage is only about 75, back out of there *fast!* You've still got a problem. (Warning: this variable-voltage test will *not* work with the saturated-core (resonant) power transformers, such as those used in Zenith sets and others. These transformers hold the output at zero until about 45 volts, and then they rise suddenly to full output. The only way to use this test in such circuits would be to disconnect the set's low-voltage DC supply and use a bench power supply plugged into the variable-voltage transformer. The clue to the use of these transformers is the 2- to 3-μF nonpolarized electrolytic capacitor, connected across the entire secondary.)

High-voltage shutdown

Another common circuit used in these sets is the high-voltage shutdown. There may be more than one of these circuits, all used for the same purpose. If these circuits are working, they do not damage anything, just turn them off. However, if the high-voltage shutdown itself is faulty, it can cause overloading. By slowly advancing the line voltage, you can check these circuits for normal operation. Many use SCR's (*S*ilicon-*C*ontrolled *R*ectifiers), that kill the horizontal oscillator, etc. In some early versions, the SCR used to shut down on normal brightness changes, program changes, etc. There are factory fixes for most of these, usually involving changing to a different SCR, or making adjustments to the gate circuit to eliminate premature tripping. (Although the temptation is great in many instances, it isn't a good idea to disable the shutdown circuit. They can save a lot of trouble.)

Now, a few words about derating. If the horizontal output transistor fails repeatedly, even though exact replacements were used, it's possible that the original transistor didn't have a high enough rating. Cross-check the type number of the original shown in any of the better transistor guides to see what substitute is recommended. For example, if the substitute transistor is rated at 800 volts V_{cbo} (collector breakdown voltage) and it's not holding up, try another one of the same type and case, having a much higher V_{cbo}. There are some transistors available that are rated up to 1200 and even 1500 volts. They also usually have higher collector-current ratings, which helps keep the junction running cooler and should increase the life of the transistor.

Capacitors

Finally and most important, problems can occur in sets using collector-shunt capacitors in the horizontal output stage. These capacitors are actually *tuning* capacitors for the retrace pulse. The worst aspect about this problem is the fault condition that can damage the new transistor is not a shorted capacitor, but an *open* one! If a capacitor opens, the retrace frequency changes, the pulse goes to tremendous heights and something pops. It is therefore advisable always to check these collector-shunt capacitors for opens. In fact, if you can't find any obvious cause for the failure of the original horizontal output transistor, it is a good idea to replace these capacitors.

You will have to use factory replacement parts because the capacitors are special types and there is currently no available data on general-purpose replacements.

With a little extra care in checking and some luck, you will be able to avoid the embarrassment and expense of having to "replace the replacement transistor" that you just finished installing! **R-E**

service questions

LOSES VERTICAL SWEEP

This GE solid-state set loses both its vertical sync and its sweep right after it warms up. I found that the Q204 collector voltage drops to only 3. I'm not too familiar with solid state. Can you help?—L. M., Pettus, WV.

I'll try. This sounds a lot like a thermal transistor. Use freeze spray on all the transistors in the vertical stage after you lose the sweep. Transistors are often extremely thermal.

(Feedback: "Right! A couple of squirts of freeze spray showed that the vertical-output transistor was bad.")

VOLTAGE TROUBLE

Here's a cute one. In a Sylvania DO-J, there was excess cathode current in the 42KN6. The grid voltage was going down to only −25 volts. After you suggested checking the 42KN6, I discovered that the +135-volt source was low. I disconnected this from several circuits; no help. Finally, I lifted the screen voltage feed to the 42KN6, and it went up. I tried a new 42KN6 tube, and this fixed it! Thanks.—Vito Shimkus, Dalton, PA.

We have run into this kind of problem in quite a few different horizontal-output tube sets. The screen seems to be taking too much current, dropping the voltage. I haven't found out the exact failure mechanism yet, but I do know that if the screen voltage drops with no apparent cause, you should try a new tube.

BURNT OHMMETER RESISTOR

Resistor R15 has burned up in the ×10 range in this Kyoritsu KEW-33 VOM. Can you tell me what the value is?—H. P., Brasilia, Brazil.

Since I've never heard of this make of VOM, I can't tell you what the value of the resistor is. However, if you want to find out, just read the resistor value in the ×100 range. The circuit diagram you sent shows this VOM is a stock ohmmeter; the ×10 resistor should be one-tenth the value of the resistor in the ×100 range. You can check this with a precision variable resistor that gives you exactly half-scale on the ×10 range, and read this.

HORIZONTAL DRIFT

This Olympic 6C124 set loses its horizontal sync after about 10 to 15 minutes. The horizontal-hold control brings it back. The horizontal oscillator coil doesn't seem to have much effect. You can give the coil several turns without doing much.—H. S., Cambridge, MD.

The horizontal oscillator coil should have a very *definite* effect on the frequency. Several things can cause this problem: The .0039 μF capacitor across the coil could be leaky. (Or perhaps it was replaced with one having the wrong value; this has happened!) Finally, this is rare but possible—run the core out of the coil and see if half of it has broken off. If so, this will upset the tuning rather badly.

turn page

Hi-Fidelity Ceiling Speakers

Revolutionary Lucite Construction
Unique Design
DK6-F
Patented
Sugg. Retail Price $59.95 each

Decorator Design
Today's Sound with a Touch of Elegance
RS69-F
Patented
Sugg. Retail Price $64.95 each

Completely Recessed
Blends Beautifully with any Decor
RSQ8-F
Patented
Sugg. Retail Price $69.96 each

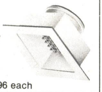

"The Perfect Marriage of Sight-N-Sound"
MONEY BACK GUARANTEE
SEND CHECK/MONEY ORDER OR
WRITE FOR EXCITING DETAILS

ROHN ELECTRONICS LTD.
5 Pearsall Ave., Glen Cove, NY 11542
(516) 671-4777
DEALER AND REP. INQUIRIES INVITED

CIRCLE 64 ON FREE INFORMATION CARD

A 20MHz OSCILLOSCOPE UNDER $500?

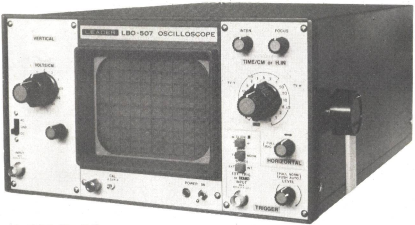

YES !! LBO - 507 by LEADER Instruments Corp.

FEATURES:
- 20 MHz bandwidth
- Unique trigger circuit for maximum display stability
- 10 MV sensitivity
- Bright display
- TV trigger
- Built-in calibration signal
- Triggered and automatic sweep
- Built-in TV vertical and horizontal sync separation circuits
- Check most digital logic circuitry, including CMOS
- 18 sweep range selections
- Sweep to .1μSEC/cm

SPECIFICATIONS
VERTICAL AMPLIFIER
SENSITIVITY: 10mV/cm – 20V/cm CALIBRATED IN 11 STEPS (1-2-5 SEQUENCE UP TO 50V/cm WITH VARIANCE CONTROL)
ACCURACY: ±3%
BANDWIDTH: (DC) DC–20MHz (-3dB, 4 cm)
(AC) 2Hz–20MHz (-3dB, 4 cm)
RISE TIME: 17.5nSec.
INPUT IMPEDANCE: 1M OHM SHUNTED BY 35pF (±5pF)
INPUT COUPLING: AC, DC, GND
MAX. INPUT VOLTAGE: 600V (DC & AC p-p)
INPUT CONNECTOR: BNC
TIME BASE
SWEEP SPEED: 0.5 MICRO SECOND/cm – 200mS/cm, 18 STEP, 1-2-5 SEQUENCE UP TO 500mS/cm WITH VARIABLE CONTROL
ACCURACY: ± 5%
MAGNIFICATION: x5 ±5% (MAX SPEED 100nS/cm)
SYNCHRONIZATION
MODE: TRIGGERED & AUTOMATIC
SIGNAL SOURCE: INTERNAL OR EXTERNAL, + OR – SLOPE
SENSITIVITY: TRIGGERED (INT.) 2Hz–15MHz AT 1cm
(EXT.) 2Hz–15MHz AT 100mVp-p
AUTOMATIC (INT.) 50Hz–15MHz AT 1cm
(EXT.) 50Hz–15MHz AT 100mVp-p
HORIZONTAL AMPLIFIER
SENSITIVITY: 200mV/cm (MAG. x5)
1V/cm (MAG. x1)
UP TO 5V/cm WITH FINE ADJUSTER

NEWCOM SHOW SPECIAL!!

master charge
For show special call our toll-free hot line.
VISA

212-687-2224
THE TEST EQUIPMENT SPECIALISTS
TOLL FREE HOT LINE
800-223-0474
54 West 45 Street, New York, N.Y. 10036
ADVANCE ELECTRONICS

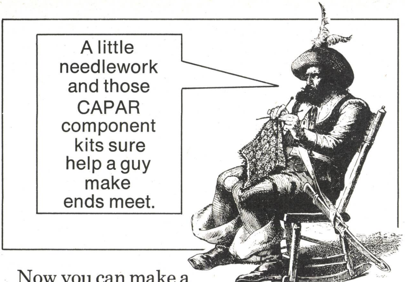
A little needlework and those CAPAR component kits sure help a guy make ends meet.

Now you can make a profit selling Capar capacitors and resistors even if you're a small retail outfit. You can sell aluminum electrolytics, dipped solid tantalums, metallized mylars, polyester film, ceramic discs, and deposited carbon resistors—without buying in large quantities. With Capar's kits you can buy small quantities of a variety of components at a price you can afford. In fact, Capar offers the most economically priced kits on the market.

Each kit contains a popular assortment of devices geared for one general area of use. We currently have an assortment of kits that are geared for use by servicemen and technicians; hobbyists and experimenters; design engineers; and distributors (new starter kits). These components are packaged in an attractive, clear plastic box, that is divided into sections, and is supplied with specification sheets.

These days we can all use a few extra dollars and here's one easy way of doing it. For more information call our toll free number 800 645-7474.

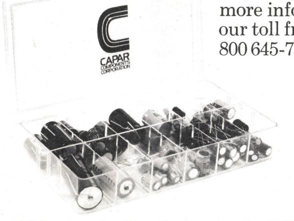

CAPAR COMPONENTS CORPORATION

303 Crossways Park Drive, Woodbury, New York 11797;
Telephone (516) 364-2610; (800) 645-7474; Telex No. 144678

See us at booth P9, Newcom Show

CIRCLE 57 ON FREE INFORMATION CARD

WEAK INTERCOMS

Two wireless intercoms built from kits are weak. The voice comes through clearly, but there's not enough volume. All voltages seem to check out OK. Any ideas?—R. A., Brooklyn, NY.

Two of them. First, check the *tuning* on both units. Each receiver must be tuned to the other transmitter. Feed an audio signal into the mike on one, and tune the other receiver; then repeat the process.

Second, this is a carrier-current system, and low-frequency RF signals travel on the AC lines between the units. If you plug one unit in on one side of your home AC line, and the other on the other side, the chances are the signals will be weak. Add a bypass capacitor from one side to the other, insulating it carefully. Check them out in the same room and same outlet. If they work then, the problem lies in the transformer.

INTERMITTENT RASTER

This Magnavox T989 comes on with 25 kV . . . momentarily. It plays for a minute or two. Pushing in the circuit breaker sometimes creates a raster for a second. I've checked or replaced everything I can think of except the flyback. Would you replace that? What ails this critter?—T. D., Bellevue, OH.

Frankly, I don't know! I've always waited until the very last to change a flyback. However, there are a couple of other things you didn't mention. First, check Zener diode Z301 in the high-voltage shutdown. There is a silicon controlled rectifier (SCR) and the Zener voltage goes to its gate, at which point it kills the horizontal *drive*. Scope the drive signal and see if it pops in then disappears. (Also check the SCR.)

(Feedback: "Zener Z301 was shorted and that fixed it. How did you know?") I'll never tell—I just guessed!—*Service Editor*

DUPLICATE FLYBACK NEEDED

I need a flyback for a Bradford BATV-60525A chassis. I can't find this chassis number listed anywhere, nor do I know of a source for a replacement part. Help!—P. L., Red Hook, NJ.

Believe it or not, the Bradford chassis was manufactured by no less than 16 different companies! However, according to the part number you indicate, the chassis *you* have was manufactured by Westinghouse. *Thordarson's Guide* doesn't show a substitute part number under Bradford but it does show an exact duplicate part number for Westinghouse—493V023D01, and FLY-445 is listed as a substitute.

PALE VIDEO, SHORT SCAN

The picture on this Zenith 16Z7C50 was pale and weak. The plate voltage on the video output tube read only +190 (270 normal). Checks showed that the

4700-ohm shunt-feed resistor was open. There are two paths for this plate voltage, one through the peaking transformer in the picture tube cathodes and another through this 4700-ohm resistor. This fixed the video problem.

Now, the raster was short. Adjusting the vertical controls lengthened it, but it was badly nonlinear. Checking around in the large resistors in the height control circuit showed a 4.7-megohm resistor that read more than 7.0 megohms. This fixed the linearity problem.

NO RASTER

The raster is dark on this Magnavox T-950. I've got plenty of high voltage and the picture tube is good. What is this?—E. C., Napanoch, NY.

Check the focus voltage. If this is down to zero, the raster won't light.

(Feedback: "That's it. They never told me in school that this would cause a no-raster condition! How did you know?")

The same way you did, the hard way! After spending a good deal of time checking everything out, I said "Well, there's no high voltage." I reached into the set; there was a loud ZAP and a scream, which told me I had *plenty* of high voltage. Some time later, I read the focus voltage, which was zero, just like yours; it was caused by a dead focus rectifier. I highly recommend using a high-voltage meter. Much less painful than the way I did it then.

VERTICAL HOLD

This GE LX chassis has a vertical hold problem. I can't get the picture to stop, with the hold control all the way to the end.—J. G., Flushing, NY.

You've got a time-constant problem, apparently. The oscillator cannot be brought close enough to the right frequency to lock. Check all the resistors in the control grid circuit, including the height control and R205, the 150K fixed resistor to ground. If these resistors are OK, then check capacitors C203 and C204 very carefully for leakage; same result.

(Feedback: "You're 100% right. I changed capacitor C203 and fixed it. Thanks!")

TAPE-SPEED CHECK

I have two questions: One, how much variation can there be in a tape player running at each of the three standard speeds? Second question: Are there test tapes available that can be used to check speed?—J. B., Landis, NC.

First, that's a good question and I'm sorry you asked! I don't know the exact tolerance in speed. However, it is pretty darn small. You can usually tell by listen-

turn page

MATHEMATICS
ELECTRONICS
ENGINEERING MATHEMATICS
ADVANCED MATHEMATICS

These unusual courses are the result of many years of study and thought by the President of Indiana Home Study, who has *personally* lectured in the classroom to *thousands* of men, from all walks of life, on mathematics, and electrical and electronic engineering.

You will have to see the lessons to appreciate them!

NOW you can master mathematics and electronics and actually *enjoy* doing it!

WE ARE THIS SURE:—you order your lessons on a money-back guarantee.

In plain language, *if you aren't satisfied you don't pay,* and there are no strings attached.

Write today for more information and your outline of courses.

You have nothing to lose, and everything to gain!

The INDIANA
HOME STUDY INSTITUTE
P.O. BOX 1189
PANAMA CITY, FLA 32401

CIRCLE 23 ON FREE INFORMATION CARD

NEW LBO-508
DUAL TRACE
OSCILLOSCOPE

A 20MHz OSCILLOSCOPE AT A 10MHz PRICE

ANOTHER QUALITY
TEST INSTRUMENT BY **LEADER Instruments Corp.**

SPECIFICATIONS

VERTICAL AMPLIFIER	(IDENTICAL FOR BOTH CHANNELS)	
	SENSITIVITY:	10mV/cm – 20V/cm CALIBRATED IN 11 STEPS (1-2-5 SEQUENCE UP TO 50V/cm WITH VARIANCE CONTROL)
	ACCURACY:	±3%
	BANDWIDTH:	(DC) DC–20MHz (-3dB, 4 cm) (AC) 2Hz – 20MHz (-3dB, 4 cm)
	RISE TIME:	17.5nSec.
	INPUT IMPEDANCE:	1M OHM SHUNTED BY 35pF (±5pF)
	INPUT COUPLING:	AC, DC, GND
	MAX. INPUT VOLTAGE:	600V (DC & AC p-p)
	CHANNEL 2 POL:	INVERTS CH-2 POLARITY
	INPUT CONNECTOR:	BNC
TIME BASE		
	SWEEP SPEED:	0.5 MICRO SECOND/cm – 200mS/cm 18 STEP, 1-2-5 SEQUENCE
	ACCURACY:	±5%
	MAGNIFICATION:	x5 ±5% (MAX SPEED 100nS/cm)
DUAL TRACE DISPLAY		
	MODE:	CH1, CH-2, X-Y, DUAL, ADD.
	CHOP (AUTOMATIC SEL IN DUAL MODE):	200mS/cm – 0.5mS/cm
	ALT (AUTOMATIC SEL IN DUAL MODE):	200 MICRO SECONDS/cm – 0.5 MICRO SECONDS/cm
	ADD:	SUM OR DIFFERENCE (WITH CHANNEL 2 INVERT)
X-Y DISPLAY		
	(X = CH 1 Y = CH 2)	
	SENSITIVITY:	Y AXIS: 10mV/cm – 20V/cm X AXIS: 10mV/cm – 20V/cm
	BANDWIDTH:	X AXIS: DC OR 2Hz – 800KHz (-3dB, 10cm)
	X-Y PHASE:	LESS THAN 3%AT 100KHZ
SYNCHRONIZATION		
	MODE:	TRIGGER, AUTOMATIC
	SIGNAL SOURCE:	INTERNAL (CH1 OR CH2) OR EXTERNAL, + OR – SLOPE
	TRIGGER SENSITIVITY:	TRIGGERED (INT) 2Hz – 15MHz AT 1 cm (EXT) 2Hz – 15MHz AT 100mV p-p

NEWCOM SHOW SPECIAL
For show special
call our toll-free
hot line.

FOR MORE INFORMATION OR TO ORDER CALL
master charge THE INTERBANK CARD
TOLL FREE HOT LINE
800-223-0474
VISA®

ADVANCE ELECTRONICS®
54 West 45 Street, New York, N.Y.10036 212-687-2224
THE TEST EQUIPMENT SPECIALISTS

AVANTI®
CB ANTENNAS
CAN GIVE YOU
50 TIMES
MORE OUTPUT
AND
RECEPTION.

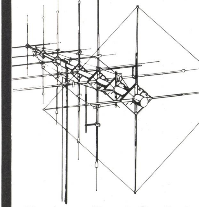

The famous Moonraker® Six by AVANTI is designed to be the ultimate in C.B. antennas. The Moonrakers 17 db gain gives you power multiplication of 50 times. On both vertical **and** horizontal polarities.

For all your antenna needs...AVANTI has a full range of hi-performance base antennas plus high performance "Racer" mobile antennas for better CB, VHF, and marine uses.

AVANTI also makes T.V. interference filters, switchboxes, mounting hardware, and many other accessories.

Write today for a free color catalog in Spanish or English.

avanti

Avanti Research & Development, Inc.
Established 1964
340 Stewart Ave., Addison, IL 60101 USA

creators of the famous MOONRAKER®

©Copyright 1977,
All rights reserved

CIRCLE 72 ON FREE INFORMATION CARD

ing to musical selections. At slow speed, the music will be flat; at fast speeds it will be sharp (excluding rock music and synthesizers).

Second, yes, there are quite a few test tapes available. The Audiotex Division of General Cement (Rockford, IL 61101), for one, has test tapes for 8-track cartridges, cassettes and reel-to-reel units. These tapes have standard-frequency runs, single-tone sequences, etc. You can connect a scope on the output, run the 1000-Hz band and check its frequency. A frequency counter is also very good for this kind of test.

NO SERVICE DATA

I can't find the service data on this RCA stereo. There are several numbers on the chassis, including the serial number RC1223C, and some others. Can you help me find this data?—W. T., Fremont, CA.

I've been looking for an easy question all day and this is it! You have already found the data you need. The "RC-1223C" serial number is RCA's *chassis* number for radio components. You can find this number listed in the back part of the RCA section in the Sams *Photofact Index*. It is in 930-7, in fact.

WATCH FOR KEY CLUE!

I had just gotten through chewing out a friend for walking right over a key clue when a technician in Longmont, CO wrote me about a set of waveform readings, P-P voltages, etc., in a vertical sync problem. I told him to check the integrator, etc. He wrote me back saying that didn't help.

To my horror, I then saw that I had walked right over the key clue in his first letter that had been right there in the schematic. His composite-sync waveform at the sync-separator output read only *1.5 volts* P-P! Of course, this should have been 50 volts P-P. So, I apologized and told him to check that sound-sync amplifier stage, which was definitely close to the cause of the problem.

SEVERE HEIGHT LOSS

I wrote about a severe loss of height in a Sylvania DO-2. You told me to check several places, including the cathode circuit. This checked out OK, so I started checking capacitors. I found that C336, 0.0056 μF, 2-kV, was shorted. I can't quite see how this caused such a loss in height; most of the bias upsets I've found have caused a severe foldover! Thanks for the lift, anyhow.—R. C., Toledo, OH.

You're welcome even if I didn't do so well! Capacitor C336, by the way, is actually in the feedback loop. It seems to be the lower part of a saw-forming network from the feedback loop back to the input-section control grid. The capacitor probably reduced the feedback pulse so that the oscillator couldn't deliver enough amplitude! (From the crystal-ball department.) **R-E**

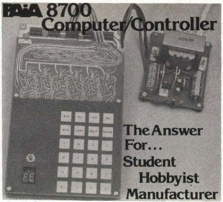

PAIA 8700 Computer/Controller

The Answer For... Student Hobbyist Manufacturer

8700 Processor: 6503 MPU, Wear free "Active Keyboard", Micro-Diagnostic®, Extensive documentation, Fully Socketed.

Piebug Monitor: User Subroutines, Relative address calculator, Pointer High-low, Back-step key.

Cassette Interface: Load & Dump by file #, Positive indication of operation, Tape motion control.

Applications systems from $90 (10 unit quantity)
Development systems from $149 (single unit)

TELL ME MORE I want to see for myself that the 8700 is The Answer.
( ) Please send documentation $10 enclosed.
( ) send price lists & FREE Catalog of other PAIA kits.
name: ____________
Address: ____________
City: ________ State: ______ zip ______

PAIA ELECTRONICS DEPT. 5-R • 1020 W. Wilshire Blvd. • Oklahoma City, OK 73116 •

CIRCLE 15 ON FREE INFORMATION CARD

RCA
SelectaVision
VIDEO CASSETTE RECORDER

- Optional black & white camera
- Record up to 4 hours
- Ease of operation
- Remote pause control
- Tape counter with memory
- Built-in electronic digital clock/timer
- Optional microphone
- RCA cassettes are available with up to 2- or 4-hour recording capacity

LIST PRICE $1,000.00
SPECIAL PRICE $850.00
PLUS $10 SHIPPING

TAPE PRICES: VK-125 - 2 HR - $17.95
VK-250 - 4 HR - $24.95

No sales tax charged if bought out of State of Minnesota.

PHONE (507)245-3335

HODAPP T.V. SALES
322 Main
St. Clair, Minnesota 56080

new products

More information on new products is available from manufacturers of items identified by a Free Information number. Free Information Card is inside back cover.

FREQUENCY COUNTER, *model LDC-822*, features 8-digit LED display and operation to 80 MHz; variable sensitivity to 20-mV to eliminate stray RF signals; and a 10-MHz timebase with 5-ppm accuracy. Comes with test leads, and is suitable for both industrial and field/bench applications. Price: $299.95.—**Leader Instruments Corp.,** 151 Dupont St., Plainview, NY 11803.

CIRCLE 107 ON FREE INFORMATION CARD

TRIGGER EXPANDER, *model 10*, is a 16-bit add-on to the 8-bit *model 100A Logic Analyzer*, forming an integrated 24-bit logic analyzer package for microprocessor troubleshooting, training and system development.

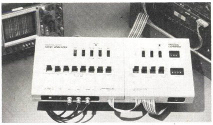

The *model 10* captures and displays the instruction and data flow on the microprocessors data bus at the occurrence of a particular 16-bit address. The combination *model 10/model 100A* package can display a 16-word deep data-domain truth table of both lower and upper address bytes and the date byte, which can be viewed via a three-position switch. A 25th input called a "qualifier" permits selected machine states, such as read, store, etc., to be collected for display. A clock delay feature allows up to 1000 steps of a program without changing the reference trigger word. The *model 10* can also be used to display the state of the machine after "n" passes through the loop.

Both the *model 10* and the *model 100A* are available as kits or assembled and come with buffered data probes terminated with gold-plated "universal" pin connectors. Optional baseplate locks both units together. Each unit contains both owners manual and 100-page applications manual. Prices: *model 10* kit, $229; assembled, $295. *Model 100A* kit, $198.50; assembled, $272. Optional baseplate, $12.—**Paratronics, Inc.,** 800 Charcot Ave., San Jose, CA 95131.

CIRCLE 108 ON FREE INFORMATION CARD

ELECTROLYTIC ALUMINUM CAPACITORS, *Series TDA*, is a complete line of axial-lead devices having values to 22,000 µF. Designed to operate in temperatures from −40°C to +85°C, the

NEW **LBO 520**

30MHz DUAL TRACE OSCILLOSCOPE WITH DELAY

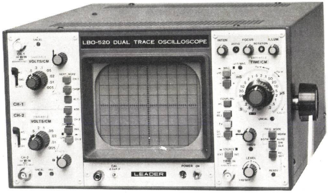

150 INCLUDES 2 PROBES

NEWCOM SHOW SPECIAL
NORMAL PRICE **$999.95**

SAVE $150

ON LBO-520 OSCILLOSCOPE
SPECIAL PRICE **$849.95**

OFFER EXPIRES AUG. 31, 1978

150 INCLUDES 2 PROBES

master charge THE INTERBANK CARD

BANKAMERICARD

FEATURES:

- 5mV sensitivity
- 11.7nS rise time
- Fixed delay (120nS)
- 20nS/cm sweep capability

SPECIFICATIONS

VERTICAL	CRT:	5"
	DISPLAY AREA:	8cm (VERT.) x 10cm (HORIZ.)
	ACCELERATOR VOLTAGE:	4.8kV/1.2kV
	BANDWIDTH:	DC - 30MHz (8cm BASE - 3dB)
	SENSITIVITY:	5mV/cm - 5V/cm, 10 STEPS, 1-2-5 SEQUENCE UNCALIBRATED AND CONTINUOUSLY VARIABLE IN BETWEEN STEPS
	INPUT IMPEDANCE:	1M OHM 35pF
	INPUT VOLTAGE:	600V (DC AND AC PEAK)
	DISPLAY MODES:	CHANNEL 1, CHANNEL 2, ALTERNATE, CHOP (230KHz), X-Y (CH-1 = X, CH-2 = Y)
	RISE TIME	11.7nS
	TRIGGERING:	CH-1; CH-2
	SIGNAL DELAY:	120nS
HORIZONTAL	SWEEP TIME:	0.2uS/cm - 0.5 Sec/cm MAX. SWEEP 20nS/cm WITH MAG. x 10 UNCALIBRATED AND CONTINUOUSLY VARIABLE IN BETWEEN STEPS
	MODE:	AUTO: SYNCHRONIZE TO REPEATED WAVE-FORM OVER 20Hz. FREE RUN BELOW 20Hz AND UNDER NO TRIGGER CONDITIONS. NORMAL: NO SWEEP UNDER NO TRIGGERING SINGLE: ONE TIME SWEEP ONLY
	COUPLING:	AC, HF REJ, TV, DC (EXT.)
	SIGNAL SOURCE:	INTERNAL CH-1 CH-2 EXTERNAL
	POLARITY:	+ AND –
	SENSITIVITY:	0.5cm 20Hz - 30MHz (AC) 5mV/cm - 5V/cm X–AXIS & Y–AXIS

LEADER Instruments Corp.

ALL CONTROLS ON FRONT PANEL FOR EASY OPERATION, LAMP INDICATION FOR UNCALIBRATED AND TRIGGERED CONDITIONS. BEAM ROTATOR ADJUSTS FOR MAGNETIC FIELDS. HANDLE SERVES AS LOCKING BALE.

POWER SUPPLY:	50/60Hz 100V/115V/200V/215V/230V
SIZE:	11½" (W) x 6⅞" (H) x 14 3/4" (D)
WEIGHT:	19 lbs.
ACCESSORIES:	PROBE COMBINATION DIRECT/LOW CAP LPB-16X (2) BNC TERMINAL ADAPTOR (2)

TOLL FREE HOT LINE
800-223-0474

THE TEST EQUIPMENT SPECIALISTS

54 West 45 Street, New York, N.Y. 10036 212-687-2224

ADVANCE ELECTRONICS

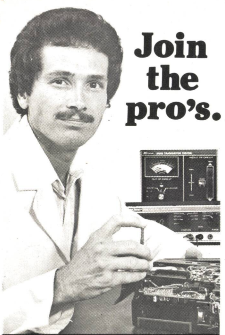
Join the pro's.

For technical specialists career prospects are good. Forecasts show that job openings in many technical areas are increasing.

In photography a high skill level as a camera repair technician commands a good salary and opens doors to advancement. As with other fields where the jobs are, good training is the key to success. National Camera has successfully trained photo equipment technicians for 25 years. And popular interest in new electronically controlled cameras is helping to create more opportunities than ever for you as a camera technician.

Expand your talents into a new area—work full time or part time, independently or for a wide variety of employers. Learn at home in spare time, or attend intensive training program in Colorado.

Founded 1952
Accredited member NHSC, NATTS.
Approved for Veterans' training.
Eligible institution,
Federal financial aid programs.
Resident training also available.

National Camera
Technical Training Division
2000 West Union Avenue Dept. GBC
Englewood, Colorado, 80110 U.S.A.

Return coupon today for free booklet. No salesman will call.
I am interested in ☐classroom
☐home study ☐Check here if veteran
Please print:
Name____________________
Address____________________
City____________________
State__________ Zip__________
Send to: National Camera
2000 West Union Ave., Dept. GBC
Englewood, Colorado 80110

CIRCLE 8 ON FREE INFORMATION CARD

Series TDA devices have a capacitance range of 0.47 µF–22,000 µF, with a DC voltage range from 6.3 to 50. A 10,000-µF capacitor (shown) measures less than 1 × 2-in., and costs $29.50 per 5000.—**International Components Corp.**, 105 Maxess Rd., Melville, NY 11746.

CIRCLE 109 ON FREE INFORMATION CARD

SELF-STUDY COURSE in photographic electronics—eight lessons and supplements in looseleaf form. Course features electricity and electronics fundamentals and their application to camera repair, as well as special circuit coverages. Comes with step-by-step illustrations, self-test quizzes and optional final exam.—**National Camera, Inc.**, Larry Lyells, 2000 W. Union Ave., Englewood, CO 80110.

CIRCLE 110 ON FREE INFORMATION CARD

40-CHANNEL CB BASE TRANSCEIVER, *model CBB-1040*, is base-station version of *model CB-640 Aircommand* mobile unit. Base transceiver features power mike, dual-conversion superheterodyne receiver, Channel-9 priority scanner, LED readout (with automatic power switch), Mod/Power/Cal/SWR meter, automatic noise limiter and blanker, and delta fine tune control. Price: $389.95.—**Superscope, Inc.**, 20525 Nordhoff St., Chatsworth, CA 91311.

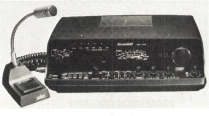

CIRCLE 111 ON FREE INFORMATION CARD

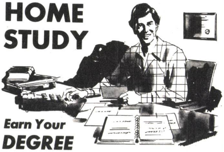

Put Professional Knowledge and a
COLLEGE DEGREE
in your Electronics Career through
HOME STUDY

Earn Your DEGREE
by correspondence, while continuing your present job. No commuting to class. Study at your own pace. Learn from complete and explicit lesson materials, with additional assistance from our home-study instructors. Advance as fast as you wish, but take all the time you need to master each topic. Profit from, and enjoy, the advantages of directed but self-paced home study.

The Grantham electronics degree program begins with basics, leads first to the A.S.E.T. degree, and then to the B.S.E.E. degree. Our *free* bulletin gives complete details of the program itself, the degrees awarded, the requirements for each degree, and how to enroll. Write for *Bulletin R-78*,

Grantham College of Engineering
2000 Stoner Avenue
P. O. Box 25992
Los Angeles, CA 90025

Worldwide Career Training thru Home Study

CIRCLE 4 ON FREE INFORMATION CARD

CB FREQUENCY COUNTER/CLOCK, *model FT-76*, has a 10-Hz resolution with 0.0003% accuracy. It is used to measure the transmitted signal from a CB transceiver. An optional receiver frequency adapter, *model FA-70*, enables the unit to measure received frequencies with same degree of accuracy. Clock can be used either for 12- or 24-hour operation and contains crystal-controlled oscillator accurate to 10 sec/year. Has built-in AC/DC power supplies with quick-disconnect cables for mobile or base-station operation, plus high-impedance input. Prices: *model FT-76*, $199.95; *model FA-70*, $49.95.—**Communications Power, Inc.**, 1280 Reamwood Ave., Sunnyvale, CA 94086.

CIRCLE 112 ON FREE INFORMATION CARD

SOLDERLESS BREADBOARDS, *Unicard I, II*, contain double rows of terminals, each with 5 tie points; *Unicard I* has 960 tie points, *Unicard II* offers 1620 tie points. Tie points (made of nickel-silver) require no patch cord and can be plugged into standard 5¼-in. card racks. Unit accommodates all DIP's, TO-5's or other discrete components having lead diameters to 0.032 in. Also featured are protective rubber feet and extractor handle; predrilled buses, tin-plated copper printed circuits and glass-epoxy bases. Prices start at $31.50 for *Unicard I*.—**A P Products, Inc.**, Box 110, 72 Corwin Dr., Painesville, OH 44077.

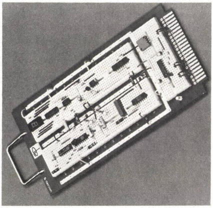

CIRCLE 113 ON FREE INFORMATION CARD

IC TEST CLIP, *model 4140*, 40-pin DIP test clip for attaching test probes permits handfree testing. Has nontarnishable nickel-silver contacts; lower contacts measure 1.022 mm wide and mate with DIP contacts, square, serrated upper-end test points measure 0.63 mm and are designed for mini test clips. Nylon casing can withstand temperatures to 240°C. Price: $19.95.—**ITT Pomona Electronics**, 1500 E. Ninth St., Pomona, CA 91766.

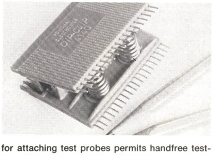

CIRCLE 114 ON FREE INFORMATION CARD

MICROCALCULATOR, *model 85*, interfaces with 8-bit microprocessors and with most 8-bit interface devices, such as Intel's 8255, via a bidirectional 8-bit port. Operation requires less than 256 bytes of memory. Control and interface circuitry permit the microprocessor to enter instructions and display the answer on 14-digit LED readout. The *model 85* contains a four-register stack and nine memory addresses. Problem-solving capabilities include logarithms, sines and tangents; polar/rectangular coordinate conversions; multiple storage registers; four U.S. metric unit constants for metric conversions; plus mean and standard deviations. Unit comes with handbook and 1-year membership in manufacturer's users group. Price: $189.—**Artisan Electronics Corp.,** 5 Eastmans Rd., Parsippany, NJ 07054.

CIRCLE 115 ON FREE INFORMATION CARD

VIDEO CAMERA KIT, *model 202*, features 100-bit by 100-bit self-scanning charge-coupled device and CCD 202C image sensor for both visible and infrared viewing. Camera can be used under many atmospheric conditions, including underwater. All clock voltages operate at 6 volts, with a higher video output signal. Comes with power board and two-level TTL output for interfacing. Also included are semiconductors, PC boards, data sheets, diagrams, resistors, capacitors and an 8-mm lens. Price: $349.—**Solid State Sales,** Box 74D, Somerville, MA 02143.

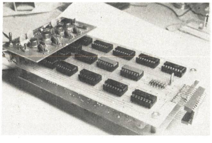

CIRCLE 116 ON FREE INFORMATION CARD

CASSETTE TAPE DECK, *model SC-3100*, comes in simulated walnut-grain finish. *Directo-O-Matic* front-loading system lets you make fast checks of tape status and permits easy accessibility. *Tape-Lead-In* feature allows leader bypass, beginning portion of tape can be omitted. Separate three-position bias and equalization switches handle three different types of tape.

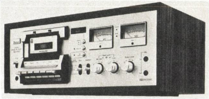

Model SC-3100 specifications: wow and flutter, 0.06%; S/N ratio, 57 dB (before Dolby); frequency

burglar–fire alarm catalog

FREE!

MORE THAN
900 PRODUCTS

detectors,
controls,
sounders,
locks,
tools

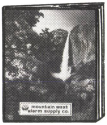

EVERYTHING NEEDED
TO PROTECT HOME,
BUSINESS, INSTITUTION

Huge selection of high quality professional alarm products. 64 fact-filled pages with detailed specs, diagrams, technical notes. Products range from basic switches, controls, bells, sirens to most sophisticated detectors — radar, modulated or passive infrared, microwave, ultrasonics, ion, data links using pulse code multiplex, FSK radio, automatic phone dialers, leased line connections and display panels. Full selection of tools, relays, wire, foil, terminals, books.

WRITE FOR FREE CATALOG TODAY!

(Outside U.S., send $1.00.)

mountain west alarm
box 10780 • phoenix, az 85064
(602) 263-8831

CIRCLE 6 ON FREE INFORMATION CARD

PHILIPS
B+K PRECISION
HICKOK
LEADER
NLS Non-Linear Systems
FLUKE®
DATA PRECISION
Simpson
ECD
TRIPLETT
VIZ formerly RCA
CONTINENTAL SPECIALTIES CORPORATION
CSC

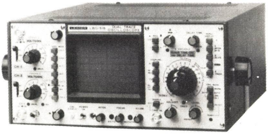

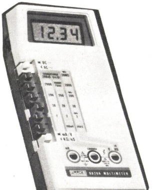

B&K-PRECISION
Model
1474

Dual-Trace 5"
30MHz Triggered
Scope With Signal Delay

SUPER SPECIAL
$699.95

SALE ENDS JULY 31, 1978
PROBES NOT INCLUDED IN PRICE

We give you immediate off the shelf delivery on Oscilloscopes, Power Supplies, Audio & R.F. Generators, Digital Multimeters, Frequency Counters, Logic Probes, Tube & Transistor Testers, Wow & Flutter Meters, Distortion Analyzers, Bridges, and Accessories. For more information call us Toll Free: 800-223-0474.

212-687-2224
THE TEST EQUIPMENT SPECIALISTS
TOLL FREE HOT LINE
800-223-0474
54 West 45 Street, New York, N.Y. 10036
ADVANCE ELECTRONICS

You Can Count On DAVIS!

NEW CTR-2A
500 MHz & 1 GHz COUNTERS
NOW WITH
PERIOD MEASUREMENT (Optional)
AND BUILT-IN PREAMP

- 8 Digit .3" LED Display
- High Stability TCXO Time Base
- Built-in VHF-UHF Prescaler & Preamp
- Period 1us to 1 sec. (optional)
- TCXO Std. ± 2 ppm
- Input Diode Protected
- 12V-DC Operation (optional)
- Oven Crystal ± .5 ppm (optional)
- Selectible Gate Times .1 sec. & 1 sec.

500 MHz kit CTR-2A-500K	$249.95
500 MHz assembled CTR-2A-500A	349.95
1 GHz kit CTR-2A-1000K	399.95
1 GHz assembled CTR-2A-1000A	549.95

OPTIONS:

(02) Oven Crystal	$49.95
(03) .43" LED	10.00
(04) 12 V-DC	10.00
(05) 10 sec. Time Base	10.00
(06) Period Option	15.00

DAVIS

DAVIS ELECTRONICS
636 Sheridan Drive
Tonawanda, NY 14150
716/874-5848

master charge VISA

CIRCLE 56 ON FREE INFORMATION CARD

response (normal tape) 25 Hz–14 kHz (30 Hz–13 kHz ± 3 dB) and (CrO_2 tape) 25 Hz–16 kHz (30 Hz–14 kHz ± 3 dB).

Other features include automatic memory and playback (with timer); Dolby system; mike/line-mixing capability; and large VU meters. Instrument measures $17\frac{15}{16}$ H × $7\frac{13}{16}$ H × $12\frac{3}{4}$-in. D and weighs 18.3 lbs. Price: approximately $430.—**Sansui Electronics Corp.,** 55–11 Queens Blvd., Woodside, NY 11377.

CIRCLE 117 ON FREE INFORMATION CARD

POWER/SWR METER, *model WM-7000,* uses a 30-dB directional coupler to read a 1.8 MHz–30 MHz frequency to a 1.1:1 ratio. Meter reads peak or average power on three scales (20, 200 and 1000 watts). Useful for SSB measurements and for adjusting mike and speech compressor controls. Price: $69.95.—**Communications Power, Inc.,** 1280 Reamwood Ave., Sunnyvale, CA 94086.

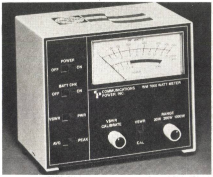

CIRCLE 118 ON FREE INFORMATION CARD

PHONE VOICE SCRAMBLER, *Privacom M13,* insures complete telephone privacy. You notify caller you are scrambling, specify one of 25 codes (from Alpha to Yankee), turn code-phone switch on and turn code dials to desired setting. Remove telephone from *Privacom* unit and place conventional handset into unit and talk. Unit measures 3½ × 4½ × 9 in. and contains 4-volt mercury battery. Price per unit, $325 (two units needed for operation).—**Mountain West Alarm Supply Co.,** Box 10780, Phoenix, AZ 85064.

CIRCLE 119 ON FREE INFORMATION CARD

HIGH BLOOD PRESSURE.
Treat it...and live.
The National High Blood Pressure Education Program,
U.S. Department of Health, Education, and Welfare.

EIGHT
INSTRUMENTS IN ONE

- Out-of-Circuit Transistor Analyzer
- Dynamic In-Circuit Transistor & Radio Tester
- Signal Generator
- Signal Tracer • Voltmeter
- Milliammeter
- Battery Tester
- Diode Checker

Transistor Analyzer Model 212
Factory Wired & Tested—**$30.57**
Easy-to-Assemble Kit—**$20.36**

YOU DON'T NEED A BENCH FULL OF EQUIPMENT TO TEST TRANSISTOR RADIOS! All the facilities you need to check the transistors themselves — and the radios or other circuits in which they are used — have been ingeniously engineered into the compact, 6-inch high case of the Model 212. It's the transistor radio troubleshooter with all the features found only in more expensive units. Find defective transistors and circuit troubles speedily with a single, streamlined instrument instead of an elaborate hook-up.

Features:
Checks all transistor types — high or low power. Checks DC current gain (beta) to 200 in 3 ranges. Checks leakage. Universal test socket accepts different base configurations. Identifies unknown transistors as NPN or PNP.

Dynamic test for all transistors as signal amplifiers (oscillator check), in or out of circuit. Develops test signal for AF, IF, or RF circuits. Signal traces all circuits. Checks condition of diodes. Measures battery or other transistor-circuit power-supply voltages on 12-volt scale. No external power source needed. Measures circuit drain or other DC currents to 80 milliamperes. Supplied with three external leads for in-circuit testing and a pair of test leads for measuring voltage and current. Comes complete with instruction manual and transistor listing.

EMC, 625 Broadway, New York 12, N.Y.

Send me **FREE catalog of the complete value-packed EMC line, and name of local distributor.**

NAME________________ RE-5

ADDRESS________________

CITY________ZONE____STATE____

EMC
ELECTRONIC MEASUREMENTS CORP.
625 Broadway, New York, N.Y. 10012

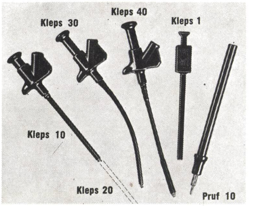

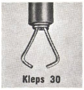

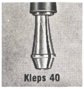

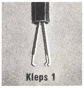

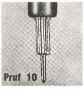

Clever Kleps

Test probes designed by your needs — Push to seize, push to release (all Kleps spring loaded).

Kleps 10. Boathook clamp grips wires, lugs, terminals. Accepts banana plug or bare wire lead. 4¾″ long.	**$1.39**
Kleps 20. Same, but 7″ long.	**$1.49**
Kleps 30. Completely flexible. Forked-tongue gripper. Accepts banana plug or bare lead. 6″ long.	**$1.79**
Kleps 40. Completely flexible. 3-segment automatic collet firmly grips wire ends, PC-board terminals, connector pins. Accepts banana plug or plain wire. 6¼″ long.	**$2.59**
Kleps 1. Economy Kleps for light line work (not lab quality). Meshing claws. 4½″ long.	**$ .99**
Pruf 10. Versatile test prod. Solder connection. Molded phenolic. Doubles as scribing tool. "Bunch" pin fits banana jack. Phone tip. 5½″ long.	**$ .89**

All in red or black - specify. (Add 50¢ postage and handling).
Write for complete catalog of - test probes, plugs, sockets, connectors, earphones, headsets, miniature components.

Available through your local distributor, or write to:

rye INDUSTRIES

RYE INDUSTRIES INC.
126 Spencer Place, Mamaroneck, N.Y. 10543
In Canada: Rye Industries (Canada) Ltd.

CIRCLE 65 ON FREE INFORMATION CARD

new lit

More information on new lit is available from the manufacturers of items identified by a Free Information number. Use the Free Information Card inside the back cover of this issue.

BINARY BIT WEIGHTS AND RESOLUTION. Pocket card provides a quick reference for determining the necessary resolution for a particular A/D or D/A application. Contains % resolution and ppm resolution for 1 to 20 bits. Also included is a quick selection guide covering manufacturer's products for data acquisition systems, A/D and D/A converters, instrument amplifiers, gain-programmable and sample-hold amplifiers, and voltage references.—**Micro Networks,** 324 Clark St., Worcester, MA 01606.

CIRCLE 120 ON FREE INFORMATION CARD

SEMICONDUCTOR REPLACEMENT GUIDE, *SPG-202W,* was prepared to aid service technicians, engineers and all those who work with solid-state devices. The guide contains 240 pages of the RCA SK-series replacement transistors, rectifiers, thyristors, IC's and high-voltage triplers—more than 750 devices, replacing over 141,000 domestic and foreign components. Also included are an Index of SK-series semiconductors, necessary mounting hardware and schematics. The guide sells for $1.50, and is available from RCA distributors and the manufacturer.—**RCA Distributor and Special Products Div.,** Box 85, Runnemede, NJ 08078.

CIRCLE 121 ON FREE INFORMATION CARD

COMPUTER HARDWARE/SOFTWARE CATALOG, 13 pages, contains many hardware and software packages, including a text editing package, a complete FORTRAN IV package, a video display board, disc software in two formats, five XITAN-alpha packages, plus basic ZPU card and system monitor board. Complete specifications on all system components are given. Separate price list.—**Technical Design Labs,** Research Park, Bldg. H, 1101 State Rd., Princeton, NJ 08540.

CIRCLE 122 ON FREE INFORMATION CARD

COMPONENTS CATALOG, 12-page folder listing many different varieties of IC's, diodes, power transformers, LED's. Also featured are prototyping boards and sockets.—**Albia Hobbies,** 24 Albia St., Box 1833, New Haven, CT 06508.

CIRCLE 123 ON FREE INFORMATION CARD

SPEAKER SPECIFICATIONS, *Form 77-1,* describes 11 8-inch speakers, covering a wide price/installation/performance spectrum. Included are single-cone PA models, single and dual-cone background music formats, flame-retardant models, and standard intercom and outdoor units. Speakers feature precision-centered voice coils, heavy-gauge metal baskets and rugged construction. Spec sheet and other informative literature available free on request.—**Quam-Nichols Co.,** 234 E. Marquette Rd., Chicago, IL 60637.

CIRCLE 124 ON FREE INFORMATION CARD

Microprocessor Accessories.

Get the complete Bugworks® catalog and see E&L's complete line of micro-accessories and aids for versatile, professional circuit design. All compatible with both E&L Microprocessor systems and many others: from Hex Keypads for E&L's Mini Micro-Designer® (MMD-1) and MMD-1 Student Stations, to breadboarding cards and aids for the Altair/Imsai and DEC systems. E&L has the products, instruments and educational materials to help you master the world of electronics. See them in your free copy of the complete Bugworks catalog.

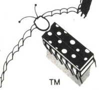

E&L INSTRUMENTS, INC.
61 First Street, Derby, Conn. 06418
(203) 735-8774 Telex No. 96 3536

TM

CIRCLE 41 ON FREE INFORMATION CARD

WE PUT THE WICK WHERE IT BELONGS

IN A UNIQUE, BUILT-IN DESOLDERING TOOL—YOURS FREE, AS A LIMITED-TIME INTRODUCTORY OFFER TO SD5.

Imagine having desoldering wick, right where you can get at it fastest, when you need it most . . . while you're soldering. It's our new patent-pending, refillable SD5 solder/desolder system with 2½ inch heat-resistant, telescoping Teflon* probe.

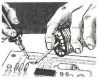

Precision application even in high density circuits

Snapped right into the center of a pound spool of our high quality 16, 18 or 21 gauge MIL-spec solder is D5—our easy-to-use desoldering tool. D5 contains 5 feet of pure copper wick that lets you see the absorption of solder... so you never overheat boards or components by working with a used portion of wick. Its non-activated, pure water-white rosin flux coating quickly removes all solder, without corrosive residue.

Nothing beats the D5 dispenser tool for easy desoldering without burnt fingers. Its 2½ inch probe reaches right into tight areas. And by applying tension to the probe, you can shape or "web" the wick to provide a greater absorption surface. You also use less wick, dispensing the right amount as you need it.

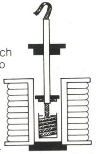

Modular construction—D5 tool is removable; 2½" probe snaps into wick refill

SD5 is the total system for maximum soldering/desoldering efficiency. Alone, the D5 tool is perfect for times when you want to pocket the wick and leave the solder behind. And D5 is also refillable . . . just snap out the Teflon* probe and plug in a D5 refill, available in two gauges—.10 inch and .06 inch.

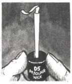

Snap out, pocket D5

The Chemtronics modular solder/desolder system can be purchased separately as half or one-pound spools of solder, D5 desoldering tool and D5 wick refill. Or as a complete SD5 unit with free D5 desoldering tool. Take advantage of this limited-time offer at your Chemtronics distributor now.

*Reg. DuPont Trademark

FREE! $2.45 VALUE!

CHEMTRONICS INC.
WHERE CHEMISTRY MAKES ELECTRONICS WORK BETTER
45 Hoffman Avenue, Hauppauge, N.Y. 11787 (516) 582-3322 /(212) 895-1930

CIRCLE 63 ON FREE INFORMATION CARD

PRO SPEAKERS

continued from page 64

shown in Fig. 4. The foam can be molded into shapes that are difficult to manufacture with wood. In addition, the structural foam is extremely rugged and impervious to temperature and humidity extremes.

The second construction item to check is the external covering. If the speaker system is visible, the cabinet should look good and remain that way.

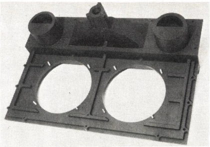

FIG. 4—THERMOPLASTIC is being used as a basic cabinet material instead of wood as shown in the above thermoplastic baffle.

For permanent installations, durability is usually not a problem. In this case, a wood veneer or painted cabinet is sufficient. These materials will be satisfactory as long as they are not given much abuse. Recessed baffle boards or rear panels can protect painted or veneered surfaces, as well as connectors and knobs. But, for portable use, durable surface finishes are required.

For extensive portable use, the surface should be covered with vinyl or an equally rugged material. The vinyl material is the same as or similar to that used on automobile roofs. It is scuff- and tear-resistant, which is what you need for a portable cabinet covering.

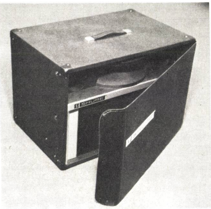

FIG. 5—REMOVABLE FRONT COVER protects speaker during transport.

You might also want a removable shipping cover. Since most damage usually occurs during transport, the cover is use-

NLS LEADS AGAIN!!

NEW MS-215 DUAL TRACE MINISCOPE

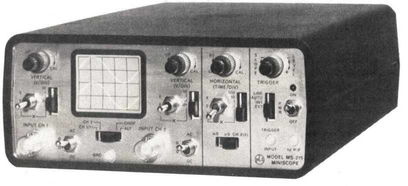

15MHz PORTABLE OSCILLOSCOPE

- 15 megahertz bandwidth.
- External and internal trigger.
- Time Base—0.1 microseconds to 0.5 Sec/div—21 settings.
- Battery or line operation.
- Automatic and line sync modes
- Power consumption less than 15 W.
- Vertical Gain—0.01 to 50 volts/div —12 settings.
- Weight is only 3 pounds.

RECHARGEABLE DUAL TRACE

PORTABLE
2.7"H x 6.4"W x 7.5"D

AVAILABLE NOW

$395
With Rechargeable Batteries & Charger Unit

master charge THE INTERBANK CARD

FREE PROBE

BUY ONE GET ONE FREE
With the purchase of the MS-215 you get two deluxe 10:1 and direct switchable probes. Price 2 for $30.
OFFER EXPIRES AUG. 31, 1978

BANKAMERICARD

212-687-2224 THE TEST EQUIPMENT SPECIALISTS

TOLL FREE HOT LINE
800-223-0474
54 West 45 Street, New York, N.Y. 10036

ADVANCE ELECTRONICS

Want to cut out a career as a two-way radio technician?

MTI offers the only training for professional FM two-way radio available. Qualified technicians are employed in government, industry, and public service. But training is your key.

You could cut out a career as a two-way radio technician by cutting out this coupon. We'll send you information on how you can learn more about this specialized field, at home.

Name ____________
Address ____________
City ____________
State/Zip ____________
SS3

MTI
Mobile Training Institute
Summerdale, Pennsylvania 17093

CIRCLE 32 ON FREE INFORMATION CARD

ful . . . either a full cover or a baffle-board cover (Fig. 5), depending on the system.

A corner protector also shields speaker systems from damage. Usually made from steel, corner protectors fit over all exposed corners. Since corners are extremely vulnerable, the protectors can keep them from getting crushed.

If you want a permanent mounting, you should look for mounting provisions that will add to convenience. Wall-mount swivel brackets, similiar to those shown in Figs. 6 and 7, add greatly to positioning flexibility. The bracket shown in Fig. 6 allows vertical positioning. If a wall or ceiling is not handy for mounting, stands are available that can raise a speaker more than six feet off the floor.

If you are handy, you can install your own hardware. Eyebolts are useful be-

turn page

BETTER THAN A THIRD HAND!

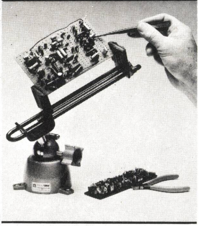

PANAVISE TILTS, TURNS, AND ROTATES TO ANY POSITION. IT HOLDS YOUR WORK EXACTLY WHERE YOU WANT IT.

PanaVise has great strength yet is gentle enough to firmly hold delicate objects.

Quite possibly the finest new tool you will buy this year, PanaVise is built to exacting professional standards. We guarantee it!

Illustrated is the Electronics Vise Model 396. Three other bases and a wide variety of heads are available. All interchange! Buy a basic unit, then add on to create your system.

Available through your dealer. Write for a free catalog.

PANAVISE® Dept. 5E
10107 Adella Ave., South Gate, CA 90280
In Canada: 25 Toro Rd., Downsview, Ont. M3J 2A6

A Division of Colbert Industries
CIRCLE 86 ON FREE INFORMATION CARD

You have your own calculator. Why not a DMM?

Finally, a digital multimeter that's yours, just like your pocket calculator, and more useful. Only $169.*

You pack only 13 ozs. in your pocket or service kit, but size is deceptive. The 8020A has more useful features than any other multimeter available—at *any* price! Features like 26 ranges and seven functions, including *conductance*. 2000-count resolution. Hi/lo power ohms.

And it's rugged. The high-impact case protects a minimum number of component parts (47 in all), and they're all readily available from any of the worldwide Fluke service centers. Your 8020A is factory calibrated by NBS traceable equipment. And we guarantee it'll live up to published specs for a full year.

The 8020A is a true field instrument, designed with a highly readable LCD display, and inexpensive 9V transistor battery power for continuous use up to 200 hours. Reliability, quality and value: *that's* Fluke tradition.

To get your hands on one, **call (800) 426-0361, toll free.** Give us your charge-card number and we'll ship an 8020A the same day. Or, we'll tell you the location of the closest Fluke office or distributor (where you can save by buying a ten-pack of 8020As for only $1521*).

*U.S. price only.

The DMM for Home Electronics Experts.

FLUKE®

2507-7104

CIRCLE 83 ON FREE INFORMATION CARD

"POOR BOY" TUNER SUB

ONLY $19.95

Since all tuner subs that we know of are modified TV Tuners, we decided to market an excellent performing yet very low cost sub for the technician who has to get all he can for his money . . . a "Poor Boy's Sub" for *only* $19.95.

This was not an easy task since cabinets, knobs and controls would push the price far above $19.95 . . . We searched for a tuner that needed no cabinet and no controls . . . one that the tech could scounge the knobs from most any old TV . . .

It took over two years but we finally found it. The gain is excellent . . . Battery drain is very low (only 18 mils). It's self biasing so there is no R.F. gain control to fiddle with . . . It works equally well on tube or transistor sets . . . b/w or color . . . and is as easy to use as starting a fight with your wife (well, almost). All you need do is hook the set's IF cable to the "Poor Boy" and view the picture . . . That's it . . . no set up controls to confuse you.

We compared the "Poor Boy" with other subs costing over twice the price and found it to work just as well on *all* the comparison tests we made . . . and often a lot easier to use . . . Even though instructions aren't needed . . . you get those too.

The "Poor Boy" is small enough to easily hold in one hand . . . no wires or controls dangling around. It comes completely wired and tested *including batteries* and *ready to use.* Send a check for only $19.95, and we even pay the shipping (how about that?) or we will ship COD. ($1.85 C.O.D. Fee)

Try it for 10 days . . . If not completely satisfied . . . return for full refund.
Call us toll free 1-800-433-7124.

ALL ORDERS SHIPPED THE SAME DAY RECEIVED!!

TEXAS TUNER SERVICE
4210 N.E. 28TH STREET, FORT WORTH, TEXAS 76117
TEXAS CUSTOMERS PHONE (817) 834-8201

Please rush me the "Poor Boy" Substitute Tuner.

I understand that I can return it within 10 days for a full refund if I'm not completely satisfied . . . with no questions asked.

☐ I am enclosing full amount of $19.95 and will not be charged shipping.

☐ Ship C.O.D. and I will pay an extra $1.85 shipping and C.O.D.

RE—5/78

Name: ______

Street Address: ______

City: ______ State: ______ Zip: ______

CIRCLE 69 ON FREE INFORMATION CARD

For faster service

USE ZIP CODE

on all mail

PRO SPEAKERS

continued from page 101

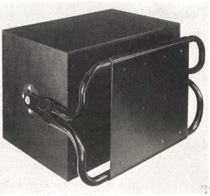

FIG. 6—MOUNTING BRACKET fastens to the sides of the speaker cabinet and permits vertical positioning.

cause they are easy to install and allow flexible positioning, especially if you hang the speaker from a ceiling. When installing eyebolts, make sure the cabinet is sturdy; if it isn't, you must add bracing. Mount the eyebolts to the cabinet sides, not the top of the cabinet. Otherwise, the stress may cause the top to pull loose.

Finally, if you plan to do your own repairs, you should check out driver accessibility. Is the access through the front or rear of the cabinet? It can make a difference with permanently mounted

GET ALL THE FACTS ON THE NEW GTS-10 GENERAL TELEVISION SERVICER - the concept that is changing the course of TV servicing!

SEND FOR A FREE GTS-10 TWO-VOLUME OWNER'S MANUAL!

In addition to a free two-volume set of the GTS-10 owner's manuals you will receive a comprehensive 6-page full color brochure - describing its profit making potential and its many unique patterns as well as information on our 30-day Shop Trial offer of the GTS-10 General Television Servicer.

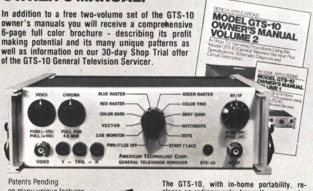

BENCH APPLICATIONS
MODEL GTS-10 OWNER'S MANUAL VOLUME 2
In-Shop TV Servicing Procedures Using the Model GTS-10 General Television Servicer Plus Specifications, Schematic Diagrams and Circuit Description.
IN-HOME APPLICATIONS
MODEL GTS-10 OWNER'S MANUAL VOLUME 1
VIDEO
CHROMA
BLUE RASTER
RED RASTER
COLOR BARS
VECTOR
3.58 MONITOR
PWR/I'LCE OFF
GREEN RASTER
COLOR TRIO
GRAY QUAD
HATCHDOTS
DOTS
START I'LACE
RF/IF
PUSH (–VID) PULL (+VID)
PULL FOR 4.5 MHZ
PUSH (RF) PULL (IF)
VIDEO
V – TRIG – H
AMERICAN TECHNOLOGY CORP.
GENERAL TELEVISION SERVICER
GTS-10
RF/IF

Patents Pending on many unique features.

The GTS-10, with in-home portability, replaces an ordinary color bar pattern generator and includes the most used functions of a substitute tuner and an analyst. It also provides capabilities that none of these other instruments can match.

Advanced yet sensibly priced at $349.00 the GTS-10 is the ultimate instrument for increasing servicing profits.

FOR IMMEDIATE REPLY TO THIS OFFER SEND COUPON OR WRITE DIRECT TO

For VISA and MASTER CHARGE orders call (303) 275-8991.

ATC
AMERICAN TECHNOLOGY CORP.
225 Main Street,
Canon City, Colorado 81212 RE05

Send $1.00 if First Class delivery is desired.

Name ______ Phone ______

Company ______

Address ______

City ______ State ______ Zip ______

CIRCLE 81 ON FREE INFORMATION CARD

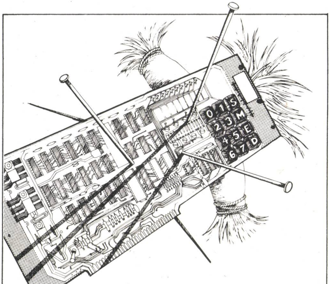

DON'T HEX YOUR 8080

Octal (base 8) is the natural number base of the 8080 instruction set . . . so It's a natural for programming your 8080-based computer.

The 8080 Octal Reference Card from Thinker Toys™ is a handy pocket reference with everything you need to work in octal: 8080 instruction set, programming instructions, octal-ASCII table, even the S-100 and 8080 pin layouts.

For $1.50, why not have one handy? Send check or money order to Thinker Toys™. Or ask your local computer shop to order it for you.

Thinker Toys™

1201 10th St. Berkeley, CA 94710 415-527-7548 (10-4 PST)

CIRCLE 85 ON FREE INFORMATION CARD

speakers. Do all the drivers remove easily? Is the crossover network buried under layers of glass fiber material? The right answer to these questions can save much time and frustration.

Selecting a compact sound reinforcement speaker system has never been easy because of the many variables involved. It is important to select as many features as you can for the money you want to spend. You have to consider the tradeoffs of efficiency and frequency response. You must compare specifications to make sure the speaker you buy has the desired polar response, enough power handling and enough sensitivity. You should select a well-constructed cabinet with suitable surface and corner protection for your needs. You have to select covers, handles and mounting gear to facilitate transporting the speakers or installing them permanently. And, finally, you must check on parts accessibility if repairs should ever become necessary. **R-E**

References

1. Beranek, L. L., *Acoustics*, McGraw-Hill, New York, NY, 1954, p. 112.
2. Olson, H. F., *Acoustical Engineering*, Van Nostrand, Princeton, NJ, 1957, pp. 19–20.
3. Schulein, R. B., "Power Ratings for Sound Reinforcement Loudspeaker Systems," *Audio Engineering Society*, Preprint No. 1066, 1975.

Includes Functional Tilt Stand!

NEW EICO 270 3½ DIGIT DMM KIT ONLY $79.95

Introductory Offer–FREE AC ADAPTOR

The first and only lab accuracy portable DMM Kit featuring MOS/LSI IC economy and reliability. Measures DC/AC Volts, Kilohms, DC/AC milliamps in 21 ranges. Polarity indicators and overload protection are provided, and 0.5 inch LED displays give easiest-to-read digital readout to 1999. The 270 features a basic 0.5% DC accuracy, 10 Megohm input impedance, low voltage drop in all current ranges and automatically-flashing overrange indicator. **Assembled $109.95**

FREE '78 EICO CATALOG

Check reader service card or send 50¢ for first class mail. See your local EICO Dealer or call (516) 681-9300, 9:00 a.m.-5:00 p.m. EST. Major credit cards accepted.

EICO–108 New South Rd.
Hicksville, N.Y. 11801

EICO®

CIRCLE 20 ON FREE INFORMATION CARD

HOBBYISTS! ENGINEERS! TECHNICIANS! STUDENTS!

Write and run machine language programs at home, display video graphics on your TV set and design microprocessor circuits — the very first night — even if you've never used a computer before!

RCA COSMAC microprocessor/mini-computer

SPECIFICATIONS

ELF II features an RCA COSMAC COS/MOS 8-bit microprocessor addressable to 64k bytes with DMA, interrupt, 16 registers, ALU, 256 byte RAM, full hex keyboard, two digit hex output display, 5 slot plug-in expansion bus, stable crystal clock for timing purposes and a double-sided plated-through PC board plus RCA 1861 video IC to display any segment of memory on a video monitor or TV screen.

Use ELF II to ... **PLAY GAMES** using your TV for a video display ... **CREATE GRAPHICS** pictures, alphanumerics, animated effects ... learn how to **DESIGN CIRCUITS** using a microprocessor ... the possibilities are infinite!

NOW AVAILABLE

ELF II explodes into a giant when you plug the GIANT BOARD™ into ELF's expansion bus. This powerful board includes cassette I/O, RS 232-C/TTY, 8-bit P I/O and system monitor/editor...meaning your ELF II is now the heart of a full-size system with unlimited computing power! $39.95 kit. $2 p&h.
- 4k Static RAM addressable to any 4k page to 64k. $89.95 kit. $3 p&h.
- Prototype (Kluge) Board accepts up to 32 I.C.'s of various sizes. $17.00 kit. $1 p&h.
- Expansion Power Supply. $34.95 kit. $2 p&h.
- Gold plated 86-pin connector. $5.70 postpaid.

Coming Soon!

Tiny Basic

ASCII KEYBOARD * CONTROLLER BOARD * D-A, A-D CONVERTER * CABINET

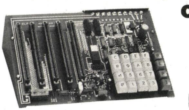

A THOUGHTFUL GIFT FOR ANYONE WHO MUST STAY UP TO DATE IN COMPUTERS AND ELECTRONICS!

ELF II $99.95

SEND TODAY

NETRONICS R&D LTD., Dept. **RE 5**
333 Litchfield Road, New Milford, CT 06776 Phone (203) 354-9375

Yes! *I want to run programs at home and have enclosed:* ☐ **$99.95** plus $3 p&h for **RCA COSMAC ELF II kit. Featured in POPULAR ELECTRONICS.** Includes all components plus everything you need to write and run machine language programs plus the new Pixie chip that lets you display video graphics on your TV screen. Designed to give engineers practice in computer programming and microprocessor circuit design, ELF II is also perfect for college and college-bound students (who must understand computers for any engineering, scientific or business career). Easy instructions get you started right away, even if you've never used a computer before!

As your need for computing power grows, five card expansion bus (less connectors) allows memory expansion, program debugger/monitor, cassette I/O, A to D and D to A converters, PROM, ASCII keyboard inputs, controllers, etc. (soon to be available as kits). Manual includes instructions for assembly, testing, programming, video graphics and games *plus* how you can get ELF II User's Club bulletins. Kit can be assembled in a single evening and you'll still have time to run programs, including games, video graphics, controllers, etc., before going to bed! ☐ **$4.95** for 1.5 amp 6.3 VAC power supply, required for ELF II kit. ☐ **$5.00** for RCA 1802 User's Manual.

☐ **I want mine wired and tested with the power transformer and RCA 1802 User's Manual for $149.95 plus $3 p&h.**
Conn. res. add sales tax.

NAME________________

ADDRESS________________

CITY________________

STATE________ZIP________

☐ Send info on other kits!

Dealer Inquiries Invited

CIRCLE 60 ON FREE INFORMATION CARD

THE UNITED STATES OF AMERICA
THIS NOTE IS NOT LEGAL ALL DEBTS, PUBLIC AND PRIVATE
C 284842
WASHINGTON
428977A
C
SCHOBER ELECTRONIC ORGAN

You can build a better organ than you can buy!

A magnificent Schober Electronic Organ

What a marvelous way to put *your* special talents to work! With our Schober Electronic Organ Kits and your skill, you can build yourself some very special satisfaction, and a lifetime of great music!

Schober Organs are literally far superior to comparably-priced "ready-made" units. You could actually pay twice as much and get no better organ...and miss the fun of assembling it yourself. A PC board at a time, component by component, you'll assemble your own "king of instruments." And when you're done, you'll wish there was more to do. And there is! For then, Schober will help you learn to play, even if you've never played a note before!

Schober Organ Kits range from $650 to $2850, and you can purchase in sections to spread costs out...or have two-year time payments. Combine the incomparable quality of Schober components with your talent...and produce a far better organ than you can buy! Thousands of others have, ever since 1955.

You can have all the details, without cost or obligation. Just send the coupon for the fascinating Schober color catalog (or enclose $1 for a record that lets you hear as well as see Schober quality.) Why not clip it right now, before you forget?

The *Schober* Organ Corp., Dept. RE-174
43 West 61st Street, New York, N.Y. 10023

☐ Please send me Schober Organ Catalog.

☐ Enclosed please find $1.00 for 12-inch L P. record of Schober Organ music.

NAME

ADDRESS

CITY STATE ZIP

CIRCLE 47 ON FREE INFORMATION CARD

HI-FI LAB TEST REPORT

continued from page 68

continuous sinewave, onto which is superimposed a brief high-frequency tone burst that is present for approximately 1 ms and repeated at about 10-ms intervals. This waveform is shown as the upper trace in Figs. 3 and 4. In Fig. 3, the suppressor switch is turned off, and the lower trace shows an extremely sharp spike appearing in the output every time the tone burst is present at the input.

Without changing the composition of the input signal, the *model MRM-101*'s suppressor switch was turned on in Fig. 4 to show that the sharp spike noted in Fig. 3 has been "tamed" or reduced substantially (see lower trace of Fig. 4). We must emphasize that the reason the spike was not completely suppressed is probably because we were not totally successful in reproducing a waveform corresponding exactly to the kind of impulse noise that is transmitted to the input when an actual record scratch is encountered.

An overall product evaluation of the Garrard *model MRM-101* is found in Table II, together with our summary comments. We believe that besides making scratched records useful once more, placing a preamplifier-equalizer right next to a record player in the *model MRM-101* is very sensible. Conceivably, Garrard might well go one step further and actually include this circuitry as an integral part of some of their better turntable systems. Admittedly, this arrangement would cause a redundancy in most hi-fi systems (since you would have an unused preamplifier-equalizer in the receiver or integrated amplifier), but this seems like a small price to pay for being able to listen to those precious old records you thought were ready for the scrap heap. **R-E**

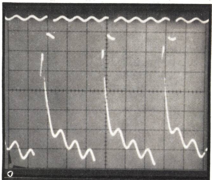

3

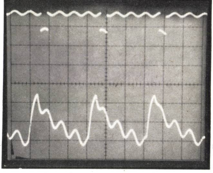

4

NLS LEADS AGAIN!!

NEW MS-15 MINISCOPE

15MHz PORTABLE OSCILLOSCOPE

- 15 megahertz bandwidth.
- External and internal trigger.
- Time Base—0.1 microseconds to 0.5 Sec/div—21 settings.
- Battery or line operation.
- Automatic and line sync modes
- Power consumption less than 15 W.
- Vertical Gain—0.01 to 50 volts/div —12 settings.
- Weight is only 3 pounds.

RECHARGEABLE

PORTABLE
2.7"H x 6.4"W x 7.5"D

AVAILABLE NOW

$289

With Rechargeable Batteries & Charger Unit

master charge THE INTERBANK CARD

FREE PROBE

With the purchase of MS-15 you get a deluxe 10:1 and direct combination probe.
NEWCOM SHOW SPECIAL
Offer Expires August 31, 1978

BANKAMERICARD

212-687-2224

THE TEST EQUIPMENT SPECIALISTS

TOLL FREE HOT LINE
800-223-0474
54 West 45 Street, New York, N.Y. 10036

ADVANCE ELECTRONICS

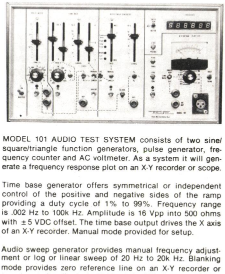

MODEL 101 AUDIO TEST SYSTEM consists of two sine/square/triangle function generators, pulse generator, frequency counter and AC voltmeter. As a system it will generate a frequency response plot on an X-Y recorder or scope.

Time base generator offers symmetrical or independent control of the positive and negative sides of the ramp providing a duty cycle of 1% to 99%. Frequency range is .002 Hz to 100k Hz. Amplitude is 16 Vpp into 500 ohms with ± 5 VDC offset. The time base output drives the X axis of an X-Y recorder. Manual mode provided for setup.

Audio sweep generator provides manual frequency adjustment or log or linear sweep of 20 Hz to 20k Hz. Blanking mode provides zero reference line on an X-Y recorder or tone burst. Amplitude is 16 Vpp into 500 ohms or 10 Vpp into 8 ohms.

Pulse generator frequency range is .002 Hz to 800k Hz. Pulse width is adjusted independent of frequency from 4 seconds to 40 nanoseconds. Outputs are complementary TTL.

AC voltmeter has full scale sensitivities from 1 mV to 250 V. Fast or slow, peak or true RMS and log or linear modes are provided. Output drives Y axis of X-Y recorder.

Frequency counter is 6 digit, 50 or 60 Hz line triggered, and reads either internal or external. Sensitivity is 10% of voltmeter full scale at 20k Hz. 1 or ½ second update.

Dimensions: 8 x 14 x 3. Shipping weight: 9 lbs. $695. Stock to 30 days. Warranty: 1 year, 3 year $70. Master Charge and Visa. Specs and operating information on request.

FIDELITY SOUND

1894 Commercenter W. #105
San Bernardino, Ca 92408
(714) 889-7623

HOBBY CORNER

continued from page 57

vaporized by heat from a hot iron.

After wiring the entire board (although you don't really *have* to wait that long!), simply touch each joint with your soldering iron. Since the insulation vaporizes immediately, apply solder for a good electrical and physical connection. If the insulation does not vaporize, your iron is not hot enough; its minimum temperature should be about 400° F.

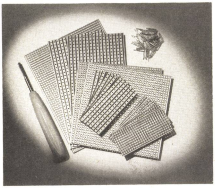

A SELECTION OF VEROBOARDS with various hole sizes, a spot face cutter used to break foil strips and discrete terminals.

This wiring process is so direct and quick that even a large board can be completed in a short time. Because of its

turn page

For faster service

USE ZIP CODE

on all mail

ALL TOGETHER NOW!

The acclaimed Equinox 100™ mainframe kit ($799) is now a complete S-100 system.

Because now there is an Equinox 100™ I/O interface kit ($120) that handles the hard work of interfacing all your peripherals.

And Equinox 100™ 4K memory kits ($109). Assembled 8K memory boards ($188). EQU/ATE™ editor/assembler and BASIC-EQ™ software on cassettes.

It all goes together. It all works together. It's all together now at special system prices.

See The Equinox System™ at your local computer shop. *Call* toll-free to 800-648-5311. BAC/MC accepted. Or *write* Equinox Division, Parasitic Engineering, P.O. Box 6314, Albany California 94706.

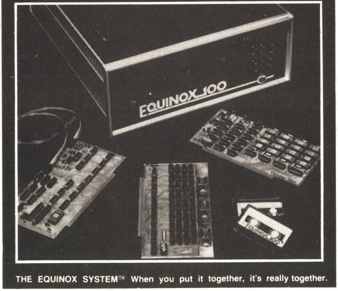

THE EQUINOX SYSTEM™ When you put it together, it's really together.

CIRCLE 75 ON FREE INFORMATION CARD

INTERNATIONAL FM-2400CH

FREQUENCY METER FOR TESTING MOBILE TRANSMITTERS AND RECEIVERS

• Portable • Solid State • Rechargeable Batteries

The **FM-2400CH** provides an accurate frequency standard for testing and adjustment of mobile transmitters and receivers at predetermined frequencies.

The FM-2400CH with its extended range covers 25 to 1000 MHz.

The frequencies can be those of the radio frequency channels of operation and/or the intermediate frequencies of the receiver between 5 MHz and 40 MHz.

Frequency stability: ±.0005% from +50° to +104°F.

Frequency stability with built-in thermometer and temperature corrected charts: ±.00025% from +25° to +125° (.000125% special 450 MHz crystals available).

- Tests Predetermined Frequencies 25 to 1000 MHz
- Extended Range Covers 950 MHz Band
- Pin Diode Attenuator for Full Range Coverage as Signal Generator
- Measures FM Deviation

FM-2400CH (meter only) Cat. No. 035320	**$595.00**
RF crystals (with temperature correction)	**24.90** ea.
RF crystals (less temperature correction)	**18.90** ea.
IF crystals	**catalog price**

Write for catalog

ICM

INTERNATIONAL CRYSTAL MFG. CO., INC.
10 North Lee / Oklahoma City, Okla. 73102

CIRCLE 62 ON FREE INFORMATION CARD

HOBBY CORNER

continued from page 105

simplicity, it is recommended for all except specialized and production boards. The pen-wiring process is hard to beat for prototyping and one-of-a-kind production of electronic projects.

Vero Electronics, Inc. manufactures the *Verowire* prototyping kit *(model 79-1738K)*. The kit contains a wiring pen, several spools of wire with the special self-fluxing polyurethane insulation, terminals, a 10X magnifying loupe, a terminal tool, a universal PC board (No. 06-0128J, 4.5 by 6.5 inches) with 44-pin edge connector and a wire cutter, all for about $29.

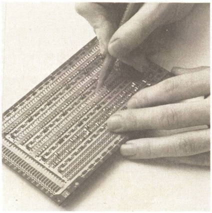

A VEROWIRE PEN being used to route heat strippable wire on a DIP board.

Vero also produces a spot face cutter ($2.20 Part No. 22-0239G) that neatly and painlessly cuts breaks in copper traces on PC boards. No longer will you have to wrestle with a knife and its potential problems when you want to alter the printed circuit on a board.

Table 3 (on page 57) should help you select the best wiring process for a given prototype. These processes also apply to projects from articles in **Radio-Electronics** since the principles of selection are the same.

Putting it all together

Sometimes we get so involved in a project that we don't stop to look at the whole circuit development/construction process to see if there is a better way to do it. It is not enough simply to select the right wiring procedure; you must make other choices.

For instance, how do you decide whether or not to use a breadboard? Perhaps you *always* use one—or you never do. And what about all the different ways to construct a circuit? Do you use the same construction method every time without questioning if it is the best one *this* time?

Properly performed breadboarding, prototyping, and construction and the various available techniques can all add to your success and satisfaction. **R-E**

The C-Meter

PRECISION, AUTORANGING CAPACITANCE METER by DORIC

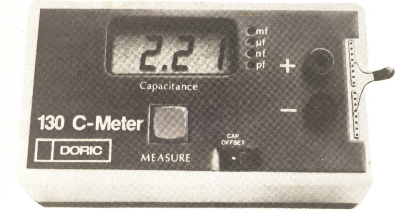

Autoranging
10 ranges are automatically selected from full scale values of 200 picofarads to 200,000 microfarads, with a maximum resolution of 0.1 picofarads.

Easy To Read
A large 3½ digit liquid crystal display, with variable decimal points, makes the C-meter very easy to read. A set of high brightness LED's indicate the capacitance ranges.

Accurate
The C-meter achieves 0.1%(±1 count) up to 200 microfarads and 1% from 200 microfarads to 200,000 microfarads. It is accurate on all ranges at temperatures from 15° to 35°C. (59° to 95°F).

Portable
It weighs in at only 15 oz. and measures 2x3x6 inches. Smaller than a brick, with no cord, the C-meter cuts clutter on the test bench and is handy in the field. Four standard AA batteries supply power to measure over 20,000 capacitors, a year or more of normal lab use, and no recharging.

Versatile
Besides its built-in connector strips, the C-meter inincludes two sets of test clips to accommodate all types of capacitors. An offset control removes up to 15 pf. stray capacitance.

DORIC
MODEL 130
C-Meter
$325.

212-687-2224 **THE TEST EQUIPMENT SPECIALISTS**

TOLL FREE HOT LINE
800-223-0474
54 West 45 Street, New York, N.Y.10036

ADVANCE ELECTRONICS

Try this exciting new hobby! Build your own electronic concert organ. It's easy. No technical knowledge required. Just follow the clearly pictured instructions of the famous Wersi do-it-yourself system. Choose from seven different models. Send $2.00 (refundable) with coupon for colorful 104 page catalog.

WERSI

Wersi Electronics, Inc.
Dept. 24, Box 5318
1720 Hempstead Road
Lancaster, PA 17601

Enclosed is $2.00 for my copy of your 104 page catalog.

Name ______
Address ______
City ______ State ______ Zip ______

CIRCLE 52 ON FREE INFORMATION CARD

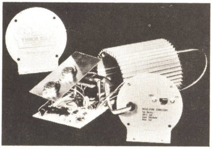

FROM KIT TO CAR IN 80 MINUTES!

Electronic ignition is "in." Update your car with the TOPS in power, efficiency and reliability — the TIGER SST capacitive discharge ignition (CD).

The TIGER delivers everything other CD's promise — and more: quicker starting, more power, more gas mileage, tune-ups eliminated, lifetime plugs and points, reduced repairs and pollution.

The TIGER can be built and installed in your car in 80 minutes. The TIGER is unique!

The TIGER comes with a switch for TIGER or standard ignition for 12V negative ground only.

Simpli-Kit $21.95
POST PAID U.S.A.

WE ACCEPT:
Mastercharge or BankAmericard.
Send check or money order with order to:

Tri-Star Corporation
DEPT. FF, P.O. Box 1727
Grand Junction, Colorado 81501

CIRCLE 44 ON FREE INFORMATION CARD

market center

CLASSIFIED COMMERCIAL RATE (for firms or individuals offering commercial products or services). **$1.50 per word (no charge for zip code) . . .** minimum 15 words.

NONCOMMERCIAL RATE (for individuals who want to buy or sell personal items) **85¢ per word . . .** no minimum.

ONLY FIRST WORD AND NAME set in bold caps. Additional bold face (not available as all caps) at 10¢ per word. Payment must accompany all ads except those placed by accredited advertising agencies. 5% discount for 6 issues, 10% for 12 issues within one year, if paid in advance. All copy subject to publisher's approval. Advertisements using P.O. Box address will not be accepted until advertiser supplies publisher with permanent address and phone number. Copy to be in our hands on the 26th of the third month preceding the date of the issue (i.e., August issue closes May 26). When normal closing date falls on Saturday, Sunday or a holiday, issue closes on preceding working day.

PLANS & KITS

CONSTRUCTION plans; over 100. From TV to telephone, from broadcasting to computers. Catalog air mailed $1.00; includes year's subscription to Electronic Newsletter. **DON BRITTON ENTERPRISES,** PO Box G, Waikiki, HI 96815

MINI-laser plans $1.00. Science projects catalog 25¢. **MOTEN,** 323 S. Franklin, #804, Chicago, Il 60606

LINEAR Amplifier: Ham only 2—30 MHz, 100 watt, solid-state. **Frequency Counter:** 300 MHz, miniportable/mobile, memory! **VOX—Compressor:** Splatter-free modulation booster. Construction plans $3.00 each. All $7.50! Kits, others, catalog available. **PANAXIS PRODUCTIONS,** Box 5516-F5, Walnut Creek, CA 94596

HOBBYIST give your project the professional look. Printed circuit boards from your sketch or artwork. Affordable prices. Rush free details. **DANOCINTHS,** Box 261, Westland, MI 48185

VIDEO cassette tape recorders RCA Selectavision. Free information. **HODAPP TV SALES,** 322 Main St., St. Clair, MN 56080

67 kHz solid-state kits for reception of music-only, medical, special-interest programs not otherwise heard on FM. No crosstalk, excellent muting, with AC power supply. Quality product. $47.50. Wired $60.00. **MUSIC ASSOCIATED,** 65 Glenwood Road, Montclair, NJ 07043. 201-744-3387.

SCR variable speed drive—industrial quality. Plans: 110V to ¾ H.P. $3.00, 220V to 3 H.P. $5.00. **VALAMCO,** Box 841, Ellenburg Depot, NY 12935

CANADA'S largest semiconductor distributor . . . IC's, electronics parts 1st quality, free catalog. **SPECTRONIQUE,** c.p. 1812, Quebec (terminus) Canada GIK 7K7 U.S. Welcome.

MULTIPROJECTOR tape-slide synchronizer, lap-dissolve plans, $5.50. Free catalog. **MILLER,** 1896 Maywood, S. Euclid, OH 44121

MANUALS for Govt. surplus radios, test sets, scopes. List 50¢ (coin). **BOOKS,** 7218 Roanne Drive, Washington, D.C. 20021

UNLOCK your future. Become professional locksmith by spare time homestudy. $13 in an hour possible. All tools, equipment included. Facts free. Send name. **LOCKSMITHING INSTITUTE** (homestudy), Dept. 1339-058, Little Falls, NJ 07424

EDUCATION & INSTRUCTION

UNIVERSITY degrees by mail! Bachelors, Masters, Ph.D's . . . Free revealing details. **COUNSELING,** Box 317-RE5 Tustin, CA 92680

GRANTHAM's FCC License Study Guide—377 pages, 1465 questions with answers/discussions—covering third, second, first radiotelephone examinations. $13.45 postpaid. **GSE PUBLICATIONS,** 2000 Stoner, Los Angeles, CA 90025

F.C.C. EXAM MANUAL

PASS FCC EXAMS! Memorize, study—Tests-Answers for FCC 1st and 2nd class Radiotelephone licenses. Newly revised multiple choice questions and diagrams cover all areas tested in FCC exams, plus Self-Study Ability Test. $9.95 postpaid. Money-back guarantee.

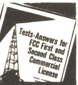
Tests-Answers for FCC First and Second Class Commercial License

COMMAND PRODUCTIONS
RADIO ENGINEERING.DIV.
P.O. BOX 26348 E
SAN FRANCISCO, CAL. 94126

TELEPHONE bugged? Don't be Watergated! Countermeasures brochure $1.00. **NEGEYE LABORATORIES,** Box 547-RE, Pennsboro, WV 26415

BUSINESS OPPORTUNITIES

CABLE FM STATION. No experience required, excellent spare-time income, others operate for you. Details free. **BROADCASTING,** Box 5516—F5, Walnut Creek, CA 94596

HIGHLY PROFITABLE ONE-MAN ELECTRONIC FACTORY

Investment unnecessary, knowledge not required, sales handled by professionals. Ideal home business. Write today for facts! **Postcard will do. Barta-RE-E, Box 248, Walnut Creek, CA 94597.**

MECHANICALLY inclined individuals desiring ownership of Small Electronics Manufacturing Business—without investment. Write: **BUSINESSES,** 92-R, Brighton 11th, Brooklyn, NY 11235

FOR SALE

FREE catalog. IC's, Semi's. **CORONET ELECTRONICS,** 649A Notre Dame W., Montreal, Que., Canada, H3C-1H8. US Inquiries.

SEEKING Japanese transistors for CB and stereo repair? Request complete list. Compare 1 to 9 prices: 2SC710 .45, 2SC517 3.95, 2SC799 3.60, 2SC1306 3.90, 2SC1678 2.25, TA7205P 3.50, BA521 3.70, BA511 3.40. See our full page ad in the Market Center of this magazine. **FUJI-SVEA ENTERPRISE,** Dept. RE, P.O. Box 40325, Cincinnati, OH 45240

FREE 88 Page CATALOG

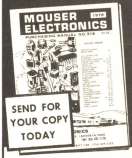

SEND FOR YOUR COPY TODAY

ELECTRONIC COMPONENTS, TEST EQUIPT, TOOLS, HARDWARE, PC AIDS Etc.

BUY DIRECT WITH CONFIDENCE

AUDIO: Speakers, earphones, microphones, headphones.
CAPACITORS: Ceramic, electrolytic, mylar, non-polar, tantalum, high-voltage, mica, trimmer, variable.
CONNECTORS: Plugs, jacks, binding posts, hardware, alligator clips, battery snaps, terminals, lugs.
LAMPS: Incandescent, argon, neon, flash, lamp holders.
MISCELLANEOUS: Batteries, holders, chassis, fuses, line cords, knobs, antennas, chemicals, kits.
PRINTED CIRCUIT AIDS: Design templates, tapes and symbols, breadboarding kits, PC fabrication kits.
RESISTORS: Composition film, power, slide, pots.
SEMICONDUCTORS: Transistor, diode, thyrister, IC.
SOCKETS: AC, IC, transistor, tube, lamp, fuseholder.
SOLDERING EQUIPMENT: Irons, holders, guns, solder tips, flux, cordless irons, tip cleaning devices.
SWITCHES: Slide, rotary, toggle, knife, push-button.
TESTERS: Precision, multimeters, cordless VTVMs.
TOOLS: Screwdrivers, nutdrivers, wrenches, pliers, snips, drill bits, punches, micrometers, cutters.
TRANSFORMERS: Filament, IF, power, audio, isolation, trigger, variable, AC adapters, line matching.

MOUSER ELECTRONICS
11511R WOODSIDE AVE., LAKESIDE, CA. 92040
Phone (714) 449-2222 TWX 910-331-1175

CIRCLE 53 ON FREE INFORMATION CARD

NEW TV CAMERA with ZOOM LENS

9 TO 30 mm f 1:9 Lens

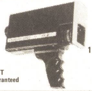

- USE WITH ANY V.T.R. ATV, SSTV, HOME SECURITY
- USE INDOORS OR OUTDOORS
- ALL SOLID STATE

15 FOOT CABLE AND PISTOL GRIP

NOT A KIT
Fully Guaranteed

$195.00 Complete

DIGITAL AUTO INSTRUMENTS

SEVEN MODELS!

#1 TACHOMETER
#2 WATER TEMP.
#3 FUEL LEVEL
#4 SPEEDOMETER*
#5 OIL PRESSURE
#6 OIL TEMP.
#7 BATTERY MONITOR

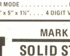

KIT INCLUDES:

- CASE & ALL HARDWARE
- PRESSURE & TEMP. SENDERS
- ASSEMBLED MAIN PC BOARD

FEATURES:

- 4" ORANGE LED'S
- 4½" x 4" x 2" ABS CASE

*ADD $10 FOR REQUIRED SPEED SENDER . $15 FOR SPEED SENDER ALONE

KIT: $49.95. . . . . . .ASSEMBLED: $59.95

SPECIFY 12 OR 24 HOURS

3½ DIGITAL CLOCK

- 4 DIGIT KIT . **$49.95**
- 4 DIGIT ASSEMBLED. **$59.95**
- 6 DIGIT KIT . **$69.95**
- 6 DIGIT ASSEMBLED. **$79.95**

117 VAC - 12 OR 24 HR MODE . . . . KIT COMES COMPLETE!
6 DIGIT VERSION: 27" x 5" x 1½". . . . 4 DIGIT VERSION: 18" x 5" x 1½"

MARK FOSKETS'
SOLID STATE TIME
P.O. BOX 2159
DUBLIN, CALIF. 94566
ORDERS (415) 828-1923

master charge THE INTERBANK CARD

PLEASE ADD $1.50 FOR POSTAGE & HANDLING

BANKAMERICARD

CALIFORNIA RESIDENTS - ADD 6% SALES TAX

CIRCLE 34 ON FREE INFORMATION CARD

SERIES SN7400 BENT PIN SPECIAL

We have a large lot of SERIES SN7400 ICs, plus a few linears,which were removed from wire wrap boards. Included are just about every SN7400 in the book, plus op amps, phase locked loops etc., and others found in a sophisticated computer system. Only defect is pins bent when removed from board. We are selling these in lots of 125 which will include a good cross section of the mixture.Money back guarantee is not 100% satisfied. No choices at this price, but you will get a good working supply of these usefull devices.

STK.NO.4591R 125 piece set, SN7400 & linears $10.00 3/25.00

AMPEX RECORDING TAPE

We have acquired an inventory of AMPEX 1.0 mil recording tape. These tapes have been used one time by government weather stations, and then we get them. On standard 7" AMPEX reel.

STOCK NO.5588R AMPEX recording tape $1.75 4/6.00

2 HEAVY DUTY TRANSFORMERS

TRANSFORMER 1.115 V Pri. Sec.130V@2A Sec.2 16.5 V@1.2A. Sec.3, 16V@3.5A. Sec.4 9.5V@3.5 A.

STOCK NO. 6677R 10 lbs. $10.95 ea. 2/20.00

TRANSFORMER 2. Pri. 115 V. Sec.1, 12V@5A, Sec.224V@9A, Sec.3 14V@20A. Sec.4125V@ 1.5 A.

STOCK NO.6675R 16 lbs. $18.95 2/36.00

VIDEOCUBE –TV/COMPUTER INTERFACE

VIDEOCUBE is a self contained RF oscillator-modulator, allowing easy interface with any video output device to a standard TV set. We provide a reprint of article from RADIO-ELECTRONICS. Approved by FCC.

STOCK NO.5500R Complete kit of parts. $13.95 2/26.00

STOCK NO.5500PR Partial kit. (Special parts) $9.95 2/18.00

DELTA ELECTRONICS

your BANKAMERICARD welcome · master charge THE INTERBANK CARD

7 OAKLAND ST., P.O. Box 2
AMESBURY, MASS. 01913 617-388-4705

ATLANTA, GA.
DELTA ELECTRONIC HOBBIES
5151 Buford Hwy. Doraville, Ga.

BOSTON, MASS.
DELTA ELECTRONICS WAREHOUSE OUTLET
590 Commonwealth Ave. Boston, Mass.

CIRCLE 43 ON FREE INFORMATION CARD

For
faster
service

USE
ZIP
CODE

on
all
mail

RECONDITIONED test equipment. $0.50 for catalog. **WALTER'S TEST EQUIPMENT,** 2697 Nickel, San Pablo, CA 94806

RADIO & TV tubes 36¢ each. One year guaranteed. Plus many unusual electronic bargains. Free catalog. **CORNELL,** 4217-E University, San Diego, Calif. 92105

SERVICEMEN—Cleaners, lubricants, adhesives for all electronic repairs. Write for free catalog. **PROJECTOR-RECORDER BELT CORP.,** Box 176, Whitewater, WI 53190 800-558-9572 ex. WI

VOX

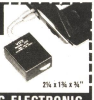

VOICE ACTIVATED CONTROL SWITCH. Self contained, solid state. Has excellent adjustable sensitivity. Recorder activated by voices or other sounds. Uses recorder mike or remote mike. Single AA bat. incl. Great for home, business etc.

2¼ x 1¾ x ¾"

2¼ x ¾ x ½"

AMAZING ELECTRONIC MICRO MINI MIKE™

World's smallest, solid state, self contained with 1.3V Merc. Bat. furn. Picks up most sounds and transmits without wires up to 300 ft. thru FM Radio. Tuneable. Use as mike, ampf., alarm & alert system, baby sitter, hot line, etc. VOX only $24.95*. Mike only $18.95* (*plus $1.00 ea. pstg. & hand.) B/A, M/C, cod. ok. Cal. res. add tax. Free data. Mail Order. Qty. disc. avail. AMC SALES, Dept. 19,
9335 Lubec St., Box 928, Downey, CA 90241

PICTURE TUBE MACHINE

We buy and sell NEW and USED CRT rebuilding machinery. COMPLETE TRAINING. Buy with CONFIDENCE from the ORIGINAL MFGR.

For complete details send name, address, zip to:

LAKESIDE INDUSTRIES
3520 W. Fullerton Ave.
Chicago, Ill. 60647
Phone: 312-342-3399

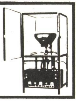

COMPUTER, peripheral, technical reports; project supplies; kits. Send $1 for **THE CPU HOBBYIST,** Box 738-RE, College Park, MD 20740

more than 20,000 different components

RECTIFIERS

	10 For	100 For
1N4001	.60	5.00
1N4002	.70	6.00
1N4003	.80	7.00
1N4004	.90	8.00
1N4005	1.00	9.00
1N4006	1.10	10.00
1N4007	1.20	11.00

VOLT. REG

LM340K-5	1.70
LM340K-6	1.70
LM340K-8	1.70
LM340K-12	1.70
LM340K-15	1.70
LM340K-18	1.70
LM340K-24	1.70
LM340T-5	1.50
LM340T-6	1.50
LM340T-8	1.50
LM340T-12	1.50
LM340T-15	1.50
LM340T-18	1.50
LM340T-24	1.50

5400 SERIES

5400	1.00
5404	1.25
5410	1.00
5426	1.25
5473	1.50
5475	1.50
5486	1.90
5493	2.00
54100	1.80
54LS04	1.00

7400 TTL

7400	.18	7442	1.08	74107	.49
7401	.21	7448	1.15	74121	.55
7402	.21	7450	.26	74122	.49
7404	.21	7451	.27	74123	1.05
7405	.24	7453	.27	74125	.60
7407	.45	7454	.41	74126	.81
7408	.25	7460	.22	74132	3.00
7409	.25	7472	.39	74141	1.15
7410	.20	7473	.45	74150	1.10
7411	.30	7474	.45	74151	1.25
7413	.85	7475	.80	74153	1.35
7416	.43	7482	1.75	74154	1.54
7417	.43	7483	1.15	74157	1.30
7420	.21	7485	1.12	74161	1.45
7422	1.50	7486	.45	74164	1.65
7425	.43	7489	2.49	74165	1.65
7427	.37	7490	.69	74166	1.70
7428	.35	7491	1.20	74174	1.95
7430	.26	7492	.82	74175	1.95
7432	.31	7493	.82	74180	1.05
7437	.47	7494	.91	74181	3.55
7438	.40	7495	.91	74191	1.50
7440	.21	7496	.91	74195	1.00
7441	1.10	74100	1.25	74197	1.00

OEM SPECIALS

1N34	.25	2N2905A	.30	2N3903	.16
1N60	.25	2N2906	.25	2N3904	.16
		2N2906A	.30	2N3905	.16
1N270	.25	2N2907	.25	2N3906	.16
1N914	.10	2N2907A	.30	2N3954A	3.75
2N173	1.75	2N2913	.75	2N3955	2.45
2N404	.75	2N2914	1.20	2N3957	1.25
2N443	2.50	2N3019	1.00	2N3958	1.20
2N508A	.45	2N3053	.30	2N4037	.60
2N718	.25	2N3054	.70	2N4093	.85
2N930	.25	2N3055	.75	2N4124	.16
2N956	.30	2N3227	1.00	2N4126	.16
2N1302	1.25	2N3247	3.40	2N4141	.20
2N1305	.75	2N3250	.50	2N4142	.20
2N1540	.90	2N3393	.20	2N4143	.20
2N1544	.80	2N3394	.17	2N4220A	.45
2N1560	2.80	2N3414	.17	2N4234	.95
2N1605	1.75	2N3415	.18	2N4400	.16
2N1613	.50	2N3416	.19	2N4401	.16
2N1711	.50	2N3417	.20	2N4402	.16
2N2102	.70	2N3442	1.85	2N4403	.20
2N2160	.70	2N3553	1.50	2N4409	.16
2N2218	.25	2N3563	.20	2N4410	.16
2N2218A	.30	2N3565	.20	2N4441	1.00
2N2219	.25	2N3638	.20	2N4442	1.15
2N2219A	.30	2N3642	.20	2N4443	1.35
2N2221	.25	2N3643	.20	2N4852	.55
2N2221A	.30	2N3645	.20	2N5061	.30
2N2222	.25	2N3646	.14	2N5064	.50
2N2222A	.30	2N3731	3.75	2N5130	.20
2N2270	.40	2N3740	1.00	2N5138	.15
2N2369	.25	2N3771	1.75	2N5296	.50
2N2484	.32	2N3772	1.90	2N5306	.20
2N2712	.18	2N3773	3.00	2N5400	.40
2N2904	.25	2N3819	.40	2N5401	.50
2N2904A	.30	2N3823	.70	2N5457	.35
2N2905	.25	2N3866	1.25	2N5458	.30

N.J. residents add 5% sales tax,
All orders add $1.00 Postage $1.50 Canada
minimum order $5.00

PARTIAL LISTING — WRITE FOR FREE CATALOG

JAPANESE TRANSISTORS

2SA484	2.44	2SC482	1.40	2SC1226A	.85	2SD170	1.50
2SA495	.60	2SC495	.85	2SC1237	4.00	2SD180	2.50
2SA497	1.44	2SC517	3.60	2SC1239	3.50	2SD188	2.70
2SA634	1.00	2SC634A	.60	2SC1306	3.50	2SD234	.85
2SA636	1.25	2SC710	.49	2SC1307	4.75	2SD235	.85
2SA673	.70	2SC711	.49	2SC1377	4.80	2SD313	1.05
2SA678	.65	2SC735	.49	2SC1383	.50	2SD314	1.50
2SA682	1.49	2SC756A	2.40	2SC1448	1.00	2SD315	1.20
2SA683	.60	2SC778	3.50	2SC1449	.85	2SD358	1.10
2SA699	1.30	2SC781	2.50	2SC1678	2.00	2SD360	1.05
2SA699A	1.45	2SC789	1.00	2SC1728	1.85	2SD427	2.55
2SA733	.49	2SC798	3.95	2SC1760	1.60	2SD525	1.50
2SA777	.99	2SC799	3.25	2SC1816	3.50	2SK19	1.25
2SB54	.49	2SC1000	.49	2SC1908	.49	2SK30A	.75
2SB56	.95	2SC1013	.95	2SC1909	3.75	2SK33	.90
2SB186	.49	2SC1014	.95	2SC1957	1.00	2SK55	1.00
2SB187	.55	2SC1017	1.20	2SC1973	.90		
2SB324	.60	2SC1018	1.00	2SC1975	3.50	3SK22Y	2.20
2SB370	.65	2SC1061	1.25	2SC2028	.80	3SK40	2.00
2SB405	.60	2SC1079	3.95	2SC2029	3.40	3SK45	2.20
2SB415	.65	2SC1096	.80	2SC2091	2.50	3SK49	2.20
2SB461	1.60	2SC1098	1.00	2SC2092	3.25		
2SB463	1.40	2SC1115	3.00				
2SB507	1.40	2SC1170B	4.95	2SD72	.80	4004	3.00
2SC371	.49	2SC1172	5.25	2SD77	1.50	4005	3.00
2SC372	.49	2SC1173	.75	2SD88	4.80	40081	1.50
2SC481	1.50	2SC1209	.75	2SD118	3.00	40082	3.00

JAPANESE CIRCUITS

AN136	2.90	LA4400FS	3.40	TA7055P	3.00	UPC20C	3.75
AN214	3.35	LA4400FR	3.40	TA7060P	1.40	UPC41C	2.80
AN239	6.50	LD3120	2.40	TA7061P	1.50	UPC563H2	8.00
AN241	2.40	M5115PR	7.80	TA7063P	1.50	UPC566H	1.25
AN315	3.50	PLL01A	13.50	TA7075P	3.75	UPC575C	2.60
BA511	3.00	PLL02A	8.50	TA7089P	2.90	UPC595C	2.95
BA521	3.40	PLL02A-G	8.50	TA7120P	1.50	UPC1001H2	3.50
HA1202	2.20	SG613	6.75	TA7150P	3.75	UPC1008C	5.75
HA1306	4.90	STK011	7.50	TA7153P	6.90	UPC1020H	3.25
HA1308	4.50	STK015	6.50	TA7203P	4.25	UPC1025H	3.50
HA1322	4.20	STK032	14.20	TA7204P	3.70	UPC1166H	4.50
LA1201	4.25	STK050	24.50	TA7205P	3.60	UPD277C	4.50
LA4031P	3.20	STK056	11.35	UH1C003	6.50	UPD857C	15.50
LA4032P	4.20	STK415	8.50	UH1C004	6.50	UPD858C	9.50
LA4051P	3.20	TA7045M	3.25	UPC16C	2.50	UPD861C	18.50

CHECK OUR NEW LOWER PRICES

NEW-TONE ELECTRONICS

PO Box 1738A Bloomfield, N.J. 07003
Phone (201) 748-6171, 6172, 6173

CIRCLE 36 ON FREE INFORMATION CARD

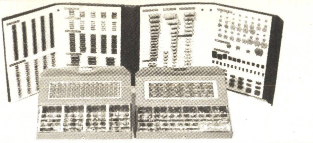

AVAILABLE IN JUNE

10% discount on orders placed before May 31st

CR Kit (Capacitor and resistor kit) **Only $79.95**

A kit containing the capacitor and resistor types and values you use. The parts are neatly packed and identified, but the kit takes up no more room than a book. This kit has 319 resistors from ½ watt to 10 watts: wire wound and carbon types, and 160 capacitors such as oil, electrolites, metalized film, polystyrene, ceramic and mica types.

Fuse Kit TFP-175 **Only $29.95**

This kit contains the fuses and lamps most often required for the repair of CB's, TV's, stereos and other electronic equipment. 1 to 6 amp standard fuses - 60 pcs. ½ to 2 amp small fuses - 40 pcs. 10 to 20 amps - 30 pcs.

Temp. fuse strip 120 C. to 150 C. - 30 pcs. Pilot lamps, 6.3 to 8 volts - 10 pcs.

Pot Kit TYR-109 **Only $34.95**

5 different sizes and 12 different values/size. The kit contains 109 pcs: 200, 500, 1K, 2K, 5K, 10K, 20K, 50K, 100K, 200K, 500K, 1MEG.

Seeking Original Japanese Replacement Parts for CB, TV and Stereo Repair Use?

2SA

2SA 49	.59
2SA 52	.59
2SA 53	.59
2SA 70	1.10
2SA 101	.45
2SA 102	.59
2SA 234	.59
2SA 235	1.00
2SA 240	.90
2SA 329	.70
2SA 342	.90
2SA 353	.70
2SA 377	2.00
2SA 440	.90
2SA 473	.70
2SA 483	3.00
2SA 484	2.50
2SA 485	2.00
2SA 489	1.60
2SA 490	.90
2SA 493	.59
2SA 495	.45
2SA 496	1.10
2SA 497	1.60
2SA 505	1.20
2SA 509	.70
2SA 525	.70
2SA 530	1.30
2SA 537A	2.25
2SA 539	.59
2SA 545	.59
2SA 561	.59
2SA 562	.59
2SA 564A	.59
2SA 565	1.10
2SA 566	3.40
2SA 606	1.60
2SA 607	1.60
2SA 624	1.10
2SA 627	3.60
2SA 628	.59
2SA 634	.70
2SA 640	.59
2SA 643	.70
2SA 653	2.80
2SA 659	.59
2SA 661	.70
2SA 663	4.90
2SA 666	.70
2SA 672	.70
2SA 673	.70
2SA 678	.70
2SA 679	
SUB 2SA 744	
2SA 680	
SUB 2SA 744	
2SA 682	1.50
2SA 683	.70
2SA 684	.70
2SA 695	.70
2SA 697	.70
2SA 699A	.90
2SA 705	.70
2SA 706	1.60
2SA 715	1.40
2SA 719	.59
2SA 720	.59
2SA 721	.59
2SA 725	.59
2SA 726	.59
2SA 733	.59
2SA 738	.70
2SA 740	2.65
2SA 743A	1.60
2SA 744	4.90
2SA 745R	4.90
2SA 747	5.80
2SA 748	1.00
2SA 750	.59
2SA 755	1.60
2SA 756	3.70
2SA 758	5.80
2SA 764	4.40
2SA 774	.59
2SA 777	1.00
2SA 794A	1.00
2SA 798	.70
2SA 810	1.40
2SA 814	1.90
2SA 815	1.00
2SA 816	.70
2SA 818	1.30
2SA 839	2.15
2SA 841	.59
2SA 844	.59
2SA 847	.59
2SA 850	.59
2SA 872A	.59
2SA 885	.70
2SA 908	11.00
2SA 913	1.20

2SB

2SB 22	.59
2SB 54	.59
2SB 55	.59
2SB 75	.45
2SB 77	.45
2SB 173	.45
2SB 175	.45
2SB 176	.45
2SB 178	.70
2SB 186	.45
2SB 187	.45
2SB 202	1.60
2SB 220	.70
2SB 303	.59
2SB 324	.70
2SB 337	1.60
2SB 346	.70
2SB 367	1.50
2SB 368	2.15
2SB 379	1.10
2SB 381	
SUB 2SB 415	
2SB 400	.59
2SB 405	.59
2SB 407	1.40
2SB 411	
DISC. BY MFR.	
2SB 415	.59
2SB 434	1.20
2SB 435	1.40
2SB 440	1.00
2SB 449	1.60
2SB 461	1.20
2SB 463	1.20
2SB 471	1.60
2SB 472	2.80
2SB 473	1.20
2SB 474	1.00
2SB 481	1.20
2SB 492	1.00
2SB 507	1.60
2SB 509	1.60
2SB 511	1.10
2SB 514	1.90
2SB 523	1.00
2SB 526C	1.30
2SB 527	1.60
2SB 528D	1.60
2SB 529	.90
2SB 530	
SUB 2SB 541	
2SB 531	3.40
2SB 536	1.60
2SB 537	1.60
2SB 539	4.90
2SB 541	4.40
2SB 554	10.00
2SB 556	4.90
2SB 557	3.40
2SB 561B	.70
2SB 564	.70
2SB 566	2.80
2SB 595	1.90
2SB 596	
SUB 2SB 507	
2SB 600A	7.00

2SC

2SC 183	.59
2SC 184	.59
2SC 281	.59
2SC 283	
SUB 2SC 458	
2SC 284	1.20
2SC 317	1.20
2SC 352A	2.50
2SC 353A	2.50
2SC 367	.90
2SC 369	.59
2SC 371	.59
2SC 372	.45
2SC 373	.45
2SC 374	.59
2SC 377	.70
2SC 380	.59
2SC 381	.59
2SC 382	.59
2SC 383	.90
2SC 387A	.59
2SC 388A	1.00
2SC 394	.59
2SC 403	.59
2SC 430	.90
2SC 454	.59
2SC 458	.59
2SC 460	.59
2SC 461	.59
2SC 478	1.10
2SC 481	1.60
2SC 482	1.50
2SC 484	
SUB 2SC 756	
2SC 485	1.60
2SC 486	1.60
2SC 493	3.90
2SC 495	.90
2SC 497	1.60
2SC 509	.70
2SC 515A	1.40
2SC 517	3.95
2SC 535	.59
2SC 536	.59
2SC 537	.59
2SC 538A	.70
2SC 562	.70
2SC 563	1.10
2SC 605	.70
2SC 619	.59
2SC 620	.59
2SC 627	2.25
2SC 631	.90
2SC 632A	.45
2SC 634A	.59
2SC 642A	5.90
2SC 644	.45
2SC 645	.70
2SC 650	1.30
2SC 665H	8.50
2SC 668	.45
2SC 680	2.80
2SC 681A	5.80
2SC 684	1.10
2SC 693B	.59
2SC 696	1.95
2SC 708	1.90
2SC 710	.45
2SC 711	.45
2SC 712	.59
2SC 717	.59
2SC 727	1.90
2SC 730	4.40
2SC 731	5.80
2SC 732	.59
2SC 733	.59
2SC 734	.59
2SC 735	.59
2SC 738	.59
2SC 756	2.80
2SC 756A	3.00
2SC 763	.59
2SC 772	.45
2SC 773	.70
2SC 774	2.00
2SC 775	1.95
2SC 776	2.65
2SC 777	3.50
2SC 778	3.60
2SC 781	2.65
2SC 783R	3.60
2SC 784	.59
2SC 785	.59
2SC 789	1.00
2SC 793	2.80
2SC 799	3.60
2SC 802	
SUB 2SC 799	
2SC 815	.59
2SC 828	.45
2SC 829	.45
2SC 830H	5.90
2SC 838	.59
2SC 839	.59
2SC 867	4.25
2SC 870	.59
2SC 871	.59
2SC 897	3.40
2SC 898	4.40
2SC 900	.45
2SC 923	.45
2SC 929	.45
2SC 930	.45
2SC 941	.59
2SC 943	.70
2SC 945	.45
2SC 959	1.50
2SC 971	1.00
2SC 982	.90
2SC 983	1.00
2SC 984	.90
2SC 994	3.90
2SC 996	3.40
2SC 1000BL	.59
2SC 1012	1.50
2SC 1013	1.10
2SC 1014	1.10
2SC 1017	1.40
2SC 1018	1.20
2SC 1030C	2.80
2SC 1047	.70
2SC 1051	4.40
2SC 1060	1.40
2SC 1061	1.40
2SC 1079	5.90
2SC 1080	4.40
2SC 1096	1.00
2SC 1098	1.10
2SC 1111	3.40
2SC 1114	3.70
2SC 1115	4.40
2SC 1116	4.90
2SC 1116A	6.60
2SC 1124	1.30
2SC 1127	1.40
2SC 1161	1.90
2SC 1162	1.10
2SC 1166	.59
2SC 1167	6.60
2SC 1170B	6.60
2SC 1172B	8.50
2SC 1173	.90
2SC 1175	.90
2SC 1177	14.00
2SC 1189	1.20
2SC 1209	.70
2SC 1211D	.59
2SC 1212A	1.40
2SC 1213	.70
2SC 1215	.70
2SC 1222	.45
2SC 1226A	1.00
2SC 1237	4.25
2SC 1239	3.90
2SC 1279	.70
2SC 1306	3.90
2SC 1307	4.90
2SC 1310	.59
2SC 1312	.59
2SC 1313G	.59
2SC 1317	.45
2SC 1318	.45
2SC 1325A	7.60
2SC 1327	.59
2SC 1330	.70
2SC 1335	.70
2SC 1342	.59
2SC 1344	.59
2SC 1345D	.59
2SC 1346	.70
2SC 1347	.70
2SC 1358	5.90
2SC 1359	.59
2SC 1360	1.00
2SC 1362	.59
2SC 1364	.70
2SC 1377	4.90
2SC 1383	.59
2SC 1384	.59
2SC 1396	.70
2SC 1398	1.10
2SC 1400	.59
2SC 1402	4.90
2SC 1403	4.90
2SC 1407	.90
2SC 1419	1.10
2SC 1444	2.80
2SC 1447	1.60
2SC 1448	1.60
2SC 1449	1.00
2SC 1451	2.25
2SC 1452	1.60
2SC 1475	1.40
2SC 1478S	.70
2SC 1509	1.10
2SC 1567	1.10
2SC 1567A	1.10
2SC 1569	1.40
2SC 1584	8.50
2SC 1586	7.60
2SC 1624	1.30
2SC 1626	1.10
2SC 1628	1.30
2SC 1647	1.00
2SC 1669	1.60
2SC 1674	.59
2SC 1675	.59
2SC 1678	2.25
2SC 1679	4.25
2SC 1681	.70
2SC 1682	.45
2SC 1684	.59
2SC 1687	.70
2SC 1688	.70
2SC 1708	.59
2SC 1728	1.90
2SC 1730	.59
2SC 1756	1.40
2SC 1760	1.90
2SC 1765	8.80
2SC 1775	.45
2SC 1816	3.90
2SC 1846	.70
2SC 1885	.70
2SC 1908	.59
2SC 1909	3.90
2SC 1913	1.20
2SC 1945	5.60
2SC 1951	1.10
2SC 1957	1.20
2SC 1969	4.90
2SC 1973	1.10
2SC 1974	1.90
2SC 1975	4.40
2SC 2028	.90
2SC 2029	3.90
2SC 2076	.59
2SC 2091	2.80
2SC 2092	3.90
2SC 2098	4.90

2SD

2SD 16	5.90
2SD 28	2.50
2SD 72	1.10
2SD 75	
SUB 2SD 187	
2SD 77	.90
2SD 81	3.00
2SD 90	1.60
2SD 91	1.60
2SD 92	1.90
2SD 93	2.80
2SD 118	4.40
2SD 130	1.20
2SD 141	1.40
2SD 142	2.00
2SD 143	2.80
2SD 178	1.10
2SD 180	2.50
2SD 187	.59
2SD 188	3.00
2SD 201	3.40
2SD 205	1.40
2SD 213	5.90
2SD 217	4.40
2SD 218	3.40
2SD 220	2.50
2SD 223	1.90
2SD 224	1.90
2SD 226	1.60
2SD 227	.45
2SD 234	1.00
2SD 235	1.00
2SD 261	.60
2SD 287	3.70
2SD 288	1.40
2SD 300	5.60
2SD 313	1.10
2SD 314	1.20
2SD 315	1.20
2SD 325	1.10
2SD 330	1.00
2SD 341	5.60
2SD 350	5.90
2SD 352	.90
2SD 356D	1.10
2SD 357D	1.00
2SD 358	1.30
2SD 359	1.00
2SD 360	1.20
2SD 361	1.00
2SD 370	
SUB 2SD 427	
2SD 371S	2.80
2SD 380	7.60
2SD 382	1.40
2SD 388	3.40
2SD 388A	4.40
2SD 389	.90
2SD 390	1.00
2SD 424	8.50
2SD 425	6.50
2SD 426	4.60
2SD 427	3.00
2SD 525	1.60
2SD 526	1.10
2SD 555A	6.60
2SD 610	1.90
SG 613 (TV)	**5.95**

FET

2SK 19BL	.90
2SK 23	1.10
2SK 30	.70
2SK 33	1.10
2SK 34	1.10
2SK 40	.70
2SK 41	1.10
2SK 49	1.30
2SK 58	3.60
2SK 61	1.40
2SK 68	1.30
3SK 22Y	2.55
3SK 35	2.25
3SK 37	3.00
3SK 39	2.25
3SK 40	2.25
3SK 41	2.50
3SK 45	2.50
3SK 48	5.90
3SK 49	2.50
MK 10	2.00

IC

AN 203	2.50
AN 211	2.50
AN 214Q	3.00
AN 217	1.90
AN 234	4.90
AN 239	7.00
AN 240	2.15
AN 241	2.80
AN 245	4.90
AN 247	4.40
AN 264	2.00
AN 274	3.40
AN 277B	2.40
AN 288	6.60
AN 315	3.70
AN 328	3.90
AN 348	3.70
AN 362	3.00
BA 511	3.40
BA 521	3.70
HA 1137	4.90
HA 1138	4.40
HA 1149	5.60
HA 1151	4.40
HA 1156	3.00
HA 1158	5.30
HA 1159	5.80
HA 1196	4.90
HA 1197	3.90
HA 1201	1.50
HA 1202	2.25
HA 1211	1.50
HA 1306W	3.70
HA 1312	3.90
HA 1322	4.40
HA 1339	4.40
HA 1339A	4.40
HA 1342A	4.40
HA 1452	3.40
LA 1111P	2.50
LA 1201	2.50
LA 1221	2.80
LA 1364	4.40
LA 3300	3.00
LA 3301	3.00
LA 4030P	3.40
LA 4031P	3.00
LA 4032P	3.40
LA 4051P	3.70
LA 4400	3.70
LD 3120	2.50
M 5111AP	2.80
M 5112	7.00
M 5115PR	4.90
M 51513L	4.90
M 5152L	2.50
M 51841P	2.80
M 5320 OP	2.25
M 5327 3P	2.80
M 53274P	2.50
M 54730 P	8.80
M 53393	7.60
STK 011	7.60
STK 014	9.50
STK 015	6.60
STK 016B	8.50
STK 022	11.00
STK 032	14.00
STK 435	8.50
STK 437	9.80
STK 439	11.00
STK 502	8.80
STK 503	9.60
TA 7027M	3.70
TA 7045M	3.00
TA 7054P	2.50
TA 7055P	3.00
TA 7060P	1.60
TA 7061AP	1.90
TA 7062P	1.90
TA 7063P	1.60
TA 7064P	1.90
TA 7066P	2.00
TA 7074P	4.90
TA 7075P	4.90
TA 7076P	4.90
TA 7089P	3.00
TA 7092P	4.90
TA 7102	5.80
TA 7106P	4.90
TA 7108P	1.90
TA 7109P	3.40
TA 7120P	1.90
TA 7120PC	2.15
TA 7122AP	1.90
TA 7124P	1.60
TA 7129P	1.90
TA 7130P	2.80
TA 7136P	1.30
TA 7146P	4.20
TA 7150P	4.40
TA 7159P	2.50
TA 7200P	4.60
TA 7201P	4.60
TA 7203P	3.70
TA 7204P	3.40
TA 7205P	**3.50**
TA 7310P	3.95
TA 78005M	5.80
TA 8005P	5.80
TA 78012M	6.60
TA 78012P	5.80
TA 78015M	6.50
TA 78015P	5.80
TBA 810SH	3.70
TC 9100P	22.00
TD 3505AP	8.50
UPC 41C	3.70
UPC 554C	2.80
UPC 555H	2.25
UPC 566H	1.60
UPC 575C	2.80
UPC 576	3.70
UPC 577H	2.25
UPC 592HZ	1.60
UPC 1001H	4.90
UPC 1008C	7.00
UPC 1016C	3.00
UPC 1020H	3.70
UPC 1025	4.40
UPC 1026C	3.70
UPC 1032	2.25
UPC 1156	4.25
UPC 1152H	3.40
PLL 01A	8.80
PLL 02A	8.80
SN 7400	.19
SN 7490	.60

DIODES

IS 84	.60
IS 188	.25
IS 332	.45
IS 953	.25
IS 1007	.45
IS 1209	.45
IS 1211	.45
IS 1555	.25
IS 1588	.25
IS 1885	.25
IS 2076	.25
IS 2093	.45
IS 2473	.25
IN 34	.25
IN 60	.25
10D1	.40
10D10	.60
VO6B	.40
VO6C	.40
WZ-050	.45
WZ-052	.45
WZ-061	.45
WZ-070	.45
WZ-075	.45
WZ-081	.45
WZ-192	.45
WZ-260	.45
WZ-280	.45

PRICES MAY CHANGE WITHOUT NOTICE COD ORDERS WELCOMED Less than $500 no deposit required

Minimum order $5.00 Ohio residents add 4% sales tax Add $1.00 postage and handling
Quantity discount prices Ask For Our Complete Price List Manufacturer inquiries Welcomed
ALL PARTS GUARANTEED AGAINST FACTORY DEFECT

IMMEDIATE DELIVERY WITHIN 48 HOURS
ON ALL TRANSISTORS IN STOCK

TOLL FREE TELEPHONE

Nationwide 800/543-1607 LOCAL 513/874-0220
Ohio 800/582-1630 874-0223
Hours: Mon.-Fri. 10-7 Sat. 11-5

FUJI-SVEA ENTERPRISE

a Division of Fuji-Svea Incorporated
Dept.
P.O. Box 40325 Cincinnati, Ohio 45240
Telex - 21-4732

CIRCLE 14 ON FREE INFORMATION CARD

ROBOTICS Newsletter. $8 year, issued monthly. **INTERNATIONAL INSTITUTE FOR ROBOTICS,** Dept. RE, Box 615, Pelahatchie, MS 39145

SCANNERS, Bearcat 210 or Regency Touch $239.95, crystals, two-way radios. Free catalog. **GUILDERLAND COMMUNICATIONS,** Box 591, Guilderland, NY 12084

TELEPHONE recording equipment and other "unusual" electronic devices. Free info: GARRISON, Box 128-B, Kew Gardens, NY 11415

FREE KIT Catalog

STOP! Take a minute & let us send our latest kit catalog. If you like, send us the name & address of a friend who may also be interested and, we'll include to you our booklet "How to build-electronic thermometer"

contains TEST & EXPERIMENTER'S EQUIP.

DAGE SCIENTIFIC INSTRUMENTS
BOX 1054R LIVERMORE CA 94550

FREE bargain catalog, IC's, LED's, semiconductors, crystals, electron tubes. Send stamp. **ASTRAL,** P.O.B. 707RE, Linden, NJ 07036

P.C. board 21 × 18 × 1/16″ double-sided $6.00. Projection picture tube 5TP4 N1B $95.00. 50¢ postage. **Herb Hodapp,** 322 Main, St. Clair, MN 56080

OPTO-ISOLATORS-PRIME-H11A2, 2/1.00, 30/10.00, **SCR's 200V 35Amp** 85¢ each 10/5.00. **A. KHAN,** 2355 Burch Cir., Atlanta, GA 30319

SCOOP!! 4MEGABYTE TAPE RECORDER!

$269.00

QUAD 5 CHANNEL TAPE TRANSPORT, ONE FURNISHED, LOGIC FOR AUTO SELECT, REWIND, TAPE BREAK, EOT, LOW LEVEL & LAST CARTRIDGE.
POWER REQ'D 12 VOLTS 5 AMPS DC
STD RACK PANEL 12 1/8" HIGH 19" WIDE 20" DEEP, WT 85LBS
BOOK $10 SHIPPED COD–USED–GOOD COND. LIMITED QTY.

J&E ELECTRONICS INC.
P.O. BOX 4504, FORT WORTH, TEXAS, 76106; OR PHONE 817-625-2961, BANK AMERICARD, M.C. OR VIZA ACCEPTED
TEXAS RES. ADD 5% SALES TAX–NO CHECKS

Why is this the

LARGEST SELLING low cost COUNTER KIT?

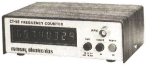

This counter is such a great seller because people like you have found that, feature for feature, the CT-50 gives you more for your money. Advanced LSI and CMOS circuitry has; lowered power consumption, increased performance, and reduced cost. Complete push button operation makes using the CT-50 a snap, and automatic decimal point positioning gives you quick, reliable readings. Battery operation is also possible becuase the CT-50 runs equally as well on 12VOC as it does on 110VAC. For ultra-accuracy we offer the CB-1 color burst adapter, it locks the CT-50's internal crystal to the television networks color standard for .001 ppm accuracy! Why sacrifice performance by using another counter when you can get professional quality at the unheard of price of $79.95? Order yours today!

SPECIFICATIONS
Sensitivity: less than 10 mv.
Frequency range: 5 Hz to 60 MHz, typically 65 MHz
Gatetime: 1 second, 1/10 second, with automatic decimal point positioning on both direct and presacle
Display: 8 digit red LED .4″ height
Accuracy: 2 ppm, internal TCXO standard.
Input: BNC, 1 megohm direct, 50 Ohm with prescale, option
Power: 110 V ac 5 Watts or 12 V dc @ 300-400 ma
Size: Approx. 6″ x 4″ x 2″, high quality aluminum case

CT 50,60 MHz Counter Kit $79.95
CT-50 wt 60 MHz Counter Wired & Tested $159.95
CT-600, 600 MHz prescaler option for CT-50, add.. $29.95

MINI-KITS

FM WIRELESS MIKE KIT
Transmit up to 300′ to any FM broadcast radio, uses any type of mike. Runs on 3 to 9V. Type FM-2 has added super-sensitive mike preamp.
FM-1 – $2.95 FM-2 – $4.95

SUPER-SLEUTH AMPLIFIER
A super-sensitive amplifier which will pick up a pin drop at 15 feet! Great for monitoring baby's room or a general purpose test amplifier. Full 2 watts of output, runs on 6 to 12 volts, uses any type of mike. Requires 8-45 ohm speaker.
Complete Kit, BN-9. . . . . $4.95

COLOR ORGAN/MUSIC LIGHTS
See music come alive! 3 different lights flicker with music or voice. One light for lows, one for the mid-range and one for the highs. Each channel individually adjustable, and drives up to 300 watts. Great for parties, band music, nite clubs and more.
Complete Kit, ML-1. . . . . $7.95

TONE DECODER KIT
A complete tone decoder on a single PC Board. Features: 400-5000 Hz adjustable frequency range, voltage regulation, 567 IC. Useful for touch-tone decoding, tone burst detection, FSK demod, signaling, and many other uses. Use 7 for 12 button touchtone decoding. Runs on 5 to 12 volts.
Complete Kit, TD-1. . . . . $4.95

LED BLINKY KIT
A great attention getter which alternately flashes 2 Jumbo LEDs. Use for name badges, buttons, or warning type panel lights. Runs on 3 to 9 volts.
Complete Kit, BL-1 . . . . $2.95

POWER SUPPLY KIT
Complete triple regulated power supply provides variable +15 volts at 200 mA and ±5 volts at 1 Amp. 50 mV load regulation good filtering and small size. Kit less transformers. Requires 6-8V at 1 Amp and 18 to 30 VCT.
Complete Kit, PS-3LT $6.95

SIREN KIT
Produces upward and downward wail characteristic of police siren. 5 watts audio output, runs on 3-9 volts, uses 8-45 ohm speaker.
Complete Kit, SM-3 . . . .$2.95

VIDEO MODULATOR KIT
Converts any TV to video Monitor, Super stable tunable over Ch. 4-6. Runs on 5-15V, accepts std. video signal. Best unit on the market.
Complete Kit, VD-1. . . . . $6.95

SIX DIGIT 12/24 HOUR CLOCK KIT

Here's a clock you can be proud of. The best looking, most complete kit on the market! Features include: time set pushbuttons, jumbo .4″ readouts, and extruded aluminum case available in 5 colors, All parts included. Colors: gold, silver, bronze, black, blue (specify)

Clock Kit, DC-5	$22.95	Alarm Clock, 12 Hr., DC-8	24.95
Mobile Clock, DC-7	25.95	Clock with HAM ID timer DC-10	25.95

Assembled and tested clocks available, add $10.00 to Kit price.

600 MHz PRESCALER

Extend the range of your counter to 600 MHz. Works with all counters. Less than 150 mv sensitivity. Specify −10 or −100. Wired, tested,

PS-1 B $59.95
Kit, PS-1 B $44.95

CALENDAR ALARM CLOCK

Has every feature one could ever ask for. Kit includes everything except case, build it into wall, station or even car!

FEATURES:

- 6 Digits, .5″ High LED
- 12/24 Hour Format
- Calendar shows mo./day
- Snooze button
- True 24 Hour Alarm
- 7001 chip does all!!
- Battery back up with built-in on chip time base.

Complete Kit, less case
DC-9 . . . . $34.95

TV TYPEWRITER KIT

A compact 5 x 10 inch PC card that requires only an ASCII keyboard and a TV set to become a complete interactive terminal for connection to your microprocessor asynchronous interface. Its many features are single 5-volt supply, crystal controlled sync and baud rates (up to 9600 baud), 2 pages of 32 characters by 16 lines, read to and from memory, computer and keyboard operated cursor and page control, power-on initialization, full 64-character ASCII display, block-type, see-thru cursor. Keyboard/computer control backspaces, forward spaces, line feeds, rev. line feeds, home, returns cursor. Also clears page, clears to end of line, selects page 1 or 2, reads from or to memory. The card requires 5 volts at approx. 900 ma and outputs standard 75 ohm composite video.

TH3216 Kit	$149.95
TH3216, Assembled and Tested	239.95
VD-1 Video to RF Modulator Kit	6.95

CAR CLOCK KIT

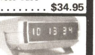

12/24 Hour 12-Volt AC or DC
- High Accuracy (1 minute/month)
- 6 Jumbo 4″ LED readouts
- Easy, no-polarity hookup
- Display blanks with ignition
- Case mounting bracket included
- Super instructions

Complete Kit, DC-11 . . . .$27.95

Auto dimmer for DC-11 . . . .$2.50

741 OP AMP SPECIAL
Prime, Mini-dip 10/$2.00

ICs		LINEAR		REGULATOR	SPECIAL	TRANSISTORS	
5314 Clock	$2.95	555	$ .50	78MG	$1.49	MRF-238 30W VHF	$11.95
7001 Clock	6.95	556	.75	309K	.89	NPN 2N3904 type	10/$1.00
5369 Cnos	1.95	566	1.49	309H	.99	PNP 2N3906 type	10/$1.00
7447	.79	567	1.49	340K-12	.99	NPN Power Tab 40W	3/$1.00
7473	.35	1458	.50	7805	.89	PNP Power Tab 40W	3/$1.00
7475	.50	LED DRIVER		7812	.89	FET MPF-102 type	3/$2.00
7490A	.55	75491	.50	7815	.89	UJT 2N2646 type	3/$2.00
74143	3.50	75492	.50	7818	.89	2N3055 NPN Power	.75

ORDER BY PHONE OR MAIL
Satisfaction guaranteed or money refunded. Add 5% for shipping and insurance. COD add $1.00. Orders under $10.00 add $.75. NY residents add 7% sales tax. Minimum order $6.00.

ramsey electronics
BOX 4072B ROCHESTER, NY 14610 (716) 271-6487

CIRCLE 35 ON FREE INFORMATION CARD

CARBON film resistors—¼W, 5% (1-4M7 ohms) 3.5¢ each. 50/value—$0.85. Postage, handling $1.00. Other components. Free catalog, resistor sample. **COMPONENTS CENTER,** Box 295R, West Islip, NY 11795

TUBES, receiving and Industrial, semiconductors, factory boxed, low prices, free price list. **TRANSLETERONIC INC.,** 1365 — 39th Street, Brooklyn, NY 11218 212-633-2800

FREE KIT Catalog

2708 - 20.00
1 amp variable powr supply $19.95
Clocks - Counters
Micro Computer
Function Generator
Fairchild Tech. Kits TM

ETRONIX BOX 321
ISSAQUAH, WA 98207

SAVE UP TO 85% GOV'T SURPLUS and NEW EQUIP'T

Powerful Battery Motor
BUILD MOTORIZED BICYCLE, ELECTRIC CAR, ETC.

$29.95
F.O.B. Lincoln
Normal Retail Over $100.00

• (ITEM #1066) - - New Factory Surplus. Use to motorize bicycles scooters childrens autos. Drive pumps tools compressors. Operates on 12, 24 or 36 VDC at 1200 2400 and 3600 RPM respectively. 3.5 HP at 36-volts. 61 in. lbs torque. Shaft diam. 3/4. 4-hole 6 diam. mtg flange. Motor 3-1/2 diam. x 9 long incl. shaft

COMPACT 12-V. BATTERY FOR USE WITH ABOVE MOTOR
• (ITEM #2803) - - New 12-volt 10.2-amp. hr. lead acid type. Dry (75%) charged. Put in electrolyte charge and use. Compact WISCO EV10-30 5 x 5 x 3 (7 lbs.)

Normal Retail Over $30.00
$14.95

BIG, Equipt. Catalog
Send 25¢ Coin or Stamps

LOWEST PRICES ON
HYDRAULICS COMPRESSORS
SURVEYING INST'S
GEAR MOTORS
WINCHES POWER PLANTS
CABLE SPEED REDUCERS
WELDERS BINOCULARS
WEED SPRAYING
ELECTRONICS
TELEPHONES PUMPS HOSE
MANY OTHERS

SURPLUS CENTER RE-058 Lincoln, Nebraska Zip Code 68501

NEW, adjustable, three output, regulated power supply, plus 900 parts worth over $400.00 in complete **cartrivision** television electronics assembly. Documentation included. Perfect for **microprocessor** and all electronic applications. $17.95 plus $3.50 S&H. Master Charge, BankAmericard. Free brochure. **MADISON ELECTRONICS,** 369, Madison, AL 35758. **Satisfaction guaranteed**

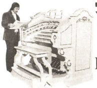

YES, YOU CAN BUILD AN ELECTRONIC ORGAN

That has a PIPE ORGAN SOUND

With **DEVTRONIX easy to build assemblies.**
Own the ultimate in organ design & sound at ⅓ the cost of commercial organs.
Several models to choose from.
BROCHURE AND DEMO RECORD $1.00

Devtronix ORGANS, INC.
Dept. B
5872 Amapola Dr.
San Jose, CA 95129

INTO TV ANTENNA SYSTEMS? YOU'LL BE INTO TASCO!

Below wholesale prices on a full line of antenna installation surplus shipped from stock. Unbelievable prices on connectors, wall plates, splitters, transformers, amplifiers, etc. Write for free catalogue. Order now & compare. **TASCO. PO Box 30143 Houston Tex 77009**

POWER booster, in car, 25 watts stereo, transformerless. Guitar amplifier, up to 250 watts. Schematic, parts list, $5.00 each, $7.50 both. **BURMON,** P.O. Box 2483, Dearborn, MI 48123

BLITZ ZOINK ZATT: UNSCRAMBLE these fascinating police communications with our CODE-BREAKER and keep informed. Tunes all scramble frequencies, works with all scanners, and is factory built and guaranteed. $34.95PP. UNSCRAMBLER KIT: Latest Technology, 2¾X2¼X½-inch, complete instructions, only $19.95PP. Thousands of satisfied customers. Catalog 50¢. Order from KRYSTAL KITS, BOX 445, BENTONVILLE, ARK. 72712. COD orders. 501-273-5340.

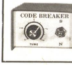

Radio Shack: No. 1 Parts Place

Buy Off-the-Shelf! Low Prices! Huge Selection!

Top-quality devices, fully functional, carefully inspected. Guaranteed to meet all specifications, both electrically and mechanically. All are made by well-known American manufacturers, and all have to pass manufacturer's quality control procedures. These are not rejects, not fallouts, not seconds. In fact, there are none better on the market! Always count on Radio Shack for the finest quality electronic parts.

Linear ICs

By National Semiconductor and Motorola — first quality

Type	Cat. No.	ONLY
301CN	276-017	49¢
324N	276-1711	1.49
339N	276-1712	1.49
386CN	276-1731	99¢
555CN	276-1723	79¢
556CN	276-1728	1.39
566CN	276-1724	1.69
567CN	276-1721	1.99
723CN	276-1740	69¢
741CN	276-007	49¢
741H	276-010	49¢
3900N	276-1713	99¢
3909N	276-1705	99¢
3911N	276-1706	1.99
4558CN	276-038	79¢
75491	276-1701	99¢
75492	276-1702	99¢
7805	276-1770	1.29
7812	276-1771	1.29
7815	276-1772	1.29

Computer Chips

Prime Devices

8080A Microprocessor. 8-bit, NMOS.
276-2510 Reg. 17.95 . . . . **Sale 12.95**

2102 1K Static RAM. Under 450 ns.
276-2501 . . . . **2.49 Ea. or 8/14.95**

TTL and CMOS Logic ICs

Full-Spec Devices Direct from Motorola and National Semiconductor

Type	Cat. No.	ONLY
7400	276-1801	35¢
7402	276-1811	39¢
7404	276-1802	35¢
7406	276-1821	49¢
7410	276-1807	39¢
7413	276-1815	79¢
7420	276-1809	39¢
7427	276-1823	49¢
7432	276-1824	49¢
7441	276-1804	99¢
7447	276-1805	99¢
7448	276-1816	99¢
7451	276-1825	39¢
7473	276-1803	49¢
7474	276-1818	49¢
7475	276-1806	79¢
7476	276-1813	59¢
7485	276-1826	1.19
7486	276-1827	49¢
7490	276-1808	79¢
7492	276-1819	69¢
74123	276-1817	99¢
74145	276-1828	1.19
74150	276-1829	1.39
74154	276-1834	1.29
74192	276-1831	1.19
74193	276-1820	1.19
74194	276-1832	1.19
74196	276-1833	1.29
74C00	276-2301	SALE 29¢
74C02	276-2302	SALE 29¢
74C04	276-2303	SALE 29¢
74C08	276-2305	SALE 29¢
74C74	276-2310	SALE 49¢
74C76	276-2312	SALE 49¢
74C90	276-2315	SALE 89¢
74C192	276-2321	SALE 1.00
74C193	276-2322	SALE 1.00
4001	276-2401	49¢
4011	276-2411	49¢
4013	276-2413	89¢
4017	276-2417	1.49
4020	276-2420	1.49
4027	276-2427	89¢
4049	276-2449	69¢
4050	276-2450	69¢
4511	276-2447	1.69
4518	276-2490	1.49

NEW 1978 Edition

BONUS OFFER
Only **99¢**
With Any $5
Parts Purchase

REGULARLY $1.95. Archer® Semiconductor Reference and Application Handbook. Complete specs and application data on every Archer semiconductor — display devices, too! 46,000 cross-reference/substitution listings plus glossary of words, symbols, abbreviations. **276-4002 . . . With Any $5 Parts Purchase, Only 99¢**

Offer good at participating Radio Shack stores and dealers

Wire Wrapping Accessories

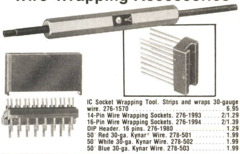

IC Socket Wrapping Tool. Strips and wraps 30-gauge wire. 276-1570 . . . . 6.95
14-Pin Wire Wrapping Sockets. 276-1993 . . . . . 2/1.29
16-Pin Wire Wrapping Sockets. 276-1994 . . . . . 2/1.39
DIP Header. 16 pins. 276-1980 . . . . 1.29
50′ Red 30-ga. Kynar® Wire. 278-501 . . . . 1.99
50′ White 30-ga. Kynar Wire. 278-502 . . . . 1.99
50′ Blue 30-ga. Kynar Wire. 278-503 . . . . 1.99

Trim Multi-Purpose Cabinets

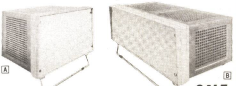

A **Compact.** Makes even your small projects look professional. 5⅞x9x4⅞″. **270-281** **10.95**

B **Low-Profile.** Slim-design — only 5⅞x11⅜x3½″. **270-282.** Reg. 14.95 . . . . **Sale 12.95**

SALE LED Digital Displays

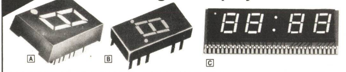

Digits	Size	Drive	Cat. No.	Reg.	SALE
A 1	0.6″	Anod.	276-056	2.99	2.29
A 1	0.6″	Cath.	276-066	2.99	2.29
B 1	0.3″	Anod.	276-053	1.99	1.49
B 1	0.3″	Cath.	276-062	1.99	1.49

Digits	Size	Drive	Cat. No.	Reg.	SALE
B 1	0.3″	Anod.	276-1210	4/6.99	4/5.49
B 1	0.3″	Cath.	276-1211	4/6.99	4/5.49
C 4	0.5″	Anod.	276-1201	6.95	5.99
C 4	0.5″	Cath.	276-1202	6.95	5.99

IC Accessories

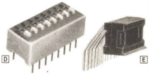

D **DIP Switch.** For changing preset logic states. **275-1301** **1.99**

E **Right-Angle 16-Pin Socket.** **276-1985** **1.49**

SALE MA1003 Automotive Clock Module

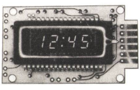

Just add switches and install! 12-hour readout, 0.3″ digits, ±0.5 sec./day accuracy. 12VDC. **277-1003.** Reg. 24.95 . . . . **Sale 19.95**

Archer® Project-Boards — Predrilled PCB's

SALE

Time Base Generator. Built-in 10 MHz xtal or ext. input. Decade selector, switch. TTL output. Requires 5VDC. Reg. $5.99. **277-115** (PCB less parts) . . . . **Sale 4.99**

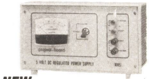

NEW

5V, 3-Amp Power Supply. Metered output current, foldback limiting. Remote sensing. For all 5V TTL projects. **277-119** (PCB less parts) **7.95**

Shown Built with Recommended Parts and Cases

Full-Wave Bridge Rectifiers

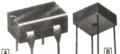

NEW

A **1-Amp, 50 PIV.** Mini DIP fits PCB or 8 and 14-pin sockets. **276-1161** . . . . **69¢**

B **6-Amp, 50 PIV.** Heavy-duty leads, heat sink mtg. hole. **276-1180** **1.99**

Mike Elements

Dynamic. Tiny yet delivers 80-10,000 Hz response. −65 dB. 200 ohms. ¾x⅞″. **270-093** **1.69**

Hi-Z Crystal. 50-8000 Hz response. −55 dB. 1½x1¼″. **270-095** **1.39**

SALE 2-Foot Mini Test Clips

Red. Reg. 1.99
278-1158 . . . . **Sale 1.49**
Black. Reg. 1.99.
278-1159 . . . . **Sale 1.49**

35VDC Electrolytic Pak

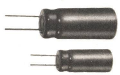

Package of 10 with two of each value: 4.7, 10, 25, 50 and 100 μF. PC mounting. **272-1035** **2.99**

WHY WAIT FOR MAIL ORDER DELIVERY?
IN STOCK NOW AT OUR STORE NEAR YOU!

Prices may vary at individual stores and dealers

Radio Shack®

A DIVISION OF TANDY CORPORATION • FORT WORTH, TEXAS 76102
OVER 6000 LOCATIONS IN NINE COUNTRIES

AUTO FM CONVERTER WITH WEATHER BAND

Reg. ~~29.99~~ AU-560 **12.99**

- Converts AM Auto Radio to FM & Instant Weatherband

NICKEL CADMIUM BATTERY PACK

1.99 Reg.

BA-327

- 3.6 VDC Total
- Standard Penlight Size
- Rechargeable Over and Over

Cassette Tape, Pkg. of 3-30 Minute. TA-879	79¢
8-Track Tape, 40 Minute. TA-907	49¢
Earphones, 8 Ohm, Less Cord. Pkg. of 4. PH-405	49¢
Singer 12 Digit MOS Calculator Chip With Data. XM-635	1.79
UHF Varactor Tuner With Data Sheet. XM-676	1.49
Ceramic Capacitors, Pkg. of 100. CC-211	1.00
RED LED, 2 Volt, 10mA. Pkg. of 5. PL-233	59¢
LCD 3½ Digit Display. XM-371	2.79
709 High Gain OP AMP. RE-131	79¢
Deluxe Stereo Headphones. PH-460	2.99
3" Fan and 120VAC Motor. MO-416	2.49
Cassette Laplel Mike, 3.5mm Plug. MM-174	1.00
3" Recording Tape, Pkg. of 5 (125' to 300'). TA-928	50¢
Slidemount For Auto Stereo or CB. AU-149	1.99
6 to 12 Volt DC Converter, 6V. Acc. On 12V. Batt. AU-297	4.99
650 RPM Motor, 5½" Shaft, 120V. AC. MO-265	1.00

OFFER GOOD ONLY IN THE CONTINENTAL U.S.

Olson. electronics
260 S. Forge St.
Dept. LB Akron, Ohio 44327

NAME ______
ADDRESS ______
CITY ______ STATE ______ ZIP ______

Qty.	Stk. #	Description	Price Ea.	Total

FREE ☐ Please Send Catalog

Tax ______
Postage ______
TOTAL ______

CIRCLE 68 ON FREE INFORMATION CARD

AMAZING ELECTRONIC PROJECTS and PRODUCTS: Lasers Super Powered, Burning, Cutting, Rifle, Pistol, Pocket. See in Dark—Shotgun Directional Mike—Unscramblers—Giant Tesla—Stunwand—TV Disrupter—Energy Producing, Surveillance, Detection, Electrifying, Ultrasonic, CB, Auto and Mech. Devices, Hundreds More—All New Plus INFO UNLTD PARTS SERVICE. Catalog $1. **Information Unlimited, Box 626, Lord Jeffery Court, Amherst, N.H. 03031.**

TAPE head cleaner. 8 oz.—$2.30. Includes postage and handling. Write: **"CLEANER,"** Box 176, Whitewater, WI 53190

NEW periodic table of chemical elements. Striking wall chart $3.00. **CIRCLON,** Greenriver George, Enumclaw, WA 98022

NAME brand test equipment. Up to 50% discount. Free catalog and price list. **SALEN ELECTRONICS,** P.O. Box 82, Skokie, IL 60076

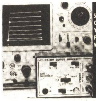

EC-101 CURVE TRACER

STILL BY FAR THE LOWEST COST FULL FUNCTION CURVE TRACER ON THE MARKET. ATTACHES TO YOUR SCOPE IN SECONDS. USED BY EDUCATORS, PROFESSIONALS AND HOBBYISTS ALL OVER THE WORLD. 30 DAY MONEYBACK GUARANTEE.

lab science

$49.50 ADD $2 P&H

COLO. RES. ADD 3½% SALES TAX

PO BOX 1972, BOULDER, COLO. 80306

PRINTED CIRCUIT

Positive Acting Photo Resist; Carbide bits; Bubble etchers; Artwork; Epoxy Glass Boards.

Send stamp & address label for flyer

TRUMBULL
833 Balra Dr., El Cerrito, CA 94530

PET owner need information? Send SASE for details. **TIS,** Box 921, Los Alamos, NM 87544

ELECTRONIC parts! Refundable $1 gets you 1978 catalog. Send to: **B.C. ELECTRONICS,** P. O. Box 226, West Lynn, MA 01905

PARTS! CORNELL TUBES!

FREE Send For FREE CORNELL'S New Color Catalog 48 Pgs. New Items

33¢ per tube IN LOTS OF 100

36¢ per tube

ORDER FREE IF NOT SHIPPED IN 24 HOURS

4215 E UNIVERSITY AVE. SAN DIEGO, CALIF. 92105

System Power Supplies

PSI: ±15 @ .5A, 5V @ 2.5A, and 0–35V with 24V @ .5A,
PS2: ±15V @ .3A, 5V @ 3.3A, and 0–16V with 12V @ 1A

Both have four excellently regulated voltages (resister programmable). From three winding; compare. Great for home computer, bench or hobby work. Just add AC cord and plug 'em in. Assembled; PS1 or PS2 $27.95.
Kit (less transformer); PSK1 or PSK2 **$19.95.**
$2.00 postage & handling; in Calif. add 6% sales tax.

PLUS+ Electronics, 1260 El Camino No.306
Millbrae Ca. 94030

TUBES: "Oldies," Latest. Supplies, components, schematics. Catalog free (stamp appreciated). **STEINMETZ,** 7519—RE Maplewood, Hammond, IN 46324

WIRE wrap wire. #30 Kynar White. 100' $1.50; 500' $5.00; 1000' $9.00. Microlab/FXR AJ310N Attenuator. 500 MHz to 6 GHz, "N" in-out. Micrometer adjustment. $22.50 each. All ppd. Send 25¢ for picture flyer. U.S. only. **STARTRONICS,** Box 683, McMinnville, OR 97128

B&K test equipment. Free catalog. Free shipping. Dinosaur discounts. **SPACETRON-DE,** 948 Prospect, Elmhurst, IL 60126

RECORDS-TAPES! Discounts to 73%; all labels; no purchase obligations; newsletter; discount dividend certificates; 100% guarantees. Free details. **DISCOUNT MUSIC CLUB,** 650 Main St., Dept. 3-0578, New Rochelle, NY 10801

MICROCOMPUTER COMPONENTS

DYNAMIC RAMS

1103	1024X	1 BIT	300 NS		1.50
2104	4096X	1 BIT	300 NS	(16 pin)	4.50
2107A	4096X	1 BIT	300 NS	(22 pin)	3.75
2107B	4096X	1 BIT	200 NS	(22 pin)	4.50
TMS4050	4096X	1 BIT	300 NS	(18 pin)	4.50
TMS4060	4096X	1 BIT	300 NS	(22 pin)	4.50
4116	16KX	1 BIT	200 NS	(16 pin)	40.00
MM5270	4096X	1 BIT	200 NS	(18 pin)	5.00

MICROPROCESSORS

Z80	8 BIT CPU	(3880) (2MHz)	24.00
Z80A	8 BIT CPU	(4 MHz)	35.00
CDP1802P	8 BIT CPU		24.00
AM2901	4 BIT CPU		22.95
6502	8 BIT CPU		12.95
6800	8 BIT CPU		19.95
8080-1	8 BIT CPU		8.75
8080A	8 BIT CPU		15.95

UARTS

AY-5-1013A	5.00
AY-5-1014A	8.00
TR-1602A	5.50
TMS-6011	6.95
IM-6402	10.00
IM-6403	10.00

SPECIALS OF THE MONTH

I.C. SOCKETS ON SALE !!

14 PIN S/T	10 FOR	$2.00
16 PIN S/T	10 FOR	$2.40
14 PIN W/W	10 FOR	$3.50
16 PIN W/W	10 FOR	$4.00
28 PIN S/T	5 FOR	$3.50
28 PIN W/W	5 FOR	$4.50

T.I. LED DISPLAY SPECIAL

TIL 305

5 X 7 Alphanumeric $3.50 ea.

TiL 311

Hexadecimal with Logic $4.50 ea.

TIL 306

7 Seg with Logic $6.70 ea.

(Counter, Latch, Decoder, and Driver built-in)

TIL 308

7 Seg with Logic $4.75 ea.

(Latch, Decoder, and Driver built-in)

8080A Support Devices

8212	3.00
8214	9.00
8216	4.00
8224	4.00
8228	8.00
8238	7.00
8251	11.00
8253	26.00

6800 SUPPORT

6810P	4.50
6820P	7.50
6828P	10.50
6834P	15.00
6850P	9.00
6852P	10.50
6860P	14.00
6862P	15.00
6880P	2.50

STATIC RAMS

21L02	1KX	1 BIT	450 NS	1.40
21L02	1KX	1 BIT	250 NS	1.80
21L11	256X	4 BIT	450 NS	4.00
2101-1	256X	4 BIT	450 NS	2.50
2114	1KX	4 BIT	300 NS	10.50
4200A	4KX	1 BIT	250 NS	11.00

PROMS

1702A	4.50	2716	32.00
2704	15.00	5203AQ	3.50
2708	16.00	5204AQ	5.00

KEYBOARD ENCODER

AY-5-2376	88 keys	13.00
AY-5-3600	90 keys	12.00

Z80 SUPPORT DEVICES

3881 Parallel 1/0 Controller	12.00
3882 Counter Timer Circuit	12.00

CHARACTER GENERATORS

2513	UP (5 volt)	9.00
2513	DOWN (5 volt)	9.00
MCM6574		14.00
MCM6575		14.00

MINIMUM ORDER $10.00. California residents add 6% sales tax.
All orders add 10% postage for out of state. Overseas countries add 15% of total order for postage.
SEND CHECK OR MONEY ORDER TO:

FORMULA INTERNATIONAL INC.
12603 CRENSHAW BOULEVARD • HAWTHORNE, CALIFORNIA 90250
For more information please call (213) 679-5162
STORE HOURS 10-7 Monday - Saturday

CIRCLE 45 ON FREE INFORMATION CARD

SUPER 15 WATT AUDIO AMP KIT

ONLY $23.50 each

Uses STK-015 Hybrid Power Amp

Kit includes: STK-015 Hybrid IC, power supply with power transformer, front Amp with tone control, all electronic parts as well as PC Board. Less than 0.5% harmonic distortion at full power ½dB response from 20–100,000 Hz. This amplifier has QUASI–Complimentary class B output. Output max is watt (10 watt RMS) at 4Ω.

30MHZ FREQUENCY COUNTER KIT

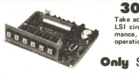

Model 250-30A

Take advantage of this new state-of-the-art counter featuring the many benefits of custom LSI circuitry. This new technology approach to instrumentation yields enhanced performance, smaller physical size, drastically reduced power consumption (portable battery operation is now practical), dependability, easy assembly and revolutionary lower pricing!

Only $59.50

Includes all parts,
PC Board and Transformer

- 0.5" red LED 6 digits display
- Resolution: 1 Hz at 1 sec. 10 Hz at 1/10 sec.
- Sensitivity: 10 Mv RMS to 30 Hz
- Internal power supply: 5.2V at 1 amp regulated
- Input connector: BNC type
- Input power required: 117V AC 50/60 Hz
- Diode protected for over voltage input

CALCULATOR
with STOPWATCH

6 Functions with % and memory
8 Digits big green display
*Built-in X'tal controlled stop watch count to 1/10 of a second.

Special Price Only
$16.50 Ea.
BATTERIES NOT INCLUDED

1Watt AUDIO AMP

All parts are pre assembled
on a mini PC Board
Supply Voltage 6 ~ 9V D.C.
SPECIAL PRICE $1.95 ea.

"FISHER" 30 WATT STEREO AMP
(15W X 2)

Kit includes: 2 pcs. Fisher PA 301 Hybrid IC all electronic parts with PC Board. Power supply: ± 16V DC (not included). Power band with (KF = 1% ± 3dB). Voltage gain: 33dB, 20Hz – 20KHz.

Super Buy Only $22.50 each kit

5W AUDIO AMP KIT

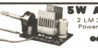

2 LM 380 with Volume Control
Power Supply 6 ~ 18V DC

only $5.00 ea.

TIMER KIT

Time Controlled from 1-100sec.

Ideal to be used as time delay unit for burglar alarm, photo service, and other purposes. Max. loading 110V, 2 AMP. Supply voltage 12-18V D.C.

FT-80 ELECTRONIC IC TIMER **$11.50 each**

ELECTRONIC ALARM SIREN

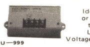

AU—999

COMPLETE UNIT
Ideal for use as an Alarm Unit, or hookup to your car back-up to make a reverse indicator
Light Output up to 130 dB.
Voltage Supply 6~12V **$7.50**

19 KEY HEXADECIMAL KEY PAD

- 1–0
- Homekey
- ABCDEF
- ←→Key

SPECIAL $10.50 ea.

Low Cost Hexadecimal 16 Key Pad

Designed for Calculator
Can be used for Computer
Data Entry Pad or Digital Lock
All key tops blank with super good touch feeling **$0.95 ea.**

DIGITAL ELECTRONIC LOCK KIT

$6.50 ea.
CMOS I.C.
IN CIRCUIT

for auto ignition, entry door, burglar, alarm, etc.
4 Digits Programable to Any Combination

400Ω RELAY AND KEY PAD NOT INCLUDED

POWER SUPPLY KIT

0-30V D.C. REGULATED

Uses UA723 and ZN3055 Power TR output can be adjusted from 0-30V, 2 AMP. Complete with PC board and all electronic parts.

0-30 POWER SUPPLY **$10.50 each**

Transformer for Power Supply, 2 AMP 24V x 2 $6.50
30V DC Panel Meter $4.20

MA1003, 12V DC CLOCK MODULE

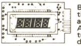

Built in X'TAL controlled time base. Protected against automotive volt transients. Automatic brightness control with 0.3" green color display. Display turnoff with ignition "OFF".

$19.50

MECHANICAL DIGITAL CLOCK

WITH DAY AND DATE OF THE WEEK

This clock is beautifully designed. Case is made from high quality die cast alloy. Movement is the popular flip type with a back up light.

Supply Voltage 110V AC. limited quantity **$15.50 ea.**

QUARTZ CRYSTALS

1 MHZ	$4.95
2 MHZ	$5.25
4 MHZ	$5.25
10 MHZ	$5.25
3.579 MHZ Color TV Type	$1.25

ELECTRONIC SWITCH KIT

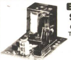

CONDENSER TYPE
Touch on Touch Off
use 7473 I.C.
and 12V relay
$5.50 each

VHF MODULATOR

For TV Game or Computer

This unit converts the Video Signal to RF Signal
Video Input IVDC RF Output 1.5 MV
61.25 MHZ (channel 3)
Frq. Adjustable + 3 MHZ

ONLY $4.50

TI 1955
Alternative AY3-8500-1
6 Game (28 Pin Dip)
TV Game Chip with Data
Tennis Squash hockey, practice & 2 shooting.
Special Only $6.50

PC Board for TV Game with Data $2.50 ea.
Switch Box between Game & TV $1.25 ea.

LED ALARM CLOCK

COMPLETE UNIT
NOT A KIT

- 0.5" RED LED READ OUT
- 24 HRS. ALARM SET
- 10 MINS. SNOOZE SET
- AM/PM ALARM INDICATORS
- SECOND DISPLAY SWITCH
- AUTOMATIC BRIGHTNESS CONTROL
- COMPACT AND HANDSOME PACKING
- 110V AC 60HZ INPUT

$17.50 EACH

5" MUFFIN FAN

HEAVY DUTY
5 Blade Type
110V 50/60HZ
Case made of Die-Cast metal used but almost brand new
SPECIAL PRICE $9.60 ea.

BIPOLAR LED

Jumbo Size red/green change color when reverse polarity of voltage. Ideal for go/nogo indicator.

Two for $1.00

I.C. TEST CLIPS

Same as the E-Z clips
With 20" Long Leads
In Black and Red Colors
$2.75 per pair

12V D.C. AUTO DIGITAL CLOCK

Complete Unit
Not a Kit!

0.4" blue color 4 digits display. Turn off readouts when car is not running. X'tal controlled time base for time accuracy. Special designed case for easy mounting on top of your dashboard. Ideal for car, boat and campers.

ONLY $28.50 ea.

WIRE WRAPPING TOOL

$29.50

Wire Wrapping In Bulk

100'	$2.00
500'	$8.50

Sub Mini Size PANEL METER

500 UA
ONLY $1.20 ea

PANEL METER (D.C. Type)

$5.50 ea.

Size 60MM X 66MM
White Face Type

0-50 UA	0-30V
0-1MA	0-50V
0-5MA	0-100V
0-100MA	

TRANSFORMERS

ALL 117 VOLT INPUT

12V CT		2-5 amp	$5.50 ea.
24V CT		2-5 amp	$6.50 ea.
36V CT		2-5 amp	$6.50 ea.
48V CT		2-5 amp	$6.50 ea.
12V or 24V	at	2 amp	$3.90 ea.
24V CT	at	800MA	$1.80 ea.
0.8V–12V	at	400MA	$1.80 ea.

AC POWER SUPPLY

Adapter Type Transformer
12V AC Output 200 MA
$2.75 each

6V DC	Output	130MA	$1.90 ea.
8.7V DC	Output	130MA	$1.90 ea.
12V DC	Output	100MA	$1.90 ea.

150UA METER

only
$1.50 ea.

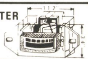

HOUR INDICATOR

This unit is 1 5/8" long operating voltage 4V D.C. will tell you how many hours your circuit or machine has been in service up to 100 hours.

Limited Quantity ONLY $1.75 ea.

DIGITAL CASSETTE TAPE C-60

Type A – With Leader Tape
Type B – Without Leader Tape
- Without B.O.T. E.O.T.
- 60 Minutes Recording Time
- Write Enable Tab
- ANSI Notch
- ANSI Support Plane

COMPUTER RECORDING
All these tapes made in U.S.A. by a top cassette tape Co.
Never Recorded—Reg. $6.80 ea.
3 packs/$5.00
Can be used in Audio Recording as well.

SOUND ACTIVATED SWITCH

All parts completed on a PC Board
SCR will turn on relay, buzzer or trigger other circuit for 2 ~ 10 sec. (adjustable)
Ideal for use as door alarm, sound controlled toys and many other projects
Supply voltage 4.5V ~ 9V D.C.
$1.75 ea./2 for $3.00

Sub-Mini Size Condenser Microphone

$2.50 each
FET Transistor Built-in

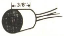

SIGMA 78REI, 12DC RELAY

400Ω COIL SPDT
$1.30 ea. or 10 for $10.00
ALL BRAND NEW UNITS

COMPUTER GRADE CAPACITORS

5,600	MFD	60V	$2.20 ea.
9,000	MFD	50V	$3.25 ea.
11,500	MFD	75V	$3.95 ea.
34,800	MFD	50V	$4.25 ea.
85,000	MFD	25V	$4.10 ea.
100,000	MFD	6V	$3.50 ea.

HEAVY DUTY CLIP LEADS

10 pairs – 5 colors
Alligator clips on a 22" long lead. Ideal for any testing.

$1.85/pack

MINI-SIZED I.C. AM RADIO

Size smaller than a box of matches!!
Receives all AM stations
Batteries and ear phone included

Only $8.50

MINI-MINI

TOGGLE SWITCH

Half-size of submini toggle switch rated 3 amp 125V AC contact

		1–9	10–99
MS 2432P	SPST	0.90	0.80
MS 244	SPDT	1.00	0.90
MS 245	DPDT	1.20	1.10

LARGE QUANTITY AVAIL FOR OEM

SUBMINIATURES TOGGLE SWITCHES

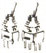

SPDT	On Off	$1.30 ea.
DPDT	On Off	$1.50 ea.
3PDT	On Off	$1.75 ea.

Mini Size Rocker Type
Also Available at the Same Price

JOY STICK

only $5.50

4 100K Volume pot in one unit, vary resistance proportional to the angle of the stick. Perfect for electronic games or model remote control.

PUSH-BUTTON SWITCH

N/Open Contact
Color: Red, White, Blue, Green, Black. **4/$1.00**
N/Close also Available **50¢ ea.**
LARGE QTY. AVAILABLE

SOLID STATE ELECTRONIC BUZZER

Mini Size 1"x3/4"x3/4"
Supply voltage 1.5V 12V
Ideal for Alarm or Tone Indicator
$1.50 each

MINIMUM ORDER $10.00. California residents add 6% sales tax.
All orders add 10% postage for out of state. Overseas countries add 15% of total order for postage.
SEND CHECK OR MONEY ORDER TO

FORMULA INTERNATIONAL INC.

12603 CRENSHAW BOULEVARD • HAWTHORNE, CALIFORNIA 90250
For more information please call (213) 679-5162
STORE HOURS 10-7 Monday - Saturday

master charge

your BANKAMERICARD welcome

CIRCLE 29 ON FREE INFORMATION CARD

MOBILE NOISE

continued from page 50

the same kind of choke shown as L1 in Fig. 7. The choke is a common stock item available in car radio repair shops or in stereo sales outlets. Those made by Delco seem to have a lower DC resistance for a given inductance. A DC resistance of 0.20 ohms may not seem like much, until you key the transmitter and draw 30 amperes through the coil. Even if it didn't burn up (it will!), the voltage drop by Ohm's law would be 6 volts. This technique can be used successfully with a low-powered 2-meter mobile rig, but if you have a high-powered transmitter, it is advisable to separate the DC lines from the receiver section, if possible, and bring them out on their own connectors.

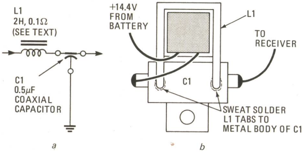

FIG. 9—L-SECTION FILTER shown in *a* is added to power supply line feeding radio. L-section filter is constructed as shown in *b*.

Inductive and capacitive pickup

Up to this point we have discussed almost every type of noise encountered in automotive installations. The sources that remain are often very difficult to locate, although most are easy to fix once found.

Figure 10 shows one example. The exhaust pipe on your car may reradiate noise, and if it is of the correct length, it may also resonate the noise components inside the RF band. This problem is particularly prevalent in 10-meter and 11-meter CB installations. The solution is to ground the tailpipe. It is generally assumed that the tailpipe is already grounded at the engine, but three other factors can contribute to interference: gaskets, rust and the tailpipe length being close to a one-quarter wavelength. Install ground clamps every few feet to reduce the severity of this problem.

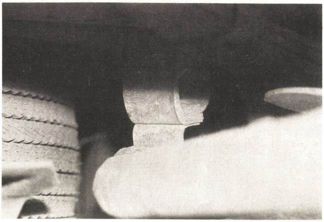

FIG. 10—INSULATED TAILPIPE HANGERS can make tailpipe RF source.

The chrome strips on some cars can also cause motor noise in mobile rigs. If the strips are an appreciable fraction of a wavelength on the band of interest, then it could reradiate if the grounding action of the holding clamps is reduced by corrosion or loss of the clamps. This was the cause of a very tiring and most perplexing source of noise that I had to troubleshoot once many years ago. I still get a backache just thinking about it!

Noise detector

Channel Master has developed a device that is probably the first tool specifically designed to track down sources of motor noise. This is the *model 5270* RF noise detector, also called the *Sleuth* and shown in the head photo.

The *Sleuth,* which sells for about $17, is approximately 25 inches long, and 1 inch in diameter. It has a 17-foot coaxial cable fitted at the free end with a PL-259 coaxial connector. This connector is attached to the radio's antenna connector, so that the receiver can be used as a noise indicator. **Do not key the transmitter with the *Sleuth* connected!**

When the *Sleuth,* which is nothing more than a directional RF detector, comes in close contact with the offending noise source, it lets you know through the radio speaker. The device will pinpoint noise sources wherever they are located, even most reradiation sources; such as the tailpipe, the emergency brake cable, a wire or cable bundle or the various rods and linkages passing through the firewall. Most reradiation problems can be then cured by grounding, bypassing or shielding. **R-E**

COMPUTER CORNER

continued from page 83

similar action to $\overline{\text{NMI}}$. The locations for the two interrupt processing routines for $\overline{\text{NMI}}$ and $\overline{\text{IRQ}}$ are held in memory locations FFFA/FFFB$_{16}$ and FFFE/FFFF$_{16}$, respectively. They, of course, must be initialized by the program before any interrupt can occur. (This also means that if interrupts are used in the system, there *must* be a small segment of memory in address area FFFX$_{16}$).

The remaining two lines are $\overline{\text{RES}}$ and SO. $\overline{\text{RES}}$ is an input whose action is similar to that of an interrupt. When the line is brought from low to high, the reset sequence is entered. The CPU loads the CPU *program counter* with the contents of memory locations FFFC/FFFD$_{16}$ to start program execution at a meaningful place. Signal SO is an input signal that allows external logic to set an *overflow* flip-flop in the CPU and is normally not used.

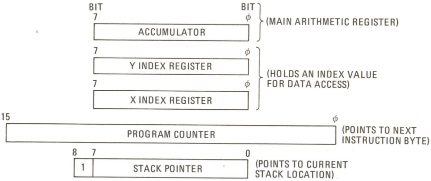

CPU registers

Figure 3 shows the CPU registers that are accessible to the user. The primary arithmetic register is an 8-bit *accumulator.* Arithmetic and logic operations, such as adds or exclusive OR's, are performed between the contents of the accumulator and other operands.

The *program counter* register is 16 bits wide and controls memory addressing for program instructions. As each instruction is executed, the program counter is incremented by one to point to the next byte of the instruction or to the next instruction, operating identically with other microprocessors such as the 6800 or the 8080.

An 8-bit *stack pointer* register points to the *memory stack,* an area of RAM set

continued on page 116

ADVANCED COMPUTER PRODUCTS

THE FIRST TO OFFER PRIME PRODUCTS TO THE HOBBYIST AT FAIR PRICES NOW LOWERS PRICES EVEN FURTHER!

1. Proven Quality Factory tested products only, no re-tests or fallouts. Guaranteed money back. We stand behind our products.

2. Same Day Shipment All prepaid orders with cashiers check, money order or charge card will be shipped same day as received.

MOTOROLA 6800 COMPATIBLE MODULES

MEK 6800 D2 KIT	$235.00
9600 6800 MPU	595.00
9601 16 Slot Mother Bd.	175.00
9602 16 Slot Card Cage	75.00
9603 8 Slot Mother Bd.	100.00
9610 Proto Board	36.00
9615 4K EPROM Module (1702A)	250.00
9620 16 Port Parallel I/O	375.00
9626 8K Static RAM Module	295.00
9626K 8K Static RAM Kit	225.00
9630 Extender Card	60.00
9650 8 Port Duplex Asyn Serial I/O	395.00
Connectors $6.50	6/84.00

All assembled & tested not Kits

PLUS MOTOROLA TV MONITORS-PRIME

Model M3560-155 L01 12" display	219.95
Model M2000-155 9" display	199.95

Add $10.00 for shipping

LOGOS 8K STATIC MEMORY

$125.99 Kit

Assembled & tested	$179.95
250 ns. Kit	149.95
Assembled & tested	199.95

Features: Lowpower, Dip Switch Selectable memory protect down to 256 Bytes, addressing on 1K Boundaries, No wait states, fully buffered, battery back-up.

NOW 1 Year Field Experience

SPECIAL OFFER:
Buy 4 Units Only $117.00 ea.

BYTEUSER 8K EPROM $64.95

Assembled & tested	$ 94.95
Bare PC Board w/Data	21.95
8K EPROM (8) 2708	$112.00

Features: Power on Jump, Reset Jump, all socketed with top quality PC Board material.

SPECIAL OFFER:
Buy 4 Units Only $59.95 ea.

Z-80 CPU KIT $129.95 Kit

Low Price
(regular price 269.95)

Assembled & tested $199.95

FEATURES:
S-100 IMSAI/Altair compatible, completely compatible to TDL hardware and software. Can be used at 4MHz with Z-80A.
Add $7.00 for sockets.
Add $5.00 for Z80 manual.

NOW IN STOCK
FOR IMMEDIATE SHIPMENT.

DATA BOOKS

NSC Digital	$ 3.95
NSC Linear	4.95
NSC Linear A/N Vol. I	2.95
NSC Linear A/N Vol. II	2.95
NSC CMOS	2.95
NSC Audio	2.95
NSC Voltage Reg	2.95
NSC Memory	3.95
Intel Data Book	3.95
Intel MCS 85 Manual	4.95
Intel MCS 80 Manual	7.95
Intel MCS 40 Manual	4.95
AMD 8080 Microproc. Handbook	7.95
AMI MOS Catalogue	3.95
Raytheon Linear	2.50
Raytheon Quads/Duals	1.95
GI MOS Catalogue	4.95
Osborne Intro to Micro Vol 0	7.50
Osborne Intro to Micro Vol I	7.50
Osborne Intro to Micro Vol II	15.00
Osborne 8080 Programming	7.50
Osborne 6800 Programming	7.50
Osborne Z80 Programming	7.50

AMI 6800 KIT EVK 99

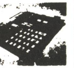

only $133.00

Send for complete details

EVK 99 Kit	$133.00
EVK 100 Kit	269.95
EVK 200 Kit	449.95
EVK 300 Assembled	699.00
Universal Kluge Board	95.00
16K Byte RAM Board	75.00
6 Slot Motherboard	35.00
Extender Board	45.00
Video Board (avail. future)	95.00
Connectors $6.50	12/59.95
Solid Frame Chassis	120.00
Frame Chassis	69.95
Micro Assembler ROM	30.00
Proto ROM	30.00
Tiny Basic Papertape	20.00
Tiny Basic EPROM	125.00
Hardware or Programming Manuals	15.00 ea.

8080A CPU KIT $99.95 Kit

Assembled & tested $129.95

FEATURES:
S-100 bus compatible, complete CPU with eight level vector interrupt. Includes sockets.
Add $5.00 for 8080 Manual

16K SUPERFAST RAM'S

µp D 416/4116 350ns. PRIME

Buy 8 pcs. – Only **$29.95 each**

Buy 16 pcs. – Only **$27.95 each**

Larger quantity or group buys call for current price quote.

TARBELL FLOPPY INTERFACE

Complete Kit Only	$179.95
Assembled & tested	$269.95

FEATURES: S100/Altair/IMSAI compatible, compatible to most disc drives including Persci, Innovex, GSI, Shugart and others.

SOFTWARE: Uses CPM which is available for $70.00
CPM documentation add $20.00

Same Day Shipment

NAKED PC BOARD SALE S-100

Z-80 CPU	$31.95
2708 EPROM 8K	21.95
8K Static RAM	21.95
32K Static RAM	59.95
Floppy I/O	$39.95
Cassette I/O	29.95
Proto Bd.	27.95
Extender	15.95

UV "EPROM" ERASER

Model UVS-11E only $59.95

Holds (4) chips at a time. Special holding tray with UVA Absorber. Exclusive safety interlock system.

Backed by 45 years UV experience.

WOW 1771 FLOPPY SPECIAL

$32.95

While they last $32.95
regular price $55.95

Western digital P/N 1771A with App. Note & Data

Only 100 units available

MICROPROCESSORS

● Z-80	$21.95
Z-80A	29.95
F-8 (3850)	19.95
2650	24.95
CD1802	19.95
8080A	12.95
8085	29.95
8008-1	14.95
2901	21.95
2901A	29.95
TMS 9900JL	89.95
CP1600	39.95
6502	19.95
IM6100	29.95
● 6800P	19.95
6802P	32.95

SUPPORT DEVICES

● 3881 (Z80 PIO)	$12.95
● 3882 (Z80 CTC)	12.95
3851 (F8 Program)	14.95
3853 (F8 Memory I/O)	14.95
8212 8 bit I/O	3.50
8214 Priority Interrupt	9.95
8216 Bus driver	3.75
8224 Clock Gen.	4.85
8224-4 4MHz CLK Gen.	12.95
● 8T26 Busdriver	2.25
8226 Busdriver	3.95
8228 Sys Controller	7.95
8238 Sys Controller	9.95
8251/9551 Prog. Comm. I/O	11.95
8253 Interval Timer	21.95
8255/9555 Prog. Periph. I/O	11.95
8257 DMA Control	32.95
8259 Prog. Interrupt	32.95
6810-1 128 × 8 RAM	4.95
● 6820 PIA	7.95
6834-1 EPROM 4K	14.95
6834 EPROM 4K	16.95
6850 ACIA	9.95
6852 Serial Adapter	11.95
6860 Modem	14.95
6862 RPS Modulator	17.95
● 6871B 1.0 MHz Clock OSC	26.95
6880 MPU Busdriver	2.95
68 MinII Minibug 2	49.95
68 MinIII Minibug 3	74.95
6831/10224 Micro Assembler Rom	30.00
6831/11003 Proto Rom	30.00
1821SCD 1K RAM	15.95
1822SCD 256 × 4 RAM	16.95
1824CD 32 × 8 RAM	9.95
1852CD 8 bit I/O	10.95
1856CD I/O	8.95
1857CD I/O	8.95

PROM'S

● 2708	$14.95
2708S 650ms.	9.75
1702A	7.95
● 1702-6	3.50
5204	16.95
● IM5610	2.95
6834	16.95
6834-1	14.95
82S123	2.95
82S126	4.50
82S129	2.95
8223	2.95
5203	6.95

Programming Available

RAMS DYNAMIC

● 4115	$18.95
4116 16K	34.95
TMS4050	4.95
TMS4060 22 pin	4.25
WD4060 22 pin	3.25
4096 16 pin	4.95
2104	4.95
2107	3.95
● 2107B-4	4.25
MM5261	3.95
MM5262	1.95
MM5270	4.95
MM5280	4.95
1103	1.95
4008 L	2.95

FLOPPY DISK

WD 1771 Floppy	32.95
WD 1771 B01	52.95

CHARACTER GENERATORS

R032513 Upper 5V	$10.95
R032513 Lower 5V	9.95
HD0165	9.95
MC6571A	10.80
MC6574	14.50
MC6575	14.50

KEYBOARD ENCODERS

AY52376	$14.95
AY53600	14.95

UARTS/USRTS

AY51013A (5V)	$ 5.50
TR1602B (5V)	4.50
AY51014 (5-14V)	8.95
AY51015 (5V)	9.95
IM6402 (5V)	12.95
IM6403 (5V)	12.95
S2350	10.95
WD1671B Astros	19.95

BAUD RATE GENERATORS

MC14411	$11.95
WD1941 Dual	9.95
34702	13.95

TV CHIPS

● MM5320 TV Synch	$ 9.95
MM5369 Prescaler	3.95
MM57100 Game Chip	16.95
MM57104 Clock	3.75
LM1889 Modulator	3.95
CW300 Saw Function	1.50
AY38500-1 TV Game	9.95
AY38600-1 Color TV Game	24.95
AY38615-1 Color Converter	8.95
● AY38700-1 Tank Chip	29.95
RF Modulator	8.95

ORGAN CHIPS

MM5554 MM5555 MM5556	(1 each)	NSC Set $19.95

CLOCK CHIPS

MM5314	$ 4.95
MM5316	4.95
MM5375	4.95

STATIC RAM HEADQUARTERS

We maintain largest inventory of Static Rams in the West

	1-24	25-99	100				
● 21L02 (450 ns.)	1.30	1.25	1.15	2114 (450 ns.)	14.95	14.25	13.45
21L02 (250 ns.)	1.95	1.80	1.50	4200A	12.95	12.25	11.45
2102	1.25	1.15	1.10	● upD410 (4200)	10.95	10.50	9.95
2102-1	1.30	1.25	1.15	4402	12.95	12.25	11.65
91L02APC	1.75	1.65	1.50	5101C-E	11.95	11.25	10.25
21L11-1	4.25	4.10	3.95	74C89	3.25	3.05	2.85
2111-1	4.10	3.95	3.85	7489	2.25	1.99	1.88
2112-1	3.00	2.80	3.69	8599	1.88	1.75	1.63
21L01-1	2.95	2.85	2.75	74S189	4.50	4.30	4.25
2101-1	2.95	2.85	2.75	74S200	4.50	4.30	4.25
2114 (650 ns.)	12.95	12.25	11.45	74S201	4.50	4.30	4.25
				1101A	1.49	1.29	1.10
				3107	3.95	3.70	3.25

A TO D CONVERTORS

8700CJ	$13.95
8701CN	21.95
8750CJ	13.95
1408L8	5.95
● 148L6	3.95

DISPLAYS/OPTO

DL 704/707 CC/CA .300	1.25
FND359 CC .357	.95
FND 500/507 CC/CA .500	1.35
FND 503/510 CC/CA .500	.95
FND 800/807 CC/CA .800	2.50
Bowmar 9 digit bubble	.99
FSC 8024 4 digit CC .800	4.95
HP7340 HEX Display	15.95
TIL 305 5 × 7 Array	4.50
TIL 306 7 seg w/logic	8.95
TIL 308 7 seg w/logic	8.95
TIL 309 7 seg w/logic	7.95
TIL 311 HEX Display	9.25
MA1003 12 auto clock	17.95
MA1002 4 digit clock module	9.95
MA1010 4 digit clock module	9.95
NSN 373/374 dual CC/CA .300	2.20
NSN 583/584 dual CC/CA .500	2.60
NSN 783/784 dual CC/CA .700	3.00
4N25 Opto Isolater	3/1.99
MCT 2 Opto Isolater	.89
4N33 Darlington ISOL	1.75
Red Led's .185 Dia.	5/1.00
Green/Yellow	4/1.00

SOCKETS

8 Pin ww	.32	8 Pin S/T	.17
14 Pin ww	.37	14 Pin S/T	.20
16 Pin ww	.38	16 Pin S/T	.22
18 Pin ww	.60	18 Pin S/T	.31
20 ww	.90	22 Pin S/T	.35
22 Pin ww	.93	24 Pin S/T	.41
24 Pin ww	.93	28 Pin S/T	.49
40 Pin ww	1.45	40 Pin S/T	.63

CONNECTORS

6 Pin Single S/E	1.49
15/30 Dual S/E	1.95
18/36 Dual S/E	2.35
22/44 Dual S/E	2.95
43/86 Dual S/T	6.50
43/86 Dual W/W	6.50
50/100 IMSAI W/W	4.75
50/100 IMSAI S/T	4.75
50/100 Altair W/W	5.95
50/100 Actair S/T	5.95

25 Pin-D Subminature

DB25P	3.25
DB25S	3.75
Hood	1.25

IMSAI Card Guides 4/1.00

RS232
CONNECTOR
SET
W/Hood
$6.50

CRYSTALS

1.0MH$_3$	$ 5.85	10.0MH$_3$	4.95
2.0	5.85	13.0	4.95
2.097152	5.85	14.31818	4.95
2.4576	5.85	18.0	4.95
3.579545	3.95	18.432	5.95
4.0	4.95	20.0	4.95
4.194304	5.95	22.1184	5.95
4.91520	5.95	27.000	5.95
5.0	4.95	36.000	5.95
5.7143	5.95	48.000	5.95
6.0	4.95	100KC	12.95

NEW CTS DIPSWITCHES

CTS206-4	$1.75	CTS208-8	$1.95
CTS206-5	$1.75	CTS209-9	$1.95
CTS206-6	$1.75	CTS209-10	$1.95
CTS207-7	$1.75		

We also stock full of 7400, 74LS, 74L Linear and CMOS Send for pricing or use our competitors STD catalog pricing.

NEW
1978 CATALOGUE
AVAILABLE FEB.
SEND .25 POSTAGE

74LS00 TTL

74 LS00	.22	LS86	.55	LS163	1.39	LS367	.99
LS02	.24	LS90	1.10	LS164	1.39	LS368	.99
LS04	.24	LS92	1.10	LS174	1.39	LS377	1.29
LS05	.28	LS93	1.10	LS175	1.39	74200	5.95
LS08	.28	LS95	1.69	LS190	2.49	74251	1.69
LS10	.28	LS107	.56	LS191	2.49	74279	1.10
LS13	.79	LS109	.56	LS192	2.49	74298	1.99
LS14	1.69	LS112	.56	LS193	2.49	74365	.79
LS20	.26	LS113	.56	LS194	2.49	74366	.79
LS27	.38	LS123	.99	LS195	.52	74367	.79
LS30	.26	LS132	1.10	LS251	1.39	74368	.79
LS32	.34	LS136	.99	LS253	1.49	LS378	1.29
LS40	.26	LS138	1.39	LS257	1.29	81LS95	1.10
LS42	1.10	LS139	1.49	LS258	1.29	81LS96	1.10
LS51	.26	LS151	1.49	LS279	1.10	81LS97	1.10
LS73	.56	LS153	1.29	LS283	1.10	81LS98	1.10
LS74	.56	LS155	1.49				
LS75	.79	LS157	1.29				
LS76	.59	LS158	1.29				
LS83	1.69	LS161	1.39				
LS85	1.99	LS162	1.39				

MONTHLY SPECIALS

up D371 Mag Tape Control	$49.95
AY5-3550 4-3/4 Digit DVM	24.95
MK5007/5009 Counter	6.95
AY5-3507 DVM Chip	12.95
ICM7208IPI Ctr./Disp/Driv.	16.95
ICM7209 IPI Ctr/Driver	19.95
ICM7045 IPI Stop Watch	18.95
G115M 6 Channel MOS FET SW.	1.50
4116/416 16K Dynamic RAM	34.95
Intel 3404 6 bit Latch	2.95
1488/1489 RS232 Driver	1.25
8T97 Buffer	1.25
8130/8131	2.45
8833/8835	1.99
74367/74368	6/5.00
75451/52/53	10/2.50
8T26	2/4.50
78L05	2/1.00
LM318H	1.00

4N25 Opto/Iso .69

SPECIAL 7/$1.00

7405 MPS6530
7416 MPS3568
7438 MPS6516
7440 MPS6522

SPECIAL 2/$1.00

7442 74123
7490 74145
7493 74153
7495 74LS195

MCT2	$ .89	MPS3642	5/1.00
2N3638A	5/1.00	MPS6571	5/1.00
2N3640	5/1.00	MPS3693	5/1.00
2N2369A	5/1.00	MPS6530	5/1.00
2N3692	5/1.00	MPS3646	5/1.00
MSPS4318	5/1.00	7525J	.50
MPS5401	5/1.00	7524J	.60
MPS6516	5/1.00	74S258	.60
MPS6544	5/1.00	7489	1.49
MPS3568	5/1.00	74145	.60
MPS6522	5/1.00	74H55	.19
MPS404A	5/1.00	715DC	1.49
2N5462	5/1.00	74199	1.00

COMP KITS & SYSTEMS:

MEK6800D2 Kit	$235.00
KIM1 6502	245.00
EVK99 6800 Kit	133.00
Technico 9900 Kit	299.00
Intercept Jr. 6100 Kit	281.00
Iasis 8080 Computer Book	499.00
NSC SC/MP Kit	99.00
NSC Keyboard Kit	95.00
Low Cost S-100-BUS with 8 slots & Power Supply	159.95
8K Ram Kit (Logos I)	125.95
Byteuser 8K Eprom Kit	64.95
ZPU Kit (Z80)	295.00
TDL ZPU Kit (Z80)	269.00
Tarbell cassette I/O	115.00
S100 8 slot Motherboard with connectors (expandable)	69.95
S100 Extender Board	15.95
S100 Proto Board	27.95
Vector 8800 Proto Board	19.95
IMSAI 8080 w/22 slot	699.00
Cromemco Z-2	595.00
TDL XITAN alpha 1	769.00
Computalker	385.00
Heuristics Speechlab	299.00
SOROC IQ120 Terminal	995.00
8K Ram Board (Logos)	21.95
8K Eprom Board	21.95
S100 32K Ram Kit	875.00
Bytesaver Kit	145.00

NOTICE

We are looking for software support packages to offer in our new catalogue. Please write or call if you want to participate.

All Shipments FCM or UPS. Orders under $100.00 add 5% handling and postage. Orders over $100.00 add 2.5% handling & postage. Mastercharge/Bankamericard/COD accepted w/25% deposit. California Residents add 6% tax. Foreign Orders add 8% handling. All parts prime factory tested guaranteed. Same day shipment. Add 25 cents for Data.

Retail pricing may vary from Mail Order Pricing

P. O. BOX 17329 Irvine, California 92713 New Phone (714) 558-8813
TELEX/TWX: 910-595-1565

Retail Store Open Mon. – Sat.
Located at 1310 "B" E. Edinger,
Santa Ana, CA 92705

CIRCLE 11 ON FREE INFORMATION CARD

FREE catalog. Video taped movies. Write **NPC**, Box 321, Maple Shade, NJ 08052

AUDiO & MUSIC SYNTHESIS
Experimenter
Write for our FREE flyer today.

GET THE FACTS

We offer ideas, kits, plans, parts, with new developments and stuff daily.

CFR ASSOCIATES
Box F
Newton NH 03858

COMPUTER CORNER

continued from page 114

aside to hold data temporarily and to store the program-counter contents during interrupts and program subroutines. Unlike the 8080, this stack area is predefined in a *page* of memory located from 0100 to $01FF_{16}$. As in the interrupt/reset cases, this memory area must be available and dedicated in the system.

The remaining two CPU registers are two 8-bit index registers. One of the great advantages of the 6502 is that it has a variety of addressing modes, or ways to access memory data. Indexing is a common access method on larger computers; here, the 6502 makes two registers available for indexing, making it easy for the program to acquire contiguous data.

6502 instructions

There are 55 basic instructions in the 6502, but since there are 13 addressing modes there are many more unique instructions than the 55. (See Table I.)

Arithmetic instructions include an add, compare, subtract, AND, OR and exclusive OR. There are several instructions that are devoted to transferring data between CPU registers and memory, or other CPU registers. The remaining instructions are concerned with conditional branching, stack operations and subroutines. Although the 6502 does not contain any spectacular instructions (such as the Z-80 block instructions), the overall instruction repertoire, especially when you consider the 6502's powerful addressing capability, makes for a well-designed versatile microprocessor.

The 6502 is by no means *over*designed. It is an efficient microprocessor IC, easy to program at an assembly-language level and much simpler to interface than the 8080. Since there are many microcomputers built around the 6502 with much software available, you should consider it if you're buying or designing a new system. **R-E**

P.O. Box 4430E Santa Clara, CA 95054
For will call only: (408) 988-1640
2996 Scott Blvd.

Quest ELECTRONICS

Same day shipment. First line parts only. Factory tested. Guaranteed money back. Quality IC's and other components at factory prices.

INTEGRATED CIRCUITS

7400TTL	
7400N	.17
7402N	.17
7404N	.19
7409N	.23
7410N	.17
7414N	.63
7420N	.17
7422N	1.39
7430N	.20
7442N	.50
7445N	.69
7447N	.60
7448N	.69
7450N	.17
7474N	.29
7475N	.49
7485N	.88
7489N	2.00
7490N	.43
7492N	.43
7493N	.43
7495N	.69
74100N	.90
74107N	.29
74121N	.34
74123N	.59
74125N	.39
74145N	.69
74150N	.95
74151N	.69
74154N	1.00
74157N	.69
74161N	.87
74162N	.87
74163N	.87
74174N	.96
74175N	.90
74190N	1.15
74192N	.87
74193N	.85
74221N	1.55
74298N	1.65
74365N	.66
74366N	.66
74367N	.66
74LS00 TTL	
74LS00N	.25
74LS02N	.25
74LS04N	.25
74LS05N	.25
74LS08N	.25
74LS10N	.25
74LS13N	.40
74LS14N	.90
74LS20N	.25
74LS22N	.25
74LS28N	.41
74LS30N	.25
74LS33N	.39
74LS38N	.30
74LS74N	.35
74LS75N	.47
74LS90N	.51
74LS93N	.51
74LS95N	1.89
74LS107N	.35
74LS112N	.35
74LS113N	.35
74LS132N	.72
74LS136N	.35
74LS151N	.67
74LS155N	.67
74LS157N	.67
74LS162N	.91
74LS163N	.91
74LS174N	.95
74LS190N	1.06
74LS221N	1.95
74LS258N	.67
74LS367N	.89
LINEAR	
CA3045	.90
CA3046	.67
CA3081	1.80
CA3082	1.90
CA3089	2.95
LM301AN/AH	.35
LM305H	.87
LM307N	.35
LM308N	.89
LM309H	1.15
LM309K	.95
LM311H/N	.90
LM317T/K	2.92
LM318	1.35
LM320K-5	1.20
LM323K-5	6.95
LM320K-12	1.35
LM320K-15	1.35
LM320T-5	1.60
LM320T-8	1.60
LM320T-12	1.50
LM320T-15	1.60
LM324N	1.15
LM339N	1.55
LM340K-5	1.10
LM340K-8	1.10
LM340K-12	1.10
LM340K-15	1.10
LM340K-24	1.10
LM340T-5	1.10
LM340T-8	1.10
LM340T-12	1.10
LM340T-15	1.10
LM340T-18	1.10
LM340T-24	1.10
LM343H	4.50
LM370	1.15
LM377	4.50
LM379	5.00
LM380N	1.00
LM381	1.60
LM382	1.60
LM703H	.40
LM709H	.28
LM723H/N	.50
LM733N	.67
LM741CH	.35
LM741N	.25
LM747H/N	.62
LM748N	.35
LM1303N	.82
LM1304	1.10
LM1305	1.27
LM1307	2.00
LM1310	2.75
LM1458	.47
LM1800	1.75
LM1812	7.50
LM1889	3.00
LM2111	1.75
LM2902	1.50
LM3900N	.60
LM3905	1.75
LM3909N	.61
MC1458V	.50
NE540L	2.89
NE550N	.65
NE555V	.43
NE556A	.79
NE565A	1.00
NE566V	1.15
NE567V	1.20
78L05	.60
78L08	.60
79L05	.70
78M05	.85
75108	1.75
75491CN	.50
75492CN	.55
75494CN	.89
A to D CONVERTER	
8038B	4.50
8700CJ	13.95
8701CN	22.00
8750CJ	13.95
LD130	9.95
9400CJV/F	7.40
ICL7103	9.50

CMOS	
CD34001	.50
CD4000	.16
CD4001	.21
CD4002	.21
CD4006	1.10
CD4007	.21
CD4008	.21
CD4009	.39
CD4010	.39
CD4011	.21
CD4012	.21
CD4013	.36
CD4014	.86
CD4015	.86
CD4016	.36
CD4017	.94
CD4018	.94
CD4019	.21
CD4020	1.02
CD4021	1.02
CD4022	.86
CD4023	.21
CD4024	.75
CD4025	.21
CD4026	1.51
CD4027	.36
CD4028	.79
CD4029	1.02
CD4030	.21
CD4035	1.02
CD4040	1.02
CD4042	.71
CD4043	.63
CD4044	.63
CD4046	1.67
CD4049	.36
CD4050	.36
CD4051	1.13
CD4060	1.42
CD4066	.71
CD4068	.40
CD4069	.40
CD4070	.40
CD4071	.21
CD4072	.21
CD4073	.21
CD4075	.21
CD4076	1.75
CD4078	.40
CD4081	.21
CD4082	.21
CD4116	.47
CD4490	5.50
CD4507	1.00
CD4508	4.25
CD4510	1.02
CD4511	.94
CD4515	2.52
CD4516	1.10
CD4518	1.02
CD4520	1.02
CD4527	1.51
CD4528	.79
CD4553	5.75
CD4566	2.25
CD4583	4.50
CD4585	1.10
CD40192	3.00
74C00	.28
74C04	.33
74C10	.28
74C14	2.10
74C20	.28
74C30	.28
74C48	2.95
74C74	.75
74C76	1.40
74C90	1.15
74C93	1.40
74C154	3.00
74C160	1.44
74C175	2.00
74C192	2.40
74C221	2.75
74C905	3.00
74C906	1.50
74C914	1.95
74C922	7.50
74C923	7.50
74C925	10.50
74C926	10.50
74C927	10.50
INTERFACE	
8095	.65
8096	.65
8097	.65
8098	.65
8T09	1.25
8T10	4.50
8T13	3.00
8T20	5.50
8T23	3.10
8T24	3.50
8T25	3.20
8T26	1.69
8T28	2.75
8T97	1.69
8T98	1.69
MOS/MEMORY	
RAM	
2101-1	4.50
2102-1	1.28
2102AL-4	1.60
21F02	1.85
2104A-4	3.95
2107B	4.00
2111-1	4.95
2112-2	7.90
MK4116	34.95
2513B	8.75
21L02-1	1.49
MM5262	.40
MM5320	5.95
MM5330	5.94
PD411D-3	4.00
PD411D-4	5.00
P5101	13.95
4200A	15.95
82S25	2.90
91L02A	2.50
HD0165-5	6.95
MM57100	9.50
GIAY38500-1	13.95
MCM6571A	10.95
9368	3.00
CLOCKS	
MM5309	3.00
MM5311	3.60
MM5312	4.80
MM5313	3.60
MM5314	3.90
MM5315	4.00
MM5316	5.00
MM5318	8.95
MM5369	2.10
MM5841	14.45
MM5865	7.95
CT7001	5.80
CT7002	8.95
CT7010	8.95
CT7015	7.25
MM5375AA/N	3.90
MM5375AB/N	4.90
7205	16.50
DS0026CN	3.75
DS0056CN	3.75
MM53104	2.50

IC SOCKETS

Solder Tin		Low Profile	
PIN	1 UP	PIN	1UP
8	.15	24	.36
14	.18	28	.43
16	.20	36	.58
18	.27	40	.61
22	.35		

3 level wire wrap gold.
14 pin .35 16 pin .39
2 level 14 pin ww .25

MICROPROCESSOR	
6800	24.50
8080A with data	11.50
Z80	29.95
8212	3.50
8214	8.00
8216	3.85
8224	3.50
8228	6.25
8251	11.50
8255	10.75
CDP1802CD	19.95
CDP1802D	25.00
CDP1861	12.95
6820	12.00
6850	15.00
6502	24.50
UART/FIFO	
AY5-1013	5.50
AY5-1014	7.50
3341	6.95
PROM	
1702A	3.95
N82S23	2.95
N82S123	3.50
N82S126	3.75
N82S129	3.75
N82S131	3.75
N82S136	8.75
N82S137	8.75
2708	16.50
DM8577	2.90
8223	2.90
2716	36.00
CONNECTORS	
44 pin edge	2.00
100 pin edge	4.50
100 pin edge WW	5.25
CRYSTALS	
1 MHz	4.50
2 MHz	4.50
4 MHz	4.25
5 MHz	4.25
10 MHz	4.25
18 MHz	3.90
20 MHz	3.90
32 MHz	3.90
32768 Hz	4.00
1.8432 MHz	4.50
3.5795 MHz	1.20
2.0100 MHz	1.95
2.097152 MHz	7.75
2.4576 MHz	7.50
3.2768 MHz	7.50
5.0688 MHz	4.50
5.185 MHz	4.50
5.7143 MHz	4.50
6.5536 MHz	4.50
14.31818 MHz	4.25
18.432 MHz	4.50
22.1184 MHz	4.50

CLOCK MODULES Complete alarm clocks ready to hook up with transformer and switches. Very compact with .50" and .84" digits.

MA1002A, C or E .50"	**8.95**
102P3 Transformer	**2.25**
MA1010A, C or E .84"	**11.95**
102P2 Transformer	**2.25**
Special transformer and six switches when purchased w/module	**2.95**
MA1003 car module .3" green fluor. display	**17.50**
Fair MCS 6300 .63"	**9.95**

RESISTORS ¼ watt 5%
10 per type .03 1000 per type .012
25 per type .025 350 piece pack
100 per type .015 5 per type 6.75

KEYBOARDS
Hex keyboard $10.95. Fully encoded w/ PC board, parts and instructs. $29.95
53 key ASCII keyboard kit 55.00
Fully assembled 65.00 Enclosure 14.95

LEDS	
Red T018	.15
Green, Orange, Yellow T018	.20
Jumbo Red	.20
Green, Orange, Yellow Jumbo	.25
Cliplite LED Mounting Clips	8/$1.25

(specify red, amber, green, yellow, clear)

CONTINENTAL SPECIALTIES in stock
Complete line of breadboard test equip.
MAX-100 8 digit Freq. Ctr. $128.95

OK WIRE WRAP TOOLS in stock
Portable Multimeter $18.00

DIGITAL THERMOMETER $48.50
Batt. oper. General purpose or medical 32°–230°F. Disposable probe cover ±.2° accuracy. Comp. assy. in compact case.

COMPUTER BOARD KITS	
8K RAM Board Kit	$134.95
4K EPROM Kit	114.95
I/O Board Kit	44.50
Extender Board w/connector	12.50
Video Interface board kit	125.00
16K EPROM board kit w/o PROMS	74.50
16K Static RAM board kit	395.00
North Star Floppy Disk Kit	$665.00
Additional Drive Kit	415.00

SPECIAL PRODUCTS	
MM5865 Stopwatch Timer	9.00
PC board	7.50
Switches Mom. Pushbutton	.27
3 pos. slide	.25
Encoder HD0165-5	6.95
3 Digit Universal Counter Board Kit Operates 5–18 Volt DC to 5 MHz typ. .125" LED display	**10.50**
Voice actuated switch	.50
Paratronics 100A Logic Analyzer Kit	**$199.00**
Model 10 Trigger Expander Kit	$299.00
Model 150 Bus Grabber Kit	$369.00
TRANSFORMERS	
12 Volt 300 ma transformer	1.25
12.6V CT 600 ma	3.75
12V 250 ma wall plug	2.95
12V CT 250 ma wall plug	3.50
24V CT 400 ma	3.95
10V 1.2 amp wall plug	4.85

DISPLAY LEDS			
MAN1	CA	.270	2.90
MAN3	CC	.125	.39
MAN72/74	CA/CA	.300	1.00
DL704	CC	.300	1.25
DL707/DL707R	CA	.300	1.00
DL727/728	CA/CC	.500	1.90
DL747/750	CA/CC	.600	1.95
DL750	CC	.600	1.95
FND359	CC	.357	.70
FND500/507	CC/CA	.500	1.35
FND503/510	CC/CA	.500	.90
FND800/807	CC/CA	.800	2.20
3 digit Bubble			.60
4 digit bubble			.80
DG8 Fluorescent			1.75
DG10 Fluorescent			1.75
5 digit 14 pin display			1.00
NSN33M 3 digit 8 pin			.39
NSN69 9 digit display			.60
7520 Clairex photocells			.39
TIL311 Hex			9.50

IC Test Clips	1	10
Red	.55	.47
Black	.55	.47

Keyer 8043 14.50
comp. w/spec./sock.

Sinclair 3½ Digit Multimeter
Batt. oper. 1mV and .1NA resolution. Resistance to 20 meg. 1% accuracy. Small, portable, completely assem. in case. 1 yr. guarantee. Best value ever! **$59.95**

Not a Cheap Clock Kit $14.95
Includes everything except case. 2-PC boards. 6-.50" LED Displays. 5314 clock chip, transformer, all components and full instrucs. Green and orange displays also avail. **Same kit w/.80" displays. $21.95**

Digital Temperature Meter Kit
Indoor and outdoor. Automatically switches back and forth. Beautiful. 50" LED readouts. Nothing like it available. Needs no additional parts for complete, full operation. Will measure −100° to +200°F, air or liquid. Very accurate. Complete instructions. **$39.95**

NiCad Batt. Fixer/Charger Kit
Opens shorted cells that won't hold a charge and then charges them up, all in one kit w/full parts & instruc. **$7.25**

RCA Cosmac VIP Kit 249.00
Video computer with games and graphics.

'78 IC Update Master Manual
1978 IC Update Master Manual **$30.00** Complete IC data selector 2175 pg. Master reference guide. Over 42,000 cross references. Free update service through 1978. Domestic postage $3.50. Foreign $6.00. Final 1977 Master closeout **$15.00**

New Cosmac Super "ELF"
RCA CMOS expandable microcomputer w/HEX keypad input and video output for graphics. Just turn on and start loading your program using the resident monitor on ROM. Pushbutton selection of all four CPU modes. LED indicators of current CPU mode and four CPU states. Single step op. for program debug. Built in pwr. supply, 256 Bytes of RAM, audio amp. & spkr. Detailed assy. man. w/PC board & all parts fully socketed. Comp. Kit **$106.95** High address display option **8.95**; Low address display option **9.95**; Custom hardwood cab.; drilled front panel **19.75** Nicad Battery Backup Kit w/all parts **4.95** Fully wired and tested in cabinet **151.70** 1802 software xchng. club; write for info.

4K Elf Expansion Board Kit with Cassette I/F $79.95
Available on board options: 1K super ROM monitor **$19.95** Parallel I/O port **$7.95** RS232 I/F **$3.50** TTY 20 ma I/F **$1.95** S-100 Memory I/F **$5.30**

Tiny Basic for ANY 1802 System
Kansas City Standard Cassette $10.00
On ROM Monitor $38.00
Super Elf owners take 30% off.

Original Cosmac "ELF" kit
All parts and instructs. **$89.50**
Board only **14.95**

Video Modulator Kit $9.95
Convert your TV set into a high quality monitor without affecting normal usage. Complete kit with full instructions.

60 Hz Crystal Time Base Kit $4.75 Converts digital clocks from AC line frequency to crystal time base. Outstanding accuracy. Kit includes: PC board, MM5369, crystal, resistors, capacitors and trimmer.

Clock Calendar Kit $23.95
CT7015 direct drive chip displays date and time on .6" LEDS with AM-PM indicator. Alarm/doze feature includes buzzer. Complete with all parts, power supply and instructions, less case.

2.5 MHz Frequency Counter Kit Complete kit less case **$37.50**
30 MHz Frequency Counter Kit Complete kit less case **$47.75**
Prescaler Kit to 350 MHz **$19.95**

Stopwatch Kit $26.95
Full six digit battery operated. 2–5 volts. 3.2768 MHz crystal accuracy. Times to 59 min., 59 sec., 99 1/100 sec. Times std., split and Taylor. 7205 chip, all components minus case. Full instruc. Molded plastic case with bezel. **$5.00**

Auto Clock Kit $15.95
DC clock with 4-.50" displays. Uses National MA-1012 module with alarm option. Includes light dimmer, crystal timebase PC boards. Fully regulated, comp. instructs. Add $3.95 for beautiful dark gray case. Best value anywhere.

TERMS: $5.00 min. order U.S. Funds. Calif residents add 6% tax. BankAmericard and Master Charge accepted. Shipping charges will be added on charge cards.
FREE: Send for your copy of our NEW 1978 QUEST CATALOG. Include 24¢ stamp.

CIRCLE 27 ON FREE INFORMATION CARD

Electronic Warning Flasher Kit
This battery operated device continuously emits bursts of intense light. Great safety device for bicycle riders, skiers, hikers, boaters & campers. Comes complete w/ all electronic parts, quality glass-epoxy P-C board & easy to understand instructions. Uses high-output xenon flash tube which flashes 2 times per second when batteries are fresh. Operates continuously for 12 hours on 2 alkaline "C" batteries. You need only to supply the batteries and, if desired, a battery holder & case.
C23207 $6.95
(3 for $18.00)

Strobe Light Kit
COMPLETE variable-rate strobe light kit. Contains all parts, including line cord, PC board and instructions. Operates on 117 VAC. $7.50 each

6 KV TRIGGER COILS 2 for $1
required to "fire" xenon flash tubes.

Green Neon
Same as NE2 but glows GREEN. Operates on 120V.
6 for $1.00

NEW
LIQUID CRYSTAL WATCH DISPLAY
WITH SPECS. $1.25
MOTOROLA MLC500

SLIDE SWITCH ASSORTMENT
20 for $1.00

MV109 TUNING DIODE
2 for $1.00

LASCR
200 VOLT
.3 AMP.
C23063 4 for $1.00

MICRO-MINIATURE ROTARY SWITCH
1 POLE,
8 POSITION
79¢

HONEYWELL STROBE 14" SHUTTER CORD $1.00

Electronic Flash Unit Guide no. 28 ASA 25.
SALE
These were to be installed in cases but the final assembly was never completed. You get a complete working flash unit. Operates on 2 AA penlight batteries. You need only supply a shutter cord, battery holder & batteries, & if desired, some sort of case. Appx. overall size of circuit board, reflector & capacitor: 3" x 2½" x 1½".
$3.95 C22867

PHOTOFLASH CAPS

350 mf	330V	1.00
720 mf	360V	1.50
520 mf	500V	2.00

REFLECTOR
Metal matte finish round reflector for electronic flash, strobes, slave lights, etc.
3-3/4" Dia. x 1-7/8"
$ 2.00

STROBE TUBE ASST.
Brand new factory prime strobe tubes. Assortment of 5 strobe tubes, w/ schematics
C23280
$ 2.00

5V REED RELAY SPST	$1.00
5V REED RELAY SPDT	1.50
JUMBO YELLOW LED	5/$1.00
78L05 5V REG.	5/$1.00
400V 8AMP SCR HSE#	3/1.00

CHANEY electronics
- Minimum order $5.00
- Please include $1 for postage
- Visa, MC and COD accepted.
- Phone orders are welcome.

P.O. BOX 27038, DENVER, CO. 80227 Ph: (303) 973-1052
Send for our FREE GIANT CATALOG of unique items !!!!

CIRCLE 74 ON FREE INFORMATION CARD

hobbi house

Send for Free Hobbi House Catalog
969 BALL AVE., UNION, N.J. 07083
Retail Store Open Mon.–Sat., 9 to 6

TERMS AND CONDITIONS

Add $1.50 postage and handling for all orders within U.S.. COD orders -- add $2.00 for postage and handling.

$7. Min. order. Phone orders accepted. $15 Min B.A./Visa, Master Charge orders. N.J. Residents add 5% Sales Tax

Outside Continental U.S. send U.S.funds only, and include sufficient postage for first class mail.

OPTO SPECIALS

Cat. #	Order by Cat. # & Type #	
01	7 seg. Display .33" 707 MAN 1 C.A. or C.C.	**.59 ea. or 10/$5.00**
03	Diffused Jumbo Red Leds 0.2"	**.7/$1.00, 100/$11.00**
04	DL741 Jumbo Displays C.A.	**$1.35**
05	25PK LEDS ASSTD Sizes & Colors	**$2.50**
06	Jumbo Red Leds	**10/$1.00, 100/$9.00**
07	9 digit display by National	**$1.00**

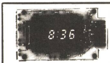

MA1003
MOBILE CLOCK MODULE (National)
$18⁹⁵ complete

Attaches directly to 9-12V Battery. Automatic Nighttime Dimming. Fluorescent Display gives Color Choice (Red, Blue, Green or Yellow) when used w/corresponding Color Filter. Includes — Module, Switches, & Filter

ALUMINUM CASE WITH FILTER. $5.75 (switches included with clock kit). In Silver, Black and Gold. Filter colors — red, blue, green, or yellow.

LM555 TIMERS 3/.99

SWITCHES

Cat. #	Order by Cat. # & Type #	
M9	**Sound Actuated Switch**	**.85**
M10	**Dry Reed Switch,** 5 AMP, 115 VAC	**.25/$1.98**
M13	**250 K Slide Volume Control** By Mallory	**.4/$1.00**
M51	**DPDT Momentary Slide Switch**	**10/$1.00**
M52	**DPDT Slide Switch** Low Profile	**10/$1.00**
M53	**DPDT Slide Switch** Long Button	**10/$1.00**
M56	**DP4T Slide Switch**	**10/$1.00**

ADAPTORS

Cat. #	Order by Cat. # & Type #	
M16	**AC DC** 120 V input 6 UDC 130 MA output	**$1.00**
M65	**AC Input** 120 VAC, 3.7w/output 9 UDC, 100 MA	**$1.50**

SPECIALS

Cat. #	Order by Cat. # & Type #	
M12	**6" Pioneer Pincusion speakers,** 3.2 OHMS, 7½ watts	**$3.95 a pair**
M17	**8 FT. Stereo Extension Cord.** RCA plugs at both ends.	**2/$1.99**
M33	**16 Pin Strip sockets,** By AMP	**10/$1.00**
M41	**6 FT. Line Cords**	**6/$1.00**
M49	**6 DC Battery Holder**	**3/$1.00**
M29	**SPDT 12 Volt Relay** 5 AMP contact, Plug in style	**$1.00**
M35	**Variable Trimmer Cap** 3-18 PF, 50 volt	**5/$1.00**
M48	**2.5 MEG Trimmer Pot**	**5/$1.00**
M69	**50K Trim Pot,** Pc mount thum wheel	**10/$1.00**

Your Store for Prime Components — Money Back Guarantee on all Orders!
Toll-Free Wats Line — 800-631-7485 • Open Saturdays
In New Jersey Call (201) 964-5206

lowest prices

Zener Diodes

Cat. #	Order by Cat. # & Type #	
D1	5.1V 1 watt	**10/$1.00**
D4	22V 1 watt	**10/$1.00**
D5	3.9V 400MW	**10/$1.00**
D7	6.8V 400MW	**10/$1.00**
D8	8.2V 400MW	**10/$1.00**
D10	30V 400MW	**10/$1.00**
D11	10V 1 Watt	**10/$1.00**

Rectifiers

Cat. #	Order by Cat. # & Type #	
D2	IN1084	**.4/$1.00**
D3	IN4384	**10/$1.00**
D6	IN645	**10/$1.00**
D13	35AMP 50V DO-5 Case	**2/$1.00**
D14	25AMP 200V Bridge Rect.	**$1.75**
D23	IN4148 Switching Diode	**50/$1.00**
D16	IN4001	**10/.55**
D17	IN4002	**10/.65**
D18	IN4003	**10/.75**
D19	IN4004	**10/.85**
D20	IN4005	**10/.95**
D21	IN4006	**10/$1.00**
D22	IN4007	**10/$1.00**

DISC Caps

Cat. #	Order by Cat. # & Type #	
C1	680 MMF 500V±10%	**20/$1.00**
C2	200 MMF 500V±10% P.C.	**20/$1.00**
C3	390 MMF 400V±10%	**20/$1.00**
C4	220 μμF 500V±10% P.C.	**20/$1.00**
C5	820 PF 1000V±10% P.C.	**20/$1.00**
C6	27 PF 500V±10%	**20/$1.00**
C7	470 μF 2kV±20%	**20/$1.00**
C8	470 PF 2kV±20%	**20/$1.00**
C34	.03 μF 100V±20% P.C.	**20/$1.00**
C41	16 μμF 500V±5% P.C.	**20/$1.00**
C42	.001 PF 100V±10% P.C.	**20/$1.00**
C45	.1 MF 50V±10%	**20/$1.00**
C47	15 PF 100V±10% P.C.	**20/$1.00**
C49	22μF 750V±10% P.C.	**20/$1.00**
C52	22 PF 500V±10%	**20/$1.00**
C54	100 PF 100V±10%	**20/$1.00**
C57	16 PF 500V±5% P.C.	**20/$1.00**
C59	22 PF 150V±10% P.C.	**20/$1.00**
C61	22 PF 200V±10%	**20/$1.00**
C62	33 PF 100V±5%	**20/$1.00**

IC SOCKETS.

Cat. #	Order by Cat. # & Type #	
M1	Grain of Wheat Display Lamps	**10/$1.00**
M2	8 PIN	**5/$1.00**
M3	14 PIN	**5/$1.00**
M4	16 PIN	**5/$1.00**
M5	18 PIN	**5/$1.00**
M6	24 PIN	**2/$1.00**
M7	28 PIN	**2/$1.00**
M8	40 PIN	**2/$1.00**

Transformers

Cat. #	Order by Cat. # & Type #	
M22	**Mini Audio** 1" square	**10/$1.99**
M32	**70 Volt** Line Transformer, 10 watts	**$2.90**
M40	**6.3 Volts** 1.2 amp	**$1.49**

Transistors

CAT #	Order by Catalog # & Type #	
T1	2N918 ITT	**5/$1.00**
T2	2N2904 ITT	**5/$1.00**
T3	2N2219 ITT	**5/$1.00**
T4	2N4949 House #	**2/$1.00**
T5	MPS5172 MOTO	**10/$1.00**
T6	2N3638 S.S.	**10/$1.00**
T7	2N2102 House #	**5/$1.00**
T8	3N140 Fet N Channel	**2/$1.00**
T9	2N2907 ITT	**5/$1.00**
T10	2N914 ITT	**5/$1.00**
T11	2N2369A ITT	**10/$1.00**
T12	2N2368 ITT	**10/$1.00**
T13	2N706 MOTO	**10/$1.00**
T15	D41E1 Ge P. C.	**10/$1.00**
T16	2N3416 Sprague	**5/$1.00**
T17	MPS2369 ITT	**10/$1.00**
T18	MPS3704 ITT	**10/$1.00**
T19	2N708 MOTO	**5/$1.00**
T20	2N3055 S. S.	**2/$1.00**

Electrolytics — all Axial Leads

CAT. #	Order by Cat. # & Type #	
C15	.15μF 400 V	**5/$1.00**
C16	1μF 50 V	**5/$1.00**
C17	10μF 50 V	**5/$1.00**
C18	1.0μF 200 V	**5/$1.00**
C19	25μF 25 V	**5/$1.00**
C20	5/F 25 V	**5/$1.00**
C21	500μF 15 V	**5/$1.00**
C22	1500μF 3V	**5/$1.00**
C24	1000μF 6V	**5/$1.00**
C25	2000μF 2.5V	**5/$1.00**
C40	500μF 50V	**4/$1.00**
C46	4.7μF 50V	**4/$1.00**
C53	4.7 μF 35 V	**4/$1.00**
C56	220μF 16 V	**4/$1.00**
C63	1000MFD 35V	**4/$1.00**

Tantalum, Axial Leads

Cat.#	Order by Cat. # & Type#	
C13	.047μF 200 V	**10/$1.00**
C44	1MF 35V	**10/$1.00**
C48	15μF 35V	**10/$1.00**

Voltage Regulators

Cat. #	Order by Cat. # & Type #	
1C1	7805 Pos.	**$1.00**
1C2	7815 Pos.	**$1.00**
1C3	7806 Pos.	**$1.00**
1C4	7905 Neg.	**$1.25**
1C5	7812 Pos.	**$1.00**
1C6	7824 Pos.	**$1.00**
1C7	7915 Neg.	**$1.25**

Mylar Caps

Cat.	Order by Cat. # & Type #	
C9	1.0 100V±5%	**10/$1.00**
C11	.018MF 400V±10%	**10/$1.00**
C12	.47μF 100V±10%	**10/$1.00**

SPECIAL

WESTINGHOUSE TUBES—BOXED AND BRANDED

1V2	1.50
2AV2	2.00
3A3C	3.10
3AT2B	3.00
3CU3A	3.75
3DB3/3CY3	3.30
3HM5/3HA5	2.50
5GH8A	2.75
6AQ5A	2.00
6AU6A	2.00
6BK4C/EL4A	4.50
8BL8/ECF80	1.75
6CG3/W3/Q3	2.50
6CJ3/6CH3	2.50
6DW4B	2.50
6EA8	2.50
6EJ7/EF184	2.20
6EW6	2.20
6FQ7/6CG7	1.85
6GF7A	3.20
6GH8A	2.00
6GJ7/ECF801	2.25
6GM6	2.50
6GU7	2.50
6HB7	2.40
6HM5/6HA5	2.30
6HZ6	2.00
6JC6A	2.65
6JS6C	4.50
6JU8A	2.60
6KD6	4.90
6KE8	3.60
6KT8	3.25
6KZ8	2.40
6L6GC	3.60
6LB6	4.75
6LQ6/6JE6C	4.85
6Z10/6J10	4.30
8FQ7/8C67	2.00
12AT7/ECC81	2.00
12AU7/ECC82	2.00
12AX7/ECC83	2.00
12BY7A/V/Q	2.20
12HG7/6N7A	3.30
17JZ8	2.50
23Z9	3.00
33GY7A	3.75
36MC6	5.00
38HE7	3.85

CIRCLE 55 ON FREE INFORMATION CARD

INTEGRATED ELECTRONICS

5100 El Camino Real, Los Altos, CA 94022. (415) 969-7827

QUALITY SERVICE ECONOMY

Best parts at low prices — Immediate service

WE ARE A NEW COMPANY DEDICATED TO THE SERVICE OF THE HOBBYIST, EXPERIMENTER, STUDENT & INVENTER.

We offer—

Full line of IC's from the largest manufacturers
Sockets, tools, wires and other accessories
Calculators and digital watches

THIS MONTH'S SPECIAL—

21L02 – $1.50 each, 10 up
TI-59 Program Calculator – $225.00
This is not subject to 10% discount below

Introductory Offer—

Order from us at your price and save 10% more. Here's how— List all the IC's you need. Price them from any ad in this magazine. Total them and discount 10%. Add 5% shipping charges.

Write for free catalog

Minimum order $5.00 US currency. Check or money order only. Add 5% to cover shipping and handling charges. Calif. residents add 6% sales tax. Santa Clara Co. residents add 6.5% sales tax.

CIRCLE 79 ON FREE INFORMATION CARD

BULLET ELECTRONICS

P. O. BOX 19442R
(214) 823-3240
Dallas, Texas
75219

PHONE ORDERS ON MASTERCHARGE/VISA

8 GOOD REASONS TO BUY FROM BULLET:

1. We are an established company, in business since 1976.
2. Mail order is our *only* business . . . . Full Time.
3. Components & unassembled kits may be returned for full refund.
4. Full repair service on any kit we sell.
5. Our customers are important. We are always available for help.
6. Quality Merchandise-No Junk!
7. We tell it like it is! Parts are as described.
8. We try harder - We want your business from now on.

THE SMALL PRINT

- No COD's
- Check or MO
- MC/VISA
- TX residence add 5% Sales tax
- Orders under $10 add .75 handling
- All orders add 5% for shipping & handling
- Orders over $50 take 10% discount
- Foreign address add 10% for shipping

MOBILE CLOCK CALENDAR KIT

Seems like **everybody** sells digital clock kits, however we have the only low cost **DIGITAL CLOCK / CALENDAR** for Mobile operation. We provide quality plated through hole boards and step-by-step instructions, parts overlays and schematics. This clock has many features and we supply all the parts but a small speaker. Fantastic for car, boat or Van.

- Intergral Timebase (.01% ACC)
- Large 4 DIGIT LED display with AM/PM indicators
- Flashing color at 1HZ rate
- Special noise and overvoltage protection for mobile use
- Auxillary output will drive relay or TRIAC to control external equipment
- 5¾ Wx1¾x2½D
- Built in ignition blanking turns off readouts when not in use
- Presettable alarm with Snooze
- Special "SleepTimer"

23.50 NO CASE

12 VAC XFMR for 110 VAC 1.50
24 Hour Format add 2.00

WE STOCK A COMPLETE LINE OF QUALITY LOW COST PANEL METERS. SEND FOR FREE CATALOG TODAY.

MG-01 ELECTRONIC GRANDFATHER CLOCK

While we are talking about **clocks** check out the MINI GRANDFATHER CLOCK Reviewed in April 1978 RADIO ELECTRONICS. We have the *only* kit in the world with all the below listed features. The biggest problem is to describe how unique and fascinating this timepiece really is! The LED **"Swinging " Pendulum and Matching Tick-Tock Sound** are available only on our clock. In addition the electronic "bell" notes each hour (ie 3 times for 3 o'clock). Housed in the optional Solid Hardwood Case, the unit makes a beautiful addition to any room.

- ½" 4 DIGIT LED READOUT
- Adjustable tone & duration on chime
- Simulated swinging LED Pendulum
- All CMOS Construction
- Quality plated boards
- All electronics switches
- and XFMR included

39.95 KIT **59.95** ASEMB.

Optional Solid Hardwood Case for MG-01 Clock over 10 inches tall. Includes Ruby front. Unassembled.
SOLID HARDWOOD 17.95 SOLID WALNUT 19.95

ULTRASONIC SENDER RECEIVER KIT US-02

TOTAL SECURITY! Completely invisible ultrasonic (23KHZ) Sound beam works like a photoelectric beam but is uneffected by light, heat or noise. Seperate Transmitter and Receiver can be used from 6 inches to 25 feet! A solid object breaking the beam causes an output to go low that will sink up to 150 MA to Drive a Relay, TRIAC, etc. Complete electronics are provided. Works on 12VDC (unregulated) and draws less than 100 MA. Use it for **burgler alarms, object counters, automatic door openers, automatic door bells, electronic rat trap(?) and more.**

COMPLETE KIT LESS CASES **21.50**

Optional entry delay and Alarm Timeout Circuit 3.95 will source or sink up to 200 MA OC.

10 WATT WARBLE ALARM KIT **2.50**

It's hard to believe this little gem puts out 10 Watts of alternating dual tone screams. A real great attention getter. Great for alarms, games, toys, etc.

with PC Board speaker not included Requires 12VDC @ 1A

OTHER GREAT KITS! We have 15A power supplies, CDI's, OVP's, mini mobile clocks, clock-timers,, sound circuits and many more. It's all in our latest catalog.
FREE ON REQUEST

PARTS (many more listed in catalog)

MC1469R	½A positive Voltage Reg.	House#	1.25
MC1351P	FM IF and Sound System		.50
CA3011	Wideband IF Amp IC	House#	.50
MM5375	6 Digit Alarm Clock Chip		2.95
555	Timer & Pulse Gen Chip		.49
741	Op amps 8 pin MINI DIP		.20
LM3900	QUAD OP AMP		.45
723	Pos Voltage Reg DIP		.65
725	Ultra low noise high gain Op amp	House#	.99
NE565A	PLL DIP		.50
TCA430	Quad Audio Oscillator Dip		.69

MJ900, MJ1000, Matched Pair 8A Darlington		Pair/3.00
IN4148	Switching Diodes	25/1.00
2N3569	NPN Silicon Switching	6/1.00
2N2712	NPN Small Signal	8/1.00
2N4343	P Channel J Fet	4/1.00
2N6028	Programmable Unijunction	2/1.00
2N6111	PNP Med Power 30W T0220	3/1.00

ZENER GRAB BAG. A very nice assortment of 10 different voltages between 2.7v and 30 VDC in 400 MW, ½W and 1W. All are prime units but most have Mfg's. numbers. We supply a cross reference sheet to standard numbers.
SPECIAL PRICE 10 pieces 1.00

CAPS

.022	@	100VDC Mylar	8/1.00
.22	@	50VDC Mylar	6/1.00
1.5mfd	@	400VDC Mylar	4/1.00
.1mfd	@	35V Tant Axial	6/1.00
.47mfd	@	35V Tant Axial	6/1.00
2.2mfd	@	35V Tant Axial	5/1.00
22mfd	@	20V Dip Tant	4/1.00
33mfd	@	10V Dip Tant	4/1.00
220mfd	@	25V Alum. Axial	7/1.00
500mfd	@	35V Alum. Axial	5/1.00
1100mfd	@	35V Alum. Axial	4/1.00

HEATSHRINK TUBING
A very good Asst. of 3/32", 1/8" 3/16" & 1/4" in 6 inch lengths 12 pieces total
.75
This item FREE with purchase of 15.00 or more

Miniature 7k Pot w/switch PC Mount or panel mount 1/8" shaft
.49
Black plastic knob for above: FREE

LIMITED QTY Computer Grade FILTER CAP Screw Terminals 2" X 5½" 9500 mfd@75V
2.95 or 4/9.95

SPECIAL SALE
TIL 312 LED Common Anode 7 Segment Readout .3" Character Size Standard Pinout while they last
.65
6/3.00

UNIVERSAL 4Kx8 MEMORY BOARD KIT

$69.95

32-2102-1 fully buffered, 16 address lines, on board decoding for any 4 of 64 pages, standard 44 pin buss, may be used with F-8 & KIM

EXPANDABLE F8 CPU BOARD KIT

$99.00

featuring Fairbug PSU.1K-of static ram, RS 232 interface, documentation, 64 BYTE register

4K BASIC FOR FAIRBUG F8

on paper tape $25.00

C/MOS (DIODE CLAMPED)

4047– 1.50	4012– .16	4023– .16	4046– 1.45
4518– .89	4013– .29	4024– .66	4049– .34
4001– .16	4015– .74	4025– .16	4050– .34
4002– .16	4016– .29	4027– .37	4055– 1.25
4006– .95	4017– .78	4028– .73	4066– .58
4007– .16	4018– .78	4029– .77	4071– .24
4009– .37	4019– .37	4030– .33	4076– .97
4010– .37	4020– .84	4035– .97	74C10– .22
4011– .16	4022– .85	4042– .58	74C193 1.50

2708-8K EPROM (450 ns)	$10.95
2522 STATIC SHIFT RE6	$ 1.95
2513 CHARACTER GEN	$ 6.75
2518-HEX 32 BIT SR	$ 3.50
5203-2K EPROM	$ 4.50
21L02-1 (450 ns)	$ 1.35
21078	$ 3.50
MK 4008P	$ 1.95
5280 4K DYNAMIC RAM	$ 4.75
1702A UV PROM	$ 4.95
5204-4K PROM	$10.95
82S23	$ 1.95
AY-5-1013 UART	$ 6.95
8703C TELEDYNE 3 STAGE BINARY 8 BIT A/D CONVERTER	$13.50
8080A	$11.95

AP PROTO BOARDS USED FOR SOLDERLESS BREADBOARDING

264L	— 128 FIVE-TIE POINT TERMINALS	$12.75
212R	— POWER BOARD	$ 2.50
2248L	— 96 FIVE-TIE POINT TERMINALS	$ 9.75
209R	— POWER BOARD	$ 2.25

IC TEST CLIPS
TC-14 — $4.50 TC-16 — $4.75

CTS 206-8 eight position dip switch $1.90
CTS-206-4 four position dip switch $1.45
LIGHT ACTIVATED SCR's
TO-18, 200V 1A . . . . $ 1.10

SILICON SOLAR CELLS
2¼" diameter .4V at 500 ma $4.00

RS232 CONNECTORS
DB 25P male $2.95
DB 25S female $3.50

LED READOUTS

FND 357 C.C. .4"	$ .50	MAN-7-.3" C.A.	$ .85
FCS 8024 - 4 digit C.C. 8" display	$5.95	DL 747 C.A. .6"	$1.65
FND 503 C.C. .5"	$ .85	FND 800 C.C. .8"	$1.95
FND 510 C.A. .5"	$ .85	FND 807 C.A. .8"	$1.95
DL-704-.3" C.C.	$ .85		

PRINTED CIRCUIT BOARD

4-1/2"x6-1/2" SINGLE SIDED EPOXY BOARD 1/16" thick, unetched
$.60 ea. . . . . 5/$2.60

7 WATT LD-65 LASER DIODE IR $8.95

2N 3820 P FET	$ .45
2N 5457 N FET	$ .45
2N2646	$ .45
ER 900 TRIGGER DIODES	4/ $1.00
2N 6028 PROG. UJT	$ .65

MINIATURE MULTI-TURN TRIM POTS 100, 500, 1K,2K,5K,10K,25K,50K,100K, 200K,500K 1 Meg. $.75 each. . . . . 3/$2.00

WSU-30 Hand wire wrap tool used to wrap, unwrap & strip # 30 wire $5.30

VERIPAX PC BOARD

This board is a 1/16" single sided paper epoxy board, 4½"x6½" DRILLED and ETCHED which will hold up to 21 single 14 pin IC's or 8, 16, or LSI DIP IC's with busses for power supply connector. $4.00

MV 5691 YELLOW-GREEN BIPOLAR LED.	$ .90
FP 100 PHOTO TRANS	$ .50
RED, YELLOW, GREEN or AMBER LARGE LED's .2"	6/$1.00
1L-5 (MCT-2) OPTO-ISOLATOR	$ .75
MOLEX PINS	100/$1.00 1000/$8.00
10 WATT ZENERS 3.9, 4.7, 5.6, 8.2, 18,22,100,150 or 200V	ea. $ .60
1 WATT ZENERS 4.7, 5.6,10, 12, 15 18 or 22V	ea. $ .25
MC6860 MODEM CHIP	$9.95
MCM 6571A 7 x 9 character gen	$10.75

Silicon Power Rectifiers

PRV	1A	3A	12A	50A	125A	240A
100	.06	.14	.30	.80	3.70	5.00
200	.07	.20	.35	1.15	4.25	6.50
400	.09	.25	.50	1.40	6.50	9.50
600	.11	.30	.70	1.80	8.50	12.50
800	.15	.35	.90	2.30	10.50	16.50
1000	.20	.45	1.10	2.75	12.50	20.00

SAD 1024-a REDICON 1024 stage analog "Bucket Brigade" shift register. $18.95

IN 4148 (IN914) . . . . 15/$1.00

MCA 81 OPTICAL LIMIT SWITCH $1.50

REGULATORS

309K	$ .95	340K-12,15 or 24V.	$ .95
723	$ .50	340T-5, 6, 8, 12 15,18 or 24V	$ .95
LM 376	$ .60	78 MG	$1.35
320K-5 or 15V	$1.20	79 MG	$1.35
320T-5, 15 or 24V	$ .95		

TRANSISTOR SPECIALS

2N6233-NPN SWITCHING POWER	$ 1.95
MRF-8004 a CB RF Transistor NPN	**$ 1.50**
2N3772 NPN Si TO-3	$ 1.00
2N1546 PNP GE TO-3	$ .75
2N4908 PNP Si TO-3	$ 1.00
2N6056 NPN Si TO-3 Darlington	$ 1.70
2N5086 PNP Si TO-92	4/$ 1.00
2N404 PNP GE TO-5	5/$ 1.00
2N3919 NPN Si TO-3 RF	$ 1.50
MPSA 13 NPN Si TO-92	3/$ 1.00
2N3767 NPN Si TO-66	$ .70
2N2222 NPN Si TO-18	5/$ 1.00
2N3055 NPN Si TO-3	$ .50
2N3904 NPN Si TO-92	5/$ 1.00
2N3906 PNP Si TO-92	5/$ 1.00
2N5296 NPN Si TO-220	$ .50
2N6109 PNP Si TO-220	$ .55
2N3638 PNP Si TO-5	5/$ 1.00

TTL IC SERIES

7400– .13	7445– .65	74151– .61
7401– .13	7446– .68	74153– .61
7402– .13	7447– .58	74154– .94
7403– .13	7448– .68	74155– .58
7404– .15	7450– .15	74157– .55
7405– .13	7472– .25	74161– .55
7406– .16	7473– .28	74163– .55
7407– .20	7474– .28	74164– .85
7408– .18	7475– .45	74165– .95
7409– .18	7476– .30	74170– 1.68
7410– .13	7480– .31	74173– 1.20
7411– .18	7483– .65	74174– .95
7412– .13	7485– .87	74175– .85
7413– .36	7486– .28	74176– .75
7414– .60	7490– .42	74177– .75
7416– .22	7491– .58	74180– .65
7417– .25	7492– .43	74181– 1.90
7420– .13	7493– .43	74190– 1.00
7425– .25	7494– .67	74191– 1.00
7426– .22	7495– .65	74192– .79
7427– .19	7496– .65	74193– .79
7430– .13	74107– .28	74194– .80
7432– .22	74121– .29	74195– .85
7437– .21	74122– .38	74196– .86
7438– .21	74123– .45	74279– .55
7440– .13	74125– .40	74367– .65
7441– .70	74126– .40	75491– .50
7442– .37	74150– .94	75492– .50

1/2 Hr. DATA CASSETTES $1.25

44 Pin Solder Tail .156" Connector $2.20

MM 5387AA new clock chip which will directly drive LED's 12/24 hrs., 1 supply & alarm $5.95
NO. 24 8 CONDUCTOR SPECTRA FLAT CABLE 10' $1.50 100' $13.50
NO. 30 WIRE WRAP WIRE SINGLE STRAND 100' $1.40

ALCO MINIATURE TOGGLE SWITCHES

MTA 106 SPDT	$ 1.05
MTA 206 DPDT	$ 1.70
MTA 206 P-DPDT CENTER OFF	$ 1.85
MSD 206 P-DPDT CENTER OFF LEVER SWITCH	$ 1.85

Full Wave Bridges

PRV	2A	6A	25A
100			1.30
200	.75	1.25	2.00
400	.95	1.50	3.00
600	1.20	1.75	4.00

DIP SOCKETS

8 PIN .22	24 PIN .40
14 PIN .25	28 PIN .50
16 PIN .28	40 PIN .60
18 PIN .30	

SANKEN AUDIO POWER AMPS

Si 1010 G 10 WATTS	$ 6.80
Si 1020 G 20 WATTS	$13.70
Si 1050 G 50 WATTS	$25.90

TANTULUM CAPACITORS

.22UF 35V	5/$1.00	6.8UF 35V	4/$1.00
.47UF 35V	5/$1.00	10UF 10V	$ .25
.68UF 35V	5/$1.00	22UF 25V	$ .40
1UF 35V	5/$1.00	15UF 35V	3/$1.00
2.2 UF 20V	5/$1.00	30UF 6V	5/$1.00
3.3UF 35V	4/$1.00	47UF 20V	$ .35
4.7UF 15V	5/$1.00	68 UF 15V	$ .50

74LS SERIES		LINEAR CIRCUITS
74LS00 – .21	74LS126 – .47	LM 101 – .75
74LS02 – .21	74LS132 – .80	LM 301/748 .29
74LS03 – .21	74LS136 – .39	LM307 – .30
74LS04 – .28	74LS138 – .70	LM 308 – .75
74LS05 – .28	74LS139 – .70	LM 311 – .75
74LS08 – .21	74LS151 – .70	LM 318 – 1.20
74LS09 – .28	74LS153 – .70	LM 319 – .95
74LS10 – .21	74LS155 – .70	LM 324 – 1.05
74LS11 – .21	74LS156 – .70	LM 339 – 1.10
74LS13 – .44	74LS157 – .72	LM 358 – 1.40
74LS15 – .25	74LS160 – .88	LM 370 – 1.15
74LS20 – .24	74LS161 – .85	LM 377 – 2.50
74LS21 – .26	74LS162 – .85	LM 380 – .95
74LS22 – .26	74LS163 – .85	LM 381 – 1.25
74LS26 – .32	74LS168 – .88	LM 382 – 1.25
74LS27 – .32	74LS169 – .85	LM 537 – 2.50
74LS30 – .26	74LS170 – 1.68	LM 553 – 2.50
74LS32 – .32	74LS173 – 1.10	LM 555 – .39
74LS37 – .32	74LS174 – 1.00	LM 556 – .85
74LS38 – .32	74LS175 – .80	NE540L – 2.25
74LS40 – .26	74LS190 – .95	560 – 2.00
74LS42 – .65	74LS191 – .95	565 – .95
74LS47 – .79	74LS192 – .95	566 – 1.25
74LS51 – .26	74LS193 – .95	567 – 1.30
74LS54 – .26	74LS195 – .95	703 – .90
74LS90 – .95	74LS196 – .95	709 – .25
74LS74 – .35	74LS197 – .95	710 – .35
74LS76 – .35	74LS221 – 1.25	741C or V – .31
74LS85 – 1.30	74LS257 – .70	747 – .65
74LS90 – .55	74LS258 – .70	LM 1310 – 2.50
74LS92 – .55	74LS279 – .55	1456 – .95
74LS93 – .55	74LS365 – .55	1458 – .50
74LS109 – .38	74LS366 – .55	CA3046 – .75
74LS112 – .38	74LS367 – .55	3900 – .49
74LS113 – .38	74LS368 – .55	8038CC – 3.90
74LS114 – .38	74LS390 – 1.40	791 1.95
74LS125 – .47		LF356H – 1.75

	TRIACS			SCR'S		
PRV	1A	10A	25A	1.5A	6A	35A
100	.40	.70	1.30	.40	.50	1.20
200	.70	1.10	1.75	.60	.70	1.60
400	1.10	1.60	2.60	1.00	1.20	2.20
600	1.70	2.30	3.60		1.50	3.00

Terms: FOB Cambridge, Mass. Send Check or Money Order. Include Postage, Minimum Order $5.00, COD'S $20.00

Send 25¢ for our catalog featuring Transistors and Rectifiers
145 Hampshire St., Cambridge, Mass.

SOLID STATE SALES

P.O. BOX 74D
SOMERVILLE, MASS. 02143 TEL. (617) 547-7053

WE SHIP OVER 95% OF OUR ORDERS THE DAY WE RECEIVE THEM

CIRCLE 42 ON FREE INFORMATION CARD

J.B. Saunders Co.

3050 VALMONT ROAD
BOULDER, COLORADO 80301
Ph: (303) 442-1212

Terms

- Prices, specifications and availability subject to change without notice.
- U.S. & Canadian orders minimum $10.00.
- All other foreign orders $20.00 minimum.
- Please add $1.00 postage and handling.
- Foreign orders (exc. Canada) add 15% of total order for postage and handling.
- Colorado residents add 3½% sales tax.
- No C.O.D.'s please.
- Foreign orders send U.S. funds ONLY.

Elapsed Time Indicator

New, model ED71-001 Elapsed time indicator made by General Time Co. 120 volts, 60 cycles, 2.5 watts nominal current. 1¾" square face: 1½" diameter by 2½" deep housing. Sells retail for over $30.00 !!!

J-8000 $15.95

Reed Relay

Ultra-sensitive 5VDC, SPST reed relay. Ideal when transistors or SCR's are not suitable.

J-5000 $1.50

Keyboard

With point-closure (non-matrix) switches. Data sheet tells how to combine 3 to make alphanumeric keyboard!

J-5001 $1.95 3/$5.00

Fan Motor

117VAC fan motor for a variety of applications: Equipment cooling, hobby devices, cooling yourself off, etc. —Use your imagination !!!

J-5002 $2.25

Logi~Case®

The Logi-Case is a universal instrument enclosure designed to be attractive, as well as extremely durable and useful. The unique slide-out interior assembly is designed to hold up to 6 — 1½" x 4" PC boards (great for packing a lot of components into a very small space !!!). Made from 1/8" thick extruded, anodized aluminum. Choice of red or smoke-grey front lenses (reversible). Now available in two popular sizes !!! -Small: 4½L x 3¼D x 1¾H. Large: 6L x 4½D x 2H.

(Small) J-8001 7.95
(Large) J-8014 9.95

4N25 Opto Isolator

NPN phototransistor and PN infrared light emitting diode. 1500 volt isolation, 3ma coll.output current. Excellent frequency response to 300 Khz. New Motorola 6 pin dip w/ full data and specs.

J-4000 $1.00 10 for $9.00

PC Board

Highest quality glass-epoxy, .062" thick, 1-sided. —5 boards /pack

4" x 6"	5 for	$3.00
3" x 6"	5 for	2.25
6" x 6"	5 for	3.60
2" x 8"	5 for	2.00

PC Trimmer Pots

TYPE	PART NO.	PRICE
470 ohm, vertical	2000	.25
1K ohm, vertical	2001	.20
2.5K ohm, vertical	2002	.20
5K ohm, vertical	2003	.20
22K ohm, horizontal	2004	.25
50K ohm, vertical	2005	.20
470K ohm, horizontal	2006	.25

Speaker

High-quality miniature 8—ohm, 0.1 watt PM-type speaker. Individually boxed. Cone diameter: 1¾".

J-6000 75¢

RO170 Diode

The famous Motorola RO170 universal replacement diode, rated 1000 PIV @ 2.5A.

J-1000 20¢
100 for $14.50

Rubber Feet

Molded, adhesive-back rubber feet in peel-off sheets.

J-8002 (round) 75¢ -12
J-8003 (square) 55¢ - 12

V.O.X.

Solid state Voice Operated Switch. Complete and assembled. With schematic.

J-5003 $1.50

Ribbon Cable

Cond	Part No	1'	10'
6	S-7000	.25	2.00
12	S-7001	.45	3.95
24	S-7002	.85	7.95

Jumbo LED

.200" factory prime LED's for experimenters. Use with our LED clip shown below.

J4004 5 for $1.

Wire Special

22 ga. magnet wire with unique solder-through insulation. Buy by the pound & save. (500 feet.)

J-7003 $2.50

Toggle Switch

Heavy duty, high quality SPST toggle. Rated 15A @ 125 Volts.

J-5004 95¢

Transformer

Mini transformer for clocks, etc. 8V @ 500 ma or 12/190 ma, w/ specs.

J-5005 $1.50

Trimmer Cap

1—3 pf
Miniature trimmer cap. Ideal for crystal circuits, etc. 3/16" diam.

J-3000 75¢

Snap Switch

Mini SPDT snap switch made by Cherry. Rated 5 amps/125VDC.

J-5006 65¢

.1uf,6000V Cap

New units by Sprague. Great for those experimenting w/ high voltage

J-3001 70¢

2N3055

The king of the audio power—transistors. Now at an unbeleivable price !!!

J-1001 50¢

Heat Shrink

Much easier and faster than electrical tape, Twelve 6" peices, ass'td.

J-7004 $1.45

Telephone Wire

26 AWG telephone hook-up wire.
Single cond. 100ft/90¢
Twisted pr.100/$1.40
25 pair 1 foot/20¢

J-7005

Power Relay

Heavy duty, 25 Amps @ 115V. New by Potter & Brumfeild.

J-5007 $4.00

Pot with Switch

New by Allen Bradley. 100K mini 1/8" slotted shaft, ¼" mount. With SPST switch.

J-2008 65¢

Glue Syringe

An extremely useful tool for anybody!!! Appx. 4" long x ¾" diameter. High-impact plastic; w/ cap.

J-8004 35¢

Unique Switch

A strange but perhaps a very useful reverse action snap switch w/ lever. NC & NO connections

J-5008 75¢

Micro Switch

Miniature SPDT momentary pushbutton, rated 5A @ 125VAC.

J-5009 95¢

Strobe Tube/ Trigger Transformer

An experimenter's delight !!! —Brand new Xenon strobe tube and 4 kv trigger transformer. Dozens of uses in light shows, photography. special effects, etc.

J-4001 1.75¢

High Voltage Pot

5 megohm, insulated-shaft high voltage pot. ¼" shaft, 3/8" bushing.

J-2009 75¢

1N4148 Diode

Brand new, miniature glass type 1N4148 general purpose high-speed switching diode. Case AA.

J-1002 12 for $1.00

AA Nicad Batteries

Brand new prime quality AA nicad batteries, manufactured by Sanyo. These won't last long !!!

J-8005 $1.50

AA Battery Holder

All metal, size AA battery holder, with solder mounting tabs.

J-8006 40¢

TO-3 Heat Sink

High-heat transfer, brushed aluminum TO-3 heat sink.

J-8007 45¢

Rubber Edging

Protection from unsightly and dangerous metal edges. Contours to any shape. For material up to 1/16" thick.

J-8008 10'/$1.60
100'/$12.00

Photoflash Cap

Brand new by Rubycon, 600uf @ 360 V. Use with our strobe tube & transformer to make your own strobe light !!!

J-3002 $1.95

Toggle Switch

SPDT momentary center off (on—off—on). Rated 15A @ 125VAC, 10A @ 250VAC.

J-5010 55¢

Computer Caps

High-quality capacitors that meet the rigid demands of computer use. Brand new, 2700 uf @ 25 volts DC.

J-5011 $1.75

Transformer

Unique split primary. Wire in either series or parallel to get either 9 or 18 volts @ 1.5A. —With specs & data.

J-5012 $2.50

.01uf Disc Cap

.01 uf disc ceramic capacitor. Buy while they last!

J-5013 5¢

.02 uf Disc Cap

.02 uf ceramic disc capacitor. Buy while they last!

J-5014 5¢

47pf Mini Cap

Ultra-miniature ceramic capacitor for crystal circuits, etc

J-5015 10¢

Felt Feet

3/8" diameter. Peel off strips, 25 feet per strip.

J-8010 25¢

Comp. Clip

7/16" I.D. high impact plastic, center mount.

J-8011 10/25¢

Dixie Bell

Enclosed signal bell. 6-8VAC or 3-6VDC.

J-6001 $2.00

Barrier Strip

Black molded bakelite, 5 position barrier strip.

J-7008 25¢

.1/50V Cap

dipped mylar cap. .1uf @ 50 VDC.

J-5016 15¢

.01uf Mini Cap

Ultra-miniature .01 uf ceramic chip capacitor, axial leads.

J-5017 15¢

.01 Type MKM

Very stable metalized polycarbonate. .01uf @ 150V

J-5018 20¢

Hex Nuts

Standard size hex nuts for pots, lamps & switches, etc. 3/8".

J-7006 25 for $1.00

LED Panel Clip

Black plastic clip for mounting LED in panels.

J-4002 12/ $1.

Epoxy - Patch

Resin, hardener, mixing sticks and instructions.

J-8013 $1.25

Lamp Socket

Double contact automotive type, bayonet-base.

J-4003 20¢

8200uf Cap

8200 uf @ 15VDC. Brand new by Mallory. Axial leads.

J-5019 75¢

.5uf/5KV Cap

Hi-voltage cap for experimenting or special applications.

J-5020 2.50

PB Switch

PC mount SPST momentary contact.

J-5021 45¢

PC Trimmer

3/8" square, top adjusting, single turn. 20K ohm.

J-2011 90¢

Reed Switch

Giant 1 amp magnetic reed switch. 2-1/8" long.

J-5023 50¢

10K Pot

New from CTS, mini 1/8" shaft, ¼" mount. dia.

J-2012 65¢

TO-3 Insulator

Teflon coated aluminum. Much better than mica

J-8009 12/1.00

PC Trimmer

3/8" square top adjust, 1 turn. 50K ohm @ ½W.

SOLD OUT !

J-2010 90¢

PB Switch

PC mount push-on, push off. SPST.

J-5022 65¢

Stand-Off

Insulated stand-off terminal, 5/8" long w/ ¼" mtng screw.

J-7007 10/1.49

60 Amp

60 amp power terminator strip, 12 cont.

J-8012 $4.00

Rocker Switch

PC mount 2 pole, 3 position. (used).

J-5024 25¢

Terminal

Single bakelite solder term. strip.

J-7009 6/ 25¢

CIRCLE 30 ON FREE INFORMATION CARD

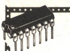

DIGI-KEY CORPORATION

Quality Electronic Components

TOLL FREE 1-800-346-5144

MINNESOTA RESIDENTS 218-681-6674

DON'T FORGET OUR DISCOUNTS WHEN COMPARING PRICES

I.C.'S • RESISTORS • TRANSISTORS • CAPACITORS • DIODES • I.C. SOCKETS & PINS • SWITCHES
CLOCK MODULES • OPTOELECTRONICS • BREADBOADING & TESTING DEVICES • DRAFTING SUPPLIES
DATA BOOKS • HEAT SINKS • WIRE • TOOLS . . . AND MORE . . . WRITE FOR FREE CATALOG . . . .

INTEGRATED CIRCUITS

TTL

7400	.21
7401	.21
7402	.21
7403	.21
7404	.21
7405	.21
7406	.25
7407	.25
7408	.21
7409	.21
7410	.21
7411	.21
7412	.21
7413	.25
7414	.89
7416	.25
7417	.25
7420	.21
7421	.25
7423	.35
7425	.35
7426	.25
7427	.33
7428	.28
7430	.21
7432	.25
7433	.30
7437	.25
7438	.25
7439	.50
7440	.21
7442	.53
7445	.70
7446	.70
7447	.70
7448	.70
7450	.21
7451	.21
7453	.21
7454	.21
7460	.21
7470	.30
7472	.30
7473	.30
7474	.30
7475	.49
7476	.32
7480	.70
7483	.70
7485	.89
7486	.28
7489	2.19
7490	.44
7491	.70
7492	.44
7493	.44
7494	.70
7495	.70
7496	.70
74100	1.28
74107	.30
74109	.33
74116	1.26
74121	.35
74122	.44
74123	.61
74125	.40
74126	.40
74128	.48
74132	.70
74141	.88
74145	.70
74147	1.63
74148	1.30
74150	1.16
74151	.70
74153	.65
74154	1.03
74155	.70
74156	.70
74157	.70
74160	.88
74161	.88
74162	.88
74163	.88
74164	.96
74165	1.15
74166	1.15
74170	2.64
74174	.98
74175	.93
74176	.79
74177	.79
74180	.70
74180	.70
74181	2.15
74182	.79
74184	2.15
74185	2.19
74189	3.50
74190	1.23
74191	1.23
74192	.88
74193	.88
74194	.88
74195	.88
74196	.88
74197	.88
74198	1.49
74199	1.49
74221	.86
74251	1.09
74279	.55
74298	.94
74365	.67
74366	.67
74367	.67
74368	.67

74LS00

74LS00	.28
74LS01	.28
74LS02	.28
74LS03	.28
74LS04	.29
74LS05	.29
74LS08	.29
74LS09	.29
74LS10	.28
74LS11	.28
74LS12	.28
74LS13	.47
74LS14	1.02
74LS15	.28
74LS20	.28
74LS21	.28
74LS22	.28
74LS26	.33
74LS27	.33
74LS28	.33
74LS30	.28
74LS32	.33
74LS33	.33
74LS37	.33
74LS38	.33
74LS40	.28
74LS42	.67
74LS47	.79
74LS48	.77
74LS51	.28
74LS54	.28
74LS55	.28
74LS73	.39
74LS74	.39
74LS74	.39
74LS75	.53
74LS76	.39
74LS78	.39
74LS83	.79
74LS85	.49
74LS86	.39
74LS90	.57
74LS92	.57
74LS93	.57
74LS95	.88
74LS96	.88
74LS107	.39
74LS109	.39
74LS112	.39
74LS113	.39
74LS114	.39
74LS125	.49
74LS126	.49
74LS132	.81
74LS136	.39
74LS138	.73
74LS139	.73
74LS151	.75
74LS153	.75
74LS154	1.10
74LS155	.75
74LS156	.75
74LS157	.75
74LS158	.75
74LS160	1.02
74LS161	1.02
74LS163	1.02
74LS164	1.02
74LS168	1.14
74LS169	1.14
74LS170	1.73
74LS173	1.34
74LS174	1.06
74LS175	.84
74LS181	2.50
74LS190	1.18
74LS191	1.18
74LS192	.98
74LS193	1.06
74LS194	.88
74LS195	.86
74LS196	.86
74LS197	.86
74LS197	.86
74LS221	1.06
74LS240	1.90
74LS241	1.90
74LS242	1.70
74LS243	1.70
74LS244	1.70
74LS247	.79
74LS248	.79
74LS249	.79
74LS251	.84
74LS253	.84
74LS257	.75
74LS258	.75
74LS260	.34
74LS261	2.00
74LS266	.39
74LS273	1.28
74LS279	.62
74LS283	.79
74LS290	.65
74LS293	.65
74LS295	1.12
74LS298	1.30
74LS365	.67
74LS366	.67
74LS367	.67
74LS368	.67
74LS377	1.50
74LS386	.39
74LS395	1.74
74LS670	2.34
81LS95	.77
81LS96	.77
81LS97	.77
81LS98	.77

INTERFACE

8093	.40
8094	.40
8095	.67
8096	.67
8097	.67
8098	.67
75450	.88
75451	.61
75452	.61
75453	.61
75454	.61
75491	.81
75492	.84
75493	1.09
75494	1.19
MC1488N	.90
MC1489N	.90

4000 CMOS

4000	.23
4001	.23
4002	.23
4006	1.23
4007	.23
4008	.79
4009	.44
4010	.44
4011	.23
4012	.23
4013	.40
4014	.96
4015	.96
4016	.40
4017	1.05
4018	1.05
4019	.23
4020	1.14
4021	1.14
4022	.96
4023	.23
4024	.84
4025	.23
4026	1.68
4027	.40
4028	.89
4029	1.14
4030	.23
4033	1.51
4034	3.50
4035	1.14
4040	1.14
4041	.79
4042	.79
4043	.70
4044	.70
4046	1.86
4049	.40
4050	.40
4051	1.26
4052	1.26
4053	1.26
4060	1.58
4066	.79
4071	.23
4072	.23
4073	.23
4075	.23
4081	.23
4082	.23
4502	.79
4510	1.14
4511	1.05
4514	2.80
4515	2.80
4516	1.23
4518	1.14
4520	1.14
4527	1.68
4528	.88
4585	1.23
74C00	.23

LINEAR

CA3046	.75
CA3086	.50
LF351N	.76
LF356N	1.20
LF357N	1.20
LF13741	.76
LM301AN	.44
LM307N	.64
LM308N	1.00
LM309K	1.80
LM311N	.90
LM317T	3.00
LM317MP	1.90
LM318N	2.70
LM320MP-5	1.30
LM320MP-6	1.30
LM320MP-8	1.30
LM320MP-9	1.30
LM320MP-12	1.30
LM320MP-15	1.30
LM320MP-18	1.30
LM320MP-18	1.30
LM320MP-24	1.30
LM323K	7.50
LM324N	.72
LM325N	2.70
LM326N	2.70
LM327N	2.70
LM339N	1.15
LM340T-5	1.25
LM340T-6	1.25
LM340T-8	1.25
LM340T-10	1.25
LM340T-12	1.25
LM240T-15	1.25
LM340T-18	1.25
LM340T-24	1.25
LM341P-5	.98
LM341P-6	.98
LM341P-8	.98
LM341P-10	.98
LM341P-12	.98
LM341P-15	.98
LM341P-18	.98
LM341P-24	.98
LM348N	1.60
LM349N	1.60
LM358N	.72
LM1310N	.84
LM1800N	.94
LM1801N	1.70
LM1812N	4.80
LM1830N	1.30
LM1889N	2.00
LM2111N	1.25
LM2907N	1.50
LM2917N	1.50
LM3089N	1.30
LM3900N	.88
LM3900N	.88
LM3905N	1.40
LM3909N	.69
LM3911N	1.50
MC1456V	1.00
MC1458V	.53
MC1496N	.70
MC3302P	1.15
NE536T	2.50
NE540L	2.04
NE555V	.48
NE556A	.88
NE558N	2.40
NE559N	2.40
NE560B	2.50
NE561B	2.50
NE562B	2.50
NE565A	1.25
NE566V	1.28
NE567V	1.36
UA709CV	.44
UA710CA	.44
UA711CA	.53
UA723CA	.60
UA733CA	.75
UA741CV	.44
UA747CA	.70
UA748CV	.49
UA7805CU	1.25
UA7806CU	1.25
UA7808CU	1.25
UA7812CU	1.25
UA7812CU	1.25
UA7815CU	1.25
UA7818CU	1.25
UA7824CU	1.25
UA78L05ACZ	.40
UA78L06ACZ	.40
UA78L08ACZ	.40
UA78L1oACZ	.40
UA78L12ACZ	.40
UA78L15ACZ	.40
UA78L18ACZ	.40
UA78L24ACZ	.40
UA7905CU	1.70
UA7906CU	1.70
UA7908CU	1.70
UA7909CU	1.70
UA7912CU	1.70
UA7915CU	1.70
UA7918CU	1.70
UA7924CU	1.70

MISC IC

MM5314N	3.75

NEW! 74C SUPER QUALITY SUPER PRICES

74C00

74C00N	.25
74C02N	.25
74C04N	.27
74C08N	.25
74C10N	.25
74C14N	.90
74C20N	.25
74C30N	.25
74C32N	.25
74C42N	.98
74C48N	1.28
74C73N	.72
74C74N	.48
74C76N	.72
74C83N	1.38
74C85N	1.38
74C86N	.40
74C90N	.98
74C93N	.98
74C95N	1.10
74C107N	.70
74C150N	2.90
74C151N	1.90
74C154N	2.90
74C157N	1.90
74C160N	1.18
74C161N	1.18
74C162N	1.18
74C163N	1.18
74C164N	1.10
74C165N	1.10
74C173N	1.30
74C174N	1.16
74C175N	1.16
74C192N	1.38
74C193N	1.38
74C195N	1.10
74C221N	1.90
80C95N	.48
80C96N	.48
80C97N	.48
80C98N	.48
74C901N	.48
74C902N	.48
74C909N	1.78
74C926N	7.80

STRANDED HOOK UP WIRE

20 ga PVC	2.50/100'	10.00/500'
22 ga PVC	2.80/100'	11.25/500'
24 ga PVC	2.10/100'	8.50/500'
26 ga PVC	2.10/100'	8.50/500'

Digi-Key Stocks the Entire AP Line

SILICON DIODES

1N4001	.64/10	5.50/C
1N4002	.66/10	5.60/C
1N4003	.68/10	5.80/C
1N4004	.70/10	5.95/C
1N4005	.82/10	7.05/C
1N4006	.90/10	7.75/C
1N4007	.99/10	8.60/C
1N4148	.40/10	3.50/C

FREE CATALOG

SLIDE SWITCHES

SPST	.15	1.25/10	10.00/C
SPDT	.19	1.70/10	13.00/C
DPDT	.23	2.00/10	19.00/C

50 VOLT DISCS

100 PF	.40/10	3.50/C
220 PF	.40/10	3.50/C
470 PF	.40/10	3.50/C
.001 UF	.40/10	3.50/C
.0022 UF	.40/10	3.50/C
.0047 UF	.40/10	3.50/C
.01 UF	.45/10	3.65/C
.022 UF	.50/10	4.00/C
.047 UF	.70/10	5.60/C
.1 UF	1.35/10	11.50/C

MICROPROCESSORS

8080A	8-BIT CPU, 2 USEC CYCLE	$12.95
8212	8-BIT I/O PORT	$ 3.95
8216	BI-DIRECTIONAL BUS DRIVER	$ 4.25
8224	CLOCK GENERATOR	$ 3.95
8228	SYSTEM CONTROLLER	$ 6.95
8251	COMMUNICATIONS INTERFACE	$12.95
8255	PERIPHERAL INTERFACE	$11.95
1702A	2K EPROM (256x8)	$ 6.95
2708	8K EPROM (1Kx8)	$29.50
2102-1	1K RAM 500 NS	$ 1.79
SC/MP	5 VOLT SC/MP CPU	$ 9.95
2650	MICROPROCESSOR 1.25 MH-2 CLOCK 40 DIL	$24.95

I.C. SOCKETS

8 PIN SOLDER	.17	1.60/10	14.50/C
14 PIN SOLDER	.20	1.90/10	17.00/C
16 PIN SOLDER	.22	2.10/10	18.75/C
18 PIN SOLDER	.29	2.75/10	24.50/C
20 PIN SOLDER	.30	2.85/10	25.25/C
22 PIN SOLDER	.33	3.15/10	27.75/C
24 PIN SOLDER	.38	3.60/10	32.25/C
28 PIN SOLDER	.45	4.25/10	38.25/C
40 PIN SOLDER	.63	6.00/10	53.50/C
8 PIN W-W	.24	2.30/10	20.50/C
14 PIN W-W	.26	2.50/10	22.00/C
16 PIN W-W	.30	2.85/10	25.50/C
18 PIN W-W	.60	5.70/10	51.00/C
20 PIN W-W	.70	6.65/10	59.50/C
22 PIN W-W	.84	8.00/10	71.50/C
24 PIN W-W	.96	9.10/10	81.50/C
28 PIN W-W	1.12	10.00/10	95.20/C
40 PIN W-W	1.36	12.50/10	115.00/C

8080A CHIP SET

ONE EACH 8080A, 8212, 8224 and 8228 PLUS SIXTEEN 2102-1's ALL FOR — **$49.95**

MOLEX I.C. SOCKET PINS

.85/C 8.20/M 38.20/5M 275.00/50M

PLESSEY SAMPLER

AN ASSORTMENT OF METALIZED POLYESTER CAPACITORS

300 CAPS 18 VALUES $26.00

MINIBOX METALIZED POLYESTER CAPACITORS

.001	.14	1.15/10	9.00/C
.0022	.14	1.15/10	9.00/C
.0033	.14	1.15/10	9.00/C
.0047	.14	1.15/10	9.00/C
.0068	.14	1.15/10	9.00/C
.01	.14	1.15/10	9.00/C
.022	.15	1.25/10	10.00/C
.033	.15	1.25/10	10.00/C
.047	.15	1.25/10	10.00/C
.068	.15	1.25/10	10.00/C
.1	.17	1.35/10	11.00/C
.22	.23	1.85/10	15.00/C
.33	.30	2.50/10	20.00/C
.47	.36	3.00/10	24.00/C

ELECTROLYTIC CAPACITORS

VALUE	RADIAL LEADS			AXIAL LEADS		
.47/50V	.08	.65/10	5.41/C	.11	.90/10	7.65/C
1/50V	.08	.65/10	5.41/C	.11	.90/10	7.65/C
2.2/50V	.08	.65/10	5.41/C	.12	.90/10	7.82/C
3.3/50V	.08	.65/10	5.41/C	.12	1.00/10	8.31/C
4.7/35V	.08	.65/10	5.41/C	.12	.95/10	7.91/C
4.7/50V	.08	.68/10	5.75/C	.12	1.00/10	8.31/C
10/16V	.08	.65/10	5.41/C	.11	.90/10	7.65/C
10/25V	.08	.65/10	5.66/C	.12	1.00/10	8.31/C
10/35V	.09	.70/10	6.12/C	.13	1.10/10	8.94/C
10/50V	.10	.75/10	6.58/C	.14	1.15/10	9.56/C
22/16V	.08	.67/10	5.66/C	.12	1.00/10	8.31/C
22/25V	.09	.70/10	6.09/C	.13	1.05/10	8.74/C
22/35V	.11	.85/10	7.29/C	.15	1.19/10	9.98/C
22/50V	.12	1.00/10	8.48/C	.17	1.32/10	11.22/C
33/16V	.09	.75/10	6.90/C	.12	1.00/10	8.48/C
33/25V	.10	.81/10	7.50/C	.14	1.15/10	9.56/C
33/35V	.13	1.05/10	9.65/C	.17	1.34/10	11.23/C
33/50V	.14	1.13/10	10.41/C	.19	1.52/10	12.89/C
47/10V	.09	.71/10	6.52/C	.13	1.04/10	9.50/C
47/16V	.10	.81/10	7.47/C	.14	1.15/10	9.56/C
47/25V	.13	1.05/10	9.65/C	.17	1.30/10	11.22/C
47/35V	.14	1.13/10	10.41/C	.19	1.51/10	12.89/C
47/50V	.15	1.21/10	11.16/C	.21	1.71/10	14.55/C
100/10V	.10	.77/10	6.58/C	.14	1.13/10	9.56/C
100/16V	.11	.85/10	7.28/C	.17	1.30/10	11.22/C
100/25V	.13	1.10/10	9.15/C	.20	1.55/10	13.30/C
100/35V	.17	1.41/10	11.85/C	.25	1.93/10	16.50/C
100/50V	.21	1.71/10	14.55/C	.29	2.30/10	19.70/C
220/10V	.13	1.08/10	9.15/C	.18	1.42/10	12.05/C
220/16V	.15	1.16/10	9.86/C	.20	1.55/10	13.30/C
220/25V	.21	1.71/10	14.55/C	.29	2.35/10	19.96/C
220/35V	.25	2.03/10	17.26/C	.35	2.79/10	23.70/C
220/50V	.29	2.35/10	19.96/C	.40	3.23/10	27.44/C
330/6V	.14	1.12/10	9.50/C	.19	1.48/10	13.71/C
330/10V	.15	1.16/10	9.83/C	.21	1.64/10	15.13/C
330/16V	.21	1.66/10	14.14/C	.31	2.45/10	22.70/C
330/25V	.23	1.86/10	15.79/C	.38	3,07/10	28.38/C
330/35V	.33	2.66/10	24.59/C	.43	3.43/10	31.68/C
330/50V	.54	4.30/10	39.73/C	.60	4.81/10	44.45/C
470/6V	.15	1.21/10	11.16/C	.20	1.64/10	15.13/C
470/10V	.21	1.71/10	14.55/C	.31	2.45/10	22.70/C
470/16V	.23	1.81/10	15.39/C	.33	2.66/10	24.59/C
470/25V	.29	2.35/10	19.96/C	.43	3.43/10	31.68/C
470/35V	.41	3.27/10	30.26/C	.47	3.78/10	34.99/C
470/50V	.54	4.30/10	39.73/C	.75	6.03/10	55.80/C
1000/6V	.22	1.90/10	16.50/C	.35	2.76/10	25.54/C
1000/10V	.24	1.96/10	16.62/C	.38	3.07/100	28.38/C
1000/16V	.29	2.35/10	19.96/C	.43	3.43/10	31.68/C
1000/25V	.42	3.33/10	28.27/C	.68	5.42/10	50.13/C
1000/35V	.60	4.81/10	44.45/C	.75	6.03/10	55.81/C
2200/6V	.36	2.86/10	26.48/C	.43	3.43/10	31.68/C
2200/10V	.42	3.33/10	28.27/C	.60	4.81/10	44.45/C
2200/16V	.54	4.30/10	36.58/C	.68	5.42/10	50.13/C

LED DIGITS AND LAMPS

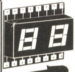

FND357 .375" Single Digit, CC, Red	$1.35
FND500 .5" Single Digit, CC, Red	1.35
FND507 .5" Single Digit, CC, Red	1.35
FND800 .8" Single Digit, CC, Red	2.50
FND807 .8" Single Digit, CA, Red	2.50
NSN373 .3" Dual Digits, CC, Red	2.20
NSN374 .3" Dual Digits, CA, Red	2.20
NSN583 .5" Dual Digits, CC, Red	2.60
NSN584 .5" Dual Digits, CA, Red	2.60
NSN783 .7" Dual Digits, CC, Red	3.00
NSN784 .7" Dual Digits, CA, Red	3.00
NSL5053 Dif. Red T-1¾ Lamp w/Mtg. Hdwe	$1.80/10 $16.00/100
NSL5056 Dif. Narrow Angle Red T-1¾ Lamp w/Mtg. Hdwe	$1.80/10 $16.00/100

5% CARBON FILM RESISTORS

¼ WATT RESISTOR ASSORTMENTS

Catalog Number	Description	PRICE
RS125	Set of 5 each of the 73 standard 5% ¼ watt cabon film resistors in the series 1.0, 1.2, 1.5, 1.8, 2.2, etc., through 1.0 meghom (365 total pcs.)	$9.90
RS225	Set of 5 each of the 72 standard 5% ¼ watt cabon film resistors in the series 1.1, 1.3, 1.6, 2.0, 2.4, etc., through 910 kilohm (360 total pcs.)	$9.90

½ WATT RESISTOR ASSORTMENTS

Catalog Number	Description	PRICE
RS150	Set of 5 each of the 73 standard 5% ½ watt carbon film resistors in the series 1.0, 1.2, 1.5, 1.8, 2.2, etc., through 1.0 meghohm (365 total pcs.)	$9.90
RS250	Set of 5 each of the 72 standard 5% ½ watt carbon film resistors in the series 1.1, 1.3, 1.6, 2.0, 2.4, etc., through 910 kilohm (360 total pcs.)	$9.90

Bishop Graphics 5"x6"

1X Scale PC Design Template

The Digi-Key Catalog features many more quality Bishop Graphics products.

3365-Nd **12.50**

CLOCK MODULES

The MA1002 and MA1010 series clock modules by National Semiconductor are fully assembled and tested clocks using a 4 digit LED display and an MOS integrated circuit on the same board. Simply connect switches and our special transformer and you have a fully functioning clock.

The MA1003 clock module is a fully assembled and tested 12 hour clock using a high brilliance green flourescent display and crystal time base making it perfect for ar, boat or other portable use. It operates directly from 12 volts DC so no transformer is needed. Our price includes three push button switches for setting the time.

MA1002A	.5" LED 12 Hour AM-PM Clock Module	$10.50
MA1002A SET	Module with Transformer & Switches	$13.95
MA1002C	.5" LED 24 Hour Clock Module	$10.50
MA1002C SET	Module w/Transformer & Switches	$13.95
MA1003	12 Volt Car Clock with Switches	$24.95
MA1010A	.84" LED 12 Hour AM-PM Clock Module	$13.00
MA1010A SET	Module w/Transformer & Switches	$16.45
MA1010C	.84" LED 24 Hour Clock Module	$13.00
MA1010C SET	Module w/Transformer & Switches	$16.45

MA1002 0.5" High Digits

Actual Size: 1.375"x3.05"

MA1010 0.84" High Digits

Actual size: 1.75"x3.75"

0.3" Digits Actual Size 1.75"x3.05" **MA1003** $24.95 NEW!

DATA BOOKS

TTL DATA BOOK, 592 P, NAT. SEMI.	9101B	$4.00
LINEAR DATA BK, 952 P, NAT. SEMI.	9011B	$4.00
CMOS DATA BK, 77 EDIT, 555 P, NAT. SEMI.	9012B	$3.00
POWER TRANSISTORS, 151 P, NAT. SEMI.	9013B	$3.00
MEMORY DATA BK. 592 P, NAT. SEMI.	9014B	$3.00
MOS/LSI DATA BK 713 P, NAT. SEMI.	9015B	$4.00
INTERFACE DATA BK, 464 P, NAT.	9016B	$4.00
VOLTAGE REG. BK, 128 P, NAT. SEMI.	9017B	$3.00
LIN. APPLIC. BK, VOL. 1, 432 P, NAT. SEMI.	9018B	$4.00
LIN. APPLIC. BK, VOL. 2, 246 P, NAT. SEMI.	9019B	$4.00
AUDIO HANDBOOK, 196 P, NAT. SEMI.	9020B	$4.00
8080A MICRO. SYS. DESIGN MAN, NAT. SEMI.	9021B	$5.00
SC/MP MICRO. APP. HANDBK, NAT. SEMI.	9022B	$5.00
SPECIAL FUNCTION DATA BK, NAT. SEMI.	9023B	$3.00
CMOS I.C.'S, 278 P, SOLID STATE SCIENT.	9030B	$3.00
SIGNETICS ANALOG MANUAL, 637 P	9031B	$5.95

MICROPROCESSOR BOOKS ADAM OSBORNE

(NON-DISCOUNTABLE)

AN INTRODUCTION TO MICROCOMPUTERS, VOL I BASIC CONCEPTS	9000B-ND	$ 7.50
AN INTRODUCTION TO MICROCOMPUTERS, VOL. II SOME REAL PRODUCTS	9001B-ND	$15.00
8080 PROGRAMMING FOR LOGIC DESIGN	9002B-ND	$ 7.50
6800 PROGRAMMING FOR LOGIC DESIGN	9003B-ND	$ 7.50

SAMS BOOKS

(NON-DISCOUNTABLE)

CMOS COOKBOOK	21398-ND	$ 9.45
THE BIG CMOS WALLCHART	21399-ND	$ 2.80
FET CIRCUITS	21439-ND	$ 4.70
IC TIMER COOKBOOK	21416-ND	$ 9.42
PRINCIPLES & APPLIC. OF INVERT. & CONV.	21454-ND	$ 7.55
ABC'S OF CAPACITORS (2ND EDIT.)	20849-ND	$ 4.04
ABC'S OF INTEGRATED CIRCUITS	20823-ND	$ 3.33
ABC'S OF RESISTANCE & RESISTORS	21126-ND	$ 3.75
ABC'S OF VOLTAGE-DEPENDENT RESISTORS	20771-ND	$ 3.09
ACTIVE-FILTER COOKBOOK	21168-ND	$14.20
COLLECTED BASIC CIRCUITS	20784-ND	$ 5.23
HOW TO DESIGN & USE MULTIVIBRATORS	21043-ND	$ 3.75
HOW TO USE IC LOGIC ELEMENTS	21081-ND	$ 4.70
IC OP-AMP COOKBOOK	20969-ND	$12.30
LED CIRCUITS AND PROJECTS	21006-ND	$ 4.99
MOS DIGITAL IC'S	21299-ND	$ 6.18
PRACTICAL SOLID-STATE CIRCUIT DESIGN	21018-ND	$ 6.18
RC CIRCUITS	21332-ND	$ 4.70
REGULATED POWER SUPPLIES	20844-ND	$ 5.23
RTL COOKBOOK	20715-ND	$ 5.46
TRANSISTOR SPECIFICATIONS MAN. (8TH ED.)	21335-ND	$ 6.60
TRANSISTOR SUBSITUTION HDBK (16TH ED.)	21333-ND	$ 4.70
ABC'S OF FET'S	20789-ND	$ 2.80
ABC'S OF TRANSISTORS (3RD ED.)	21146-ND	$ 4.04
ABC'S OF ZENER DIODES	21045-ND	$ 3.75
FET PRINCIPLES, EXPER., & PROJECTS (2ND)	21167-ND	$ 8.08
LINEAR IC PRINC., EXPER., & PROJECTS	21019-ND	$ 8.50
MICROMINIATURE ELECTRONICS	20582-ND	$ 5.46
SEMICONDUCTOR REPLACEMENT GUIDE	21092-ND	$ 3.75
TRANSISTOR FUNDAMENTALS — A CAREFULLY PLANNED PROGRAMMED COURSE IN SEMICONDUCTOR THEORY AND CIRCUITRY:		
VOL. 1—BASIC SEMICOND. & CIRC. PRINC.	20641-ND	$ 4.99
VOL. 2—BASIC TRANSISTOR CIRCUITS	20642-ND	$ 4.99
VOL. 3—ELECTRONIC EQUIP. CIRCUITS	20643-ND	$ 4.99
VOL. 4—DIGITAL & SPECIAL CIRCUITS	20644-ND	$ 4.99
4 VOLUME SET	20645-ND	$18.53
TRANSISTOR-TRANSISTOR LOGIC	20967-ND	$ 6.17
TUBE SUBSTITUTION HDBK (19TH EDIT.)	21225-ND	$ 2.14
SPECIAL TWIN-PAK TUBE SUB. PACKAGE	21227-ND	$ 2.80
SOLID-STATE COMPONENTS	21099-ND	$ 3.75
SOLID-STATE IGNITION SYSTEMS	21049-ND	$ 4.70
SOLID-STATE POWER SUPPLIES & CONV.	20310-ND	$ 3.33
TRANSISTOR AUDIO AMPLIFIERS	20838-ND	$ 5.62
TTL COOKBOOK	21035-ND	$ 8.50
USER'S GUIDE TO TTL	21080 ND	$ 2.38
TV TYPEWRITER COOKBOOK	21313-ND	$ 9.45
UNDERSTANDING CMOS I.C.'S	21129-ND	$ 4.70
UNDERSTANDING IC OPERATIONAL AMPLIF.	20855-ND	$ 3.75
UNDERSTANDING OSCILLATORS	20837-ND	$ 4.70
UNIQUE IC OP-AMP APPLICATIONS	21163-ND	$ 4.70
HOW TO BUY & USE MINI & MICROCOMPUTERS	21351-ND	$ 9.45
HOW TO PROGRAM MICROCOMPUTERS	21459-ND	$ 8.50
MICROCOMPUTER PRIMER	21404-ND	$ 7.55
THE 8080A BUGBOOK: MICROCOMPUTER INTERFACING & PROGRAMMING	21447-ND	$ 9.45
COMPUTER DICTIONARY (2ND EDIT.)	20943-ND	$ 8.50
COMPUTER DICT. & HANDBOOK (2ND EDIT.)	20850-ND	$18.53
COMPUTERS & PROGRAMMING GUIDE FOR ENGIN.	20950-ND	$12.30

½ WATT ZENER DIODES

.15 1.30/10 11.00/C

1N5226B	3.3V	1N5242B	12V
1N5227B	3.6V	1N5243B	13V
1N5228B	3.9V	1N5244B	14V
1N5229B	4.3V	1N5245B	15V
1N5230B	4.7V	1N5246B	16V
1N5231B	5.1V	1N5247B	17V
1N5232B	5.6V	1N5248B	18V
1N5233B	6.0V	1N5249B	19V
1N5234B	6.2V	1N5250B	20V
1N5235B	6.8V	1N5251B	22V
1N5236B	7.5V	1N5252B	24V
1N5237B	8.2V	1N5253B	25V
1N5238B	8.7V	1N5254B	27V
1N5239B	9.1V	1N5255B	28V
1N5240B	10V	1N5256B	30V
1N5241B	11V	1N5257B	33V

HARDWARE

2-56 1/4 SCREW	.99/C
2-56 1/2 SCREW	.99/C
4-40 1/4 SCREW	.55/C
4-40 1/2 SCREW	.60/C
6-32 1/4 SCREW	.65/C
6-32 1/2 SCREW	.75/C
8-32 3/8 SCREW	.90/C
8-32 5/8 SCREW	.99/C
2-56 HEX NUT	.55/C
4-40 HEX NUT	.55/C
6-32 HEX NUT	.60/C
8-32 HEX NUT	.60/C
NO 2 LOCKWASHER	.85/C
NO 4 LOCKWASHER	.45/C
NO 6 LOCKWASHER	.45/C
NO 8 LOCKWASHER	.45/C

FREE CATALOG

SILICON TRANSISTORS

MPS918	.16	1.55/10	13.60/C	130.00/M
MPS930	.16	1.55/10	13.60/C	130.00/M
MPS2222A	.16	1.55/10	13.60/C	130.00/M
MPS2369A	.16	1.55/10	13.60/C	130.00/M
MPS2907A	.16	1.55/10	13.60/C	130.00/M
MPS3393	.16	1.55/10	13.60/C	130.00/M
MPS3393	.16	1.55/10	13.60/C	130.00/M
MPS3394	.16	1.55/10	13.60/C	130.00/M
MPS3395	.16	1.55/10	13.60/C	130.00/M
MPS3563	.16	1.55/10	13.60/C	130.00/M
MPS3565	.16	1.55/10	13.60/C	130.00/M
MPS3638A	.16	1.55/10	13.60/C	130.00/M
MPS3640	.16	1.55/10	13.60/C	130.00/M
MPS3641	.16	1.55/10	13.60/C	130.00/M
MPS3643	.16	1.55/10	13.60/C	130.00/M
2N3904	.16	1.55/10	13.60/C	130.00/M
2N3906	.16	1.55/10	13.60/C	130.00/M
2N4124	.16	1.55/10	13.60/C	130.00/M
2N4126	.16	1.55/10	13.60/C	130.00/M
2N4401	.16	1.55/10	13.60/C	130.00/M
2N4403	.16	1.55/10	13.60/C	130.00/M
2N4410	.16	1.55/10	13.60/C	130.00/M
2N5087	.16	1.55/10	13.60/C	130.00/M
2N5089	.16	1.55/10	13.60/C	130.00/M
2N5210	.16	1.55/10	13.60/C	130.00/M
2N3055	.99	9.20/10	85.00/C	800.00/M
MPF102	.36	3.35/10	30.60/C	300.00/M
2N5457	.48	4.50/10	41.00/C	400.00/M
MPSA13	.28	2.60/10	24.00/C	230.00/M
MJ2955	.99	9.20/10	85.00/C	800.00/M
TIP120	.99	9.20/10	85.00/C	800.00/M

DOUBLE DIGIT DISCOUNTS SAVE YOU EVEN MORE!

HANDLING CHARGES

$ 0.00-$ 4.99	Add $2.00
$ 5.00-$24.99	Add $0.75
$ 25.00-$49.99	Add $0.50
$ 50.00-$99.99	Add $0.25
$100.00 & Up	No Charge

VOLUME DISCOUNT & HANDLING CHARGE

All items except those with catalog numbers ending with the suffix-ND may be combined for discount. First—total all discountable items and apply the volume discount. Then add to this subtotal the nondiscountable items. Add the handling charge. This is your total cost. We pay all shipping and insurance to addresses in the U.S.A. and Canada.

VOLUME DISCOUNT

$ 0.00-$ 24.99	NET
$ 25.00-$ 99.99	Less 10%
$ 100.00-$499.99	Less 15%
$ 500.00-$999.99	Less 20%
$1000.00 & Up	Less 25%

your BANKAMERICARD welcome

Orders Accepted by Phone or Mail
MasterCharge • Bank-Americard • COD • Check • Money Order
P.O. Box 677, Thief River Falls, Minn. 56701 (218) 681-6674

DIGI-KEY CORPORATION

Quality Electronic Components

P.O. Box 677 Thief River Falls, MN 56701 (218) 681-6674

CIRCLE 91 ON FREE INFORMATION CARD

INTERNATIONAL ELECTRONICS UNLIMITED

IC, LED SALE

TTL	
7404	$.14
7410	.13
7430	.15
7437	.15
7447	.49
7474	.23
7485	.69
7493	.28
7495	.49
74123	.23
74141	.65
74151	.49

CMOS	
4002	.19
4006	.95
4007	.19
4009	.39
4011	.16
4014	.79
4019	.25
4021	.87
4022	.89
4023	.18
4051	.89

LINEAR		
301m	Prec. Op Amp	$.19
302H	Volt Follower	.39
308H	Prec Op Amp	.49
311N	Hi Perf V Comp.	.59
340T6v	Pos. V Reg.	.59
540H	Power Amp	1.59
565N	Genl Purp PLL	.99
723N	Volt Reg	.45
733H	Diff Video Amp	.49
739N	Dual Audio Preamp	.69
1414N	Dual Diff Comp.	.99

MAN 1	.27" Red CA LHD	.99
MAN 2	.30" Red 5x7 LHD	3.95
MAN 5	.27" Green CA LHD	.99
MAN 7	.27" Yellow CA LHD	.49
MAN 54	.30" Green CC RHD	1.19
MAN 66	.60" Red CA LHD	1.19
MAN 72	.30" Red CA LHD	.59
MAN 82	.30" Red CA LHD	.99
MAN 3610	.30" Orange CA RHD	.69
MAN 3640	.30" Orange CC RHD	.69
MAN 4610	.40" Orange CC RHD	.59
MAN 6660	.56" Orange CA RHD	.59
DL 10A	.27" Red CA LHD	.99
DL 702	.30" Red CC LHD	.79
DL 707	.30" Red CA RHD	.79
DL 747	.60" Red CA LHD	1.19
FND 359	.375" Red CC RHD	.59
FND 500	.50" Red CC RHD	.69
FND 507/510	.50" Red CA RHD	.69
NSN 74R	.30" Red CC RHD	.69

MAN 6610	2 Dig .56" Orng CA RHD	.69
MAN 6630	1-1/2 Dig .56" Orng CA RHD	.59
MAN 6640	2 Dig .56" Orng CC RHD	.69
MAN 6650	1-1/2 Dig .56" Orng CC RHD	.59
MAN 6710	2 Dig .56" Red CA RHD	.69
MAN 6730	1-1/2 Dig .56" Red CA RHD	.59
MAN 6740	2 Dig .56" Red CA RHD	.69
MAN 6750	1-1/2 Dig .56" Red CC RHD	.59
DL 33B	3 Dig .17" Red CC	.29
DL 33B	2 Dig .17" Red CC	.49
NSN 33	3 Dig .17" Red CC	.39
HP 5082	4 Dig .11" Mag. RHD	.39
HP 5082	5 Dig .11" Mag. RHD	.49
SP425-09	9 Dig Gas Discharge	.69
Calc Disp	9 MAN 3s on board Red	.79
TI 434	9 Dig Red	.49

ELECTRONIC DOOR CHIME KIT

WITH TI TMS 1000 MICROPROCESSOR CHIP PROGRAMMED TO PLAY 24 DIFFERENT TUNES

INTERNATIONAL FLAVOR — PLAYS NATIONAL ANTHEMS OF U.S., BRITAIN, FRANCE AND WEST GERMANY PLUS OTHER FOLK TUNES, CLASSICAL AND TRADITIONAL MELODIES

- SUPPLIED WITH ALL PARTS INCLUDING PC BOARD, SPEAKER, CASE AND COMPLETE INSTRUCTION MANUAL WITH FULL CIRCUIT DETAILS
- USES 2 9V TRANSISTOR BATTERIES (NOT SUPPLIED)
- LOW POWER CONSUMPTION
- INTERNAL SELECTION OF TUNE, VOLUME, TEMPO AND TIMING FUNCTIONS
- PROGRAMMED MATHEMATICALLY TO PLAY IN PERFECT PITCH PERMANENTLY
- ATTRACTIVE CASE, CONVENIENT WALL MOUNT

$39.50 SHIPPING $1.00

IASIS MICROCOMPUTER APPLICATIONS HANDBOOK

$5.95

2510	Dual 50 bit Shift Reg.	.95
2511	Dual 100 bit Shift Reg.	.95
2518	Hex 32 bit Shift Reg.	1.25
2522	Dual 132 bit Shift Reg.	.95
MM5016	500/512 bit Shift Reg.	.95
SL-5-4025	Quad 25 bit Shift Req.	.59

MV10B TO-18 clear 15/$1.00

2513(caps)	Char. Gen.	2.95
2513(L.C.)	Char. Gen.	2.95
MM1101	256 bit RAM	.65
MM1103	1K RAM	.75
1702A	EROM	4.75
MM5261	1K RAM	.55
MM5262	1K RAM	.95
F93410	256 bit RAM	.95
2708	8K EROM	$8.95

EXAR	
320	1.19
2206	3.90
2207	1.49
2567	1.49
4136	.69
4202	.69
4212	.69
4739	.69

KEYBOARD
20 Keys - 2 slide switches
3" x 3-3/4" $1.00/3

BUGBOOKS

I & II - Logic, memory text & experiments $17.00 /set
Instructors Manual (for 1 & 2) $ 3.00 ea.
IIA - Introduction, use of UART $ 5.00 ea.
V & VI - Experiments in Digital 8080A programming & interfacing $ 9.50 ea. 19.00 /set
555 - Timer applications, experiments $ 6.95 ea.
CMOS - Designers primer and handbook $ 6.00 ea.
SK10 - E & L Solderless Breadboard $16.50 ea.

IC SOCKETS TT

Low Profile Solder Tail

8 pin	$.16	24 pin	$.36
14 pin	.19	28 pin	.44
16 pin	.21	40 pin	.61
18 pin	.28		

Wire Wrap

8 pin	.45
14 pin	.49
16 pin	.55

LINEAR ASSORTMENT
1 each of following - all functional
301M, 302H, 307M, 311N, 340T-5, 340T-6, 340T-15, 380-8, 385K, 723N, 739N, 741M, 748M, 75453M
$4.75

5 BACK ISSUES OF ELEKTOR MAGAZINE containing a variety of electronic projects, with schematics, PC layouts, parts list. PC boards are available. Regular $1.50/copy
$4.00/5 issues
25 26 29 30 31

PLASTIC CASES

VERO - dark and light gray
nominal O.D.

2514F	2"x4"x1"	$4.34
2516G	2"x4"x1.6"	4.90
2518H	2.6"x 4.7"x1.6"	5.48
2520J	3.2"x6"x2"	6.24
2522K	4.3"x7.4"x2.4"	8.28
2755G	2.6"x4.7"x2.6"	6.74
2760D	4.3"x7.4"x2.4" (w/ handle/stand)	10.78
2525F	2.8"x5.4"x2.4" (ventilated)	5.40
HAMMOND - blue		
1591C	2.6"x4.8"x1.6"	2.65

METAL FILM RESISTORS
± 1%, 1/4w, ± 50 PPM/°C
Standard Decade Values 10.5 - 464K

Qty.	Ea.	Min 10/value	Min 100/value
1-99	$.20	$.15	
100-999	.20	.10	$9.00/100
1000-			8.00/100

CERAMIC DISC CAPACITORS - 50V

1pf	22pf	56pf	120pf	270pf	820pf	.022uf
5pf	27pf	68pf	150pf	390pf	.001uf	.030uf
7pf	33pf	82pf	180pf	470pf	.0047uf	.050uf
10pf	47pf	100pf	220pf	600pf	.01uf	

0-10 per value..$.10ea 10-up per value $.05ea
10-up per value $.05ea

REGULATED POWER SUPPLY

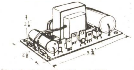

Plus & minus 5V, 12V and 15V. Uses 3 LM340T and 3 LM320T regulators, 115V/29V CT transformer plus PC board capacitors & diodes. All parts, schematic, instructions
PS-29.........$12.95 + $1.00 Shppng.

PRECISION RESISTOR PACKAGE
Metal Film ± 1% 1/4 watt
Starter Kit - 2ea. 60 values
120 Resistors 10.5 ohm- 464K
$14.95
Supplied in 15 Drawer 60 Comp. Cabinet - $26.50 + $2.00 Sh.

CAPACITOR KIT - ceramic disc
50V, 24 values, 10 capacitors each

1pf	33pf	82pf	220pf	820pf	.022uf
5pf	47pf	100pf	270pf	.001uf	.030uf
10pf	56pf	150pf	470pf	.0047uf	.050uf
22pf	68pf	180pf	600pf	.01uf	.1uf

capacitors only...$11.95
Packeged in 15 drawer, 60 compartment cabinet....$19.95 plus $2.00 shipping

BEZELS - with red filters

140-2	cut-out 1.125" x 2.375" max .062" panel thickness	$1.75
140-4	cut-out 1.160" x 4.375" max .125" panel thickness	$2.75

DIODES

Silicon SW diode assorted 400 mw	$.05ea
1N4148 (1N914) Silicon diode 400 mw	.10
1N3064 Silicon SW diode 400 mw	.10
1N4006 Silicon rect. diode 600V 400mw	.10
Zener diode 400 mw - 2.4V, 3.6V, 5.1V, 6.5V, 6.8V, 10V, 12V, 14.5, 15V, 120V	.15
Germanium diode 400 mw	.08

PC BOARDS - for use with ELEKTOR MAGAZINE PROJECTS
MAGAZINE PROJECTS

ELEKTOR #32 Dec 77........................		$ 1.50
music synthesiser (E25-31)	9724-1	7.45
CPU - SC/MP	9851a	18.80
UHF TV modulator	9864	2.95
microphone preamp	9866	1.30
ANALOG FREQ. METER	9869	2.40
heating controller	9877	7.05
MW reflex receiver	9880	1.85
sensitive lightmeter	9886	1.30
stylus balance (E12)	9343	1.05
signal generator (E24)	9765	1.10
knotted handkerchief (E27/28)	9830	.45
ELEKTOR #31 Nov 77........................		1.50
music synthesiser	9723-1	18.35
CCIR TV pattern generator	9800-3	5.65
video biofeed back		
display generator	9825-1	5.60
alpha amplifier	9825-2	4.60
electrometer	9826-1	1.50
sensors for electometer	9826-2	1.40
magnetiser	9827	1.45
CPU-SC/MP		
RAM-1/0	9846-1	12.70
SC/MP Board	9846-2	3.95
model car track (E24-E30)		
transmitter power supply	9218	2.20
chassis	9850	6.35
ELEKTOR #20 Oct 77........................		1.50
CCIR TV pattern generator (E29)	9800-2	7.35
infrared transmitter	9822	5.55
ioniser	9823	6.60
Kirlian camera (set) 4523,	9831	5.00
model car track (E24-26,29)		
infrared receiver	9848-1	1.80
multiplex decoder	9848-2	1.90
ELEKTOR #29 Sept 77		1.50
FM intercom	9359	10.75
music synthesiser (E25,26)		
interface receiver	9721-2	2.80
power supply	9721-3	9.15
keyboard divider(1 ocatave)	9721-4	1.70
logarithrimic timer	9797	3.35
CCIR TV test pattern generator	9800-1	13.10
model car track (E24-26)		
motor speed control	9829-1	1.20
proptester	9829-2	3.45

UNIVERSAL BREADBOARD

Silver placed copper circuits fits any IC and related components. 2 triple rows of 27 holes for DIP. 3-3/16"x5-1/16"
$1.00

ELECTRONIC BUZZER

Miniature, Solid State
6V 15ma (4-9V oper.) $1.69 ea.
12V 15ma (8-20V oper.) $1.69 ea.

Carbon Film Fesistors ± 5% 1/4w, 1/2w

Qty.	Ea.	Min 10/value	Min 100/value
1-99	$.10	$.05	
100-999	.10	.04	$3.00/100
1000-			2.50/100

TANTALUM CAPACITORS - solid dipped

.1u/35V	$.20	6.8/6	$.25	15/50	$.40
.22/35	.20	6.8/16	.25	22/16	.40
.33/35	.20	6.8/50	.30	33/10	.50
1/35	.20	10/16	.30	47/6	.50
2.2/20	.25	10/25	.35	47/25	.55
2.2/35	.25	10/50	.35	56/6	.65
3.3/35	.25	15/10	.35	150/15	1.25
4.7/16	.25	15/20	.35		

I C BREADBOARD

Silver plated copper circuits holds 5 - 16 pin DIP IC's and interconnection holes. $1.00

RESISTOR PACKAGE

Carbon Film ± 5% 1/4w or 1/2w
Usage Evaluated Assortment
5 to 20 ea of 44 values.
$12.95
Supplied in 15 Drawer 60 Comp. Cabinet. $22.95 + $2.00 Sh.

TANTALUM CAPACITOR KIT
solid dipped, 12 values, 5 each

.1uf/35V	2.2/35	10/25	33/10
.33/35	4.7/16	15/20	47/25
1/35	6.8/16	22/16	56/6

capacitors only......$14.95
supplied in styrene utility box.. ... .$19.95

BIMBOARD - BREADBOARD KIT

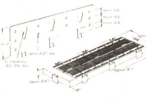

Solderless breadboard section has 94 breadboard strips of 5 sockets each. 2 bus strips of 40 sockets each. Component bracket for switches lamps etc., accepts leads .01" to .035" diameter. $11.95 ea.

RESISTOR PACKAGE

Carbon Film ± 5% 1/4 w or 1/2 w
15 ea. of 12 values:
100, 220, 470, 1K, 1.5K, 3.3K 4.7K 6.8K, 10K, 33K, 100K, 1M.
$5.45

TRANSISTORS

2N1132	PNP Gen Purp. Ampl TO-5	$ .69
2N2218A	NPN Low Power Trans TO-5	.69
2N2222A	NPN Low Power Trans TO-18	.29
2N2223	NPN Low Power Trans. TO-5	.69
2N2369	NPN Low Power Trans TO-5	.29
2N2904	PNP Low Power Trans TO-5	.49
2N2905A	PNP Low Power Trans TO-5	.76
2N3227	NPN Low Power Trans TO-18	.69
2N3904	NPN Low Power Trans TO-92	.17
2N3906	PNP Low Power Trans TO-92	.17
SCA 13572	NPN Pwr Trans - 200V TO-5	1.75

CLOCK KIT - Mark I
6 digit clock kit with one PC board. Accommodates MM5314 clock chip and 6 FND 359 displays contains all components except transformer. Includes 3 switches. Board has terminals for remote displays. $10.95

with 12V/300 ma transformer
$13.95

TRIMPOT - 25 turn
Bourns - Cermet 3299W
PC Mount, vert. adj.
2K, 10K, 20K $1.75 ea

VECTOR BOARD - Phenolic
169P44-062 (.1"spacing .42" dia.)
4-1/4" x 4-1/2" x .0625"...$1.15 ea.

TRIMPOT - Single Turn
Mepco - Cermet 8014
.5w, ± 100 PPM/°C ± 20%
500 ohm, 2K, 10K, 25K, 50K, 100K, 500K, 1M. $.75 ea.
.69/10-

COMPLETE SATISFACTION GUARANTEED. SHIPMENT TO US AND CANADA PREPAID UNLESS INDICATED OTHERWISE. OTHER COUNTRIES ADD 10% - EXCESS REFUNDED. ORDERS SHIPPED IN 3 WORKING DAYS FROM RECEIPT. MINIMUM ORDER $10.00 CALIFORNIA RESIDENTS ADD SALES TAX. MINIMUM COD OR CHARGE ORDER $15.00

INTERNATIONAL ELECTRONICS UNLIMITED
VILLAGE SQUARE, P.O. BOX 449, CARMEL VALLEY, CA 93924 USA
TELEPHONE 408 659-3171

SC-5
With
Rechargeable
Batteries &
Charger
Unit **$89**

FM-7
With
Rechargeable
Batteries &
Charger
Unit **$195**

NLS

Features Include: • By using the new NLS SC-5 Prescaler, the range of the FM-7 Frequency Meter, which is 10 Hz to 60 MHz, may be extended to 512 MHz (the upper VHF & UHF frequency bands). • The FM-7 utilizes an LED readout, providing 7-digit resolution. • The FM-7 can be calibrated to an accuracy of 0.00001%. • The SC-5 is accurate to one part per million. • Each unit has 30 millivolts sensitivity, is battery powered and has a charger unit included. • Dimensions of each are 1.9'' H x 2.7'' W x 3.9'' D. • The units may be obtained separately or as a ''Frequency Duo.'' • Parts & Labor guaranteed 1 year.

Tilt stand option	$ 3.50
Leather case	$16.00

MS-15 MINISCOPE $289

With Rechargeable Batteries & Charger Unit

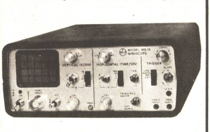

- 15 megahertz bandwidth.
- External and internal trigger.
- Time base — .1 microsec. to 0.5 Sec/div - 21 settings . ± 3%.
- Battery or line operation.
- Automatic & line sync modes.
- Power consumption < 15 watts.
- Vertical Gain — .01 to 50 V/div - 12 settings ± 3%.
- Viewing area 1.1'' x 1.35''.
- Case size 2.7''H x 6.4''W x 7.5''D, 3 pounds.
- Parts & Labor guaranteed 1 year
- 10 to 1, 10 meg probe $24.50
- Leather carrying case $30.00

NLS

PROBE 1¢ with the purchase of SCOPE and the MENTION of this MAGAZINE

NEW VOLKSMETERS!

With LCD Display—
Excellent Readability in Direct Sunlight!

NLS

1%
LM-300
Full three digits
$99.50*

0.5%
LM-350
3½ digits
$125.00*

FEATURES

- Measures DC volts, AC volts, ohms and current.
- Automatic polarity, decimal and overload indication.
- No zero adjustment and no full scale ohms adjust.
- Large LCD display for easy reading without interpolation.
- Size: 1.9'' H x 2.7'' W x 4.0'' D.
- Parts and labor guaranteed for one year.

SPECIFICATIONS

MODE	RANGE	ACCURACY LM-300	ACCURACY LM-350	RESOLUTION	INPUT RESISTANCE	TEST CURRENT
VOLTS DC*	1 10 100 1000	±1% Reading†	±0.5% Reading†	1 mV 10 mV 100 mV 1 V	10 MΩ	
VOLTS AC*	1 10 100 1000	±1% Reading† 50-400 Hz	±0.7% Reading† 50-400 Hz	1 mV 10 mV 100 mV 1 V	10 MΩ, 20 pF	
KILOHMS**	1 10 100 1000 10000	±1% Reading†	±0.5% Reading†	1 Ω 10 Ω 100 Ω 1 kΩ 10 kΩ		1 mA 100 µA 10 µA 1 µA 100 nA
CURRENT	1 mA 10 mA 100 mA 1 A	±2% Reading†	±2% Reading†	1 µA 10 µA 100 µA 1 mA	1 kΩ 100 Ω 10 Ω 1 Ω	

* 1000 vdc or peak ac maximum any range. †±2 Digits
**Test Voltage (Ohms) 1 vdc Full Scale - LM-300; 2 vdc Full Scale - LM-350
LM-350 has 100% over-range - full scale readings are 1.999, 19.99, etc.

Tilt Stand Option, add	$3.50
Leather Case	$16.00
3AA NiCad-Batts. & Charger	$12.00

Standard AA-size batteries provide up to 20 hours of operation.
Rechargeable NiCad batteries and charger unit available as optional equipment.
°Batteries not included.

LEDU

MG 10A
List $72.00

Perfectly balanced, fluorescent lighting with precision magnifier lens. For prof'l, techn'l & hobbist. Has die cast protective shade, inst. start 3 diopter lens. 42'' reach.

$44⁹⁵

with T-9 fluorescent lamp (required)
$49.95
colors: Gray or Black
Chocolate Brown
2 choices please

$44⁹⁵
SPECIAL

8803 MOTHER BOARD FOR S100 BUS MICRO-COMPUTERS

Vector

- Kit includes 12 tantalum capacitors for +5, +12, —12 buses and insulated mounting spacers.
- Wiring side shown. Component side bare epoxy glass with white markings for component locations.
- G10 epoxy glass board with 2 ounce copper, solder plated and .038 diameter holes for leads.
- Solder mask with solder windows on etched circuits to avoid accidental short circuits.
- Mounts 11 receptacles with 100 contacts (2 rows) on .125 centers with .250 row spacing, Vector part number R681-2; or mounts 10 receptacles plus interconnections to smaller mother board for expansion.
- Includes etched circuits and instructions for option of active, pull-up, or floating terminations.
- Large buses: +5V and GND (10 AMPS), ± 12V or 16V (7 AMPS). Current ratings are per MIL-STD-275 with 10°C rise.
- Fits in Vector-pak enclosures.
- Fits in IMSAI 8080 microcomputer as expander board.

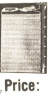

Price:
$29.50

Vector Plugboards

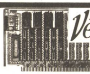

8800V

Universal Microcomputer/processor plugboard, use with S-100 bus. Complete with heat sink & hardware. 5.3'' x 10'' x 1/16''

1-4	5-9	10-24
$19.95	$17.95	$15.96

8801-1

Same as 8800V except plain; less power buses & heat sink.

1-4	5-9	10-24
$14.95	$13.46	$11.96

3682 9.6'' x 4.5''
$10.97
3682-2 6.5'' x 4.5''
$9.81

Hi-Density Dual-In-Line Plugboard for Wire Wrap with Power & Grd. Bus Epoxy Glass 1/16'' 44 pin con. spaced .156

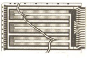

3677 9.6'' x 4.5''
$10.90
3677-2 6.5'' x 4.5''
$9.74

Gen. Purpose D.I.P. Boards with Bus Pattern for Solder or Wire Wrap. Epoxy Glass 1/16'' 44 pin con. spaced .156

3662 6.5'' x 4.5''
$7.65
3662-2 9.6'' x 4.5''
$11.45

P pattern plugboards for IC's Epoxy Glass 1/16'' 44 pin con. spaced .156

R644 P.C. recepticle 22/44 cont. .156 ctrs. pierced solder eyelets tails gold	$3.45
R644-3 P.C. recepticle 22/44 cont. .156 ctrs. Wire Wrap tails gold	$4.49

S-100
Bus P.C. Edge Connectors

R681 DIP solder tails on .140'' spaced rows for ALTAIR mother boards. Fits .042'' dia. holes, gold	$7.35
R681-1 .025'' sq., 3 wrap lengths posts (.62 long) on .250 spaced rows, gold	$5.00
R681-2 .025'' sq., 1 wrap length posts (.22 long) on .250 spaced rows for wrapping or DIP solder for IMSAI mother boards, gold	$5.85
R681-3 pierced solder eyelet tails, gold	$7.35

1/16 Vector BOARD

.042 dia holes on
0.1 spacing for IC's

Phenolic

PART NO.	SIZE	PRICE
64P44-062XXP	4.5 x 6.5''	$ 1.49
169P44-062XXP	4.5 x 17''	$ 3.51

Epoxy Glass

PART NO.	SIZE	PRICE
64P44-062	4.5 x 6.5''	$ 1.70
84P44-062	4.5 x 8.5''	$ 2.10
169P44-062	4.5 x 17''	$ 4.30
169P84-062	8.5 x 17''	$ 6.39

SLIT-N-WRAP

Wraps insulated wire on .025'' square posts
FOUR TIMES FASTER
than regular manual wrap-post tools

P180
with two 100' spools of 28 ga. wire

$24.50

P160-4T
includes charger, wire
$75.00

Vector

NO PRE-STRIPPING*
NO PRE-CUTTING*
SPOOL-FED WIRE*

*The spooled wire passes through the tool past a slitting edge next to the wrap post. A narrow longitudinal cut is made in the insulation where it presses the square post corner, the bared copper is indented by the sharp edge (7 turns = 28 contacts)
Insulation is slit where wrapped but not between terminal posts when led straight out of the tool

''Daisy-chain'' runs
Reliable and easy to use
Manual or power operation

SLIT-N-WRAP WIRE $2⁷⁵ Package
NO. 28 GAGE INSULATED WIRE, 100' SPOOLS

W28-2-A-Pkg. 3, Green
W28-2-B-Pkg. 3, Red
W28-2-C-Pkg. 3, Clear
W28-2-D-Pkg. 3, Blue

2708

8K 450 ns

EPROM
FACTORY PRIME

1-9	$12.00
10-24	$11.50

25 + *Call for Price*

---

14 & 16 PIN 3 LEVEL WIRE WRAP SOCKETS

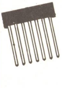

14-T3 100 for **$30.00**
16-T3 100 for **$30.00**

50 of ea. for **$32.00**

ACE • All-Circuit Evaluator

for fast, solderless, plug-in circuit building and testing

Model 236

Just plug in any components with leads to .032'' dia. Interconnect with solid wire up to 20 ga. Assembled models too!

10% OFF

ACE Model No.	Tie Points	DIP Capacity	No. Buses	No. Posts	Board Size (inches)	Price Each
200-K (kit)	728	8 (16's)	2	2	4-9/16 x 5-9/16	$18.95
208 (assem.)	872	8 (16's)	8	2	4-9/16 x 5-9/16	28.95
201-K (kit)	1032	12 (14's)	2	2	16 x 7	24.95
212 (assem.)	1224	12 (14's)	8	2	4-9/16 x 7	34.95
218 (assem.)	1760	18 (14's)	10	2	6-1/2 x 7-1/8	46.95
227 (assem.)	2712	27 (14's)	28	4	8 x 9-1/4	59.95
236 (assem.)	3648	36 (14's)	36	4	10-1/4 x 9-1/4	79.95

Gold-anodized aluminum base/ground; non-corrosive nickel-silver terminals; 4 rubber feet.

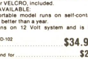

SALE

LIQUID CRYSTAL DIGITAL CLOCK-CALENDAR

- For Auto, Home, Office
- Small in size (2x2½x½)
- Push button for seconds release for date.
- Clocks mount anywhere with either 3M double-sided tape or VELCRO, included.
- 2 MODELS AVAILABLE:
  LCD-101, portable model runs on self-contained batteries for better than a year.
  LCD-102, runs on 12 Volt system and is back-lighted.
- LCD-101 or LCD-102 your choice .... **$34.95** ea.
- Clear desk stand for **$2.00**

---

3 LEVEL GOLD WIRE WRAP SOCKETS

	1-24	25-49	50-99
8 pin	.47	.42	.37
10 pin	.45	.41	.37
14 pin	.39	.38	.37
16 pin	.43	.42	.40
18 pin	.75	.68	.62
22 pin	1.00	.97	.95
24 pin	1.00	.94	.75
28 pin	1.09	.98	.84
36 pin	1.59	1.45	1.30
40 pin	1.49	1.39	1.29

Vector

MICRO-KLIP
for .042 dia. holes
(all boards on this page)

T42-1 pkg. 100	$ 1.50
T42-1 pkg. 1000	$11.00
P-149 hand installing tool	$ 2.03

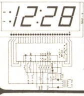

.8'' LED ALARM CLOCK

12 hr. LED Alarm Clock uses 3½ digit .8'' LED Display with AM/PM indicators and colons. Direct drive, PIN to PIN interface with S1998A I.C. Just add switches, AC Supply, Alarm. Display and I.C. only.

$7.95 or 2/$15.00

Price Breakthrough! **$17⁹⁵**

MA1003 CAR CLOCK

Bright Green Fluorescent Display Crystal Time Base Assembled, just add switches and 12 VDC.

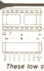

SPECIAL

14CS2 100 for $14⁰⁰
16CS2 100 for $16⁰⁰
14 pin CS2 10 for $2⁰⁰
16 pin CS2 8 for $2⁰⁰

These low cost DIP sockets will accept both standard width plugs and chips. For use with chips, the sockets offer a low profile height of only .125'' above the board. These sockets are end stackable.

WRAP POST
for .042 dia. holes
(all boards on this page)

T-44 pkg. 100	$ 2.28
T-44 pkg. 1000	$14.00
A-13 hand installing tool	$ 2.80

PRIORITY ONE ELECTRONICS

VISA

10031 S Woodley Ave. Sepulveda CA. 91343

master charge

Terms: VISA, MC, BAC, check, Money Order, C.O.D., U.S. Funds Only. CA residents add 6% sales tax. Minimum order $10.00. Orders less than $75.00 include 10% shipping and handling; excess refunded. Just in case . . . please include your phone no. **"Sorry, no over the counter sales"** **Good thru June 15, 1978**

Send for our latest brochure.

phone orders welcome (213) 893-8202

OEM and Institutional inquiries invited.

---

24 PIN DIP PLUGS WITH COVERS

3 / $1.00
40 / $10.00

CIRCLE 2 ON FREE INFORMATION CARD

600 MHZ. FREQUENCY COUNTER
±0.1 PPM TCXO

OPTO-8000.1

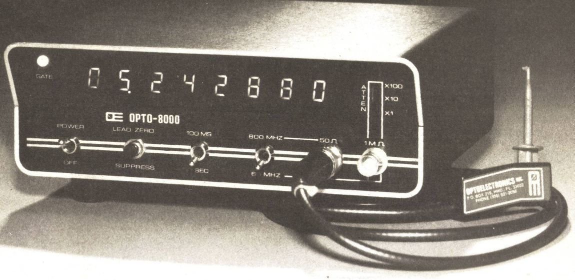

This new instrument has taken a giant step in front of the multitude of counters now available. The Opto-8000.1 boasts a combination of features and specifications not found in units costing several times its price. Accuracy of ±0.1 PPM or better — *Guaranteed* — with a factory-adjusted, sealed TCXO (Temperature Compensated Xtal Oscillator). **Even kits require no adjustment for guaranteed accuracy!** Built-in, selectable-step attenuator, rugged and attractive, black anodized aluminum case (.090″ thick aluminum) with tilt bail. 50 Ohm and 1 Megohm inputs, both with amplifier circuits for super sensitivity and both diode/overload protected. Front panel includes "Lead Zero Blanking Control" and a gate period indicator LED. AC and DC power cords with plugs included.

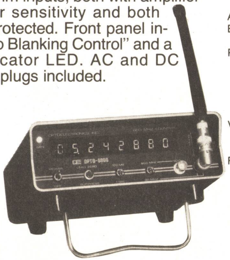

OPTOELECTRONICS, INC.

5821 NE 14 Avenue
Ft. Lauderdale, FL 33334
Phones: (305) 771-2050   771-2051
Phone orders accepted 6 days, until 7 p.m.

master charge
THE INTERBANK CARD
BANKAMERICARD
welcome here

SPECIFICATIONS:
Time Base—TCXO ±0.1 PPM GUARANTEED!
Frequency Range—10 Hz to 600 MHz
Resolution—1 Hz to 60 MHz; 10 Hz to 600 MHz
Decimal Point—Automatic
All IC's socketed (kits and factory-wired)
Display—8 digit LED
Gate Times—1 second and 1/10 second
Selectable Input Attenuation—X1, X10, X100
Input Connectors Type —BNC
Approximate Size—3″h x 7½″w x 6½″d
Approximate Weight—2½ pounds
Cabinet—black anodized aluminum (.090″ thickness)
Input Power—9-15 VDC, 115 VAC 50/60 Hz
or internal batteries

OPTO-8000.1 Factory Wired	**$299.95**
OPTO-8000.1K Kit	**$249.95**

ACCESSORIES:

Battery-Pack Option—Internal Ni-Cad Batteries and charging unit	**$19.95**
Probes: P-100—DC Probe, may also be used with scope	**$13.95**
P-101—LO-Pass Probe, very useful at audio frequencies	**$16.95**
P-102—High Impedence Probe, ideal general purpose usage	**$16.95**
VHF RF Pick-Up Antenna-Rubber Duck w/BNC #Duck-4H	**$12.50**
Right Angle BNC adapter #RA-BNC	**$ 2.95**

FC-50 — Opto-8000 Conversion Kits:
Owners of FC-50 counters with #PSL-650 Prescaler can use this kit to convert their units to the Opto-8000 style case, including most of the features.

FC-50 — Opto-8000	**Kit $59.95**
*FC-50 — Opto-8000F	**Factory Update $99.95**
FC-50 — Opto-8000.1 (w/TCXO)	**Kit $109.95**
*FC-50 — Opto-8000.1F	**Factory Update $149.95**

*Units returned for factory update must be completely assembled and operational

TERMS: Orders to U.S. and Canada, add 5% to maximum of $10.00 per order for shipping, handling and insurance. To all other countries, add 10% of total order. Florida residents add 4% state tax. C.O.D. fee: $1.00. Personal checks must clear before merchandise is shipped.

CIRCLE 13 ON FREE INFORMATION CARD

MINI MINI TOGGLE

EXTRA SMALL D.P.D.T.
3A 125VAC CONTACTS
each $1.50
8 — 10.
100 —$105.

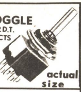

LOOK new

RCA 40374

250V - 2A NPN TO66

POWER TRANSISTOR MOUNTED ON A FACTORY ASSEMBLED HEAT SINK - 5.8 WATTS @ AMBIENT OF 25C

$.75 ea. 10 for $6

BISTABLE RELAY

SPDT 6VDC 200 OHM COILS
1 AMP 20 WATT DC CONTACTS
LONG LIFE (1×10^9) OPER.
HIGH SPEED (500 HZ)
HERMETICALLY SEALED

3/8X3/8X3/4"

$2.95 ea.

ELEC-TROL REED RELAY

12 vdc
440 Ω coil
dpst n.o.

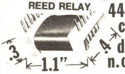

PICTURE IS APPROXIMATION, RELAY HAS FOUR PINS ON ONE END AND TWO ON OTHER, PINS ARE SPACED .1" X 1". 1/2A CONTACTS.

$1.75 ea.-ten $15

POTTER BRUMFIELD

Type KHP Relay
4 PDT 3A Contacts
24VDC COIL
650 ohms
120VAC
10.5MA

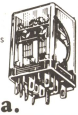

$1.60 ea.

DIP TRIMMER

12 TURN, 1/4"x1/4"x1/4
5K or 200K only
mfg. DALE
$.50 TEN FOR $4

$1.35 10·$12

C & K #7103
Single pole double throw center off (3 position) toggle switch.........

1/8 WATT RESISTORS

10 ea.-390, 1.8k, 3.9k, 6.8k, 11k 43k, 68k, 240k - 5 percent tol.

80 FOR $4

2A,50V bridge 39¢ea

ultra sensitive relay

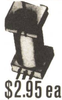

Single pole normally open dry reed relay. Unbelievable sensitivity,1800 ohm coil with 3 volt pull-in (that's less than 3 ma.) A TTL gate will drive many of these. A CMOS buffer will directly actuate this nifty relay.... MFG. unknown, but I was told they came from IBM. 600 available

$2.95 ea.

-SUPER SPECIALS-

DIAC 27 TRIGGER DIODE . . .	.20
PULSE XFMR. 1/1 TOROID-ENCASED	.25
600MFD. 360VDC PHOTO FLASH CAP.	.90
1702A 2K, 1us, EPROM	7.95
SP425 SPERRY 9 digit ¼" HV multiplexed 7 seg.	1.25
MM5369 time base osc. chip	1.75
T.V. crystal for above.....	1.75
1101A 256 x 1 MOS RAM	.59
93410 256 x 1 45NS RAM . . .	.85
75451 peripheral driver . .	.40
7402 TTL nor gate	.16
7430 TTL nand gate	.14
CERAMIC FILTER 10.7 MHz. . .	1.20
MM5058 1024 bit static SR . .	1.50
UA715 60MHz. op-amp	1.20
74S206 256 x 1 45NS RAM . . .	.90
78L2.6 2.6V TO92 .1A +regul.	.29
78L05 5.0V " " "	.29
78L6.2 6.2V " " "	.29
78L12 12V " " "	.29
78L15 15V " " "	.29
78M05 5V tab .5A + regul.	.59
78MG 4 term. adj. .5A + reg.	1.29
79MG " " " " - reg.	1.39
7805T tab 1A 5v regul	.89
7812 to-3 1A +12V regul.	.59

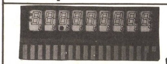

SPERRY 9 DIGIT PLASMA DISPLAY, COMMON CATHODES, 1/4" HIGH DIGITS--
DM8880 IC DRIVER FOR "NIXIE" ABOVE DISPLAYS 0123456789AbCdEF WITH 0-15 BINARY INPUT............

DISPLAY or IC $1.50 BOTH $2.75

FANTASTIC

RCA 40536
2A 400V TRIAC

TO5

FACTORY ASSEMBLED ON HEAT SINK READY TO PUT IN YOUR CIRCUIT BD.

$.90 ea. 10 for $7.50

TOLL-FREE TELEPHONE SERVICE

24 HOURS A DAY

$15 minimum order

To order by phone

7 DAYS A WEEK

NOTE: Operators can only handle orders, so please address all inquiries and questions directly to our company.

DIAL: 800 423 2355 EXT 307

Any Time Day or Night *(California Residents Please Dial 800-232-2175)*

PHONE ORDERS CAN ONLY BE CHARGED TO MASTER CHARGE OR VISA/BANKAMERICARD

PO BOX 41778
Sacramento, Ca.
95841
916 334 2161

Money back guarantee - $5 minimum order. we pay post on orders for $10 or more. All payment must be in U.S. funds Foreign orders must include post BAC & MC are not prepaid orders and shipping is added

4811 MYRTLE AVE

BABYLON ELECTRONICS

Your BANKAMERICARD welcome here

CIRCLE 78 ON FREE INFORMATION CARD

WIREWRAP

PRECUT WIRE

Why buy wire on rolls?

PRECUT & STRIPPED WIRE IS:

- **Fast** - No more cutting & stripping by hand
- **Reliable** - Good, clean, uniform strip
- **Economical** - Cheaper than using bulk wire

Precut Wire	Bulk Wire
100 pcs of 3" at $.82 = **3¼¢/ft.**	50 ft. roll at $1.99 = **4¢/ft.**
100 pcs of 6" at 1.06 = **2¢/ft.**	100 ft. roll at 2.95 = **3¢/ft.**
Wire Kit 1 at $6.95 = **2 1/3¢/ft.**	

30 Kynar stripped 1" on each end. Lengths are overall
Colors: Red,Blue,Green,Yellow,Black,Orange,White
Wire packaged in plastic bags. Add 25¢/length for tubes.

	100	500	1000	5000
2½ in.	.78	2.40	4.30/K	3.89/K
3 in.	.82	2.60	4.71/K	4.22/K
3½ in.	.86	2.80	5.12/K	4.55/K
4 in.	.90	3.00	5.52/K	4.88/K
4½ in.	.94	3.21	5.93/K	5.21/K
5 in.	.98	3.42	6.34/K	5.52/K
5½ in.	1.02	3.65	6.75/K	5.86/K
6 in.	1.06	3.85	7.16/K	6.19/K
6½ in.	1.15	4.05	7.57/K	6.52/K
7 in.	1.20	4.25	7.98/K	6.85/K
7½ in.	1.25	4.45	8.39/K	7.18/K
8 in.	1.29	4.65	8.80/K	7.53/K
8½ in.	1.32	4.85	9.21/K	7.84/K
9 in.	1.36	5.05	9.62/K	8.17/K
9½ in.	1.40	5.25	10.03/K	8.50/K
10 in.	1.45	5.51	10.44/K	8.83/K
Addl. in.	.10	.41	.82/K	.66/K

WIRE KITS

# 1	$6.95		
250	3"	100	4½"
250	3½"	100	5"
100	4"	100	6"

# 2	$19.95				
250	2½"	250	4½"	250	6"
500	3"	250	5"	100	6½"
500	3½"	100	5½"	100	7"
500	4"	1 250 ft. Roll Bulk			

Choose One Color
or Assortment

WIRE WRAP SOCKETS

	1-9	10-24	25-99	100-249	250-999	1K-5K
8 pin*	.41	.38	.35	.31	.29	.27
14 pin*	.42	.39	.36	.32	.29	.27
16 pin*	.46	.43	.39	.35	.32	.30
18 pin*	.63	.58	.54	.47	.44	.41
20 pin	.84	.78	.71	.63	.59	.54
22 pin*	1.30	1.20	1.10	.95	.90	.84
24 pin	.91	.84	.78	.68	.64	.59
28 pin	1.25	1.15	1.08	.95	.89	.82
40 pin	1.65	1.55	1.42	1.25	1.15	1.09

Gold 3-level Closed Entry Sockets
End & Side Stackable All prices include gold
Tin sockets and 2-level sockets available

WIRE WRAP TOOLS

$34.95

HOBBY WRAP
Model BW 630
With Free Wire Kit 1
($6.95 Value)

Batteries & Charger	$11.00
WSU 30 Hand Wrap-Unwrap Strip Tool	5.95
WSU 30M, for Modified Wrap	6.95
BT 30 Extra Bit	2.95

INTERCONNECT CABLES

Ribbon cable connectors for connecting boards to front panels, or board to board.

	SINGLE ENDED			DOUBLE ENDED		
	14 pin	16 pin	24 pin	14 pin	16 pin	24 pin
6"	1.24	1.34	2.05	2.24	2.45	3.37
12"	1.33	1.44	2.24	2.33	2.55	3.92
24"	1.52	1.65	2.63	2.52	2.76	4.31
48"	1.91	2.06	3.40	2.91	3.17	5.08

PAGE DIGITAL ELECTRONICS
135 E. Chestnut Street 4A
Monrovia, California 91016
Phone (213) 357-5005

Ordering Information:

- Orders under $25 and COD's, add $2
- All others, shipped Ppd in U.S. via UPS
- For Blue Label (Air) or 1st Class, add $1
- We accept Visa & Mastercharge
- Most orders shipped same day

Dealer Inquiries Invited

CIRCLE 3 ON FREE INFORMATION CARD

Why Wait?

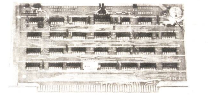

The Tarbell Cassette Interface

- Plugs directly into your IMSAI or ALTAIR*
- Fastest transfer rate: 187 (standard) to 540 bytes/second
- Extremely Reliable — Phase encoded (self-clocking)
- 4 Extra Status Lines, 4 Extra Control Lines
- 37-page manual included
- Device Code Selectable by DIP-switch
- Capable of Generating Kansas City tapes also
- No modification required on audio cassette recorder
- Complete kit $120, Assembled $175, Manual $4

TARBELL ELECTRONICS

20620 S. Leapwood Ave., Suite P, Carson, Ca. 90746
(213) 538-4251

California residents please add 6% sales tax

*ALTAIR is a trademark/tradename of MITS, INC.

CIRCLE 5 ON FREE INFORMATION CARD

ETCO ELECTRONICS

T.M.

$1,000,000 SURPLUS SALE

6 Position, 5 Gang
LOW LOSS ROTARY SWITCH!

A beautiful switch, 3 widely spaced wafers afford afford many interesting switching combinations. As two of the wafers are double sided you get a total of 5 rotary switches. 1¼" dia., 4½" long. ¼" shaft. 3000 in stock. (5 Oz.) J082SW.

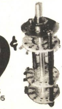

99¢

10/$8.95
50/$39.95

"Snap-in" Rear Mount
PILOT LAMP SOCKET!

Compare! Save!..

Standard miniature bayonet base socket riveted to snap-in 5/8" hole plug. A neat push-in mount. Excellent for back lighting your projects, panel meters, etc. Snaps out easily for bulb change. Solder tab terminal - other side of socket grounded. (1 oz.) **J176BB.**

19¢

25/$4.49
100/$16.95

TEN "MICRO" L.E.D.'S!

FREE

—with every order of $10 or more from this page! Prime stock. Dialight No. 521-9186 - red. exactly as pictured. Request 10 No. J155DR. (A $2 value!).

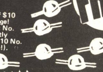

LOW POWER TRANSISTOR SPECIALS!

PRIME FACTORY-FRESH INVENTORY!

SALE!

2SA673B: Silicon PNP, 400mw @ 25° C. Planar epitaxial. Max. ratings: BVcbo 50V, BVebo 4V. Ic 500 ma., Hfe 40. Order ETCO **J171DS.** (1 oz.)

69¢

2SC1213: As above, but BVcbo-35 V. Order ETCO **J170DS** (1 oz.)

10/$5.95

POTTER & BRUMFIELD
4PDT 110 VDC RELAY!

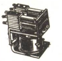

FACTORY SURPLUS!

2.95

3/$7.95

Low cost all-purpose multiple-contact; use for many industrial control applications. tinned solder terminals. Silver contacts, rated 5A @ 28 VDC or 120 VAC. Self cleaning. P & B No. GA2290. Easily converted to 110 VAC operation with diode. Coil res. 6,050 ohms. Draws 18 ma. Brand new. (4 oz.) **J062RL.**

MICRO TRIMMERS!

VALUE!

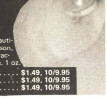

Photographed on a thumbnail - beautiful for micro,mini work. By Johanson, and Erie. Brand new surplus at a fraction of the regular price. 3/16" dia. 1 oz.

J277CC – 3.5-20 pf. $1.49, 10/9.95
J058CC – 5-30 pf $1.49, 10/9.95
J249CC – 7-40 pf $1.49, 10/9.95

MICROTEMP Fire Prevention
THERMAL CUTOFF SWITCHES!

29¢

10/$2.49
100/$19.95
1000/$149.00

Microtemp No. 4168A. Tiny "one-shot" protection devices that "cut out" at 76° C. Use these to protect expensive appliances and equipment. UL and CSA approved. Protect motors, projectors, coffe machines, solenoids, heaters, electric blanket controls, etc. Over 15,000 in stock. (1 oz.) **J316SU.**

Surplus Scanner
9-CHANNEL SELECTOR SWITCH!

impossible low price!

Nine **not interlocked** DPDT switched on a strip. Each is push-on, push-off. Strip is 5¾" long. Exactly as pictured. 500 in stock. (4 oz.) **J054SW.**

99¢

10/$8.95

8--ROCKER DIP SWITCH!

INCREDIBLE ETCO VALUE!

8 SPST on-off switches - for easy programming of logic circuitry. Plugs into any 16 pin DIP socket. Excellent value. Brand new Factory surplus. (1 oz.) **J122SW.**

1.79

10/$14.95

Intriguing!
ELECTRONIC CAMERA SHUTTER!

Delightful experimenters and inventors item. Complex mechanism includes photocell, solenoid, pressure switches, PC, transistors, resistors, caps. Automatically light-controls a camera shutter. Excellent educational item. These are brand new surplus worth many times our price. Exactly as pictured. (6 oz.) **J1200OP.**

1.49

SPECIAL OFFER

10/$12.49

40 KHz ULTRASONIC MICROPHONE!

Brand new Factory surplus. Build remote controls, signalling devices, intrusion alarms, etc. etc. A great experimenters item. (2 oz.) **J037SU.**

CLOSE-OUT!

1.95

10/$16.95

2-20pf MICA TRIMMER!

SAVE!

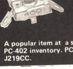

99¢

10/$7.95

A popular item at a surplus price. Brand new Arco No. PC-402 inventory. PC board tabs. ½" x 3/8" (1 oz.) J219CC.

New ITEMS!

LAST MINUTE ARRIVALS - NO SPACE TO SHOW - BUT WE HAVE THESE IN STOCK FOR IMMEDIATE SHIPMENT!

J288BB - F15T5CW 15" fluorescent copier bulb (GE)(3 0z.) **99c ea. 10/7.95, 100/59.95**
J310SU - SYLVANIA 4 channel LF FM receiver used in wireless classroom systems (12 oz.) **$9.95**
J311SU - XEROX No. 600S60311 billing kit (2 lb.) . . **$14.95**
J180HM—AIRPAX magnetic pickup transducer(4 oz) **$9.95**
J307SU - 2 x 8W surplus stereo amplifier (2lb.) **$12.95**
J168DS - RCA 40536 triac c/w heatsink (1 oz.) **1.29, 10/9.95**
J169DS - RCA 40374 pwr. transistor (1 oz.) **$1.39, 10/10.88**
J126HP - 12 V AC/DC mini alarm horn (4 oz.). **99c, 10/$8.95**
J023SP - 2" underwater speaker/mike (2 oz.) **$1.95, 10/17.95**
J097PT - 5 lb. electronics surprise box (5 lb.) **$2.95**
J012SP - LESLIE 8" rotating organ speaker (15 lb.) . . **$49.95**

Takes 8 Crystals –
MULTI-CRYSTAL SOCKET!

SPECIAL PURCHASE!

NEW!

Brand new surplus from scanner manufacturer. Holds 8 standard crystals with 3/16" pin spacing. Exactly as pictured. 1½" x 7/16" x 5/16"H. (1 oz.) **J002XT.**

99¢

10/$8.95

Westinghouse 4" 80 AMP DC PANEL METER!

SURPLUS

5.95

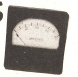

Beautiful surplus - requires 80 amp, 50 mv external shunt. Calibrated for 1/8" steel panel. F.S. = 50 mv. Westinghouse Style No. FE-13606-22 (1¼ lb.) **J595TE.**

LIMITED QUANTITY!

We Have 18,000 of These –
Brown Plastic TELEPHONE WALL PLATES!

super buy

Incredible value! Ideal for telephone cords, CCTV, MATV and cable TV outlets, intercom and speaker cables, etc. Use in apartments, hospitals, offices, schools, multi-room areas. At this low price, the plate can be used as a "chassis", adding standard fittings for the fabrication of custom plates. New, GE cello packed with fittings as pictured. Brown. (4 oz.) **J054HD.**

29¢

10/$2.49
100/$19.95
1000/$99.00

RECORD CLEANING CLOTH SPECIAL!

ETCO SCOOP!

29¢

Silicone treated!

Individually sealed- may be stored for future use (1 oz.) **J117MS.**

10/$2.49
100/$19.95

TELEPHONE YOUR ORDERS – Phone in your charge-card orders at low station-to-station rates!

CALL: 1 - 518 - 561 - 8700.

SURPLUS WANTED - Contact our buying office at 1-514-695-0400 or send list and samples to Plattsburgh address below.

CANADIANS – Ordering from this ad is simple. Please remit in U.S. funds (or add 10% to overall total and remit in Canadian funds) - (Chargex and Mastercharge welcome). We do the paperwork and ship to you direct from the U.S.A. at low American prices. You pay duty and tax to Canadian Customs (Canadian schools are exempt). We have stores in Canada, too! Write for Canadian catalogs. We invite you to visit our Plattsburgh store - just 50 minutes from Montreal on U.S. 87!

ETCO ELECTRONICS

T.M.

Rush Your Order Today . . . . .
Shipped to you direct from our new mailorder headquarters and warehouse store!

ETCO ELECTRONICS CORP. U.S.A.
North Country Shopping Center,
Route No. 9, Plattsburgh, N.Y. 12901.

MERCHANDISE SUBJECT TO PRIOR SALE. Full remittance with each order, please. Money Order, Certified check, BANKAMERICARD, VISA, MASTERCHARGE or CHARGEX. Add 20% for UPS (or postage) and handling (we refund excess). Please try to bring your order total to $10 or more. Worldwide export orders solicited. Open account to Government agencies, schools, institutions and triple "A" rated industrial & commercial accounts. Special quotes for quantities. N.Y. state residents: add 7% sales tax.

CIRCLE 9 ON FREE INFORMATION CARD

RADIO HUT

1-800-527-2304

Use Our Toll Free Watts Line

For Master Charge and BankAmericard Orders

VISA

master charge

VARIABLE POWER SUPPLY KIT NO. 1

ONLY $10.95

- Continuously variable from 5V to 20V
- Excellent regulation up to ½ Amp
- Kit includes all components
- Drilled fiberglass P.C. Board
- Case Included
- 4400 Mfd of filtering
- One hour assembly

VARIABLE POWER SUPPLY KIT NO. 2

Same as above but with a 1 Amp output, also with case

ONLY $13.95

This model will power a 5 watt transistorized CB Radio

LOOK AT THIS SPECIAL FROM RADIO HUT

- Power Supply Kit: 5V1 amp reg.
- Line regulation .005%
- Load regulation 50mV

Kit includes components, PC board, transformer, fuse and pilot light. Line cord not included.

Only $6.50

60 Hz. Crystal Time Base for Digital Clocks

$4.50

Buy 2 for $8.

A. 60 Hz. output with accuracy comparable to a digital watch.
B. Directly interfaces with all MOS clock chips.
C. Super low power consumption (1.5 ma type.)
D. Uses latest MOS 17 stage divider IC.
E. Eliminates forever the problem of AC line glitches.
F. Perfect for cars, boats, campers, or even for portable clocks at ham field days.
G. Small size, can be used in existing enclosures.

KIT INCLUDES CRYSTAL, DIVIDER IC, P.C. BOARD PLUS ALL NECESSARY PARTS & SPECS.

UNSCRAMBLER

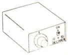

$19.95

Plugs into earphone or external speaker of any Scanner or Monitor. Guaranteed to unscramble any 1085 call.

- Easily tuned
- Full instruction included
- Drilled fiberglass P.C. Board
- One Hour Assembly
- Punched Case

7400 TTL DIGITAL CIRCUITS

7400	.11	7430	.13	7480	.31	74153	.61
7401	.13	7432	.23	7481	.55	74154	.98
7402	.13	7433	.26	7482	.57	74155	.89
7403	.13	7437	.23	7483	.67	74156	.89
7404	.15	7438	.23	7485	.89	74157	.55
74L04	.29	7440	.13	7489	1.25	74160	.55
74S04	.44	7441	.76	7490	.65	74161	.65
7405	.13	7442	.47	7491	.61	74163	.65
7406	.16	7443	.59	7492	.43	74164	.85
7407	.16	7444	.59	7493	.43	74165	.89
7408	.19	7446	.68	7494	.67	74174	.85
7409	.19	7447	.68	7495	.67	74175	.85
7410	.13	7448	.71	7496	.67	74180	.67
7411	.18	7450	.13	74100	.30	74181	1.93
7412	.26	7451	.13	74104	.49	74182	.68
7413	.37	7453	.13	74107	.28	74191	.98
7416	.15	7454	.13	74109	.31	74192	.79
7420	.13	7460	.19	74121	.29	74193	.81
7421	.13	7470	.27	74123	.48	74194	.81
7423	.25	7472	.25	74132	.99	74195	.69
7425	.29	7473	.29	74136	.99	9316	.85
7426	.24	7474	.29	745138	1.95	9601	3/$1
7427	.19	7475	.47	74141	.75	9L04	.35
7428	.26	7476	.31	74151	.61		

74LS00 LOW POWER SCHOTTKY

74LS00	.21	74LS47	.73	74LS136	.37	74LS258	.71
74LS02	.21	74LS51	.26	74LS138	.71	74LS260	.26
74LS03	.21	74LS54	.26	74LS139	.71	74LS266	.26
74LS04	.28	74LS55	.26	74LS145	1.00	74LS279	.55
74LS05	.28	74LS73	.35	74LS151	.70	74LS290	.75
74LS08	.21	74LS74	.35	74LS153	.70	74LS293	.61
74LS09	.28	74LS76	.49	74LS155	.69	74LS295	.95
74LS10	.21	74LS83	.73	74LS156	.70	74LS298	.95
74LS11	.21	74LS85	1.35	74LS157	.75	74LS365	.55
74LS13	.45	74LS86	.36	74LS158	.71	74LS366	.55
74LS14	.99	74LS90	.55	74LS160	.85	74LS367	.55
74LS15	.26	74LS92	.55	74LS161	.85	74LS368	.55
74LS20	.24	74LS93	.55	74LS162	.85	74LS390	1.75
74LS21	.28	74LS109	.38	74LS163	.85	74LS393	1.45
74LS22	.28	74LS112	.38	74LS164	1.49	74LS670	2.30
74LS26	.32	74LS113	.38	74LS168	.85	74LS192	.95
74LS27	.32	74LS114	.38	74LS169	.85	74LS193	.95
74LS30	.26	74LS122	.49	74LS170	1.69	74LS194	.95
74LS32	.32	74LS124	.99	74LS173	1.10	74LS195	.85
74LS37	.32	74LS125	.47	74LS174	1.00	74LS196	.85
74LS38	.32	74LS126	.47	74LS175	.81	74LS197	.85
74LS40	.26	74LS132	.79	74LS190	.95	74LS251	.85
74LS42	.65	74LS133	.35	74LS191	.95	74LS253	.81
						74LS257	.71

74H SERIES TTL

74H00	.18	74H21	.29	74H53	.29	74H73	.39
74H05	.29	74H40	.29	74H61	.25	74H74	.39
74H20	.29	74H50	.20	74H72	.45		

CMOS

CD400	.19	CD4017	.95	CD4040	1.00	CD4071	.19
CD4001	.19	CD4018	.95	CD4041	.69	CD4081	.19
CD4002	.19	CD4019	.19	CD4042	.69	CD4507	.35
CD4006	1.20	CD4020	.97	CD4043	.60	CD4508	2.80
CD4007	.19	CD4021	.97	CD4044	.60	CD4510	1.00
CD4009	.47	CD4022	.97	CD4046	1.39	CD4512	1.10
CD4010	.39	CD4023	.19	CD4047	1.50	CD4516	.79
CD4011	.19	CD4024	.75	CD4049	.35	CD4518	1.10
CD4012	.29	CD4025	.19	CD4050	.39	CD4520	.69
CD4013	.32	CD4027	.39	CD4051	1.19	CD4528	.85
CD4014	.78	CD4028	.85	CD4053	1.19	74C02	.45
CD4015	.78	CD4029	.99	CD4056	1.15	74C04	.32
CD4016	.32	CD4030	.35	CD4066	.78	74C107	.79

TTL SPECIAL!

9002/7400	10/1.00
9003/7410	10/1.00
9004/7420	10/1.00
9006/7460	6/1.00
9007/7430	10/1.00
9009/7440	10/1.00
9016/7404	8/1.00
9024/74109	3/1.00
9300/74195	3/1.00

9000 series parts prime from ITT. Pin for Pin compatible with 7400 series.

DTL

932	Dual 4 Input Buffer	8/$1
934	Dual 5 Input NAND Gate	10/$1
941	One Shot Multivibrator	5/$1
945	JK F/F	8/$1
946	Quad 11 Input Gate NAND/NOR	8/$1
948	JK F/F	8/$1
950	F/F	10/$1
951	One Shot Multivibrator	5/$1
1800	(see 934 above)	10/$1
1806	Quad 2 Input NAND Gate	10/$1
9093	Dual JK F/F	8/$1
9094	Dual JK F/F	8/$1
9097	Dual JK F/F	8/$1
9099	Dual JK F/F	8/$1
9109	Hex Inverter	7/$1
9110	Hex Inverter	7/$1
9112	Hex Inverter	7/$1
9601	One Shot	3/$1
9930	Dual 4 Input Ext. NAND	8/$1
9932	Quad 2 Input NAND Buffer	8/$1
9945	RS F/F	8/$1
9946	Quad 2 Input NAND	8/$1
9949	Quad 2 Input NAND	8/$1
9951	Monostable Multivibrator	8/$1
9962	Triple 3 Input NAND	8/$1

ITT HIGH LEVEL LOGIC

301	Dual 5 Input NAND Gate	.15
302	Quad 2 Input Buffer open collector	.18
303	Quad 2 Input NAND Buffer	.15
311	Master Slave F/F	.18
312	Dual JK Flip Flop	.18
321	Quad 2 Input NAND Gate	.18
322	Dual 5 Input NAND Gate	.15
323	Quad 2 Input NAND Gate	.18
324	Quad 2 Input NAND Gate	.18
325	Dual 2 Dual 3 Input NAND Gate	.13
326	Dual 2 Dual 3 Input NAND Gate	.13
331	Dual 5 Input Expander	.13
332	Hex Inverter	.18
333	Hex Inverter	.18
334	Hex Inverter	.18
335	Hex Inverter	.18
342	Dual One Shot Multivibrator	.25
343	Dual 4 Bit Comparator	.22
370	Quad D Flip Flop	.22
371	Decode Counter	.30
372	Quad Ripple Counter	.39
380	BCE to Decimal Decoder	.39
381	BCD to Decimal Decoder	.39

ITT LED DRIVERS

ITT 501 Quad Seg. Dr.	.35
ITT 502 Hex Digit Dr.	.49
ITT 503 Quad Seg. Dr.	.49
ITT 506 Hex Digit Dr.	.49
ITT 508 8 Digit Dr.	.49
ITT 509 8 Seg. Dr.	.49
ITT 511 Quad Seg. Dr.	.55
ITT 514 8 Digit Dr.	.59

We have 100's of thousands of listed parts. These parts are 100% prime.

DIODES

IN 4002 1 Amp 100 PIV	40/$1
IN 4004 1 Amp 400V	15/$1
IN 4007 1 Amp 1000V	10/$1

GERMANIUM DIODES

IN 54A	$8/$1
IN 270	10/$1

ZENER DIODES

IN 746 3.3V 400M	4/$1
IN 752 5.6V 400M	4/$1
IN 1958 8.2V 400M	4/$1
IN 5259 39V 500M	10/$1
IN 5271 100V 500M	10/$1
IN 5280 180V 500M	10/$1

HOUSE # ZENER

4.7V 500 MW	10/$1
9. V 500 MW	10/$1
10V 1 Watt	8/$1
15V 500 MW	10/$1
22V 5 Watt	6/$1

SWITCHING DIODES

IN 4148/IN914 Long Leads	20/$1
IN 4148/IN914 Cut Leads	40/$1
IN 4148/IN914 PC Leads	100/$2

IMSAI SPECIAL

S-100 Connector

$3.95 Ea.

BRIDGE RECTIFIERS

1 Amp	200V	6/$1
6 Amp	50V	1.10
10 Amp	50V	1.25
25 Amp	50V	1.39

SOCKETS

• 8 Pin Low Profile	20
• 14 Pin Low Profile	22
• 16 Pin Low Profile	25
• 18 Pin Low Profile	30
• 28 Pin Low Profile	69
• 40 Pin Low profile	89

HOUSE # TTL IC's

7400	10/1.00	7437	6/1.00
7404	10/1.00	7438	6/1.00
7408	10/1.00	74141	3/1.00
7420	10/1.00	74153	3/1.00

Please specify that you are ordering House Number TTL.

CRYSTALS

300 KHz	$1.50
3.57945	1.25

COUNTER AND CLOCK CHIPS

MK50252	Clock Chip	$4.99
MM5316	Clock Chip	3.75
MK50250	Alarm Clock	3.75
MK50380	Alarm Chip	2.95
FCM7010	Direct Drive Clock Chip	4.95
MK5005	4 Digit Counter w/Latch	8.50
MK5002	4 Digit Counter	8.95
MK50395	6 Digit UP/Down Counter	12.95
MK50397	6 Digit Elapsed Timer	8.95
CT5005	Calculator Chip w/Specs	1.25
MK5021	Cal. Chip w/sq. rt.	2.50

SOCKET SPECIAL! 28 PIN 1C SOCKET 3 FOR $1 WHEN PURCHASED W/CLOCK 1C

TRANSISTORS

INTERSIL DUAL TRANSISTORS

Originally Cost $3. each

Similar to 2N913

2 Per Pack 2/$1

GENERAL PURPOSE		POWER TRAN.	
2N 2905 PNP	4/$1	115 W 200V NPN	95
2N 3904 NPN	8/$1	TIP 29 (EP967) NPN	4/$1
2N 3906 PNP	8/$1	TIP 30 (EP929) PNP	4/$1
2N 3392 Pre-Amp	25/$1	TIP 31 P.C. Leads NPN	5/$1
2N 4400 NPN	10/$1	MJE 2370	3/$1
2N 4402 PNP	10/$1	2N 3055	75
EN 2222 NPN	8/$1	TN 2021 By RCA	95
EN 2907 PNP	8/$1	FET TIS 75 HOUSE #	5/$1

CAPACITORS

ELECTROLYTIC

AXIAL TYPE		RADIAL TYPE	
20 MFD 250V	5/$1	47 MFD 35V PC Leads	10/$1
35 MFD 25V	15/$1	68 MFD 25V PC Leads	8/$1
200 MFD 25V	5/$1	330 MFD 50V PC Leads	5/$1
470 MFD 35V	4/$1	470 MFD 16V	4/$1
470 MFD 16V	4/$1	1000 MFD 35V PC Leads	4/$1
500 MFD 35V	5/$1		
2000 MFD 16V	3/$1	150 PFD MICA 5%	10/$1

COMPUTER GRADE	
1,900 MFD 35WVDC (Mini)	3/$2
8,000 MFD 15WVDC	95 cents each
33,000 MFD 40WVDC	$4.00 Each

TANTALUM	
1 MFD20 WVDCPC Leads	15/$1
3.3 MFD35 WVDC PC Leads	8/$1
4.7 MFD10 WVDC PC Leads	5/$1
10 MFD20 WVDC PC Leads	8/$1
33 MFD10 WVDC	6/$1
22 UF10	10/$1

CERAMIC DISC			
68 PFd	50V	680 PFd	50V
100 PFd	100V	.001 Fd	
150 PFd	50V	.002 MFd	50V
220 PFd	50V	.01 MFd	200V
330 PFd	50V	.02 MFd	200V
.001 UFd	500V	3.3 PF	500V
.0015 UFd	500V	4.7 PF	500V
.005 UFd	500V	8.2 PF	500V
		100PF	500V

PC Leads 25/89 cents No Mix

RTL's BY FAIRCHILD

The most popular digital IC's ever produced. Very hard to find!

UL	DUAL 2 INPUT NOR	.99
UL923	JK FLIP FLOP	$1.19

LINEARS

709	Operational Amplifier	.25	LM 377	Dual 2W Amplifier	1.85
710	Differential Comparators	.40	LM 3900	Quad Op-Amplifier	.40
711	Dual Differential Comp.	.35	LM 741	Operational Amplifier	.25
712	Half Adder	.25	LM 748	Operational Amplifier	.25
749	Stereo Pre-Amp by Fairchild	2/$1	NE 553	Quad Timer	1.95
LM 301	Operational Amplifier	.30	NE 555	Timer	.40
LM 307	Operational Amplifier	.30	NE 556	Dual Timer	95
LM 308	Operational Amplifier	.95	NE 567	Tone Decoder	1.25
LM 309K	5V Lamp Regulator	1.49	1458	Dual Op-Amplifier	.55
LM 710	Voltage Comparator	.25,	75491	Quad Segment Driver	.35
LM 311	Voltage Comparator	.85	75492	Hex Digit Driver	.35
LM 318	Operational Amplifier	1.15	3043	IF Amplifier	.75
LM 723	Voltage Comparator	.69	8038	Voltage Cont. Osc.	3.95
LM 324	Quad Operational Amplifier				

VOLTAGE REGULATORS

7805 Pos.	5V 1 Amp	.99	7818 Pos.	18V 1 Amp	.99
7806 Pos.	6V 1 Amp	.99	7824 Pos.	24V 1 Amp	.99
7808 Pos.	8V 1 Amp	.99	7905 Neg.	5V 1 Amp	1.10
7812 Pos.	12V 1 Amp	.99	7912 Neg.	12V 1 Amp	1.10
7815 Pos.	15V 1 Amp	.99	7915 Neg.	15V 1 Amp	1.10

723 VOLTAGE REGULATORS

Output voltages variable from 2 volts to 37 volts. A very versatile and popular device.—14 PIN DIP.

69c

MOTOROLA VOLTAGE REGULATOR

MC1469R. TO-66. 9 lead package for 3 to 30V outputs. Provides 600 MA direct output or more by using an external power transistor. Regular catalog price — $4.00 each! With specs. **$1.95 each**

★ ★ ★ ★ ★ ★ ★ ★ ★

MUSICAL HORN

One tune supplied with each kit. Additional tunes — $6.95 each. Special tunes available. Standard tunes now available: — Dixie — Eyes of Texas — On Wisconsin — Yankee Doodle Dandy — Notre Dame — Pink Panther — Aggie War Song — Anchors Away — Never on Sunday — Yellow Rose of Texas — Deep in the Heart of Texas — Boomer Sooner — Bridge over River Kwai.

CAR & BOAT KIT	HOME KIT	Special Design
$34.95	**$26.90**	Case $3.50

★ ★ ★ ★ ★ ★ ★ ★ ★

UNMARKED 1702A EPROMS

3.50 Ea. or 10/$32.00

LIMITED SUPPLY

12V 1 AMP POWER SUPPLY

INPUT VOLTAGE 25V MAX. OUTPUT CURRENT 1 AMP. MAX. LOAD REGULATION 50mV. OUTPUT VOLTAGE 12V. LINE REGULATION 0.01%. KIT CONTAINS ALL PARTS EXCEPT FOR LINE CORD AND TRANSFORMER.

ONLY **$4.50**

TELEPHONE RELAY

Assembled & Tested **$29.95**

SURREPTITIOUS INTERCEPTION OF TELEPHONE CONVERSATION IS A VIOLATION OF FEDERAL LAW AND THIS DEVICE IS NOT DESIGNED NOR INTENDED FOR SUCH USE.

RADIO HUT

(All prices subject to change without prior notice.)
P.O. BOX 38323C
DALLAS, TEXAS 75238
AN EMPIRE IND. CO.

Money back guarantee. NO COD'S. Texas residents add 5% sales tax. Add 5% of order for postage and handling. Orders under $15.00 add 75 cents. Foreign orders add 20% for postage.

For your convenience, call your Bank Americard or Master Charge orders in on our Toll Free Watts Line: 1-800-527-2304. Texas residents call collect: 1-214-271-8423.

CIRCLE 71 ON FREE INFORMATION CARD

10 AMP - POWER TABS!

SCRS! TRIACS! QUADRACS!

Order by Cat. No. and voltage!
#5R1448 - TRIACS #5R1730 - SCR
#5R1590 - QUADRACS

PRV	Sale	2 for
☐ 50	$ .55	$ .56
☐ 100	.69	.70
☐ 200	.88	.89
☐ 400	1.19	1.20
☐ 600	1.59	1.60

THIS SPECIAL ONE CENT SALE IS FOR MAGAZINE ADS ONLY

POLY PAKS' PENNY-PINCHING ONE CENT SALE

THESE ONE-CENTERS ARE THE CENT-CIBLE WAY TO SHOP AND SAVE!

POLY PAKS® BIGGEST 1¢ GIVEAWAY SALE!

IT MAKES "CENTS" TO GIVE OUR CUSTOMERS THE BEST BARGAINS!

TTL'S, BUY ONE AT SALE PRICE, GET 2ND FOR ONLY 1¢ MORE

Order
By Cat.
No. 5R1981
& Type No.

Type	Each	2 for
☐ SN7400	$.19	$.20
☐ SN7401	.19	.20
☐ SN7403	.19	.20
☐ SN7404	.25	.26
☐ SN7405	.19	.20
☐ SN7406	.19	.20
☐ SN7408	.21	.22
☐ SN7410	.19	.20
☐ SN7413	.39	.40
☐ SN7414	.65	.66
☐ SN7416	.29	.30
☐ SN7420	.19	.20
☐ SN7423	.29	.30
☐ SN7426	.25	.26
☐ SN7427	.25	.26
☐ SN7430	.29	.30
☐ SN7432	.25	.26
☐ SN7437	.25	.26
☐ SN7438	.29	.30
☐ SN7440	.19	.20
☐ SN7442	.69	.70
☐ SN7443	.69	.70
☐ SN7444	.65	.66

Type	Each	2 for
☐ SN7445	.99	1.00
☐ SN7446	1.35	1.36
☐ SN7447	1.25	1.26
☐ SN7448	1.35	1.36
☐ SN7450	.19	.20
☐ SN7451	.19	.20
☐ SN7453	.19	.20
☐ SN7454	.19	.20
☐ SN7455	.19	.20
☐ SN7460	.19	.20
☐ SN7462	.19	.20
☐ SN7464	.19	.20
☐ SN7465	.19	.20
☐ SN7470	.25	.26
☐ SN7471	.25	.26
☐ SN7472	.25	.26
☐ SN7473	.55	.56
☐ SN7474	.29	.30
☐ SN7475	.79	.80
☐ SN7476	.59	.60
☐ SN7478	.59	.60
☐ SN7480	.29	.30
☐ SN7482	.39	.40

Type	Each	2 for
☐ SN7483	.99	1.00
☐ SN7485	1.49	1.50
☐ SN7486	.39	.40
☐ SN7488	1.95	1.96
☐ SN7490	.69	.70
☐ SN7491	.79	.80
☐ SN7492	.45	.46
☐ SN7493	.49	.50
☐ SN7494	.69	.70
☐ SN7495	.69	.70
☐ SN7496	.69	.70
☐ SN7498	.69	.70
☐ SN74100	1.49	1.50
☐ SN74107	.39	.40
☐ SN74112	.25	.26
☐ SN74113	.19	.20
☐ SN74114	.25	.26
☐ SN74121	.49	.50
☐ SN74123	.69	.70
☐ SN74125	.59	.60
☐ SN74126	.39	.40
☐ SN74132	1.25	1.26
☐ SN74140	.99	1.00
☐ SN74141	1.49	1.50
☐ SN74145	1.25	1.26
☐ SN74148	1.75	1.76
☐ SN74150	.99	1.00
☐ SN74151	.99	1.00
☐ SN74153	.99	1.00
☐ SN74154	1.75	1.76
☐ SN74155	.79	.80
☐ SN74156	.69	.70
☐ SN74157	.99	1.00
☐ SN74158	.99	1.00
☐ SN74160	1.25	1.26
☐ SN74161	1.25	1.26
☐ SN74163	1.19	1.20
☐ SN74164	.99	1.00
☐ SN74165	1.25	1.26
☐ SN74166	1.25	1.26
☐ SN74173	1.25	1.26
☐ SN74174	1.49	1.50
☐ SN74175	.99	1.00
☐ SN74177	.79	.80
☐ SN74179	1.49	1.50
☐ SN74180	.49	.50
☐ SN74182	.69	.70
☐ SN74190	1.49	1.50
☐ SN74191	1.75	1.76
☐ SN74192	.85	.86
☐ SN74193	.85	.86
☐ SN74194	1.25	1.26
☐ SN74195	.49	.50
☐ SN74197	.75	.76
☐ SN74199	1.75	1.76
☐ SN74200	5.50	5.51
☐ SN74251	1.75	1.76
☐ SN74284	4.50	4.51
☐ SN74285	4.25	4.26

POP-AMPS AT "CENT-CIBLE" PRICES

Case code: T=TO-220 Power Tab; V=Mini dip; K=TO-3; H=TO-5; N=DIP.

Type	Each	2 for
☐ LM300H	$.49	$.50
☐ LM301H-V	.45	.46
☐ LM308V-H	.79	.80
☐ LM309K	1.29	1.30
☐ LM311H-V	.79	.80
☐ LM318V	1.29	1.30
☐ LM320H-5, 12, 15	1.29	1.30
☐ LM320K- 15	1.29	1.30
☐ LM320T-6, 5	1.29	1.30
☐ LM322N	1.19	1.20
☐ LM324N	1.75	1.76
☐ LM339N	1.09	1.10
☐ LM340K-5, 6, 8, 12,15, 18,	1.29	1.30
☐ LM340T-5, 6, 8, 12, 15, 18, 24	1.29	1.30
☐ LM350N	.59	.60

Type	Each	2 for
☐ LM370N-H	1.29	1.30
☐ LM374H	1.79	1.80
☐ LM376V	.29	.30
☐ LM377N	2.25	2.26
☐ LM381N	1.69	1.70
☐ LM531H	1.49	1.50
☐ LM532H-N	.29	.30
☐ LM555V	.75	.76
☐ LM558V	.79	.80
☐ LM561N	1.00	1.01
☐ LM565N	.99	1.00
☐ LM703H	.49	.50
☐ LM704H	.29	.30
☐ LM709N-H	.25	.26
☐ LM710N	.39	.40
☐ LM733N	.79	.80
☐ LM739N	.89	.90

Type	Each	2 for
☐ LM741V-H	.30	.29
☐ LM1304	.80	.79
☐ LM1310	1.00	.99
☐ LM1312	2.00	1.99
☐ LM1414V	.80	.79
☐ LM1458V	.70	.69
☐ LM1800N	1.00	.99
☐ LM3028H	.66	.65
☐ LM3900N	.50	.49
☐ LM3909V	1.76	1.75
☐ LM4195	1.96	1.95
☐ LM4250	1.20	1.19
☐ LM75451	.40	.39
☐ LM75453	.40	.39
☐ LM75491	.80	.79
☐ LM75492	.80	.79
☐ LM75494	.60	.59
☐		

1N4000 Epoxy Rectifiers

• Miniature! • 1.5 Amp!
Order by Cat. No. and Type No.

Cat. No.	Type No.	PIV	Price	1¢ MORE!
☐ 5R2377	1N4001	50	10 for $.65	20 for .66
☐ 5R2378	1N4002	100	10 for .75	20 for .76
☐ 5R2379	1N4003	200	10 for .85	20 for .86
☐ 5R2380	1N4004	400	10 for .99	20 for 1.00
☐ 5R2381	1N4005	600	10 for 1.29	20 for 1.30
☐ 5R2382	1N4006	800	10 for 1.39	20 for 1.40

1.5 AMP

BULLET RECTIFIERS!

Order by Cat. No. 5R60B84 and voltage

☐ 50V	10 for $.59	20 for $.60
☐ 100V	10 for .69	20 for .70
☐ 200V	10 for .79	20 for .80
☐ 400V	10 for .89	20 for .90
☐ 600V	10 for 1.09	20 for 1.10
☐ 800V	10 for 1.19	20 for 1.20

MICRO MINI

TOGGLE SWITCHES!

3 Amps, 125 VAC contacts. with chrome handles, complete with mounting hardware.

Cat. No	Type	Sale	2 for
☐ 5R3936	SPDT	$1.29	$1.30
☐ 5R5085	SPDT*	1.39	1.40
☐ 5R4037	DPDT	1.45	1.46
☐ 5R5087	4PDT*	1.95	1.96

BUY 1 AT OUR SALE PRICE

GET 2 FOR 1¢ MORE

LYTIC KLINIC

Electrolytic capacitors

Order by Cat. No. 5R3269 and value

UF	V	Style	Sale	1¢ SALE
☐ 10	15	P.C.	10 for $1.00	20 for $1.01
☐ 50	15	P.C.	8 for 1.00	16 for 1.01
☐ 15	25	P.C.	8 for 1.00	16 for 1.01
☐ 50	25	P.C.	6 for 1.00	12 for 1.01
☐ 20	15	Axial	10 for 1.00	20 for 1.01
☐ 20	15	P.C.	10 for 1.00	20 for 1.01

6 AMP CARTWHEEL RECTIFIERS

Cat, 5R3584

*AXIAL LEADS

PIV	SALE	1¢ SALE
☐ 50	$ .29	2 for $ .30
☐ 100	.36	2 for .37
☐ 200	.45	2 for .46
☐ 400	.61	2 for .62
☐ 600	.79	2 for .80
☐ 800	.90	2 for .91
☐ 1000	1.19	2 for 1.20

LEDS!

YOUR CHOICE 5 for $1.00
1¢ SALE 10 for $1.01

Order by Cat. No.

- ☐ #5R2135 JUMBO RED LEDS
- ☐ #5R2137 MICRO RED LEDS
- ☐ #5R2790 JUMBO RED CLEAR LEDS
- ☐ #5R2792 JUMBO TAPERED AMBER
- ☐ #5R2140 MICRO GREEN LEDS

ZENERS!

Order by Cat. No. 5R5210 & voltage & wattage!

1 Watt	Sale	1¢ SALE
☐ 7.5V	5 for $1.	10 for $1.01
☐ 8.2V	5 for 1.	10 for 1.01
☐ 9.1V	5 for 1.	10 for 1.01
☐ 11.V	5 for 1.	10 for 1.01
☐ 12.V	5 for 1.	10 for 1.01
☐ 15.V	5 for 1.	10 for 1.01

5 WATTS	Sale	1¢ SALE
☐ 3.3V	3 for $1.	6 for $1.01
☐ 6. V	3 for 1.	6 for 1.01
☐ 6.2V	3 for 1.	6 for 1.01
☐ 8.2V	3 for 1.	6 for 1.01
☐ 9.1V	3 for 1.	6 for 1.01
☐ 12. V	3 for 1.	6 for 1.01
☐ 15. V	3 for 1.	6 for 1.01
☐ 18. V	3 for 1.	6 for 1.01
☐ 24. V	3 for 1.	6 for 1.01
☐ 30. V	3 for 1.	6 for 1.01

© COPYRIGHT 1978 - POLY PAKS INC.

THIS NEW LIST OF "ONE-CENTERS" HELPS FIGHT INFLATION!

Quan.	Description (Order by Cat. No. in parenthesis)	Sale	1¢SALE
☐ 1	WOODGRAIN CABINET, 3½ x 10 x ¼" deep, spkrs, alarms. (#5R5201)	$1.49	2 for $1.50
☐ 2	LCD THERMOMETER "TAPE", 88-108° F, 7" x 1". (#5R5195)	1.00	2 for 1.01
☐ 1	JOYSTICK, four 100K pots, with knob (#5R3808A)	4.95	2 for 4.96
☐ 1	EECO THUMBWHEEL SWITCH, BCD, 0-7 (#5R2870A)	1.49	2 for 1.50
☐ 1	8-TRACK TAPE TRANSPORT, with preamp (#5R3010)	9.95	2 for 9.96
☐ 1	PLESSEY TV SIDEBAND FILTER, for chan. 3 or 4 (#5R3975)	1.95	2 for 1.96
☐ 5	TRANSITORS, 2N3904 equal, NPN, switching (#5R5209)	1.00	10 for 1.01
☐ 1	METER, 50uA, 1½" square, 0-20db (#5R3705)	1.19	2 for 1.20
☐ 1	SPST RELAY, norm. open 12-24 VDC, 1250 ohms, dip style (#5R5175)	1.00	2 for 1.01
☐ 1	VEEDER ROOT COUNTER, 000-999, resettable, panel mt. (#5R5081)	1.49	2 for 1.50
☐ 2	DUAL GATE MOSFET, sim. to 3N200, 3N187, for RF & Mixer (#5R5101)	1.00	4 for 1.01
☐ 1	8-TRACK TAPE HEAD, with plug' n' cord (#5R3468)	2.50	2 for 2.51
☐ 10	CALCULATOR KEYBOARDS, 20 keys and more (5R3524)	$2.00	20 for $2.01
☐ 15	SLIDE VOLUME CONTROLS, asstd values (5R3057)	2.00	30 for 2.01
☐ 10	CRYSTALS, may include CB, Ham & more (5R3250)	2.00	20 for 2.01
☐ 150	MOLEX IC SOCKETS, on a strip, cut to length (5R3144)	2.00	300 for 2.01
☐ 100	TERMINAL STRIPS, from 2 lugs up (5R3136)	2.00	200 for 2.01
☐ 30	NE-2NEON LAMPS, all 100% good (5R2613)	2.00	60 for 2.01
☐ 40-ft.	SHIELDED CABLE, 1 cond, mikes, phonos, (#5R3577)	2.00	80 ft. for 2.01
☐ 50	TRANSISTOR ELECTROS, asstd values, styles (5R2747)	2.00	100 for 2.01
☐ 3	SOUND TRIGGERS, sound triggers scr w/amp (5R3625)	2.00	6 for 2.01
☐ 15	6V TEST INDICATORS, leads, grain-o-wheat (5R3526)	2.00	30 for 2.01
☐ 100	CAPACITOR SPECIAL, discs, mylar, lytics, more (5R2738)	2.00	200 for 2.10
☐ 30	MINI TRIMPOTS, to 1 meg, 1 turn, ¼W (5R3345)	2.00	60 for 2.01
☐ 10	VOLTAGE REGULATORS, hobby LM320, 340, TO-3 (5R3330)	2.00	20 for 2.01
☐ 30	PANEL SWITCHES, slides, rotaries, mod, etc (5R3268)	2.00	60 for 2.01
☐ 200	RESISTOR SPECIAL, ¼ to 1W, carbon, metal (5R3054)	2.00	400 for 2.01
☐ 200	HALF WATTERS, resistors, carbon, metal (5R3046)	2.00	400 for 2.01
☐ 100	NATIONAL IC BONANZA, linears, 7400s ROMS (5R2860)	2.00	200 for 2.01
☐ 40	HOBBY LEDS, asstd types, mostly useable (5R2859)	2.00	80 for 2.01
☐ 15	LM340T VOLTAGE REGULATAORS, 5 to 24V, TO-220 (5R2635)	2.00	30 for 2.01
☐ 100	TWO WATTERS, resistors, carbon-metal marked (5R2735)	2.00	200 for 2.01
☐ 100	POLYSTYRENE CAPS, asstd values, voltage, hi-Q (5R2729)	2.00	200 for 2.01
☐ 50	THERMISTORS, resistors that change with temp (5R4089)	2.00	100 for 2.01
☐ 20	BRIDGES, untested, 2, 4, 6, 10, amp, full wave (5R4022)	2.00	40 for 2.01
☐ 25	LAMP'N'SOCKET SETS, micro, 1.5V, T2 (5R3957)	2.00	50 for 2.01
☐ 15	MIXED READOUTS, hobby, untested, .127, .3, .5, etc. (5R3619)	2.00	30 for 2.01
☐ 150	QUARTER WATTERS, resistors, metal film, marked (5R3413)	2.00	300 for 2.01
☐ 100	PLASTIC TRANSISTORS, untested, RO-92 (5R2604)	2.00	200 for 2.01
☐ 200	PREFORMED RESISTORS, ¼, ½, 1W, marked, asstd (5R2608)	2.00	400 for 2.01
☐ 200	PRECISION RESISTORS, ¼, ½, 1W, 1%, 2% marked (5R2428)	2.00	400 for 2.01
☐ 60	DIPPED MYLARS, shiny finish, asst values (5R2597)	2.00	120 for 2.01
☐ 30	VOLUME CONTROLS, audio, linear, asstd values (5R2421)	2.00	60 for 2.01
☐ 5	7.5 VOLT ZENER DIODES, 1 watt (5R5187)	1.00	10 for 1.01
☐ 5	9.1 VOLT ZENER DIODES, 1 watt (5R5188)	1.00	10 for 1.01
☐ 30-FT.	WIRE WRAP WIRE, 30 gauge (5R3803)	1.19	60-ft for 1.20
☐ 5	TANTALUM CAPS, 2.2uF, 25V (5R5189)	1.00	10 for 1.01
☐ 1	ALARM CLOCK CHIP, MM5316, 4-digits (5R1759)	2.95	2 for 2.96
☐ 5	PANCAKE PHOTOCELLS, 600 to 15K ohms (5R2939)	1.00	10 for 1.01
☐ 1	100KHZ MARKER CRYSTALS, approx for marker gen. (5R3896)	1.95	2 for 1.96
☐ 1	MOTHERBOARD EDGE CONNECTOR, 106 pins, .125" (5R3987)	3.50	2 for 3.51
☐ 1	48-PIN EDGE CONNECTOR, .156" spacing (5R3963)	1.95	2 for 1.96
☐ 1	JOYSTICK, two 10K pots, for computers, TV games (5R5037)	2.95	2 for 2.96
☐ 1	CHARACTER GENERATOR, 5 × 7 Mostek MK 2002P (5R3898)	4.95	2 for 4.96

READOUTS!

		ONE CENT SALE
☐ 3½ DIGIT LCD WRISTWATCH DISPLAY, (#5R3960)	3 for $1.19	6 for $1.20
☐ GE FLUORESCENT NIXIES, 7-seg, blue (#5R3684)	1 for 1.00	2 for 1.01
☐ SPERRY FLAT NIXIES, orange dual digit (#5R5014)	2 for 1.19	4 for 1.20
☐ SPERRY FLAT NIXIES, orange, .3", 1½-dig (#5R5015)	2 for 1.19	4 for 1.20
☐ MAN-3 BUBBLE READOUT, .19" red, com cath. (#5R3338)	6 for 1.00	12 for 1.01
☐ MAN-4 READOUT, bubble, red, com anode (#5R1503)	2 for 1.00	4 for 1.01
☐ FND-10 BLOCK READOUT, .122" com cathode (#5R2082)	2 for 1.19	4 for 1.20
☐ 8-DIGIT READOUT, led, com cathod, red (#5R5190)	1 for 1.95	2 for 1.96
☐ FND-503, .5" red, com cathode, 7-seg. (#5R2949)	1.50	2 for 1.51

SPEAKERS!

	Each	2 for
☐ 6" TWIN CONE SPEAKER, hi-fi, for car'n'home (#5R5059)	$4.50	$4.51
☐ 2¼ × 5" OVAL SPEAKER, 8 ohms (#5R2553)	1.49	1.50
☐ 2 × 6" OVAL SPEAKER, 8 ohms (#5R3454)	1.49	1.50

MICROPHONES!

	Each	2 for
☐ CONDENSOR MIKES, sensitive, 500 ohms, 1½V (#5R3178)	$4.95	$4.96
☐ COMMUNICATIONS MIKE, 500 ohms, CB-HAM (#5R4074)	4.50	4.51
☐ NOISE CANCELLING MIKE, Ham-CB, 500 ohms (#5R3902)	6.95	6.96

RELAYS!

	Each	2 for
☐ SPDT 12V BLOCK RELAY, 5A contacts (#5R4032)	$1.98	$1.99
☐ SPDT 12V REED RELAY, 1A contacts (#5R4094)	1.49	1.50
☐ SPDT 12V SENSITIVE, 2000 ohm coil (#5R3044A)	1.95	1.96

AMPLIFIERS!

	Each	2 for
☐ 8 WATTS ON A BOARD, with built-in preamp (#5R5040)	$5.95	$5.96
☐ 9 WATTS ON A CHIP, Toshiba TA7205 (#5R5057)	4.95	4.96
☐ 3 WATTS ON A CHIP, G-E PA 263 (#5R1522)	1.50	1.51

TRANSFORMERS!

	Each	2 for
☐ 12V TRANSFORMER, 300ma, pc leads, 110pri. (#5R3412)	$1.49	$1.51
☐ 12V TRANSFORMER, 1A, 110/220pri, open frame (#5R4040)	2.95	2.96
☐ 24VCT TRANSFORMER, 300ma, open frame, 110pri. (#5R3323)	1.95	1.96
☐ 2.9V PLUG-IN TRANSFORMER, 125ma, 110V pri. (#5R4098)	1.95	1.96

DIP SWITCHES!

	Each	2 for
☐ 2 SWITCHES ON A DIP (#5R3668)	$ .77	$ .78
☐ 3 SWITCHES ON A DIP (#5R3669)	.88	.89
☐ 6 SWITCHES ON A DIP (#5R3671)	1.29	1.30

IC SOCKETS!

☐ 8-PIN MINI-DIP (#5R2123)	4 for $1.19	8 for $1.20
☐ 14-PIN DIP (#5R1308)	3 for 1.19	6 for 1.20
☐ 16-PIN DIP (#5R1309)	3 for 1.19	6 for 1.20
☐ 18-PIN DIP (#5R3378)	6 for 1.19	12 for 1.20
☐ 24-PIN MSI/DIP (#5R3886)	2 for 1.19	4 for 1.20
☐ 28-PIN MSI/DIP (#5R3887)	2 for 1.19	4 for 1.20
☐ 8-PIN TO-5 (#5R1307)	4 for 1.19	8 for 1.20

FULL WAVE 10 AMP

BRIDGE RECTIFIERS!

Order by Cat. No 5R2447 & voltage

PRV	Sale	2 for
☐ 50	$1.29	$1.30
☐ 100	1.49	1.50
☐ 200	1.69	1.70
☐ 400	1.99	2.00
☐ 600	2.25	2.26
☐ 800	2.50	2.51

SPECTROL "SKINNY-TRIMS"

Ohms
☐ 10**
☐ 50**
☐ 100**
☐ 200**
☐ 500*
☐ 1K*
☐ 2K**
☐ 5K*
☐ 10K*
☐ 20K**
☐ 50K**
☐ 100K**

3/8" square, screwdriver shaft, 2% tol, 1/4 watt. Cermet. PC leads. Order by Cat. No. and value.

2 for $1

☐ No. 5R3863 25 turn upright, type 64
☐ No. 5R3866 single turn, flat, type 63

*Available in all types
**Available in Cat. No. 3863 only.

RIBBON CABLE!

Order by Cat. No. 5R3939 and Conductors

Cond.	Sale	1¢ Sale
☐ 20	7-ft. $1.98	14-ft. $1.99
☐ 26	4-ft. 1.98	8-ft. 1.99
☐ 34	3-ft. 1.98	6-ft. 1.99
☐ 40	3-ft. 1.98	6-ft. 1.99

WRITE FOR
POLY PAKS
CATALOG
FEATURING
BEST BARGAINS
IN ELECTRONICS

FREE!

Terms: Add postage Rated: net 30
Phone: Wakefield, Mass. (617) 245-3829
Retail: 16-18 Del Carmine St., Wakefield,

MINIMUM ORDER — $6.00

POLY PAKS®

C.O.D.'s MAY BE PHONED

P.O. BOX 942-R5
LYNNFIELD, MA.
ZIP 01940

CIRCLE 37 ON FREE INFORMATION CARD

S-100 EXPANDABLE MOTHER BOARD

- 8-SLOT EXPANDABLE BACKPLANE—in line male and female connectors enable backplanes to be plugged together, or the female may be used in place of an extender board.

QUIET—ground plane decouples all signal lines.

RELIABLE—SAE 8100 phenolic body, gold contact connectors.

COMPLETE KIT $66^00 ASSEMBLED $89^00

DEC® LSI-11 16K MEMORY BOARD

- Q-BUS—FULLY STATIC
- BUFFERED AND NOISE SUPPRESSED
- MODULAR
- PROM COMPATIBLE
- ADDRESSABLE TO 128K WORDS
- MAPPABLE IN 4K INCREMENTS

ASSEMBLED, TESTED & **BURNED IN** $1249^00 COMPLETE KIT $1159^00

LARGEST & FASTEST STATIC MEMORY AVAILABLE

S-100 32K STATIC MEMORY BOARD

features:

1. FULLY STATIC - usable with all DMA devices
2. BUFFERED - with noise suppressed control inputs
3. MODULAR - populated in 1K increments
4. RELIABLE - single source +5V. regulator
5. PROM COMPATIBLE - monitors available on request

Available:
COMPLETE KITS or
ASSEMBLED UNITS which have been fully tested and burned in

BARE BOARD $39^00

	KIT	ASSEMBLED
8K	$278	$320
16K	$468	$515
24K	$648	$695
32K	$800	$845

S-100 EXTENDER BOARD

with Connector

A MUST for trouble-shooting your Computer boards $16^95

MICRO CPU CARD

with S-100 BUS, 3 on board regulators. Fits all standard I.C. Socket configurations. 1700+ holes 5"x10" $24^95

Leading computer manufacturer's "in-house"

UNIVERSAL BOARD

1600+ holes 4-7/8"x7-5/8" $9^95

IF YOU LIKED 8800V YOU'LL LOVE OUR BOARDS. IF NOT, WE REFUND. SEE BELOW

BIPOLAR PROMS

8223	256 BIT	$2.75
82S23	256 BIT	$3.50
6306-1	2K TRISTATE	$5.95
82S126	256x4	$4.95

4K STATIC RAMS

2114	650ns	600mW	$9.95
TMS4045-4	450ns	300mW	$11.95
HM-472114	450ns	200mW	$13.95

THESE SUCKERS GIVE EVERYONE AN EVEN BREAK.

COMPUTER KEYBOARD

KEYTOPS

assorted styles & characters

100/$6^95

CIRCUIT ASSEMBLY

INTERCONNECT CABLE

single ended
16 pin header
18" Ribbon

$1^49

OPERATIONAL AMPLIFIERS

PART	OFFSET V	OFFSET I	BIAS	DIFF IMP	3dB BW	VOLT GAIN	SLEW RATE v/µs	CMRR	$
40J	adj to 0	25PA	50PA	100M	100KHz	94dB	6	80dB	**3.95**
1402	3MV	10PA	30PA	1000M	2.5MHz	80dB	3	76dB	**8.95**
1407	10MV	10PA	150PA	100M	30.0MHz	86dB	8	80dB	**8.95**
1324	10MV	30NA	300NA	3M	10MHz	100dB	35	100dB	**8.95**

EDGE VIEW METER

CHARGE - DISCHARGE SCALE
READS +20, 0, -40
MOVEMENT +60, -120mA
0.135 Ohms. $2^49

CDS PHOTO CELL

OFF ∽20MΩ
ON ∽ 200Ω
2/99c

FOREIGN REPLACEMENTS

TA7092P	$3.95
AN214	$4.25
uPc1025H	$4.95

AUDIO I.C.'s

LM387	PREAMP	.99
LM380	2W PWR	.99
MFC9020	2W PWR	$2.25

POWER OP AMP

uA 791P5S
1 AMP $4^95

TTL COMPATIBLE

5V. REED RELAY

$1^65 ea. 7/$9^75

SOLAR CELLS

1x2cm 65mA
$.95 ea.
10/$7^50

2x2cm 130mA
$1.49 ea.
10/$9^50

10 MEG POT

1/4" shaft
3/8" long
4/99c

GOLD INLAID

I.C. SOCKETS

14 Pin	10/$1.89
16 Pin	10/$1.99
22 Pin	5/$1.69
24 Pin	5/$1.89
28 Pin	5/$1.99
40 Pin	4/$1.99

5W ZENERS 5%

PLASTIC-AXIAL LEADED

	V.		V.		V.
IN5338	5.1	IN5347	10	IN5356	19
IN5339	5.6	IN5348	11	IN5357	20
IN5340	6.0	IN5349	12	IN5358	22
IN5341	6.2	IN5350	13	IN5359	24
IN5342	6.8	IN5351	14	IN5360	25
IN5343	7.5	IN5352	15	IN5361	27
IN5344	8.2	IN5353	16	IN5362	28
IN5345	8.7	IN5354	17	IN5363	30
IN5346	9.1	IN5355	18	IN5364	33

99c ea. 10 MIX/ $7.60 100 MIX/ $59

YOUR CHOICE

CHEAP THRILLS LIMIT 10 OF EACH ITEM PER ORDER **NO EXCEPTIONS**, PLEASE!

7400	.09	7474	.20
7401	.09	7494	.35
7404	.10	74161	.40
74S04	.12	DM8880	.50
7432	.10	uA709	.19
7442	.25	LM301	.18
74L73	.20	MC1458	.39

DIODES & TRANSISTORS

MARKINGS STANDARD. HOUSE & SOME UNMARKED. BUT **ALL** MEET SPECS.

IN 91	.10	IN 4148	.05	2N 2222	.10
IN 270	.09	IN 4001	.05	2N 3904	.10
IN 3600	.10	IN 4007	.10	2N 3906	.10

NE-2 NEON BULB .08

SWITCHES
ROCKER
125V 6A 2/99c
UL APPROVED
SLIDE
125V 3A 12/99c
SPST

D/A CONVERTER

SIGNETICS NE 5008
$13^95

D/A CONVERTER

DAC-01/SH
$12^95

16 CHANNEL MULTIPLEXER

ANALOG OR DIGITAL
BREAK BEFORE MAKE SWITCHING
SCHMITT TRIGGER INPUTS
FAST SETTLING TIME
HIGH TRANSFER ACCURACY
OVERVOLTAGE PROTECTION.
EVEN WITH + Vcc = 0

LIST 40.00
NOW ONLY $13^95

POWER DEVICES

SCR'S

850 A	600 V	PUK	$99^00
225 A	800 V	STUD	$29^00

DIODES

400 A	400 V	PUK	$19^95
300 A	300 V	STUD	$14^95
250 A	1000 V	STUD	$19^95

BRIDGES

500 A	200 V	3 PHASE	$99^00
25 A	500 V		$4^95
1.5 A	400 V		$1^25
1.5 A	100 V		.75

HEWLETT-PACKARD JUMBO RED HI EFFICIENCY

LED

ON BOARD STATUS INDICATOR 6/99c

HIGH INTENSITY RED LED LAMP

FROSTED-WHITE CASE
3/99c 10/$2^25

PLASMA

READOUT

0.75" 4 digit $4^95

ELECTROLYTIC

7500 MFD at 16VDC

99c

MAIL ORDER

"GOOF PROOF" GUARANTEE

Because **MAIL ORDER CUSTOMERS** cannot inspect their parts before purchase, for them **only**, we guarantee an IMMEDIATE REFUND—NO QUESTIONS ASKED—should you be unhappy with the parts,* or should the parts fail for **any** reason.* Just ship parts to us in a protective carton with proof of purchase within 30 days of receipt of shipment.

**MOS AND LED DEVICES EXCLUDED!*

LOS ANGELES
(213) 967-4611
LMN ELECTRONICS
1042 E. GARVEY AV. W. COVINA, CA.
VINCENT & SAN BERNARDINO FWY.

PORTLAND
(503) 646-4044
WIZARD of PARTS
8225 SW CIRRUS DR., BEAVERTON, ORE.
(KOLL BUS. CNTR WASHINGTON SQUARE)

DENVER
(303) 573-5214
ELECTRONIC LOLLIPOP
5643 N. BROADWAY, DENVER, CO.
(I-25 & 58th AVE.)

IF AT ALL POSSIBLE, TRY TO DROP INTO ONE OF OUR LOCATIONS. BUT IF YOU LIVE TOO FAR AWAY YOU MAY ORDER BY MAIL FROM:

SUB-MINIATURE

CRYSTAL FILTER

455 KHz WITH DATA $2^95

NO BACK ORDERS
YOUR PARTS OR *IMMEDIATE* REFUND

WE PAY POSTAGE & HANDLING
ON U.S. ORDERS ONLY
$20 MINIMUM CALIF. RES. ADD 6%

FOR UNDER 8 HOURS PROCESSING SEND MONEY ORDER, CERTIFIED OR CASHIERS CHECK.
SORRY! WE CANNOT ACCEPT PURCHASE ORDERS, COD'S, PHONE ORDERS OR CREDIT CARDS.
CANADA, PUERTO RICO, U.S. POSSESSIONS ADD $3.50, ALL OTHER FOREIGN ORDERS ADD $7.00 **IN U.S. FUNDS**

F. Reichert Sales
1110 E. GARVEY AVE.
W. COVINA, CA. 91790

ALL ITEMS SUBJECT TO PRIOR SALE

PRICES GOOD UNTIL JUNE 3, 1978

CIRCLE 84 ON FREE INFORMATION CARD

ELECTRONIC SYSTEMS
p.o. box 212 Burlingame CA 94010
(408) 374-5984

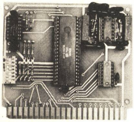

UART & BAUD RATE GENERATOR

Part no. 101
- Converts serial to parallel and parallel to serial
- Low cost on board baud rate generator
- Baud rates: 110, 150, 300, 600, 1200, and 2400
- Low power drain +5 volts and -12 volts required
- TTL compatible
- All characters contain a start bit, 5 to 8 data bits, 1 or 2 stop bits, and either odd or even parity.
- All connections go to a 44 pin gold plated edge connector
- Board only $12.00; with parts $35.00

8K STATIC RAM

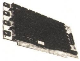

Part no. 300
- 8K Altair bus memory
- Uses 2102 Static memory chips
- Memory protect
- Gold contacts
- Wait states
- On board regulator
- S-100 bus compatible
- Vector input option
- TRI state buffered
- Board only $22.50; with parts $160.00

RS-232/TTL INTERFACE

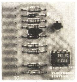

Part no. 232
- Converts TTL to RS-232, and converts RS-232 to TTL
- Two separate circuits
- Requires -12 and +12 volts
- All connections go to a 10 pin gold plated edge connector
- Board only $4.50; with parts $7.00

DC POWER SUPPLY

Part no. 6085
- Board supplies a regulated +5 volts at 3 amps., +12,-12, and -5 volts at 1 amp.
- Board has filters, rectifiers, and regulators
- Power required is 8 volts AC at 3 amps., and 24 volts AC C.T. at 1.5 amps.
- Board only $12.50

TIDMA

Part no. 112
- Tape Interface Direct Memory Access
- Record and play programs without bootstrap loader (no prom) has FSK encoder/decoder for direct connections to low cost recorder at 625 baud rate, and direct connections for inputs and outputs to a digital recorder at any baud rate.
- S-100 bus compatible
- Comes assembled and tested for $160.00

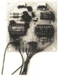

TAPE INTERFACE

Part no. 111
- Play and record Kansas City Standard tapes
- Converts a low cost tape recorder to a digital recorder
- Works up to 1200 baud
- Digital in and out are TTL-serial
- Output of board connects to mic. in of recorder
- Earphone of recorder connects to input on board
- Requires +5 volts, low power drain
- Board $7.60; with parts $27.50
- No coils

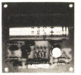

Part no. 107

RF MODULATOR

- Converts video to AM modulated RF, Channels 2 or 3
- Power required is 12 volts AC C.T., or +5 volts DC
- Board $4.50; with parts $13.50

APPLE I MOTHER BOARD

Part no. 102
- 10 slots — 44 pin (.156) connectors spaced ¾" apart
- Connects to edge connector of computer
- Pin 20 and 22 connects to X & Z for power and ground
- Board has provisions for bypass capacitors
- Board cost $15.00

TELEVISION TYPEWRITER

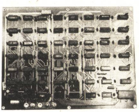

Part no. 106
- Stand alone TVT
- 32 char/line, 16 lines, modifications for 64 char/line included
- Parallel ASCII (TTL) input
- Video output
- 1K on board memory
- Output for computer controlled curser
- Auto scroll
- Non-distructive curser
- Curser inputs: up, down, left, right, home, EOL, EOS
- Scroll up, down
- Requires +5 volts at 1.5 amps, and -12 volts at 30 mA
- Board only $39.00; with parts $145.00

MODEM

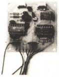

Part no. 109
- Type 103
- Full or half duplex
- Works up to 300 baud
- Originate or Answer
- No coils, only low cost components
- TTL input and output-serial
- Connect 8 ohm speaker and crystal mic. directly to board
- Uses XR FSK demodulator
- Requires +5 volts
- Board $7.60; with parts $27.50

To Order:

Mention part number and description. For parts kits add "A" to part number. Shipping paid for orders accompanied by check, money order, or Master Charge, BankAmericard, or VISA number, expiration date and signature. Shipping charges added to C.O.D. orders. California residents add 6.5% for tax. Parts kits include sockets for all ICs, components, and circuit board. Documentation is included with all products. Dealer inquiries invited. 24 Hour Order Line: (408) 374-5984.

E21

CIRCLE 40 ON FREE INFORMATION CARD

TRINICO INTERNATIONAL
(Formerly Trico)

2795 W. Lincoln Ave., Suite L, Anaheim, Ca. 92801 PHONE 714/821-0234

TERMS: Money Back Guarantee
CALIF. RESIDENTS ADD 6% SALES TAX
Please add $1.00 for postage inside Calif., $2.00 for
Out of State, Overseas add 10% of order.
Minimum Order $5.00 C.O.D. $20.00 ($1.00 handling)
STORE HOURS: Mon.-Sat., 10-7

☐ BankAmericard ☐ Master Charge

30 MHZ LOW COST FREQUENCY COUNTER KIT

Features:

- Frequency Range—100Hz to 30MHz min., resolution 100 Hz
- All TTL Circuitry—No tears in the eyes when replacing ICs
- FET Input Stage—Offers high input impedance
- High Sensitivity—15mV typical
- Xytal Time Base—0.001% 10MHz for better accuracy
- On Board Regulator—No external power supply needed
- All ICs Socketed—Easy to service
- Easy to Operate—No switches to flip
- Tin Plated & Screened Board—For easy assembly

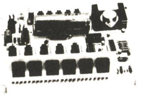

COMPARE and SAVE!

$54.95

KIT # T-250-30A

KIT INCLUDES: Detailed Instructions (22 pages). All parts including transformer (case not available).

P.C. MOUNT PUSH BUTTON SWITCHES

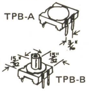

45¢ ea.
10/$4.00

PUT YOUR HAM GEAR OR CB IN YOUR HOUSE WITH THIS SPECIALLY DESIGNED POWER SUPPLY KIT!

A lot of companies offered you this kind of power supply with very poor quality. Either the ripple is too high or the output voltage is not stable. Some of them even made their power supply with a zener diode and a resistor! Nobody has ever considered the safety of your equipment. With our kit, you can be sure of high quality and your equipment is protected against any failure of your power supply by a built in OVP circuit.

KIT INCLUDES: Transformer, PC Board, Large heat sink, Large filtering capacitor and all the parts with detailed instruction.

Features:

- Output Voltage = 13.5V
- Output Current = 3.5A Min.
- Load Regulation = 0.01%
- Line Regulation = 0.02%
- Internal Current Limiting
- Over-voltage Protected

ONLY $16.95

KIT # T-700

WOW! LOOK AT THIS!

5V 10A Power Supply Kit for your TTL Circuits!

Kit Includes: Extra Large Heat Sink, Power Tr., IC Regulator, P.C. Board, with OVP Circuitry. KIT # T-500 **$11.95**

With Optional Rectifiers and Filtering Capacitor. **$14.95** (X'former not available)

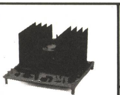

HERE'S A MUST FOR THE EXPERIMENTER!

2-20V @ 1.3A Continuously Variable Power Supply Kit. Kit Includes: P.C. Board, Transformer, Power Transistor, Heat Sink, IC Regulator & all the parts with detailed instruction. KIT # T-658 **$12.95**

6-DIGIT AUTO CLOCK KIT WITH ALARM

Features:

A. Fairchild 0.5" FND 500 Series Display
B. Display Board may be remote
C. X'tal time base
D. P.C. Boards, speaker, IC's and all parts.
E. Detailed Instructions

$19.95 KIT # T-1302

0.8" 4 Digit Jumbo Display Alarm Clock Kit

Features:

A. Fairchild 0.8" FSC8000 Display Array
B. Fairchild Super-Chip — F-3817PC
C. P.C. Board, Transformer, Speaker and all parts included (less case)
D. Detailed Instructions

THIS IS A BIG ONE!

$19.50

MINIATURE SLIDE SWITCH DPDT .20 each
10 for $1.75
100 for $15.00

PUSH BUTTON SWITCH White, green and yellow
30¢ ea.
4/$1.00

60 Hz Time Base IC
MM5369
$1.95

WIRE-WRAP TOOLS from OK

Hobby Wrap - 30	$5.45
Hobby Wrap—Model BW-630 Battery Op. (less batt.)	$30.95

POWER TRANSISTORS

MATCHED PAIR
MOTOROLA MJE2955 PNP
MJE3055 NPN
10 AMP 60 VOLT 90 WATTS
$2.25 PER PAIR

TRANSISTORS

NPN-General Purpose 30V	10/$1.00
PNP-General Purpose 30V	10/$1.00
2N2222-Switching	10/$1.50
2N3055-150W Power	10/$6.75
2N6059-Darlington Power, 20A HFE 1k Typical	$3.25 ea.

CPU 8080A
ONLY $16.95
Special from TI
2716 — 16K EROM
ONLY $39.95

CRYSTALS

1MHz	$4.50
4MHz	$4.50
10MHz	$4.50

MINIATURE TOGGLE SWITCH

SPDT	On-Off	$1.30 ea.
DPDT	On-Off	$1.50 ea.
3PDT	On-Off	$1.75 ea.

Mini-Size Rocker Type
also available at the same price

LED's

0.20"	Red	25¢	10 for $1.75
0.20"	Green	30¢	10 for $2.50
0.125"	Red	20¢	10 for $1.75
0.5"	FND503 C.C.		$1.00
0.5"	FND507 C.A.		$1.00
0.8"	FSC8000 C.C.		$5.00

INTER—COM BOARD

Fully assembled.
Works on 9~15V D.C.
2 speakers make it work.
With Schematic
ONLY $3.00

TANTALUM CAPACITORS

1µ 35V	.15
1µ 10V	.15
3.3µ 35V	.20
10µ 50V	.35
22µ 35V	.25

BOURNS TRIMPOT

Commercial Single Turn 2K 3305P
$1.25 ea. **10/$10.00**
Cermet Mil. Spec. Multi-Turn 1K & 2K RJ24CX
$3.00 ea. **10/$25.00**

SANYO SALES OF THE MONTH

**M2402A

NEW!

AM/FM CASSETTE TAPE RECORDER with AC/DC POWER and ON/OFF MONITOR SWITCH

- ☐ On/Off Monitor Switch
- ☐ Built-In Condenser Mike
- ☐ Remote Mike Jack
- ☐ Built-In AC
- ☐ Output Jack for Earphone or Speaker

Reg. $54.95
Sale: $39.95

COMPUTER GRADE CAPACITORS

6,000 µF	75V	4.50
10,000 µF	50V	4.25
27,000 µF	50V	4.50
30,000 µF	15V	3.50
36,000 µF	30V	4.00
63,000 µF	15V	3.95
100,000 µF	5V	2.00

PRIME FROM ERIE

10-40p Mini Capacitance Trimmer
50 ea. 10/$4.50

M8000
AM/FM 8-TRACK TAPE PLAYER

- ☐ Jumbo Size with Durable Shoulder Strap
- ☐ Digital Program Indicator
- ☐ 2000mW Amplifier
- ☐ Automatic or Manual Program Change
- ☐ AM/FM Radio

Reg. $44.95
Sale: $35.95

Please add $3.00 for postage and handling.

SPECIAL OF THE MONTH

AN214-4.5W Power IC with spec. Supply voltage = 13V	**$2.95 ea.**
MH0026-5MHz Clock Driver	**$1.95 ea.**
6V 130mA A/C Adaptor/charger	**$1.25 ea.**
0.2" - Red Fairchild L.E.D.	**100/$10.00**
14-pin Lo pro IC Socket	**100/$16.00**
16-pin Lo pro IC Socket	**100/$17.00**

CIRCLE 80 ON FREE INFORMATION CARD

Active Electronic Sales Corp.

May We Introduce Ourselves

$30.00

INTRODUCTORY PACKAGE

With any order valued at $30.00 or more

Post marked prior to July 31, 1978

You receive AT NO EXTRA CHARGE

- A 1978 ACTIVE ELECTRONICS Catalogue
- Your choice of any of the following packages -

PACKAGE NO. 1

UNB0400 Unitrode Semiconductor Data Book. 500 pages on rectifiers, fullwave bridges, transient voltage suppressors, zeners, programmable unijunction transistors, etc.

LCC4162 TTL Supplement. The most recent TTL functions are included in this supplement to the 2nd edition of the TTL Data Book.

RAB0606 Raytheon Selection Guide. A full line condensed quick reference source on all Raytheon Components,

LCC4151 T.I. Linear and Interface Circuits Data Book. 688 pages. Complete specifications on the 75 series of MOS interface peripheral driver, memory sense amplifiers, display interface circuits etc.

Value $16.90

PACKAGE NO. 2

FSB0104 Fairchild Bipolar Memory Data Book. Bipolar memories, ECL static memories, TTL static memories, TTL dynamic memories and macrologic.

FSB0105 Macrologic Bipolar Microprocessor Data Book. Microprogramming for implementing as many system functions as possible in one centralized logic block.

FSB0112 Fairchild Hybrid. Custom and standard product as well as reliability and design considerations.

GSB0100 Zener, Transistor and Transzorb Catalogue. Discrete devices and pertinent data and complete device characterization.

FSB0103 Fairchild Power Data Book. Basic parameter and data information as well as information on technology, safe operating area, reliability etc.

Value $14.35

PACKAGE NO. 3

ADVANCED MICRO DEVICES

AMB0203 8080A/9080A MOS Microprocessor Hand Book. Detailed descriptions of the 8080A and associated CPU components.

AMB0205 MOS/LSI Data Book. Static RAM's dynamic 4K RAM's, 2K EROM, shift registers, FIFO memories and complete microprocessor and support circuits.

AMB0206 Linear and Interface Data Book. Comparators, data conversion products, Line drivers/receivers, MOS memory and microprocessor interface, Op Amps, Voltage Regulators etc.

Value $17.85

PACKAGE NO. 4

LCC4041 T.I. Power Semiconductor Data Book. 816 pages germanium and silicon power transistors, SCR's, Triacs, darlingtons, silicon power high voltage and low voltage types etc.

SIB0303 Siliconix High Speed Analog Switches. Complete specifications, characteristics and applications of the DG300 series.

SIB0304 Siliconix FET Data Book. Complete data on selecting the right FET for your application, characteristics and PC board layout.

SIB0305 VMOS Power FET's. Technical information, application and design aids, characteristics and device / application selection for this latest in technology.

Value $16.30

PACKAGE NO 5

SIB0300 Analog Switches and their Applications. Introduction to FET Analog Switches and the way the switch control or driver circuit affect performance.

LCC4280 T.I. Peripheral Driver Data Book. Total information and typical application of complete peripheral drivers and interface.

LCC4290 T.I. Line Driver and Line Receiver Data Book. Complete data on line circuits and application information.

GIM0100 General Instrument Microelectronics. Complete specifications and data on calculator, clock and T.V. game chips, microprocessors, industrial devices, static RAM's, EAROM's and ROM's.

Value $19.30

We reserve the right to ship a package of our choice, if one or more items of a requested package is out of stock. This offer available in the United States only.

Active Electronic Sales Corp.

P.O. BOX 1035 FRAMINGHAM, MASSACHUSETTS 01701

Over - the - counter sales,
12 Mercer Rd., Natick, Mass. 01760
Behind Zayres on Rte. 9
Telephone Orders & Enquires (617) 879 - 0077

IN CANADA 2 LOCATIONS

5651 Ferrier St.
Montreal, Quebec
Tel. (514) 735 - 6425

44 Fasken Dr.- Unit 25
Rexdale, Ontario
Tel. (416) 675 - 3311

MINIMUM ORDER $10.00 ● ADD $2.00 TO COVER POSTAGE & HANDLING ● Canadian customers add 30% for exchange and handling. All federal and provincial taxes extra.

Foreign customers please remit payment on an international bank draft or international postal money order in American dollars.

CIRCLE 38 ON FREE INFORMATION CARD

SOCKET JUMPERS

Mates with two rows of .025" sq. or dia. posts on patterns of .100" centers and shielded receptacles. Probe access holes in back. Choice of 6" or 18" length.

Part No.	No. of Contacts	Length	Price
924003-18R	26	18"	$ 5.38 ea.
924003-06R	26	6"	4.78 ea.
924005-18R	40	18"	8.27 ea.
924005-06R	40	6"	7.33 ea.
924006-18R	50	18"	10.31 ea.
924006-06R	50	6"	9.15 ea.

JUMPER HEADERS

Solder to PC boards for instant plug-in access via socket-connector jumpers. .025" sq. posts. Choice of straight or right angle.

Part No.	No. of Posts	Angle	Price
923863-R	26	straight	$1.28 ea.
923873-R	26	right angle	1.52 ea.
923865-R	40	straight	1.94 ea.
923875-R	40	right angle	2.30 ea.
923866-R	50	straight	2.36 ea.
923876-R	50	right angle	2.82 ea.

INTRA-CONNECTOR

Provides both straight and right angle functions. Mates with standard .10" x .10" dual row connectors (i.e. 3m, Ainsley, etc.) Permits quick testing of inaccessible lines.

Part No.: 922576-26 **No. of contacts:** 26 **Price** $6.90 ea.

INTRA-SWITCH

Permits instant line-by-line switching for diagnostic or QA testing. Switches actuated with pencil or probe tip. Mates with standard .10" x .10" dual-row connectors. Low profile design. Switch buttons recessed to eliminate accidental switching.

Part No.: IS-26 **No. of contacts:** 26 **Price** $13.80 ea.

CRYSTALS

THESE FREQUENCIES ONLY

Part #	Frequency	Case/Style	Price
CY1A	1.000 MHz	HC33/U	$5.95
CY2A	2.000 MHz	HC33/U	$5.95
CY2.01	2.010 MHz	HC33/U	$ .99
CY3A	4.000 MHz	HC18/U	$4.95
CY7A	5.000 MHz	HC18/U	$4.95
CY12A	10.000 MHz	HC18/U	$4.95
CY14A	14.31818 MHz	HC18U	$4.95
CY19A	18.000 MHz	HC18/U	$4.95
CY22A	20.000 MHz	HC18/U	$4.95
CY30B	32.000 MHz	HC18/U	$4.95

CONNECTORS

PRINTED CIRCUIT EDGE-CARD

.156 Spacing-Tin-Double Read-Out

Bifurcated Contacts — Fits .054 to .070 P.C. Cards

15/30	PINS (Solder Eyelet)	**$1.95**
18/36	PINS (Solder Eyelet)	**$2.49**
22/44	PINS (Solder Eyelet)	**$2.95**
50/100A (.100 Spacing)	PINS (Wire Wrap)	**$6.95**

25 PIN-D SUBMINATURE (RS232)

DB25P	PLUG	**$3.25**
DB25S	SOCKET	**$4.95**
DB51226-1	COVER FOR 25S/25P	**$1.75**

LOTS OF POTS

Untested ⅜" square Spectrol Trimpots
Single-turn Printed Circuit Potentiometers

GB134	3 ea. of:	10-20-25-50 100-200-250-500 ohm	= 24 pcs.	**$2.95**
GB135	3 ea. of:	1K-2K-2.5K-5K 10K-20K-25K-50K	= 24 pcs.	**$2.95**
GB136	3 ea. of:	100K-200K-250K-500K 1Meg-2Meg-2.5Meg-5Meg	= 24 pcs.	**$2.95**

(Values subject to substitution within each group.)

'EXTRA SAVINGS' **Buy all 3 (GB134, 135 & 136) for only $7.49**

SWITCHES

¼'' mounting holes

				1-9	10+
TOGGLE (sub-minature)	JMT121	SPDT	on-off-on	$1.95	$1.43
	JMT123	SPDT	on-none-on	1.65	1.21
	JMT221	DPDT	on-off-on	2.55	1.87
	JMT223	DPDT	on-none-on	2.15	1.58
TOGGLE (Printed Circuit)	MPC121	SPDT	on-off-on	$2.05	$1.53
	MPC123	SPDT	on-none-on	1.75	1.31
	MPC221	DPDT	on-off-on	2.65	1.97
	MPC223	DPDT	on-none-on	2.25	1.68
PUSH BUTTON	PB123	SPDT	maintained	1.95	1.47
	PB126	SPDT	momentary	1.95	1.47
PUSH BUTTON Minature	MS102	DPST	momentary open	.35	.30
	MS103	SPST	momentary closed	.35	.30
DIPSWITCH SPST	206-4	8 pin dip	4 switch	1.75	1.65
	206-7	14 pin dip	7 switch	1.95	1.85
	206-8	16 pin dip	8 switch	2.25	2.15

1/16 VECTOR BOARD

	0.1'' Hole Spacing Part No.	P-Pattern L	W	Price 1-9	10 up
PHENOLIC	64P44 062XXXP	4.50	6.50	1.72	1.54
	169P44 062XXXP	4.50	17.00	3.69	3.32
EPOXY GLASS	64P44 062WE	4.50	6.50	2.07	1.86
	84P44 062WE	4.50	8.50	2.56	2.31
	169P44 062WE	4.50	17.00	5.04	4.53
	169P84 062WE	8.50	17.00	9.23	8.26
EPOXY GLASS COPPER CLAD	169P44 062WEC1	4.50	17.00	6.80	6.12

INSTRUMENT/ CLOCK CASE

Injection molded unit.
Complete with red bezel.
4½" x 4" x 1-9/16".

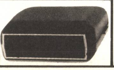

$3.49

MICROPROCESSOR COMPONENTS

8080A	CPU	$10.95	Z80	CPU	$24.95
8212	8 Bit Input/Output	4.95	CDP1802	CPU	19.95
8214	Priority Interrupt Control	7.95	MC6800	8 Bit MPU	19.95
8216	Bi-Directional Bus Driver	4.95	MC6810AP1	128 x 8 Static RAM	5.95
8224	Clock Generator/Driver	5.95	MC6820	Periph. Interface Adapter	7.95
8228	System Controller Bus Driver	5.95	MC6830L8	1024 x 8 Bit ROM	14.95

CPU'S

8080A	Super 8008	$10.95
2650	8 Bit MPU	26.50
P8085	CPU	29.95

SR'S

2504	1024 Dynamic	$ 3.95
2518	Hex 32 BIT	4.95
2519	Hex 40 BIT	4.00
2522	Dual 132 Bit SSR	2.95
2524	512 Dynamic	.99
2525	1024 Dynamic	2.95
2527	Dual 256 BIT	2.95
2528	Dual 250 Bit Static	4.00
2529	Dual 512 BIT	4.00
2532	Quad 80 BIT	2.95
2533	1024 Static	2.95
3341	Fifo	6.95
74LS670	16 x 4 Reg	1.95

UART'S

AY-5-1013	30K Baud	$ 5.95

ROM'S

2513(2140)	Char. Gen.-upper case	$ 9.95
2513(3021)	Char. Gen.-lower case	9.95
2516	Char. Gen.	10.95
MM5230	2048 BIT (512 x 4 on 256 x 8)	1.95

MM5262	2K x 1	Dynamic RAM	3 for 1.00

RAM'S

1101	256 x 1	Static	$ 1.49
2101	256 x 4	Static	5.95
2102	1024 x 1	Static	1.75
2107/5280	4096 x 1	Dynamic	4.95
2111	256 x 4	Static	6.95
TMS4044-45NL	4K	Static	14.95
7489	16 x 4	Static	1.75
8101	256 x 4	Static	5.95
8111	256 x 4	Static	6.95
8599	16 x 4	Static	3.49
21L02/91L02	1024 x 1	Static	1.95
74200	256 x 1	Static	6.95
93421	256 x 1	Static	2.95
MK4116(UPD416)	4K	Dynamic 16 Pin	5.95
MK4027(UPD414)	16K	Dynamic 16 Pin	29.95

PROMS

1702A	2048	Famos	$ 5.95
5203	2048	Famos	14.95
82S23	32 x 8	Open C	5.00
82S123	32 x 8	Tristate	5.00
74S287	1024	Static	7.95
3601	256 x 4	Fast	3.95
2708	8K	Eprom	10.95
2716 T.I.	16K	Eprom	29.95
2716 Intel	16K	Eprom	59.95
6301-1	1024	Tri-State Bipolar	3.49
6330-1	256	Open Collector Bipolar	2.95

SPECIAL REQUESTED ITEMS

FCM3817	$5.00	11C90	19.95	7205	19.95	9368	3.95
AY-3-8500-1	7.50	4N33	3.95	ICM7045	24.95	LD110/111	25.00/set
AY-5-9100	14.95	8T20	7.50	ICM7207	7.50	95H90	11.95
AY-5-9200	14.95	8T97	1.50	ICM7208	19.95	MC3061P	3.50
AY-5-9500	4.95	HD0165	7.95	ICM7209	7.50	MC4016 (74416)	7.50
AY-5-2376	14.95	MCM6571	13.50	MK50240	17.50	MC1408L7	4.95
9374	1.50	MCM6574	13.50	DS0026CH	3.75	MC1408L8	5.75
82S115	19.95	MCM6575	13.50	TIL308	10.50	74C922	9.95

CLOCK CHIPS

MM5309	$9.95
MM5311	4.95
MM5312	4.95
MM5314	4.95
MM5316	6.95
MM5318	9.95
MM5369	2.95
MM5841	9.95
CT7001	5.95

PARATRONICS

Featured on February's Front Cover of Popular Electronics

Logic Analyzer Kit Model 100A

$229.00/kit

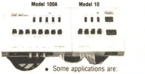

- Analyzes any type of digital system
- Checks data rates in excess of 8 million words per second
- Trouble shoot TTL, CMOS, DTL, RTL, Schottky and MOS families
- Displays 16 logic states up to 8 digits wide
- See ones and zeros displayed on your CRT, octal or hexadecimal format
- Tests circuits under actual operating conditions
- Easy to assemble — comes with step-by-step construction manual which includes 80 pages on logic analyzer operation.

(Model 100A Manual - $4.95)

- Some applications are:
  - — Troubleshooting microprocessor address, instruction, and data flow
  - — Examine contents of ROMS
  - — Tracing operation of control logic
  - — Checking counter and shift register operation
  - — Monitoring I/O sequences
  - — Verifying proper system operations during testing

PARATRONICS TRIGGER EXPANDER - Model 10

Adds 16 additional bits. Provides digital delay and qualification of input clock and 24-bit trigger word. — Connects direct to Model 100A for integrated unit).

Model 10 Kit - $229.00
Baseplate — $9.95
Model 10 Manual — $4.95

B+K PRECISION

3½-Digit Portable DMM

- Overload Protected
- .3" high LED Display
- Battery or AC operation
- Auto Zeroing
- 1mv, 1Va, 0.1 ohm resolution
- Overange reading
- 10 meg input impendence
- DC Accuracy 1% typical

Ranges: DC Voltage ±0-1000V/
AC Voltage: 0-1000V
Freq. Response: 50-400 HZ
DC/AC Current: 0-100mA
Resistance: 0-10 meg ohm
Size: 6.4" x 4.4" x 2"

Model 2800
$99.95

Comes with test leads, operating manual and spare fuse.

Accessories:

AC Adapter BC-28	**$9.00**
Rechargeable Batteries BP-26	**20.00**
Carrying Case LC-28	**7.50**

CSC

100 MHz 8-Digit Counter

- 20 Hz-100 MHz Range
- .6" LED Display
- Crystal-controlled timebase
- Fully Automatic
- Portable — completely self-contained
- Size — 1.75" x 7.38" x 5.63"
- Four power souces, i.e. batteries, 110 or 220V with charger 12V with auto lighter adapter and external 7.2-10V power supply

MAX-100 $134.95

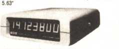

ACCESSORIES FOR MAX 100:

Mobile Charger Eliminator use power from car battery **Model 100 — CLA $3.95**

Charger/Eliminator use 110 V AC **Model 100 — CAI $9.95**

CONTINENTAL SPECIALTIES

PROTO BOARD 6

$15.95
(6'' long X 4'' wide)

Other CS Proto Boards

PB100 - 4.5'' x 6''	$ 19.95
PB101 - 5.8'' x 4.5''	29.95
PB102 - 7'' x 4.5''	39.95
PB103 - 9'' x 6''	59.95
PB104 - 9.5'' x 8''	79.95
PB203 - 9.75 x 6½ x 2¾	80.00
PB203A - 9.75 x 6½ x 2¾ (includes power supply)	129.95

PROTO CLIPS

14 PIN	$4.50
16 PIN	4.75
24 PIN	8.50
40 PIN	13.75

DESIGN MATES

DM1 - Circuit Designer $69.95
DM2 - Function Generator $74.95
DM3 - RC Bridge $74.95

LOGIC MONITOR
for DTL, HTL, TTL or CMOS Devices **$74.95**

CSC

QT PROTO STRIPS

QT type	#holes	price
QT-59S	590	12.50
QT-59B	bus strip	2.50
QT-47S	470	10.00
QT-47B	bus strip	2.25
QT-35S	350	8.50
QT-35B	bus strip	2.00
QT-18S	180	4.75
QT-12S	120	3.75
QT-8S	80	3.25
QT-7S	70	3.00

Experimentor 300	$ 9.95
Experimentor 600	$10.95

$5.00 Minimum Order — U.S. Funds Only
California Residents — Add 6% Sales Tax

Spec Sheets - 25¢ — Send 35¢ Stamp for 1978 Catalog
Dealer Information Available

NOW OPEN SATURDAYS

New 1978A CATALOG NOW AVAILABLE

James
ELECTRONICS

1021-A HOWARD AVE., SAN CARLOS, CA. 94070
PHONE ORDERS WELCOME — (415) 592-8097
Advertised Prices Good Thru May

The Incredible "Pennywhistle 103"

$129.95 Kit Only

The Pennywhistle 103 is capable of recording data to and from audio tape without critical speed requirements for the recorder and it is able to communicate directly with another modem and terminal for telephone "hamming" and communications for the deaf. In addition, it is free of critical adjustments and is built with non-precision, readily available parts.

Data Transmission Method .....Frequency-Shift Keying, full-duplex (half-duplex selectable).
Maximum Data Rate ....300 Baud.
Data Format ....Asynchronous Serial (return to mark level required between each character).
Receive Channel Frequencies ...2025 Hz for space; 2225 Hz for mark.
Transmit Channel Frequencies ..Switch selectable: Low (normal) = 1070 space, 1270 mark; High = 025 space, 2225 mark.
Receive Sensitivity ....−46 dbm accoustically coupled.
Transmit Level ....−15 dbm nominal. Adjustable from −6 dbm to −20 dbm.
Receive Frequency Tolerance ...Frequency reference automatically adjusts to allow for operation between 1800 Hz and 2400 Hz.
Digital Data Interface ....EIA RS-232C or 20 mA current loop (receiver is optoisolated and non-polar).
Power Requirements ....120 VAC, single phase, 10 Watts.
Physical ....All components mount on a single 5" by 9" printed circuit board. All components included.

Requires a VOM, Audio Oscillator, Frequency Counter and/or Oscilloscope to align.

The Original

the 3rd Hand

$9.95 each

*Leaves two hands free for working
* Clamps on edge of bench, table or work bench
* Position board on angle or flat position for soldering or clipping
* Sturdy, aluminum construction for hobbyist, manufacturer or school rooms

DIGITAL STOPWATCH

- Bright 6 Digit LED Display
- Times to 59 minutes 59.59 seconds
- Crystal Controlled Time Base
- Three Stopwatches in One Times Single Event — Split & Taylor
- Size 4.5'' x 2.15'' x .90'' (4½ ounces)
- Uses 3 Penlite Cells.

Kit — $39.95
Assembled — $49.95
Heavy Duty Carry Case $5.95

Stop Watch Chip Only (7205) $19.95

IMC

3½ DIGIT DPM KIT

- New Bipolar Unit
- Auto Zeroing
- .5″ LED
- Auto Polarity
- Low Power
- Single IC Unit

Model KB500 DPM Kit $49.00
Model KB503 5V Power Kit $17.50

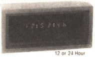

12 or 24 Hour

JE700 CLOCK

The JE700 is a low cost digital clock, but is a very high quality unit. The unit features a simulated walnut case with dimensions of 6'' x 2½'' x 1''. It utilizes a MAN72 high brightness readout, and the MM5314 clock chip.

115 VAC *KIT ONLY* **$16.95**

HEXADECIMAL ENCODER 19-KEY PAD

- 1 - 0
- ABCDEF
- Shift Key
- 2 Optional Keys

$10.95 each

New 63 KEY KEYBOARD

$29.95
IN STOCK

This keyboard features 63 unencoded SPST keys, unattached to any kind of P.C.B. A very solid molded plastic 13'' x 4'' base suits most applications.

HD0165	Encoder Chip (encodes 16 Keys)	$7.95 ea.
AY-5-2376	Encoder Chip (encodes 88 Keys)	$14.95 ea.

JE803 PROBE

The Logic Probe is a unit which is for the most part indespensible in trouble shooting logic families TTL, DTL, RTL, CMOS. It derives the power it needs to operate directly off of the circuit under test, drawing a scant 10 mA max. It uses a MAN3 readout to indicate any of the following states by these symbols (H) - 1 (LOW) - o (PULSE) - P. The Probe can detect high frequency pulses to 45 MHz. It can't be used at MOS levels or circuit damage will result.

$9.95 Per Kit
printed circuit board

T²L 5V 1A Supply

This is a standard TTL power supply using the well known LM309K regulator IC to provide a solid 1 AMP of current at 5 volts. We try to make things easy for you by providing everything you need in one package, including the hardware for only **JE225 $9.95 Per Kit**

CIRCLE 76 ON FREE INFORMATION CARD

7400 TTL

Type	Price	Type	Price	Type	Price
SN7400N	.16				
SN7401N	.18	SN7472N	.29	SN74160N	.89
SN7402N	.18	SN7473N	.35	SN74161N	.89
SN7403N	.18	SN7474N	.35	SN74162N	1.95
SN7404N	.18	SN7475N	.49	SN74163N	.89
SN7405N	.20	SN7476N	.35	SN74164N	.89
SN7406N	.29	SN7479N	5.00	SN74165N	.89
SN7407N	.29	SN7480N	.50	SN74166N	1.25
SN7408N	.20	SN7482N	.99	SN74167N	1.95
SN7409N	.20	SN7483N	.59	SN74170N	1.59
SN7410N	.18	SN7485N	.79	SN74172N	6.00
SN7411N	.25	SN7486N	.35	SN74173N	1.25
SN7412N	.25	SN7489N	1.75	SN74174N	.89
SN7413N	.40	SN7490N	.45	SN74175N	.79
SN7414N	.70	SN7491N	.59	SN74176N	.79
SN7416N	.25	SN7492N	.43	SN74177N	.79
SN7417N	.25	SN7493N	.43	SN74179N	1.95
SN7420N	.20	SN7494N	.65	SN74180N	.79
SN7421N	.29	SN7495N	.65	SN74181N	1.95
SN7422N	.39	SN7496N	.65	SN74182N	.79
SN7423N	.25	SN7497N	3.00	SN74184N	1.95
SN7425N	.29	SN74100N	.89	SN74185N	1.95
SN7426N	.29	SN74107N	.35	**SN74186N**	9.95
SN7427N	.25	SN74109N	.59	SN74188N	3.95
SN7429N	.39	SN74116N	1.95	SN74190N	1.25
SN7430N	.20	SN74121N	.35	SN74191N	1.25
SN7432N	.25	SN74122N	.39	SN74192N	.79
SN7437N	.25	SN74123N	.49	SN74193N	.79
SN7438N	.25	SN74125N	.49	SN74194N	.89
SN7439N	.25	SN74126N	.49	SN74195N	.69
SN7440N	.20	SN74132N	.75	SN74196N	.89
SN7441N	.89	SN74136N	.75	SN74197N	.89
SN7442N	.49	SN74141N	.79	SN74198N	1.49
SN7443N	.75	SN74142N	2.95	SN74199N	1.49
SN7444N	.75	SN74143N	2.95	SN74200N	5.59
SN7445N	.75	SN74144N	2.95	SN74251N	1.79
SN7446N	.69	SN74145N	.79	SN74279N	.79
SN7447N	.59	SN74147N	1.95	SN74283N	2.25
SN7448N	.79	SN74148N	1.29	SN74284N	3.95
SN7450N	.20	SN74150N	.89	SN74285N	3.95
SN7451N	.20	SN74151N	.59	SN74365N	.69
SN7453N	.20	SN74153N	.59	SN74366N	.69
SN7454N	.20	SN74154N	.99	SN74367N	.69
SN7459A	.25	SN74155N	.79	SN74368N	.69
SN7460N	.20	SN74156N	.79	SN74390N	1.95
SN7470N	.29	SN74157N	.65	SN74393N	1.95

20% Discount for 100 Combined 7400's

CMOS

Type	Price	Type	Price	74C00 Series	Price
CD4000	.23	CD4049	.49	74C00	.39
CD4001	.23	CD4050	.49	74C02	.55
CD4002	.23	CD4051	1.19	74C04	.75
CD4006	1.19	CD4053	1.19	74C08	.75
CD4007	.25	CD4056	2.95	74C10	.65
CD4009	.49	CD4059	9.95	74C14	3.00
CD4010	.49	CD4060	1.49	74C20	.65
CD4011	.23	CD4066	.79	74C30	.65
CD4012	.25	CD4068	.39	74C42	2.15
CD4013	.39	CD4069	.45	74C48	4.75
CD4014	1.39	CD4070	.55	74C73	1.50
CD4015	1.19	CD4071	.23	74C74	1.15
CD4016	.49	CD4072	.49	74C89	6.49
CD4017	1.19	CD4076	1.39	74C90	3.00
CD4018	.99	CD4081	.23	74C93	2.00
CD4019	.49	CD4082	.23	74C95	2.00
CD4020	1.19	CD4093	.99	74C107	1.25
CD4021	1.39	CD4098	2.49	74C151	2.90
CD4022	1.19	MC14409	14.95	74C154	3.00
CD4023	.23	MC14410	14.95	74C157	2.15
CD4024	.79	MC14411	14.95	74C160	3.25
CD4025	.23	MC14419	4.95	74C161	3.25
CD4026	2.25	MC14433	14.95	74C163	3.00
CD4027	.69	MC14506	.75	74C164	3.25
CD4028	.89	MC14507	.99	74C173	2.60
CD4029	1.19	CD4508	3.95	74C192	3.49
CD4030	.49	CD4510	1.39	74C193	2.75
CD4035	.99	CD4511	1.29	74C195	2.75
CD4040	1.19	CD4515	2.95	74C922	9.95
CD4041	1.25	CD4518	1.29	74C923	8.95
CD4042	.99	CD4520	1.29	74C925	14.95
CD4044	.89	MC14562	14.50	74C926	11.95
CD4046	1.79	CD4566	2.25	80C95	1.50
CD4047	2.50	MC14583	3.50	80C97	1.50
CD4048	1.35				

LINEAR

Type	Price	Type	Price	Type	Price
78MG	1.75			LM733N	1.00
LM300H	.80			LM739N	1.19
LM301H	.35			LM741CH	.35
LM301CN	.35			LM741CN	.35
LM302H	.75	LM340T-8	1.25	LM741-14N	.39
LM304H	1.00	LM340T-12	1.25	LM747H	.79
LM305H	.60	LM340T-15	1.25	LM747N	.79
LM307CN/H	.35	LM340T-18	1.25	LM748H	.39
LM308H	1.00	LM340T-24	1.25	LM748N	.39
LM308CN	1.00	LM350N	1.00	LM1303N	.90
LM309H	1.10	LM351CN	.65	LM1304N	1.19
LM309K	1.25	LM370N	1.15	LM1305N	1.40
LM310CN	1.15	LM373N	3.25	LM1307N	.85
LM311H	.90	LM377N	4.00	LM1310N	2.95
LM311N	.90	LM380N	1.25	LM1351N	1.65
LM317K	6.50	LM380CN	.99	LM1414N	1.75
LM318CN	1.50	LM381N	1.79	LM1458CN/H	.59
LM319N	1.30	LM382N	1.79	MC1488	1.95
LM320K-5	1.35	NE501N	8.00	MC1489	1.95
LM320K-5.2	1.35	NE510A	6.00	LM1496N	.95
LM320K-12	1.35	NE529A	4.95	LM1556V	1.75
LM320K-15	1.35	NE531H	3.00	MC1741SCP	3.00
LM320K-18	1.35	NE536T	6.00	LM2901N	2.95
LM320K-24	1.35	NE540L	6.00	LM3053	1.50
LM320T-5	1.25	NE550N	1.30	LM3065N	.69
LM320T-5.2	1.25	NE555V	.39	LM3900N(3401)	.49
LM320T-8	1.25	NE556	.99	LM3905N	.89
LM320T-12	1.25	NE560B	5.00	LM3909	1.25
LM320T-15	1.25	NE561B	5.00	MC5558V	1.00
LM320T-18	1.25	NE562B	5.00	LM7525N	.90
LM320T-24	1.25	NE565H	1.75	LM7534N	.75
LM323K-5	5.95	NE565N	1.25	8038B	4.95
LM324N	1.80	NE566CN	1.75	LM75450	.49
LM339N	.99	NE567H	1.25	75451CN	.39
LM340K-5	1.35	NE567V	.99	75452CN	.39
LM340K-6	1.35	NE570	10.50	75453CN	.39
LM340K-8	1.35	LM703CN/H	.45	75454CN	.39
LM340K-12	1.35	LM709H	.29	75491CN	.79
LM340K-15	1.35	LM709N	.29	75492CN	.89
LM340K-18	1.35	LM710N	.79	75494CN	.89
LM340K-24	1.35	LM711N	.39	RC4151	5.95
LM340T-5	1.25	LM723H	.55	RC4194	5.95
LM340T-6	1.25	LM723N	.55	RC4195	4.49

74LS00 TTL

Type	Price	Type	Price	Type	Price
74LS00	.23			74LS155	.69
74LS02	.23			74LS157	.69
74LS03	.23	74LS74	.35	74LS160	.89
74LS04	.29	74LS75	.49	74LS161	.89
74LS05	.29	74LS76	.35	74LS162	.89
74LS08	.23	74LS83	.75	74LS163	.89
74LS10	.23	74LS85	.99	74LS164	.99
74LS13	.49	74LS86	.35	74LS175	.79
74LS14	.99	74LS90	.49	74LS181	2.49
74LS20	.23	74LS92	.59	74LS190	.89
74LS26	.29	74LS93	.59	74LS191	.89
74LS27	.29	74LS95	.79	74LS192	.89
74LS28	.29	74LS96	.89	74LS193	.89
74LS30	.23	74LS107	.35	74LS194	.89
74LS32	.29	74LS109	.35	74LS195	89
74LS40	.29	74LS112	.35	74LS253	.79
74LS42	.69	74LS123	.99	74LS257	.69
74LS47	.69	74LS132	.79	74LS260	.55
74LS51	.23	74LS136	.39	74LS279	.59
74LS55	.23	74LS138	.69	74LS367	.59
74LS73	.35	74LS139	.69	74LS368	.59
		74LS151	.69	74LS670	1.95

BUGBOOK®

Continuing Education Series

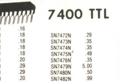

BUGBOOKS I and II — **$17.00 per set**
by Peter R. Rony, David G. Larsen, WB4HYJ

Sold as a set these two books outline over 90 experiments designed to teach the reader all he will need to know about TTL logic chips to use them in conjunction with microprocessor systems. You'll learn about the basic concepts of digital electronics including gates, flip-flops, latches, buses, decoders, multiplexers, demultiplexers, LED displays, RAM's, ROM's, and much, much more.

BUGBOOK IIa — **$5.00**
by Peter R. Rony, David G. Larsen, WB4HYJ

This volume will introduce you to the fabulous UART chip — that all important interface between data terminals, etc., and your microcomputer. It also covers current loops, and the RS 232C interface standard. Particularly recommended for any RTTY enthusiast.

THE 555 TIMER APPLICATIONS SOURCEBOOK WITH EXPERIMENTS — **$6.95**
by Howard M. Berlin W3HB

This book shows you what the 555 timer is and how to use it. Included are over 100 various design techniques, equations and graphs to create "ready-to-go" timers, generators, power supplies, measurement and control circuits, party games, circuits for the home and automobile, photography, music and Amateur Radio.

BUGBOOK III — **$15.00**
by Peter R. Rony, David G. Larsen, WB4HYJ, Jonathan A. Titus

Here is the book that puts it all together. Besides having much valuable text there are a series of experiments in which the reader completely explores the 8080 chip pin by pin and introduces you to the Mark 80 microcomputer, a unique easily interfaced system. It is recommended that you have the background on the BUGBOOKS I & II before proceeding with BUGBOOK III.

INSTRUCTOR'S MANUAL — **$3.00**

Necessary for instruction of Bugbook I and II. Answers questions regarding experiments, suggestions for further reading, philosophy of authors approach to digital electronics. A must for self-teaching individuals.

BUGBOOK V and VI — **$19.00 per set**
by David G. Larsen, Peter R. Rony, Jonathan A. Titus

Experiments in digital electronics, 8080A microcomputer programming and 8080A microcomputer interfacing. An integrated approach to self-instructed basic digital electronics, breadboarding and 8080A interfacing/programming Bugbook VI integrates the digital concepts of Bugbook V into a treatment of 8080A microcomputer programming and interfacing. Detail & laboratory experiments included with each book.

OP AMP MANUAL by Howard M. Berlin W3HB — **$9.00**

An experiment guide to application of operational amplifiers. Over 25 experiments on all phases of Op Amps.

DBUG — **$5.00**

8080 interpretive debugger. A program for entering, debugging and storing assembly language programs.

CMOS-M — DESIGNERS PRIMER AND HANDBOOK — **$6.00**

Starts at basic structure of CMOS devices through integration into MSI.

COMPLETE MANUAL FOR DIGITAL CLOCKS by John Weiss and John Brooks

Familiarizes technician or hobbyist with basic theories behind digital clocks. Includes trouble shooting guides, basic characteristics of clocks, soldering techniques, clock component data sheets and construction tips. **$3.95**

DISCRETE LEDS

.125" dia.		
XC209	Red	5/$1
XC209	Green	4/$1
XC209	Orange	4/$1
XC209	Yellow	4/$1

.190" dia.		
XC111	Red	10/$1
XC111	Green	4/$1
XC111	Yellow	4/$1
XC111	Orange	4/$1

.200" dia		
XC22	Red	5/$1
XC22	Green	4/$1
XC22	Yellow	4/$1
XC22	Orange	4/$1
SSL-22	RT	4/$1

.185" dia.		
XC526	Red	5/$1
XC526	Red	100/$8
XC526	Green	4/$1
XC526	Yellow	4/$1
XC526	Clear	4/$1

.200" dia.		
XC556	Red	5/$1
XC556	Red	100/$8
XC556	Green	4/$1
XC556	Yellow	4/$1
XC556	Orange	4/$1
XC556	Clear	7/$1

.085" dia.
MV50 - Red - 6/$1

INFRA-RED LED
¼" x ¼" x 1/16"
Flat **5/$1.00**

DISPLAY LEDS

TYPE	POLARITY	HT	PRICE	TYPE	POLARITY	HT	PRICE
MAN 1	Common Anode-red	.270	2.95	MAN 6680	Common Cathode-orange	.560	.99
MAN 2	5 x 7 Dot Matrix-red	.300	4.95	MAN 6710	Common Anode-red-D.D.	.560	.99
MAN 3	Common Cathode-red	.125	4/$1	MAN 6730	Common Anode-red ±1	.560	.99
MAN 4	Common Cathode-red	.187	1.95	MAN 6740	Common Cathode-red-D.D.	.560	.99
MAN 52	Common Anode-green	.300	1.25	MAN 6750	Common Cathode-red ±1	.560	.99
MAN 71	Common Anode-red	.300	1.25	MAN 6760	Common Anode-red	.560	.99
MAN 72	Common Anode-red	.300	.99	MAN 6780	Common Cathode-red	.560	.99
MAN 74	Common Cathode-red	.300	1.25	DL701	Common Anode-red ±1	.300	.99
MAN 81	Common Anode-yellow	.300	.99	DL702	Common Cathode-red	.300	1.25
MAN 82	Common Anode-yellow	.300	.99	DL704	Common Cathode-red	.300	.99
MAN 84	Common Cathode-yellow	.300	.99	DL707	Common Anode-red	.300	.99
MAN 3620	Common Anode-orange	.300	.99	DL741	Common Anode-red	.600	1.25
MAN 3630	Common Anode-orange ±1	.300	.99	DL746	Common Anode-red ±1	.630	1.49
MAN 3640	Common Cathode-orange	.300	.99	DL747	Common Anode-red	.600	1.49
MAN 4610	Common Anode-orange	.300	.99	DL749	Common Cathode-red ±1	.630	1.49
MAN 4640	Common Cathode-orange	.400	.99	DL750	Common Cathode-red	.600	1.49
MAN 4710	Common Anode-red ±1	.400	.99	DL33B	Common Cathode-red	.110	.35
MAN 4730	Common Anode-red	.400	.99	FND70	Common Cathode	.250	.69
MAN 4740	Common Cathode-red	.400	.99	FND359	Common Anode	.350	.75
MAN 4810	Common Anode-yellow	.400	.99	FND503	Common Cathode (FND500)	.500	.99
MAN 6610	Common Anode-orange-D.D.	.560	.99	FND507	Common Anode (FND510)	.500	.99
MAN 6630	Common Anode-orange	.560	.99	5082-7300	4 x 7 Sgl. Digit-RHDP	.600	19.95
MAN 6640	Common Cathode-orange-D.D.	.560	.99	5082-7302	4 x 7 Sgl. Digit-LHDP	.600	19.95
MAN 6650	Common Cathode-orange ±1	.560	.99	5082-7304	Overrange character (±1)	.600	15.00
MAN 6660	Common Anode-orange	.560	.99	5082-7340	4 x 7 Sgl. Digit-Hexadecimal	.600	22.50

RCA LINEAR

CA3013	2.15	CA3083	1.60
CA3023	2.56	CA3086	.85
CA3035	2.48	CA3089	3.75
CA3039	1.35	CA3091	3.50
CA3046	1.30	CA3102	2.95
CA3053	1.50	CA3123	2.15
CA3059	3.25	CA3130	1.39
CA3060	3.25	CA3140	1.25
CA3080	.85	CA3160	1.25
CA3081	2.00	CA3401	.49
CA3082	2.00	CA3600	1.75

EXAR

XR-2206KB Kit $19.95 — **XR-2206KA Kit $14.95**

WAVEFORM GENERATORS	
XR-205	$8.40
XR-2206CP	5.50
XR-2207CP	3.85

STEREO DECODERS	
XR-1310CP	$3.20
XR-1800P	3.20
XR-2567	2.99

MISCELLANEOUS	
XR-2211CP	$6.70
XR-4136	2.00
XR-1468	3.85
XR-1488	1.95
XR-1489	1.95
XR-2208	5.20

TIMERS	
XR-555CP	$.39
XR-320P	1.55
XR-556CP	.99
XR-2556CP	3.20
XR-2240CP	4.80

PHASE LOCKED LOOPS	
XR-210	5.20
XR-215	6.60
XR-567CP	.99
XR-567CT	1.25

IC SOLDERTAIL — LOW PROFILE (TIN) SOCKETS

	1-24	25-49	50-100		1-24	25-49	50-100
8 pin LP	$.17	16	15	22 pin LP	$.37	36	35
14 pin LP	20	19	18	24 pin LP	38	37	36
16 pin LP	22	21	20	28 pin LP	45	44	43
18 pin LP	29	28	27	36 pin LP	60	59	58
20 pin LP	.34	.32	.30	40 pin LP	63	62	61

SOLDERTAIL STANDARD (TIN)

14 pin ST	$.27	25	24	28 pin ST	$.99	90	81
16 pin ST	30	27	25	36 pin ST	1.39	1.26	1.15
18 pin ST	35	32	30	40 pin ST	1.59	1.45	1.30
24 pin ST	49	45	42				

SOLDERTAIL STANDARD (GOLD)

8 pin SG	$.30	27	24	24 pin SG	$.70	63	57
14 pin SG	35	32	29	28 pin SG	1.10	1.00	90
16 pin SG	38	35	32	36 pin SG	1.75	1.40	1.26
18 pin SG	52	47	43	40 pin SG	1.75	1.59	1.45

WIRE WRAP SOCKETS (GOLD) LEVEL #3

8 pin WW	$.40	.38	.35	22 pin WW	.95	.85	.75
10 pin WW	45	41	37	24 pin WW	1.05	95	85
14 pin WW	39	38	37	28 pin WW	1.40	1.25	1.10
16 pin WW	43	42	41	36 pin WW	1.59	1.45	1.30
18 pin WW	75	68	62	40 pin WW	1.75	1.55	1.40

50 PCS. RESISTOR ASSORTMENTS $1.75 PER ASST.

ASST. 1	5 ea.	10 OHM 27 OHM	12 OHM 33 OHM	15 OHM 39 OHM	18 OHM 47 OHM	22 OHM 56 OHM	1/4 WATT 5% = 50 PCS.
ASST. 2	5 ea.	68 OHM 180 OHM	82 OHM 220 OHM	100 OHM 270 OHM	120 OHM 330 OHM	150 OHM 390 OHM	1/4 WATT 5% = 50 PCS.
ASST. 3	5 ea.	470 OHM 1.2K	560 OHM 1.5K	680 OHM 1.8K	820 OHM 2.2K	1K 2.7K	1/4 WATT 5% = 50 PCS.
ASST. 4	5 ea.	3.3K 8.2K	3.9K 10K	4.7K 12K	5.6K 15K	6.8K 18K	1/4 WATT 5% = 50 PCS.
ASST. 5	5 ea.	22K 56K	27K 68K	33K 82K	39K 100K	47K 120K	1/4 WATT 5% = 50 PCS.
ASST. 6	5 ea.	150K 390K	180K 470K	220K 560K	270K 680K	330K 820K	1/4 WATT 5% = 50 PCS.
ASST. 7	5 ea.	1M 2.7M	1.2M 3.3M	1.5M 3.9M	1.8M 4.7M	2.2M 5.6M	1/4 WATT 5% = 50 PCS.

ASST. 8R Includes Resistor Assortments 1-7 (350 PCS.) **$9.95 ea.**

$5.00 Minimum Order — U.S. Funds Only
California Residents — Add 6% Sales Tax

Spec Sheets - 25¢ — Send 35¢ Stamp for 1978 Catalog
Dealer Information Available

NOW OPEN SATURDAYS

James ELECTRONICS

NEW 1978A CATALOG NOW AVAILABLE

1021-A HOWARD AVE., SAN CARLOS, CA. 94070
PHONE ORDERS WELCOME — (415) 592-8097
Advertised Prices Good Thru May

WIRE-WRAP KIT — WK-2-W

WRAP • STRIP • UNWRAP

- Tool for 30 AWG Wire
- Roll of 50 Ft. White or Blue 30 AWG Wire
- 50 pcs. each 1", 2", 3" & 4" lengths — pre-stripped wire.

$12.95

WIRE WRAP TOOL WSU-30

WRAP • STRIP • UNWRAP -$6.95

WIRE WRAP WIRE — 30 AWG

25 ft. min. $1.25 50 ft. $1.95 100 ft. $2.95 1000 ft. $15.00
SPECIFY COLOR — White - Yellow - Red - Green - Blue - Black

WIRE DISPENSER — WD-30

- 50 ft. roll 30 AWG KYNAR wire wrap wire **$3.95 ea.**
- Cuts wire to desired length
- Strips 1" of insulation **Specify** — Blue-Yellow-White-Red

REPLACEMENT DISPENSER SPOOLS FOR WD 30
Specify blue, yellow, white or red **$1.98/spool**

Prime Stock Inventory Clearance STEWART WARNER Special Offer

P/N	10(min.)	100	1000	P/N	10(min.)	100	1000
SW7401	$1.20/lot	$9.00/lot	$80.00/lot	SW7482	$4.90/lot	44.00/lot	430.00/lot
SW7407	2.20	19.00	180.00	SW7483	3.50	31.00	300.00
SW7416	2.20	19.00	180.00	SW7486	2.20	19.00	180.00
SW7417	2.20	19.00	180.00	SW7491	3.50	31.00	300.00
SW7420	1.30	11.00	100.00	SW7494	3.50	31.00	300.00
SW7423	2.20	19.00	180.00	SW7495	3.50	31.00	300.00
SW7425	1.70	14.00	130.00	SW7496	3.50	31.00	300.00
SW7427	1.50	12.00	110.00	SW74100	6.90	66.00	650.00
SW7430	1.50	12.00	110.00	SW74104	2.20	19.00	180.00
SW7432	1.50	12.00	110.00	SW74105	2.20	19.00	180.00
SW7437	1.50	12.00	110.00	SW74107	2.20	19.00	180.00
SW7438	1.50	12.00	110.00	SW74121	2.20	19.00	180.00
SW7440	1.20	9.00	80.00	SW74123	2.50	22.00	200.00
SW7443	3.50	31.00	300.00	SW74145	5.50	51.00	500.00
SW7444	3.50	31.00	300.00	SW74150	6.90	66.00	650.00
SW7445	3.50	31.00	300.00	SW74151	3.50	31.00	300.00
SW7446	4.00	36.00	350.00	SW74153	4.00	36.00	350.00
SW7450	1.20	9.00	80.00	SW74156	4.00	36.00	350.00
SW7453	1.20	9.00	80.00	SW74180	4.50	41.00	400.00
SW7454	1.20	9.00	80.00	SW74181	9.90	96.00	950.00
SW7460	1.20	9.00	80.00	SW74182	4.50	41.00	400.00
SW7472	2.20	19.00	180.00	SW9601	2.50	22.00	200.00
SW7475	3.50	31.00	300.00	SW9602	4.90	44.00	430.00
SW7480	2.90	26.00	250.00				

Pre-tubed • No mixing or combining prices

TV GAME CHIP SET — $7.95

Includes AY-3-8500-1 Chip and 2.010 mhz crystal
(2.010 crystal — $.99 ea/AY-3-8500-1 Chip — $7.50 ea.)

ZENERS — DIODES — RECTIFIERS

TYPE	VOLTS	W	PRICE	TYPE	VOLTS	W	PRICE
1N746	3.3	400m	4/1.00	1N4005	600 PIV	1 AMP	10/1.00
1N751A	5.1	400m	4/1.00	1N4006	800 PIV	1 AMP	10/1.00
1N752	5.6	400m	4/1.00	1N4007	1000 PIV	1 AMP	10/1.00
1N753	6.2	400m	4/1.00	1N3600	50	200m	6/1.00
1N754	6.8	400m	4/1.00	1N4148	75	10m	15/1.00
1N959	8.2	400m	8/1.00	1N4154	35	10m	12/1.00
1N965B	15	400m	4/1.00	1N4305	75	25m	20/1.00
1N5232	5.6	500m	28	1N4734	5.6	1w	28
1N5234	6.2	500m	28	1N4735	6.2	1w	28
1N5235	6.8	500m	28	1N4736	6.8	1w	28
1N5236	7.5	500m	28	1N4738	8.2	1w	28
1N456	25	40m	6/1.00	1N4742	12	1w	28
1N458	150	7m	6/1.00	1N4744	15	1w	28
1N485A	180	10m	6/1.00	1N1183	50 PIV	35 AMP	1.60
1N4001	50 PIV	1 AMP	12/1.00	1N1184	100 PIV	35 AMP	1.70
1N4002	100 PIV	1 AMP	12/1.00	1N1185	150 PIV	35 AMP	1.50
1N4003	200 PIV	1 AMP	12/1.00	1N1186	200 PIV	35 AMP	1.80
1N4004	400 PIV	1 AMP	12/1.00	1N1188	400 PIV	35 AMP	3.00

SCR AND FW BRIDGE RECTIFIERS

C36D	15A @ 400V	SCR	$1.95
C38M	35A @ 600V	SCR	1.95
2N2328	1.6A @ 200V	SCR	.50
MDA 980-1	12A @ 50V	FW BRIDGE REC.	1.95
MDA 980-3	12A @ 200V	FW BRIDGE REC.	1.95

TRANSISTORS

MPS A05	.30	2N3638	5/$1.00	PN4250	4/$1.00
MPS A06	5/$1.00	2N3702	5/$1.00	2N4400	4/$1.00
2N918	4/$1.00	2N3704	5/$1.00	2N4401	4/$1.00
2N2219A	3/$1.00	2N3705	5/$1.00	2N4402	4/$1.00
2N2221	4/$1.00	2N3706	5/$1.00	2N4403	4/$1.00
2N2222A	5/$1.00	2N3707	5/$1.00	2N4409	5/$1.00
2N2369	5/$1.00	2N3711	5/$1.00	2N5086	4/$1.00
2N2369A	4/$1.00	2N3724	$ .65	2N5087	4/$1.00
2N2484	4/$1.00	2N3725	$1.00	2N5088	4/$1.00
2N2906A	4/$1.00	2N3772	$2.25	2N5089	4/$1.00
2N2907A	5/$1.00	2N3903	5/$1.00	2N5129	5/$1.00
2N2925	5/$1.00	2N3904	4/$1.00	2N5138	5/$1.00
2N3035	2/$1.00	2N3905	4/$1.00	2N5139	5/$1.00
2N3055	$ .89	2N3906	4/$1.00	2N5209	5/$1.00
MJE2955	$1.25	2N4013	3/$1.00	2N5210	5/$1.00
MJE3055	$1.00	2N4014	3/$1.00	2N5432	$2.00
2N3392	5/$1.00	2N4123	6/$1.00	2N5449	3/$1.00
2N3398	5/$1.00	PN4249	4/$1.00	2N5951	5/$1.00
PN3567	3/$1.00			C106B1SCR	2/$1.00
PN3568	4/$1.00			40409	$1.75
PN3569	4/$1.00			40410	$1.75

CAPACITOR CORNER

50 VOLT CERAMIC DISC CAPACITORS

	1-9	10-49	50-100		1-9	10-49	50-100
10 pf	.05	.04	.03	.001µF	.05	.04	.035
22 pf	.05	.04	.03	.0047µF	.05	.04	.035
47 pf	.05	.04	.03	.01µF	.05	.04	.035
100 pf	.05	.04	.03	.022µF	.06	.05	.04
220 pf	.05	.04	.03	.047µF	.06	.05	.04
470 pf	.05	.04	.035	.1µF	.12	.09	.075

100 VOLT MYLAR FILM CAPACITORS

.001mf	.12	.10	.07	.022mf	.13	.11	.08
.0022	.12	.10	.07	.047mf	.21	.17	.13
.0047mf	.12	.10	.07	.1mf	.27	.23	.17
.01mf	.12	.10	.07	.22mf	.33	.27	.22

+20% DIPPED TANTALUMS (SOLID) CAPACITORS

.1/35V	.28	.23	.17	1.5/35V	.30	.26	.21
.15/35V	.28	.23	.17	2.2/25V	.31	.27	.22
.22/35V	.28	.23	.17	3.3/25V	.31	.27	.22
.33/35V	.28	.23	.17	4.7/25V	.32	.28	.23
.47/35V	.28	.23	.17	6.8/25V	.36	.31	.25
.68/35V	.28	.23	.17	10/25V	.40	.35	.29
1.0/35V	.28	.23	.17	15/25V	.63	.50	.40

MINIATURE ALUMINUM ELECTROLYTIC CAPACITORS

Axial Lead				Radial Lead			
.47/50V	.15	.13	.10	.47/25V	.15	.13	.10
1.0/50V	.16	.14	.11	.47/50V	.16	.14	.11
3.3/50V	.14	.13	.10	1.0/16V	.15	.13	.10
4.7/25V	.16	.14	.12	1.0/25V	.16	.14	.11
10/25V	.15	.13	.10	1.0/50V	.16	.14	.12
10/50V	.16	.14	.12	4.7/16V	.15	.13	.10
22/25V	.17	.15	.12	4.7/25V	.15	.13	.10
22/50V	.24	.20	.18	4.7/50V	.16	.14	.11
47/25V	.19	.17	.15	10/16V	.14	.12	.09
47/50V	.25	.21	.19	10/25V	.15	.13	.10
100/25V	.24	.20	.18	10/50V	.16	.14	.12
100/50V	.35	.30	.28	47/50V	.24	.21	.19
220/25V	.32	.28	.25	100/16V	.19	.15	.14
220/50V	.45	.41	.38	100/25V	.24	.20	.18
470/25V	.33	.29	.27	100/50V	.35	.30	.28
1000/16V	.55	.50	.45	220/16V	.23	.17	.16
2200/16V	.70	.62	.55	470/25V	.31	.28	.26

CIRCLE 77 ON FREE INFORMATION CARD

Beautiful Boards

OUR BEST SELLER: ECONORAM II™

S-100 Compatible 8K × 8 in a cost-effective package. Buffering on all lines, 0 wait states with the 8080, low power consumption, configured as two separate 4K blocks for addressing flexibility, handles DMA, memory protect with vector interrupt provision if you try to write into protected memory, fully socketed, gold-flashed edge fingers, solder masked and legended board . . . this is the board that doesn't cut any corners, but cuts the price instead.

(See the 1/77 issue of **Kilobaud** magazine for a product profile that tells just about everything you'd ever want to know about Econoram II . . . or send a self-addressed, stamped envelope to "Kilobaud Article" c/o our address and we'll send you a reprint. But if you **really** want to be convinced . . . talk to somebody who owns one!)

Kit form: $135.00
3 kits: $375.00
Assembled, tested: $155.00

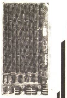

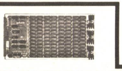

SUPER MEMORY FOR A SUPER MACHINE: H8 COMPATIBLE ECONORAM VI™

Users of the S-100 buss have found out why our memories are their best value . . . now H8 owners can find out too. This 12K × 8 kit offers the same basic features as our ECONORAM series . . . static design, configuration as two blocks (one 8K and one 4K), switch selected protect, sockets for all ICs, full buffering on address and data lines . . . plus the required hardware and edge connector to mate mechanically with the H8. As a bonus, **all** sockets and bypass capacitors are pre-soldered to the circuit board so you can start right in on the fun part of building this high-quality memory.

Kit form: $235.00

WE ALSO SPEAK DYNAMIC: ECONORAM III™

If you want a dynamic memory, might as well get one that works right. Econoram III is inexpensive, completely assembled and tested, and ready to plug into your S-100 machine. Low power, 0 wait states with 8080 CPU, configured as two 4K blocks, fully socketed.
$149.00, assembled and tested only.

ANNOUNCING . . . THE 16K ECONORAM IV™

We'll be ready to ship these soon, so we thought you'd like a sneak preview. The price? Under **$400**. The performance? All that you've come to expect from the Econoram line, along with impressively low power consumption and a couple of other tricks we have up our sleeve. If you've been waiting for a 16K board, you'll be happy you waited for us.

ACTIVE TERMINATOR BOARD

The active termination circuitry in our motherboard kits minimizes the ringing, crosstalk, overshoot, scrambled data, and noise problems that can occur with unterminated lines. But even if you don't have a Godbout motherboard, you can trick your computer into thinking you do by adding this useful peripheral. Simply plug into any S-100 machine, and gain the benefits of active circuitry.
#CK-017, $29.50. Kit form only.

DEALER NOTE

We'd like to thank the ever-growing number of dealers who are spreading the Econoram word to their customers . . . you will be happy to know that we have **doubled** the capacity of our Compukit™ division in order to continue handling the massive response. We're glad you like what we're doing . . . and we're going to keep on doing it!

TERMS: Please allow up to 5% for shipping; excess refunded. Californians add tax. COD orders accepted with street address for UPS. For VISA*/Mastercharge* orders call our 24 hour order desk at **(415) 562-0636.** Prices good through cover month of magazine.

FREE FLYER: These are just a few of the items we carry for the computer enthusiast. We also stock a broad line of semiconductors, passive components, and hobbyist items. We will gladly send you a flyer describing our products upon receipt of your name and address.

GODBOUT
BILL GODBOUT ELECTRONICS
BOX 2355, OAKLAND AIRPORT, CA 94614

CIRCLE 46 ON FREE INFORMATION CARD

DON'T MISS ANY

Get every single issue of Radio-Electronics delivered right to your door, and before it appears on the newsstand. Use this coupon and subscribe now.

Mail to: Radio-Electronics
SUBSCRIPTION DEPT., P.O. BOX 2520,
BOULDER, COLO. 80322

name **(please print)**

address

city **state** **zip code**

check offer preferred

- ☐ 1 Year—12 issues **ONLY $9.98**
- ☐ 2 Years—24 issues **SAVE MORE $19.00** **(You save $5.00 over newsstand)**
- ☐ 3 Years—36 issues **GREATER SAVINGS $27.00** **(You save $9.00 over newsstand prices)**
- ☐ Payment enclosed ☐ Bill Me
- ☐ Check here if this is a new subscription
- ☐ Check here if you are extending or renewing your subscription

Extra Shipping: Canada $3.00 per year, all other countries $5.00 per year.

40E8

MORE NEW ITEMS!

JUMBO LED READOUT ARRAY

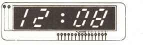

By Bowmar. .5 in. character common cathode. Designed for use with multiplexed clock chips 4 digits in 1 pack!

$1.95 LIMITED STOCK

3W. AUDIO AMP

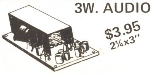

Assembled & tested. Not a kit. Has tapped output for either 4, 8 or 16 OHMS. With schematic.

CMOS SPECIAL

CD4001—5/$1	CD4011—5/$1
CD4013—3/$1	CD4040—$1 ea.
CD4042—2/$1	CD4049—3/$1

LAB PACK #1 DIPPED MICA CAPACITORS

Ten each of the following values:

10PF 100PF 500PF
24PF 150PF 1000PF
39PF 180PF 1800PF
68PF 280PF
82PF 300PF

WOW!
A $40.00 VALUE

(Pack of 130 Pcs.)
$12.95

All New!
Best Cap for general purpose use.

2708 EPROMS 1KX8

Prime new units from a major mfg. 450 N.S. access time. Equivalent to 4-1702 A's in 1 package! **450 ns**

$15.75 each

MOTOROLA 7805R Voltage Regulator

Same as standard 7805 except 750 MA output. **TO—220. 5VDC output.**

44c each 10/$3.95

4K STATIC RAM'S

2114. The new industry standard. Arranged as 1K x 4. Equivalent to 4-21 L02's in 1 package! 18 pin DIP. 2 chips give 1Kx8.

2 for $24. 8 for $85.

OPCOA LED READOUT

SLA-1 Common Anode. .33 inch character size. The original high efficiency LED display.

75c ea. 4/$2.50

TRANSFORMER

12 Vac. 600 MA. PRI-115 VAC 60 HZ. Perfect for clocks or power supplies! Small Size.

$1.95

LED IC Counter Kit

You Get: 1—7490; 1—7475; 1—7447; 1—Led Readout. All this for **$1.99** (Led Readout is famous SLA-1. .33 in. By Opcoa.)

POWER RECTIFIER #2

Motorola IN1187. Prime! 35 AMP 300 PIV. $4.72 Value Each

$1.19 ea. 4 FOR $3.50

DISC CAPACITORS

.1 MFD 16V. P.C. leads. Most popular value! By Sprague.

20 for $1.00

Full Wave Bridge

4 Amp 200 PIV
69¢ea. 10/5.75

5V. NI-CAD Battery 4 cell Pack. Rated 500 MAH. NEW!
$3.95 pack
By Union Carbide!

2N3904-House No.

TO—92. NPN.
VCEO-45.
HFE 100 to 300

10 for $1.00

Jumbo Red Leds

New by G.E. Like MV5024. Number SSL-22.

6/$1. 25/$3.75

Motorola PNP Power!

2N4905 TO-3 case. 90W. VCEO-60. HFE-100 max. at 2.5A. Good mate for the 2N3055. PRIME!

75¢ ea. 4/$2.50

GE POWER TRIAC

SC 146D. House #. 10 AMPS 400 PIV TO-220 CASE 75¢ea.

4 FOR 2.50

LS SERIES TTL

74LS00—33c	74LS74—49c
74LS02—35c	74LS90—69c
74LS04—35c	74LS138-89c
74LS08—35c	74LS154-1.49
74LS10—33c	74LS175-1.10
74LS20—33c	74LS367-75c
74LS73—49c	74LS368-85c

Motorola Quad Op-Amp MC3401. Pin for Pin Sub for popular LM3900.

3/$1.00

Digital Research Corporation

(OF TEXAS)
P. O. BOX 401247 • GARLAND, TEXAS 75040 • (214) 271-2461

TERMS: Orders under $15. add 75c. No COD's. We accept VISA, MasterCharge and American Express Cards. Money Back Guarantee on all items! Texas Residents add 5% Sales Tax. **WE PAY POSTAGE!**

CIRCLE 90 ON FREE INFORMATION CARD

NEW LSI TECHNOLOGY

FREQUENCY COUNTER

TAKE ADVANTAGE OF THIS NEW STATE-OF-THE-ART COUNTER FEATURING THE MANY BENEFITS OF CUSTOM LSI CIRCUITRY. THIS NEW TECHNOLOGY APPROACH TO INSTRUMENTATION YIELDS ENHANCED PERFORMANCE, SMALLER PHYSICAL SIZE, DRASTICALLY REDUCED POWER CONSUMPTION [PORTABLE BATTERY OPERATION IS NOW PRACTICAL], DEPENDABILITY, EASY ASSEMBLY AND REVOLUTIONARY LOWER PRICING!

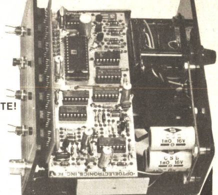

KIT #FC-50 C . . . . 60 MHZ COUNTER WITH CABINET & P.S. . . . . . $119.95 COMPLETE!
KIT #PSL-650 . . . . 650 MHZ PRESCALER [NOT SHOWN] 29.95
MODEL #FC-50WT . . . . 60 MHZ COUNTER WIRED, TESTED & CAL. 165.95
MODEL #FC-50/600 WT . . 600 MHZ COUNTER WIRED, TESTED & CAL. 199.95

SIZE:
3" High
6" Wide
5½" Deep

FEATURES AND SPECIFICATIONS:

DISPLAY: 8 RED LED DIGITS .4" CHARACTER HEIGHT
GATE TIMES: 1 SECOND AND 1/10 SECOND
PRESCALER WILL FIT INSIDE COUNTER CABINET
RESOLUTION: 1 HZ AT 1 SECOND, 10 HZ AT 1/10 SECOND.
FREQUENCY RANGE: 10 HZ TO 60 MHZ. [65 MHZ TYPICAL].
SENSITIVITY: 10 MV RMS TO 50 MHZ, 20 MV RMS TO 60 MHZ TYP.
INPUT IMPEDANCE: 1 MEGOHM AND 20 PF.
[DIODE PROTECTED INPUT FOR OVER VOLTAGE PROTECTION.]
ACCURACY: ± 1 PPM [± .0001%]; AFTER CALIBRATION TYPICAL.
STABILITY: WITHIN 1 PPM PER HOUR AFTER WARM UP [.001% XTAL]
IC PACKAGE COUNT: 8 [ALL SOCKETED]
INTERNAL POWER SUPPLY: 5 V DC REGULATED.
INPUT POWER REQUIRED: 8-12 VDC OR 115 VAC AT 50/60 HZ.
POWER CONSUMPTION: 4 WATTS

KIT #FC-50C IS COMPLETE WITH PREDRILLED CHASSIS ALL HARDWARE AND STEP-BY-STEP INSTRUCTIONS. WIRED & TESTED UNITS ARE CALIBRATED AND GUARANTEED.

PLEXIGLAS CABINETS

Great for Clocks or any LED Digital project. Clear-Red Chassis serves as Bezel to increase contrast of digital displays.

CABINET I
3"H,6¼"W,5½"D

CABINET II
2½"H,5"W,4"D

Black, White or Clear Cover

$6.50 ea.

RED OR GREY PLEXIGLAS FOR DIGITAL BEZELS
3"x6"x1/8" **95¢** ea. **4/$3**

SEE THE WORKS Clock Kit
Clear Plexiglas Stand

- 6 Big .4" digits
- 12 or 24 hr. time
- 3 set switches
- Plug transformer
- all parts included

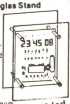

Plexiglas is Pre-cut & drilled

Kit #850-4 CP

Size: 6"H,4⅓"W,3"D

$23.50 ea. 2/$45. Assembled **$29.95**

60 HZ.

XTAL TIME BASE
Will enable Digital Clock Kits or Clock-Calendar Kits to operate from 12V DC.
1"x2" PC Board
Power Req: 5-15V (2.5 MA. TYP.)
Easy 3 wire hookup
Accuracy: ± 2PPM
#TB-1 (Adjustable)
Complete Kit **$4.95**
Wir & Cal $9.95

SPECIAL PRICING!

PRIME - HIGH SPEED RAM

21L02-3 400 NS

LOW POWER - FACTORY FRESH

1-24	$1.75 ea.	100-199	$1.45 ea.
25-99	1.60 ea.	200-999	1.39 ea.

1000 AND OVER **$1.29** ea.

6-DIGIT LED CLOCK CALENDAR KIT

DATE-TIME-SNOOZE ALARM & MORE... KIT 7001

FOR THE BUILDER THAT WANTS THE BEST. FEATURING 12 OR 24 HOUR TIME — 29-30-31 DAY CALENDAR. ALARM. SNOOZE AND AUX. TIMER CIRCUITS

Will alternate time (8 seconds) and date (2 seconds) or may be wired for time or date display only, with other functions on demand. Has built-in oscillator for battery back-up. A loud 24 hour alarm with a repeatable 10 minute snooze alarm, alarm set & timer set indicators. Includes 110 VAC/60Hz power pack with cord and top quality components through-out.

KIT - 7001B WITH 6 - .5" DIGITS $39.95
KIT - 7001C WITH 4 - .6" DIGITS & 2 - .3" DIGITS FOR SECONDS $42.95
KIT - 7001X WITH 6 - .6" DIGITS $45.95

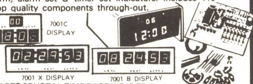

7001 X DISPLAY
7001 B DISPLAY

KITS ARE COMPLETE (**LESS CABINET**)
ALL 7001 KITS FIT CABINET I AND ACCEPT QUARTZ CRYSTAL TIME BASE KIT # TB-1

JUMBO DIGIT CLOCK

A complete Kit (less Cabinet) featuring: six .5" digits, MM5314 IC 12/24 Hr. time, PC Boards, Transformer, Line Cord, Switches and all Parts. Ideal Fit in Cabinet II

Kit #5314-5 **$19.95** **2/$38.**

JUMBO DIGIT CONVERSION KIT **$9.95** ea.

Convert small digit LED clock to large .5" displays. Kit includes 6 - LED's, Multiplex PC Board & Hook up info.
Kit #JD-1CC For Common Cathode
Kit #JD-1CA For Common Anode

PRINTED CIRCUIT BOARDS for CT-7001 Kits sold separately with assembly info. PC Boards are drilled Fiberglass, solder plated and screened with component layout.

Specify for 7001

B, C or X - $ 7.95

MOBILE LED CLOCK

12/24 HR **.4" DIGITS!**

MODEL #2001

12 VOLT AC or DC POWERED

- 6 JUMBO .4" RED LED'S BEHIND RED FILTER LENS WITH CHROME RIM
- SET TIME FROM FRONT VIA HIDDEN SWITCHES • 12/24-Hr. TIME FORMAT
- STYLISH CHARCOAL GRAY CASE OF MOLDED HIGH TEMP. PLASTIC
- BRIDGE POWER INPUT CIRCUITRY — TWO WIRE NO POLARITY HOOK-UP
- OPTIONAL CONNECTION TO BLANK DISPLAY [Use When Key Off in Car, Etc.]
- TOP QUALITY PC BOARDS & COMPONENTS - INSTRUCTIONS.
- MOUNTING BRACKET INCLUDED

KIT #2001 COMPLETE KIT **$27.95** EA. 3 OR MORE **$25.95** ea. 115 VAC Power Pack #AC-1 **$2.50** EA.

ASSEMBLED UNITS WIRED & TESTED
ORDER #2001 WT [LESS 9V. BATTERY]
Wired for 12-Hr. Op. if not otherwise specified.
$37.95 EA. 3 OR MORE **$35.95** ea.

AUTO BURGLAR ALARM KIT

AN EASY TO ASSEMBLE AND EASY TO INSTALL ALARM PROVIDING MANY FEATURES NOT NORMALLY FOUND. KEYLESS ALARM HAS PROVISION FOR POS. & GROUNDING SWITCHES OR SENSORS. WILL PULSE HORN RELAY AT 1HZ RATE OR DRIVE SIREN. KIT PROVIDES PROGRAMMABLE TIME DELAYS FOR EXIT, ENTRY & ALARM PERIOD. UNIT MOUNTS UNDER DASH - REMOTE SWITCH CAN BE MOUNTED WHERE DESIRED. CMOS RELIABILITY RESISTS FALSE ALARMS & PROVIDES FOR ULTRA DEPENDABLE ALARM. DO NOT BE FOOLED BY LOW PRICES! THIS IS A TOP QUALITY COMPLETE KIT WITH ALL PARTS INCLUDING DETAILED DRAWINGS AND INSTRUCTIONS OR AVAILABLE WIRED AND TESTED.

KIT #ALR-1 $9.95
#ALR-1WT WIRED & TESTED $19.95

VARIABLE REGULATED 1 AMP POWER SUPPLY KIT

- VARIABLE FROM 4 to 14V
- SHORT CIRCUIT PROOF
- 723 IC REGULATOR
- 2N3055 PASS TRANSISTOR
- CURRENT LIMITING AT 1 Amp

KIT IS COMPLETE INCLUDING DRILLED & SOLDER PLATED FIBERGLASS PC BOARD AND ALL PARTS (Less TRANSFORMER) **KIT #PS-01 $8.95**

TRANSFORMER 24V CT will provide 300MA at 12V and 1 Amp at 5V. **$3.50**

OPTOELECTRONICS, INC.

5821 N.E. 14th AVENUE,
FORT LAUDERDALE, FLA. 33334
PHONE (305) 771-2050 / 771-2051

ORDER BY PHONE OR MAIL
COD ORDERS WELCOME

ORDERS TO USA & CANADA ADD 5% FOR SHIPPING, HANDLING & INSURANCE. ALL OTHERS ADD 10%. ADDITIONAL $1.00 CHARGE FOR ORDERS UNDER $15.00 - COD FEE $1.00. FLA. RES. ADD 4% STATE TAX.

master charge THE INTERBANK CARD
BANKAMERICARD welcome here

CIRCLE 48 ON FREE INFORMATION CARD

ALDELCO ELECTRONICS COMPANY

NEW IMPROVED DIGITAL ALARM CLOCK KIT
0.5 LED Display 12 hour format
Snooze Feature
Elapsed Timer
Simulated Wood Grain or Black Leather Cabinet $24.95
12 or 24 Hour Clock Kit. Similar to above but without Alarm or Timer features Only $23.95
Crystal Time Base Kit for 12 Volt DC use 4.95

COMBINATION FREQUENCY COUNTER & CLOCK. 0.4 LED Display. .00005% accuracy. 12 or 24 Hour Clock uses 8 AA Nicad batteries (not supplied). Assembled Unit $99.95
8 Size AA Nicad Batteries 17.50
110 Volt AC Power Supply & Battery Charger 5.95

VOLTAGE REGULATORS
TO220 Package

Positive	Negative
$1.00	$1.25
7805	7905
7806	7906
7808	7912
7812	7915
7815	7918
LM309H	$1.10
LM309K	1.10
LM723	.55

CAPACITOR SPEC.
25 for $1.00
.1 .033 470pF
.01 20pF 510pF
.001 100pF 800pF
.01 Disc 30 volt 100 for $3.50
500 for $15.50

TURNER PTT Hand Mike Model J360DM with 5 pin DIN. GOOD for Ham CB marine and aviation only $10.95

Kit of parts for power supply.
includes schematic
5 Volt, 6 Amp $17.95
+15 and −15 2 Amp $16.95

FETS 40673 1.55
MPF102 .55

We have transistors.
Send stamp for catalog.

MA 1003 National Car Clock Module
With 3 push button switches and filters $19.95
New aluminum cabinet for MA 1003 $6.95

MC1458P SPEC.
Only .49

Monsanto MV5053 Jumbo Red LED and LED Holder .25 each
MAN82 CA 0.3 yellow display .88
Green, Yellow or Orange LEDS 5 for $1.00
FND 70 CC 0.3 Display LED .49
FND 500 CC 0.5 Display LED .89
CLOCK FILTERS 2⅛ x 5¾" Red, Blue, Green or Amber .60 ea

AMATEUR TV CONVERTER
Covers 420 to 450 AM TV BAND. Works on unused Commercial TV Channel
KIT ONLY $39.95
ASSEMBLED $49.95

BLINKEY-FLASHER-TIMER KIT
Includes 555, PC Board Parts & Instructions $2.50

ACCUKEYER KIT. Uses TTL, includes IC's, sockets, Speaker, PC Board, instructions and all parts ONLY $19.95
MEMORY KIT. Matches above & other accukeyer kits ONLY $19.95

VARIABLE POWER SUPPLY KITS. .5 Amps 5-15 Volt DC $6.95
add $1.00 per kit shipping .5 Amps 12-28 Volt DC 6.95

Visit Our Store. Hours 9:00 AM to 6:00 PM Mon. to Fri. Sat. 9:00 AM to 2:00 P.M. Phone Orders accepted. Visa & Master Charge. ADD 5% FOR SHIPPING. ORDERS UNDER $10.00 add $1.00. Foreign Orders add 15% shipping (Except Canada & Mexico) send Certified Check or Money Order in USA funds.

ALDELCO
2281R BABYLON TURNPIKE, MERRICK, N.Y. 11566
(516) 378 4555

CIRCLE 21 ON FREE INFORMATION CARD

MESHNA SPECIALS

PHOTO FLASH complete on PC board w/flash tube in reflector, 2 ni-cads & camera connecting cable. Cycles in 3 seconds	$6.00
8 SWITCHES in MINI DIP	1.80
10 SWITCHES in MINI DIP	2.00
AA NI-CADS fast charge	1.25
5 WAY BINDING POST US made	.35
U-FIX-EM TV games, w/power pack & video Cube in original boxes (sold for $50)	11.00
JUMBO LED .187 diam. long leads	6/1.00
TV CHEATER CORDS 6 ft	.75
LIQUID CRYSTAL thermometer, reads 86 to 108 degrees F	4/1.00
MULTI USE xfmr puts out 140 volts, 12.6, 6, 33.5 volts Many home projects	1.50
SEISMIC DETECTOR radio transmitter, used in Viet Nam for troop detection.	4.00
COPY LENS FROM ZEROX in mount. 8¼ focal length iris f4.5 to f8	10.50
U-FIX-EM hand calculator 4 function	3.00
LAMBDA solid state regulated slim line power supply 12 volts DC 8 amps	50.00
ULTRA SONIC transducer 37 or 40 Khz	$2.00
The above includes data on alarm system	
PL 259 coax connector	.75
SO-239 coax socket	.60
TOUCH TONE ENCODER KIT, pad, chip & instructions	12.95
IR NIGHT VIEWER, new ready to use, see in the dark	199.00

All above FOB LYNN MASS (you pay shipping)
Amazing 64 page catalog free

JOHN MESHNA JR, INC. PO Box 62, E. Lynn Mass. 91904

CIRCLE 54 ON FREE INFORMATION CARD

ADVERTISING INDEX

RADIO-ELECTRONICS does not assume any responsibility for errors that may appear in the index below.

Free Information Number		Page
38	Active Electronics	131
11	Advanced Computer Products	115
	Advance Electronics	17,91,93,95,97,100,104,106
21	Aldelco	136
	A M C Sales	108
81	American Technology	102
26	Arrow Fastener Co., Inc.	85
72	Avanti Research & Development	94
78	Babylon Electronics	124
	Karel Barta	107
	Forest Belt's Training Workshop	33
73	B & K Precision/Dynascan Co.	26
	Bullet Electronics	118
57	Capar	92
	C F R Associates	116
74	Chaney Electronics	116
25	Channellock	22
63	Chemtronics	99
	CIE—Cleveland Institute of Electronics	60-63
	Command Productions	107
28	Continental Specialties	Cov. 3
	Cornell Electronics	112
	CREI—Div. of McGraw Hill Continuing Education	86-89
	Dage Scientific Instruments	110
56	Davis Electronics	98
43	Delta Electronics	108
	Devtronix Organ Products	110
91	Digi-Key	120
90	Digital Research Corporation	134
31	Edmund Scientific	29
20	EICO	103
24	Electronics Book Club (Tab)	5
41	E & L Instruments	99
84	Electronic Lollipop	128
40	Electronic Systems	129
	EMC—Electronics Measurement	98
82	Energy Control Systems	85
9	Etco Electronics	125
	Etronix	110
	Fidelity Sound	104
83	Fluke	101
59	Fordham Radio Supply	34,35
45,29	Formula International	112,113
14	Fuji-Svea	109
	GFN	15
46	Godbout Electronics	134
4	Grantham College of Engineering	96
87	Gould	32
33	GTE Sylvania—Consumer Renewal	Cov. 2
100	Heath	18-21
19	Hickok Electrical Instruments	83
55	Hobbi House	117
	Hodapp T.V. Sales	94
79	IE Integrated Electronics	118
23	Indiana Home Study	93
	Information Unlimited	112
	Interface Age Magazine	23
62	International Crystal Mfg. Co.	105
12	International Electronics	121
76,77	James Electronics	132,133
	J & E Electronics	110
	Krystal Kits	110
	Lab Science	112
	Lakeside Industries	108
54	Meshna	136
85	Morrow's Micro Stuff	102
6	Mountain West Alarm Supply	97
53	Mouser Electronics	107
32	MTI—Motorola Training Institute	100
58	Multicore Solders	83
7,8	National Camera Supply	83,96
	National Radio Institute (NRI)—Div. of McGraw Hill Continuing Education Center	8-11
	National Technical Schools	25
60	Netronics	103
36	New-Tone Electronics	108
51	O.K. Machine & Tool	30
68	Olson	112
13,48	Optoelectronics	123,135
3	Page Digital	124
15	PAIA	94
66	Panasonic	2
86	Panavise	101
75	Parasitic Engineering	105
	Plus Electronics	112
37	Poly Paks	127
2	Priority 1 Electronics	122
88	PTS Electronics	24
27	Quest	116
71	Radio Hut	126
	Radio Shack	111
35	Ramsey Electronics	110
	RCA	16
64	Rohn Electronics Ltd.	91
65	Rye Industries	98
	Sabtronics	7
	H. W. Sams	13
30	J. B. Saunders	119
47	Schober Organ	103
17	Sencore	28
42	Solid State Sales	118
34	Solid State Time	107
18	Southwest Technical Products	1
1	Spacekom	27
	Surplus Center	110
5	Tarbell Electronics	124
	Tasco	110
69	Texas Tuner Service	102
16	TK Enterprises	85
80	Trinico	130
44	Tri-Star	106
	Trumbull	112
70	Vaco	Cov. 4
61	Vitek Electronics, Inc.	31
39	VIZ Mfg.	36
52	Wersi Electronics	106

MOVING?

Don't miss a single copy of **Radio-Electronics.** Give us:

Six weeks' notice

Your old address and zip code

Your new address and zip code

ATTACH
LABEL
HERE

name (please print)

address

city state zip code

Mail to: Radio-Electronics
SUBSCRIPTION DEPT., P.O. BOX 2520,
BOULDER, COLO. 80322

FREQ. OUT.

CSC's done it again.

Broken the price and performance barriers with new MAX-100. The multimode, professional portable frequency counter that gives you more range, visibility, accuracy and versatility than any comparable unit at anywhere near its low, low price.

MAXimum performance. MAX-100 is a cinch to use. It gives you *continuous readings* from 20Hz to a *guaranteed 100MHz*, with 8-digit accuracy. Fast readings with 1/6-sec. update and 1-sec. sampling rate. Precise readings, derived from a crystal-controlled time base with 3ppm accuracy. High-sensitivity readings from signals as low as 30 mV, with diode overload protection up to 200V peaks.

Input signals over 100MHz automatically flash the most significant digit. And to indicate low-battery condition and extend remaining battery life, the *entire* display flashes at 1Hz.

MAXimum versatility. Wherever and whenever you need accurate frequency readings, MAX can do the job. Use it with clip-lead cable supplied. Mini-whip antenna. Or low-loss in-line tap with UHF connectors. For AM or FM; CB, ham, business radio and R/C transmitter or receiver alignment. Monitoring audio and RF generators. Checking computer clocks and other digital circuits. Repair of depth sounders and fish spotters. Troubleshooting ultrasonic remote controls. For these, and hundreds of other applications, you'll find it indispensable.

MAXimum visibility. MAX-100 features a big, bright 0.6″ multiplexed *8-digit* LED display, with leading-zero blanking. So you don't have to squint, or work up close. And, MAX's flip-up stand is *built-in.*

MAXimum flexibility. MAX-100 operates from *four* power sources, for use in lab or field. Internal alkaline or NiCad batteries. 110 or 220V with charger/eliminator. 12V with automobile cigarette-lighter adapter/charger. And external 7.2-10V supply.

MAXimum value. With all its impressive specs, you'd expect MAX to cost a lot more than a low $134.95, complete with clip-lead cable and applications/instruction manual. But that's another nice thing about MAX: though it's accurate enough for lab use, it's well within the reach of hobbyists' and CB-ers' budgets.

Order today. Call 203-624-3103 (East Coast) or 415-421-8872 (West Coast): 9 a.m.-5 p.m. local time. Major credit cards accepted. Or see your CSC dealer. Prices slightly higher outside USA.

Specifications.

Range: 20 Hz to 100 MHz, guaranteed. **Gatetime:** 1 sec. **Resolution:** 1 Hz. **Accuracy:** ± 1 count + time base error. **Input Impedance:** 1 MΩ/56 pF. **Coupling:** AC. **Sine Wave Sensitivity:** 30 mVRMS @ 50 MHz. **Internal Time Base Frequency:** 3.579545 MHz crystal osc. **Setability:** ± 3 ppm @ 25°C. **Temp-Stability:** Better than 0.2 ppm/°C, 0-50°C. **Max. Aging:** 10 ppm/year. **Display:** Eight .6″ LED digits; anti-glare window. **Lead-zero blanking:** decimal point appears between 6th and 7th digit when input exceeds 1 MHz. **Overflow:** with signals over 99,999,999 Hz, most significant (left hand) digit flashes, allowing readings in excess of 100 MHz. **Display update:** 1/6-second plus 1 sec. gate time. **Low Battery Indicator:** When power supply falls below 6.6 VDC, all digits flash @ 1 Hz rate. Flashing display extends battery life. **Power:** 6 AA Alkaline or NiCad cells (internal); **External:** 110 or 220/VAC Eliminator/charger; Auto cigarette lighter adapter; 7.2-10 VDC ext. supply; **Bat. Charging:** 12-14hr. **Size (HWD):** 1.75″x 5.63″ x 7.75″ (4.45 x 14.30 x 19.69 cm.) **Weight:** Less than 1.5 lb. (0.68 kg) w/batteries. **Accessories Included:** Clip-lead input cable; manual.

CONTINENTAL SPECIALTIES CORPORATION

CSC

70 Fulton Terrace, Box 1942, New Haven, CT 06509
203-624-3103 TWX 710-465-1227
WEST COAST: 351 California St., San Francisco, CA 94104,
415-421-8872 TWX 910-372-7992
GREAT BRITAIN: CSC UK LTD.
Spur Road, North Feltham Trading Estate,
Feltham, Middlesex, England.
01-890-8782 Int'l Telex: 851-881-3669
CANADA: Len Finkler Ltd.; Ontario

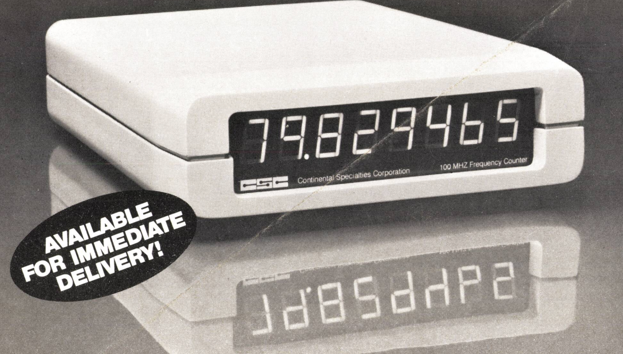
79.829465
CSC
Continental Specialties Corporation
100 MHZ Frequency Counter
AVAILABLE FOR IMMEDIATE DELIVERY!

CIRCLE 28 ON FREE INFORMATION CARD

Vaco.

Send for your FREE

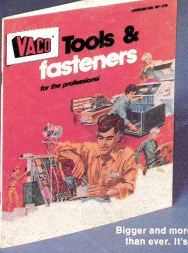

Bigger and more colorful than ever. It's Super!

1978 VACO catalog!

Super Case

Vaco means value and variety.

Like our Super Case. A great value with great variety. 48 professional problem-solving tools from screwdrivers and nutdrivers to pliers, wrenches, crimping tools, and more! All right at hand. And all unconditionally warranted.

You'll find the Super Case and all the other fine Vaco tools in our exciting new 72-page 1978 catalog. FREE for the asking! Just write:

Vaco Products Company, 1510 Skokie Boulevard, Northbrook, Illinois 60062

CIRCLE 70 ON FREE INFORMATION CARD